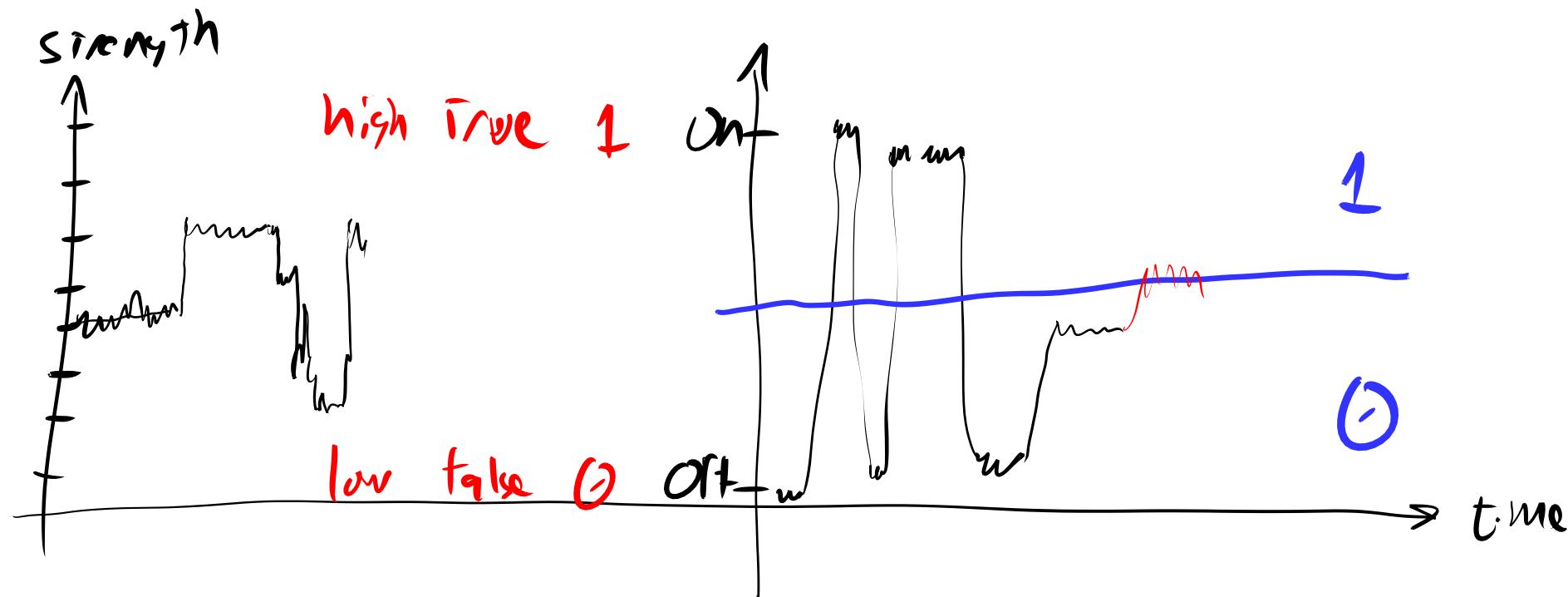




O1

Claude Shannon

b.i.T



binary

trinary

Quaternary

⋮

decimal

George

Boole

True

Boolean

False

and

or


nor

& &

||



!

Transistor

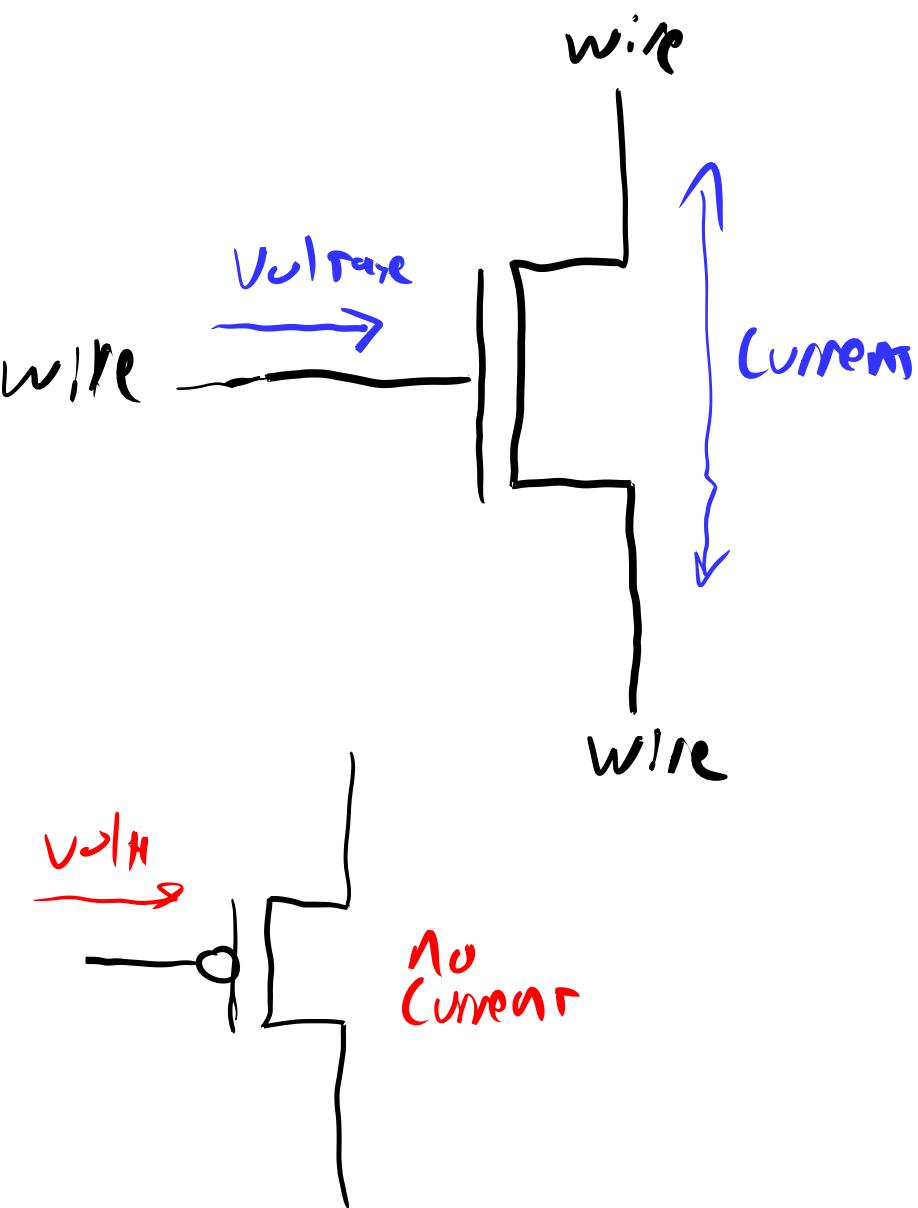

Voltage - pressure
Current - flow

source of voltage (1)

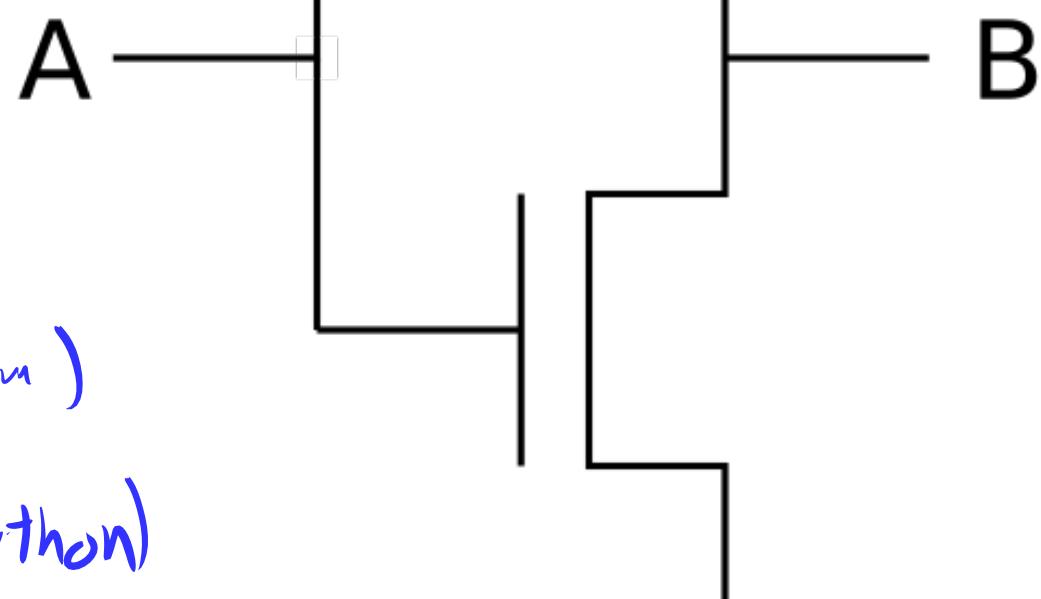
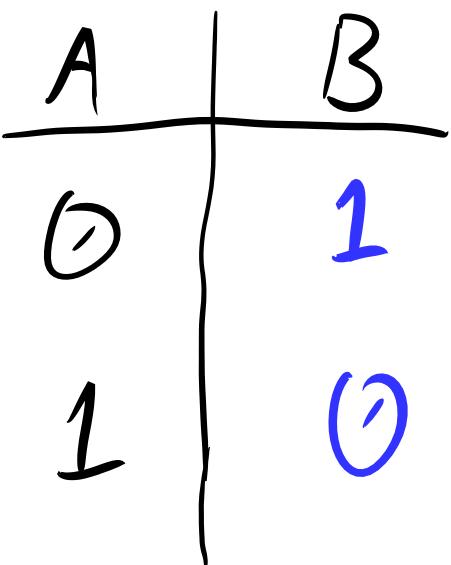


$$B = !A \quad (\text{Jav})$$


$$B = \sim A \quad (\text{Python})$$

ground (0)


source of voltage (1)

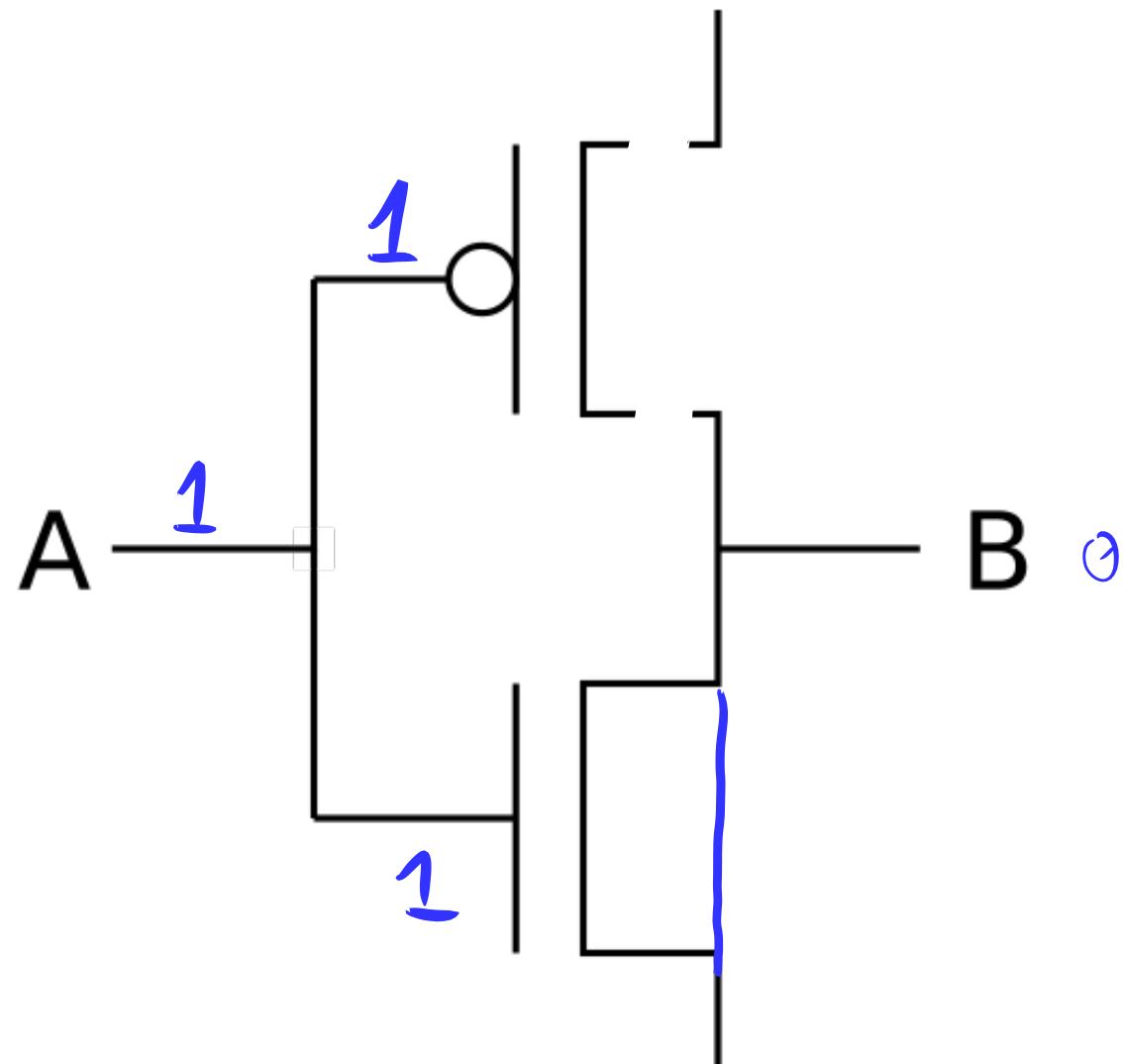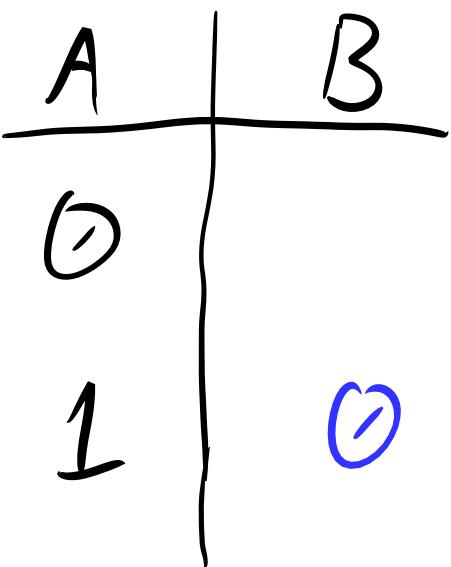


ground (0)

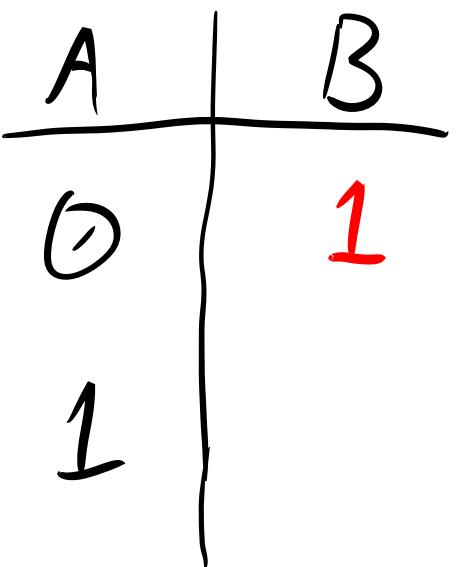


source of voltage (1)

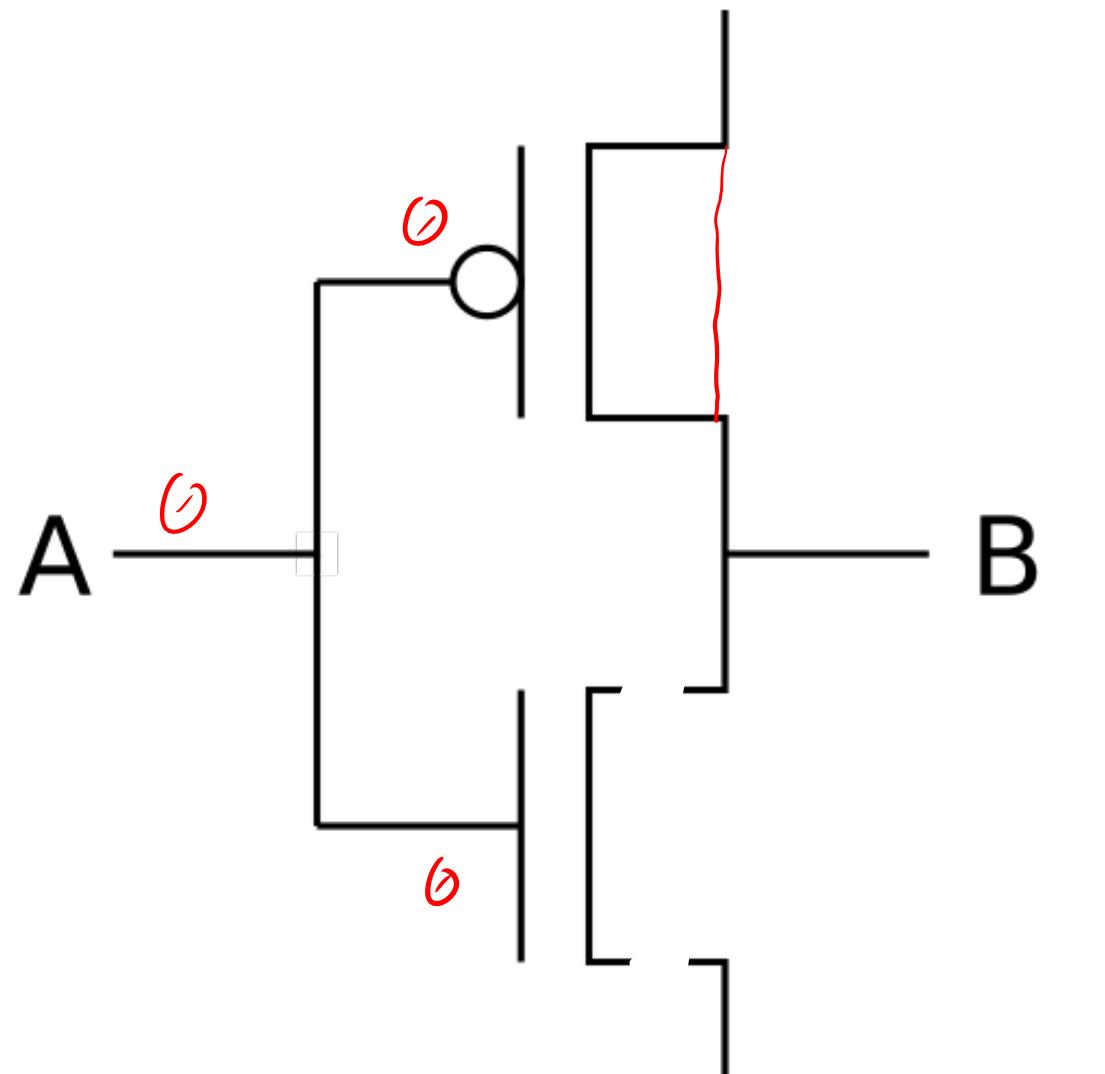

ground (0)

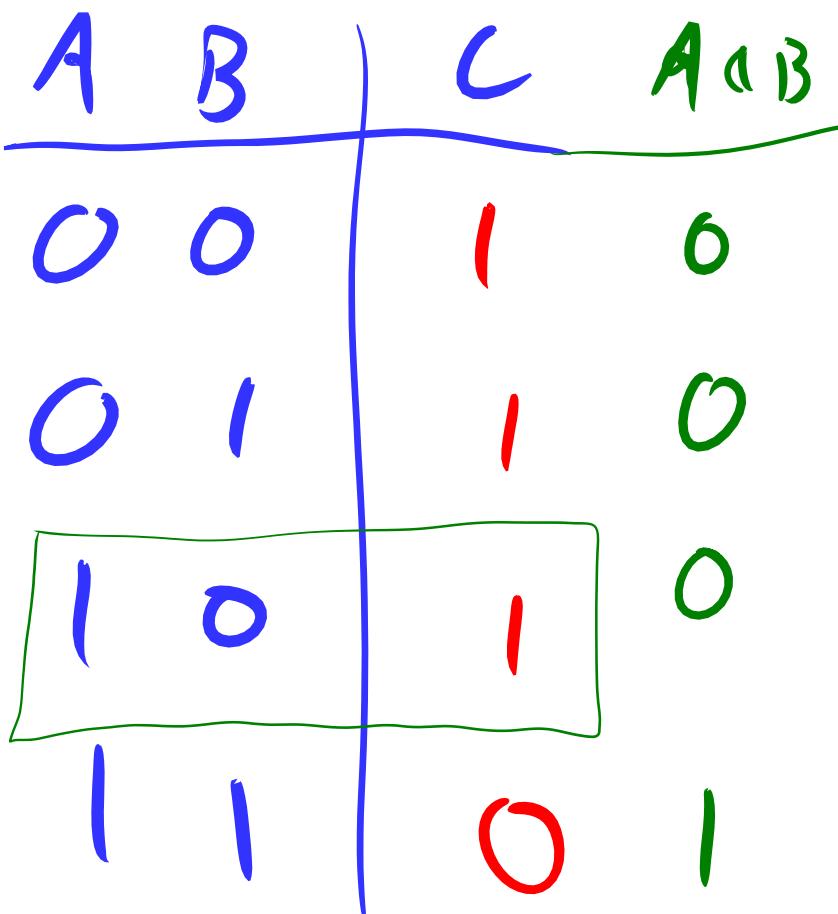


source of voltage

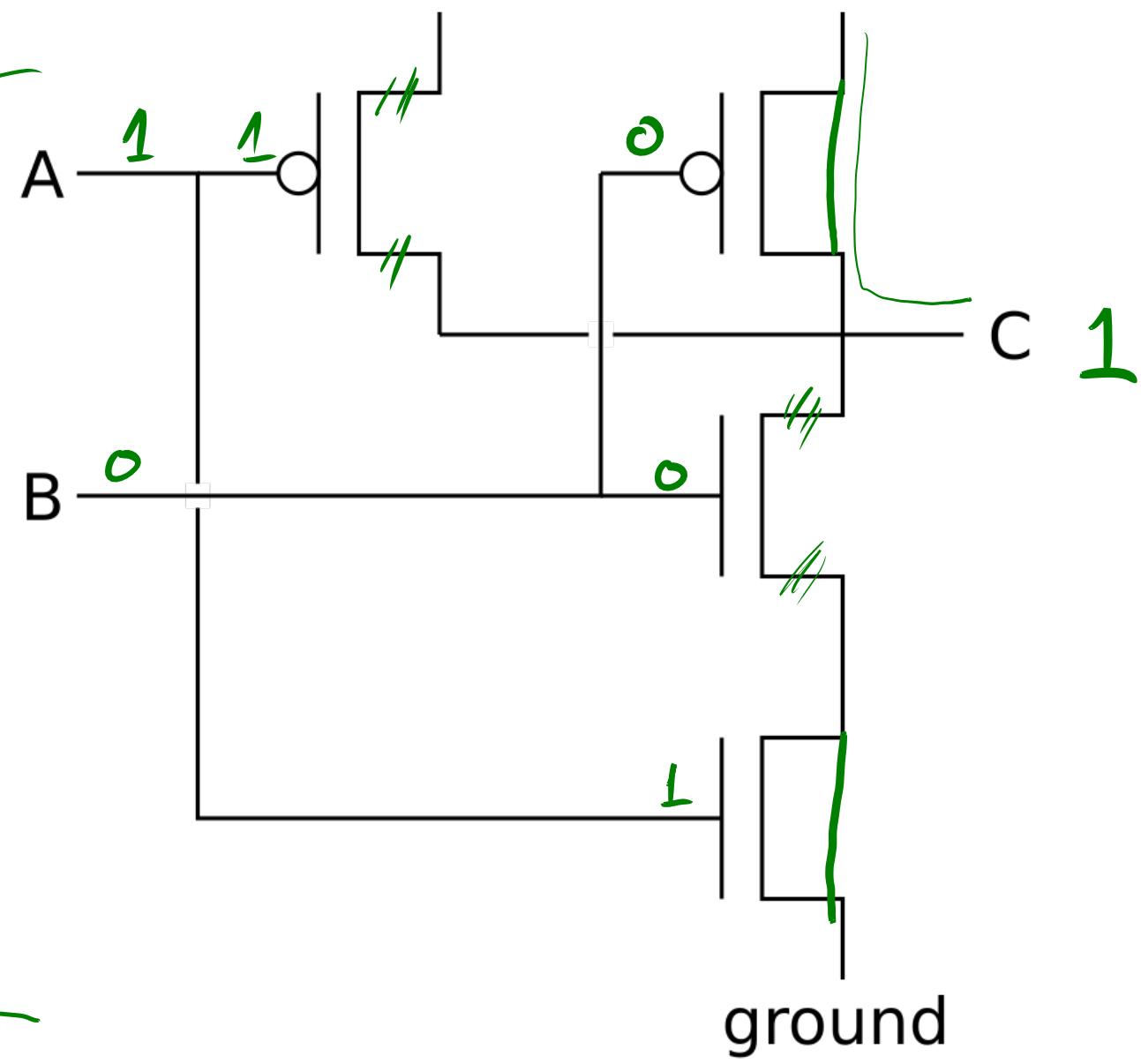

0 and
1 or
not

a	b	c	$a?b:c$
0			c
1			b

Ternary operator

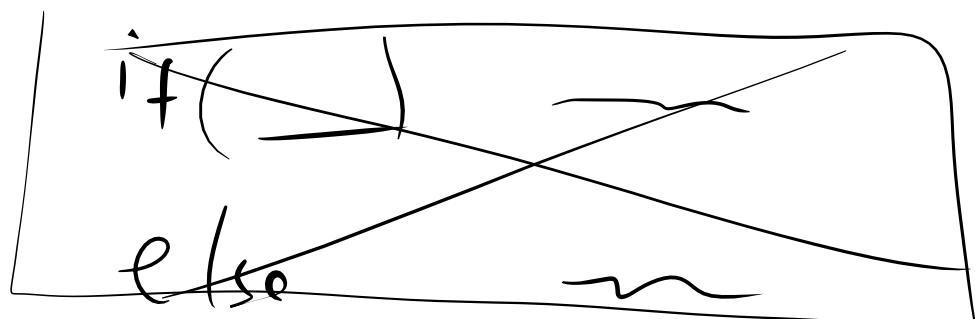


$x = b \text{ if } a \text{ else } c$

$x = a? b:c$

$$x = a?b:c$$

a	b	c	x
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

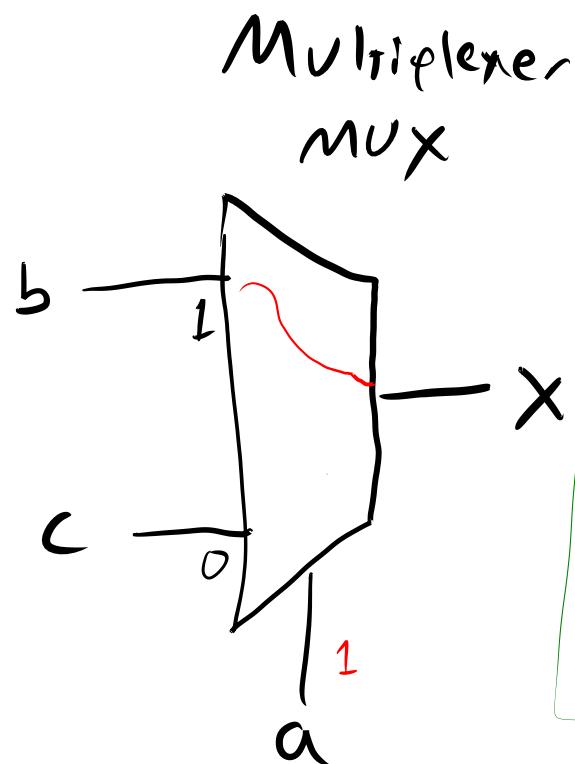

$$x = \begin{cases} !a \& !b \& c \\ (!a \& b \& c) \\ (a \& b \& !c) \\ (a \& b \& c) \end{cases}$$

