

Skills:

- ① Design an adder.

Add two binary
Constrain we only want to use logic operations

Table the position of the binary numbers

Input 1

x_1	x_3	x_2	x_1	x_0
0	...	0	0	0

Input 2

y_4	y_3	y_2	y_1	y_0
0	0	0	0	0

Output

z_n	...	z_3	z_2	z_1	z_0
0	0	0	0	0	

Let's consider the case of add two binary number that are 1 bit long

$$x_0 + y_0$$

Let write out the truth table for this addition

x_0	y_0	z_0	c_0
0	0	0	-
0	1	1	-
1	0	1	-
1	1	0	1

Special case because the result is 10
we call this extra one the carry bit


Question can we design a circuit that outputs

 z_0

$$x_0 \oplus y_0 = z_0$$

↗
xor

could you
design

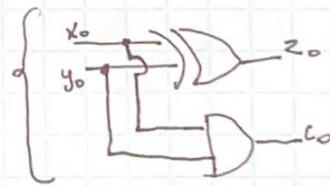

* Gate reminder

But what about the carry bit

$$x_0 \wedge y_0 = c_0$$

What about binary number that are longer than 2 bits


Consider case with two binary number

$$\begin{array}{r}
 \text{carry}^{(\text{out})} \leftarrow \text{carry} (\text{in}) \\
 \text{---} \quad \downarrow \quad \downarrow \\
 \text{c}_1 \quad \text{c}_2 \quad + 11 \\
 \hline
 \text{Example 2.1} \quad 110
 \end{array}$$

Let's write out the truth table.


c_1	x_1	y_1	z	c_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

← The case we looked from example 2.1

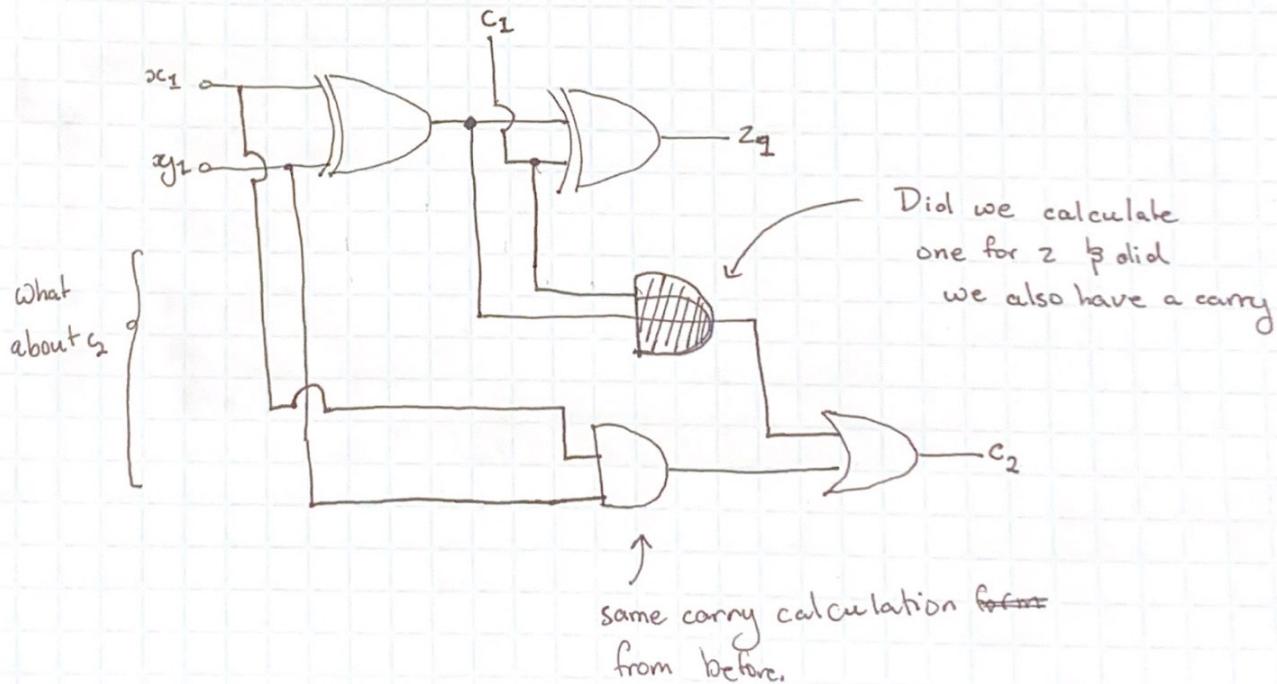


Then how do we scale to number of bits

Page 3

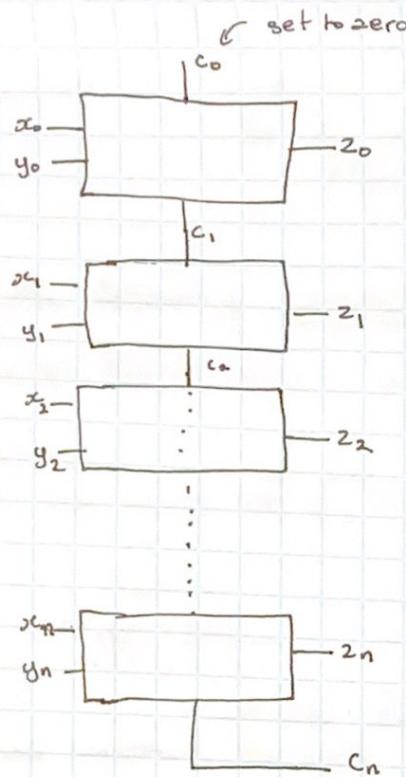

Commonly referred
to as a ripple carry adder.

Now we final have
our adding box

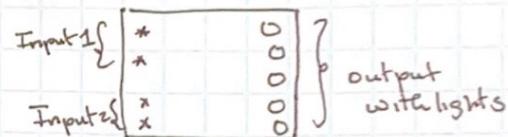

- * review of ~~two~~ bitwise operators, ↗ Masking

- * Maybe sum bit puzzles.

2. Operators.

8 Bitwise and

1 Bitwise or

\wedge Bitwise and.

\gg Bitwise to the right no sign extension

\ll Bitwise shift to the left no sign extension.

Masking

$\begin{array}{r} 001110000 \\ \sqcup \end{array}$ construct a sequence of one or zero
that you can use to extract or
flip information / binary values

Consider the following examples.

$x = 110111 \leftarrow$ Set the forth bit of this number to one

$x | 0010000$
 \leftarrow we could ~~use~~ ^{or} ~~with~~ the following mask,

$$\begin{array}{r} 110111 \\ \text{or } 001000 \\ \hline 111111 \end{array}$$

\leftarrow we've set the forth bit to one.

How could we construct the mask

~~001000~~

• ↓

~~1 << 4~~

$x |= 1 << 4 \leftarrow$ Set the forth bit of x to one

$$x = x | 1 << 4$$

Clear (we normal use ands)

$x = 1111$

~~1111~~ clear the first, third and forth bits

~~we could do that by anding with 0010~~

$$\begin{array}{r} 1111 \\ \wedge 0010 \\ \hline 0010 \end{array}$$

$$x \&= 1 << 1$$

Clear (and)

$x = 1111$ clear just the second bit

we could and with 1101

$$\begin{array}{r} \text{---} \\ 1101 \\ \wedge 1111 \\ \hline 1101 \end{array}$$

↑ just clears the second bit

How do we create
the mask 1101

$$y = 0001$$

$$y \ll 1 = 0010 \leftarrow y \ll 1$$

$$\sim y = 1101 \leftarrow \sim y \text{ (not of } y\text{) write } \sim y \text{ inc.}$$

Use or to set
Use and to clear

But how would you flip.

$$\begin{array}{l} 1101 \rightarrow 1111 \\ 1111 \rightarrow 1101 \end{array}$$

} Think about this for a second.

$$\text{mask} = 0010$$

$$x = 1101$$

$$x \wedge \text{mask} = 1101$$

$$\begin{array}{r} \oplus 0010 \\ 1111 \\ \hline \text{flipped} \end{array}$$

$$\text{mask} = \cancel{1001}$$

$$\text{mask} = 0010$$

$$x = 1101$$

$$x \wedge \text{mask} = 0010$$

$$\begin{array}{r} \oplus 1111 \\ 1101 \\ \uparrow \\ \text{flipped} \end{array}$$

Parity bit

01101~~1~~

even odd.

0 1

~~even parity number~~

parity { 0 if even number of 1
 1 if odd number of 1

parity = 0

repeat 32



parity \wedge ($x \bmod 1$)
 $x \gg= 1$

0



1

Puzzle.

x y

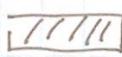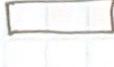$x' =$  

\ggg

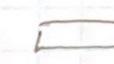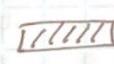
$y' =$  

\lll

or together,

⊕
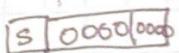
$$\begin{array}{r} *0=1 \\ \cancel{*1}=0 \end{array}$$







two complement
flip +1
add.