

Pipelining

last time

HCLRS components

- data memory
- register file

more choices

- textbook adds 0 for irmovq, you don't have to

- textbook uses 'M' port for memory results, you don't have to

building CPUs approach 1: working stage-by-stage

- systematically: what values for what instructions

- figure out what MUXes you need

- example: RSP/rA/rB for decode (register read)

building CPUs approach 2: figuring out MUXes

- textbook has a *solution* for what MUXes to use
- what lets us read/write the correct values?

SEQ: instruction fetch

read instruction memory at PC

split into separate wires:

`icode:ifun` — opcode


`rA, rB` — register numbers

`valC` — call target or mov displacement

compute next instruction address:

`valP` — $PC + (\text{instr length})$

instruction fetch

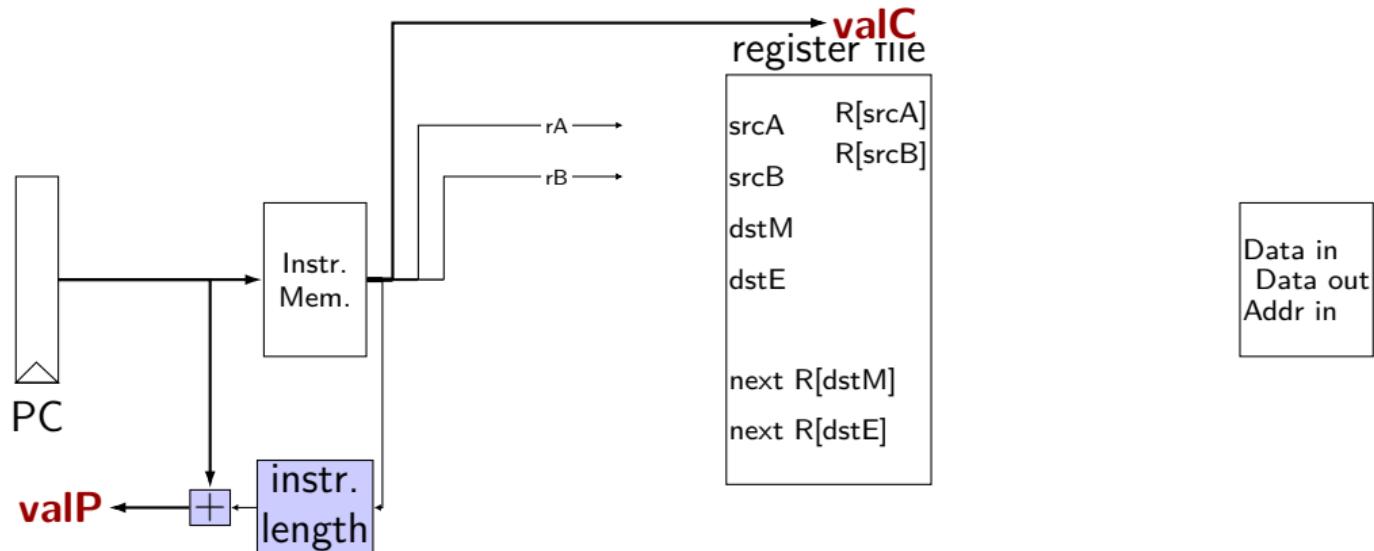


SEQ: instruction “decode”


read registers

valA, valB — register values

instruction decode (1)

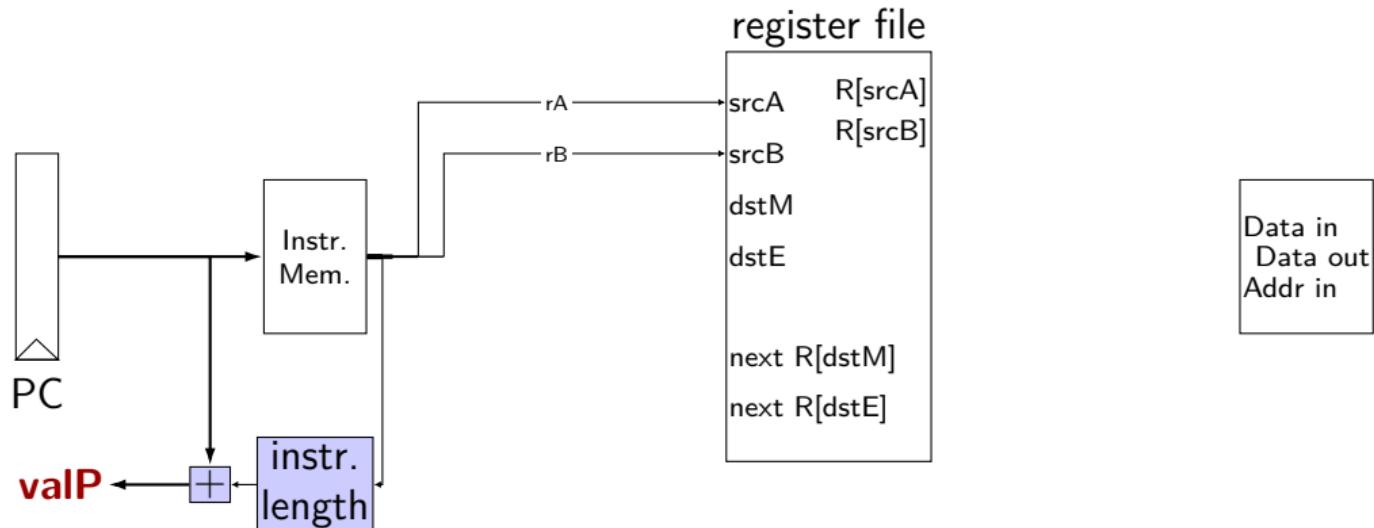

instruction decode (1)

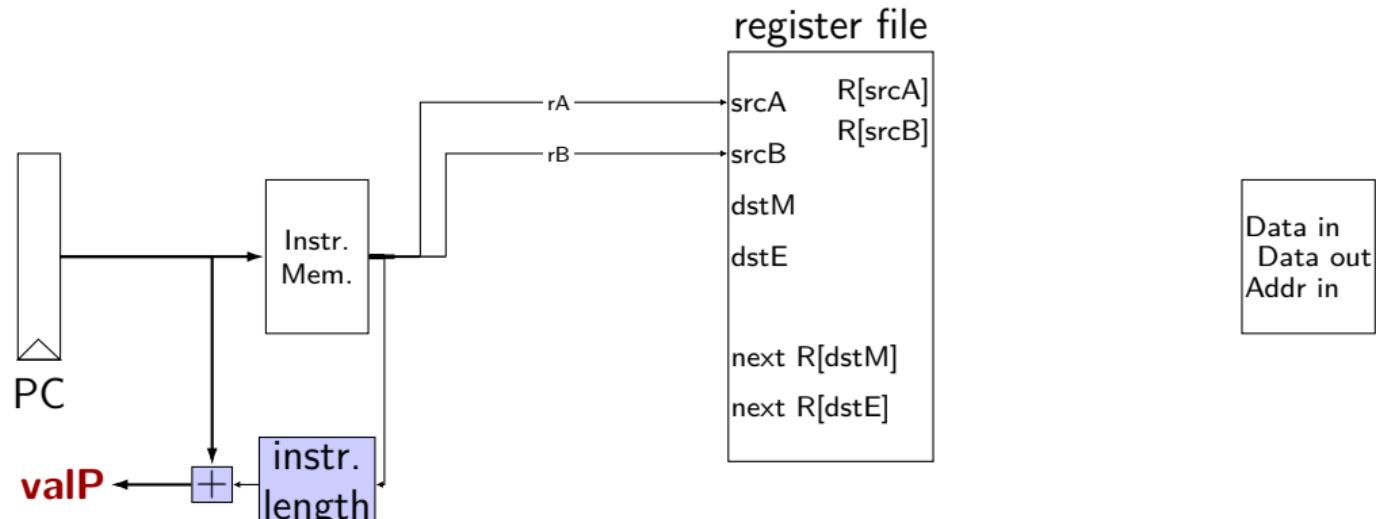

exercise: which of these instructions can this **not** work for?
nop, addq, mrmovq, popq, call,

SEQ: srcA, srcB

always read rA, rB?

Problems:


- push rA
- pop
- call
- ret

extra signals: srcA, srcB — computed input register

MUX controlled by icode


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmoveCC, rrmovq	rA	none
mrmmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

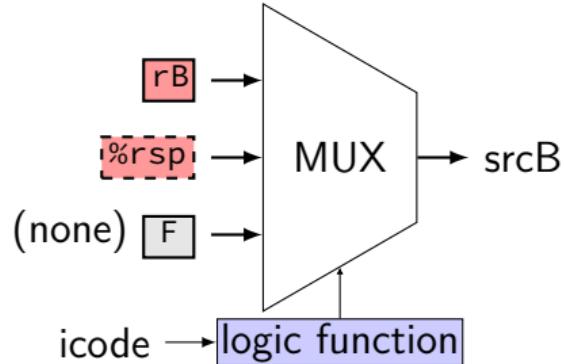


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmoveCC, rrmovq	rA	none
mrmmovq	none	rB
rrmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

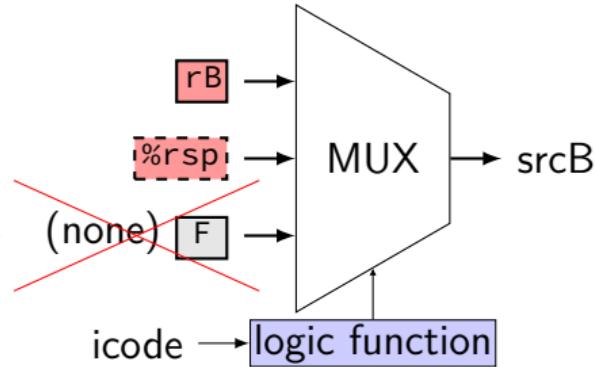

instruction decode (2)

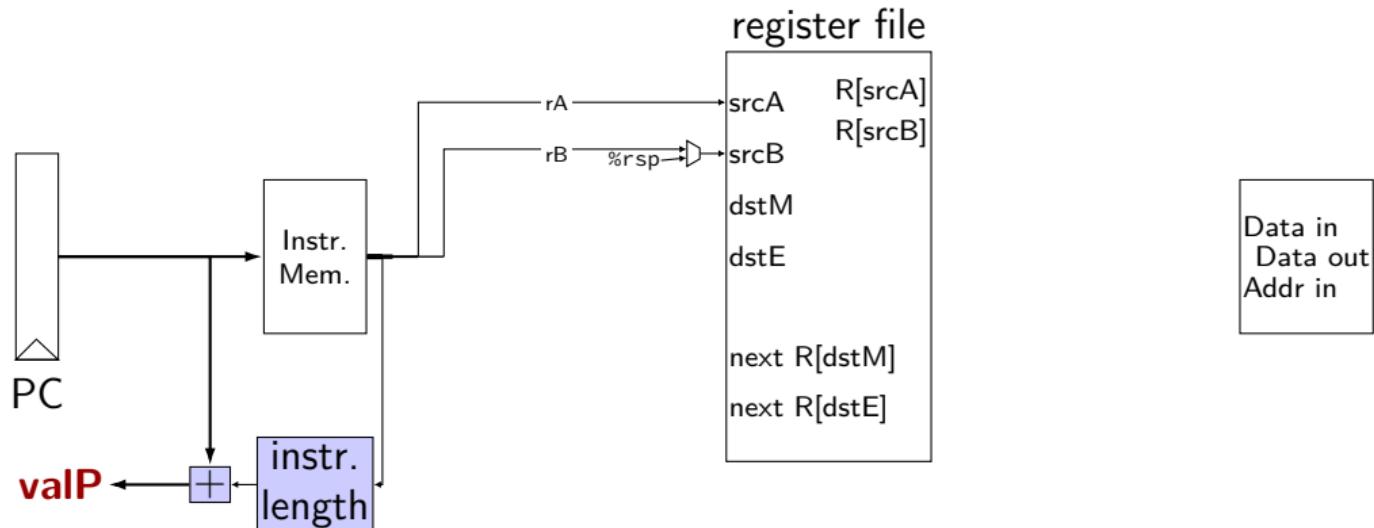

SEQ: execute

perform ALU operation (add, sub, xor, and)


valE — ALU output

read prior condition codes


Cnd — condition codes based on ifun (instruction type for jCC/cmovCC)

write new condition codes


using condition codes: cmov

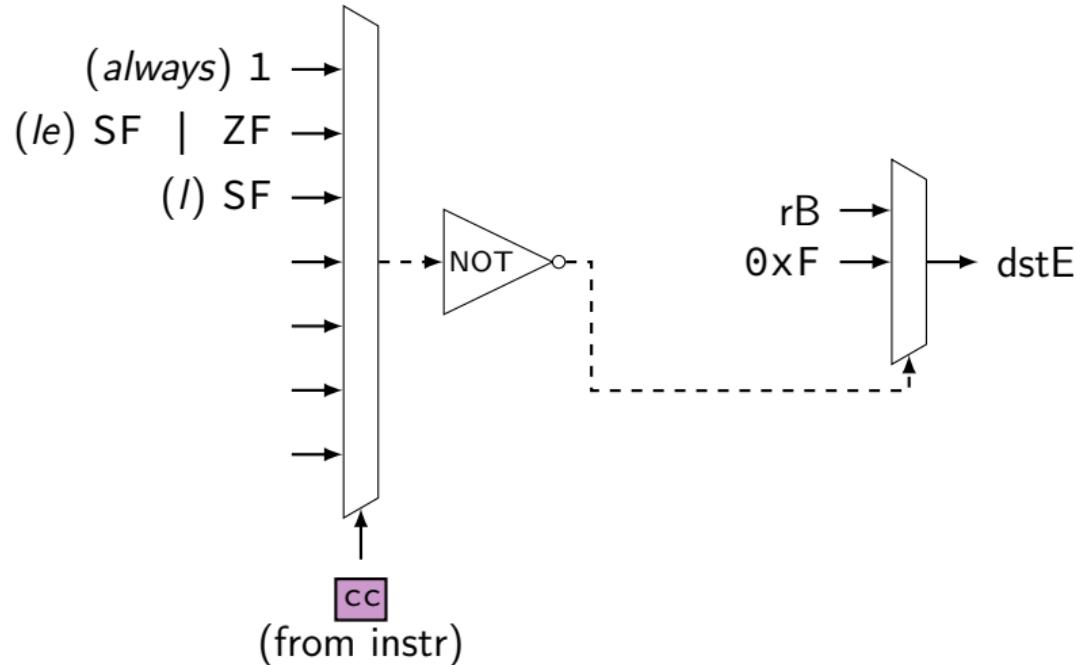

execute (1)

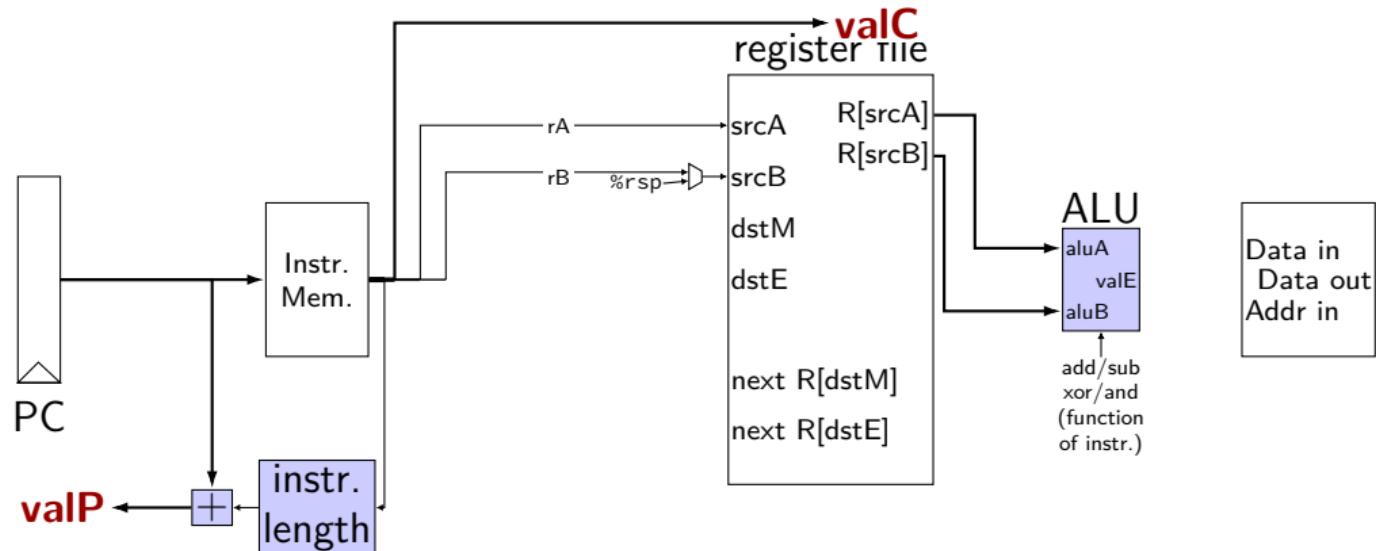

execute (1)

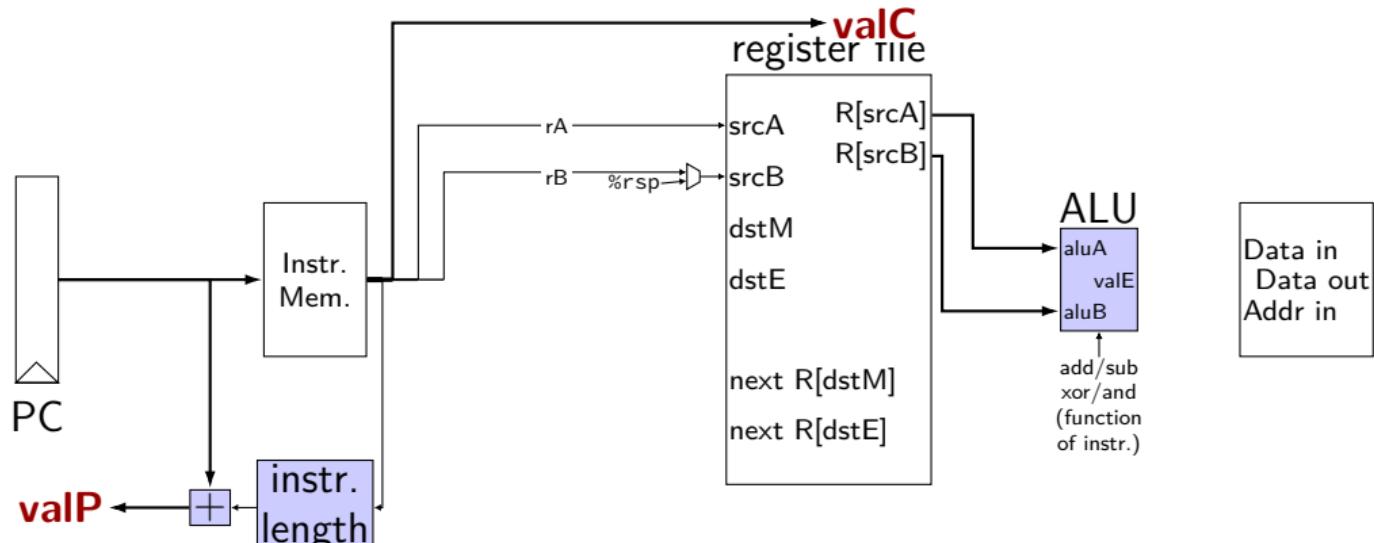


exercise: which of these instructions can this **not** work for?
nop, addq, mrmovq, popq, call,

SEQ: ALU operations?

ALU inputs always **valA**, **valB** (register values)?

no, inputs from instruction: (Displacement + rB)

mrmovq
rmmovq

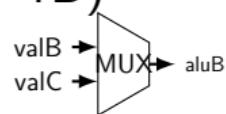


no, constants: (rsp +/- 8)

pushq
popq
call
ret

extra signals: **aluA**, **aluB**

computed ALU input values

execute (2)

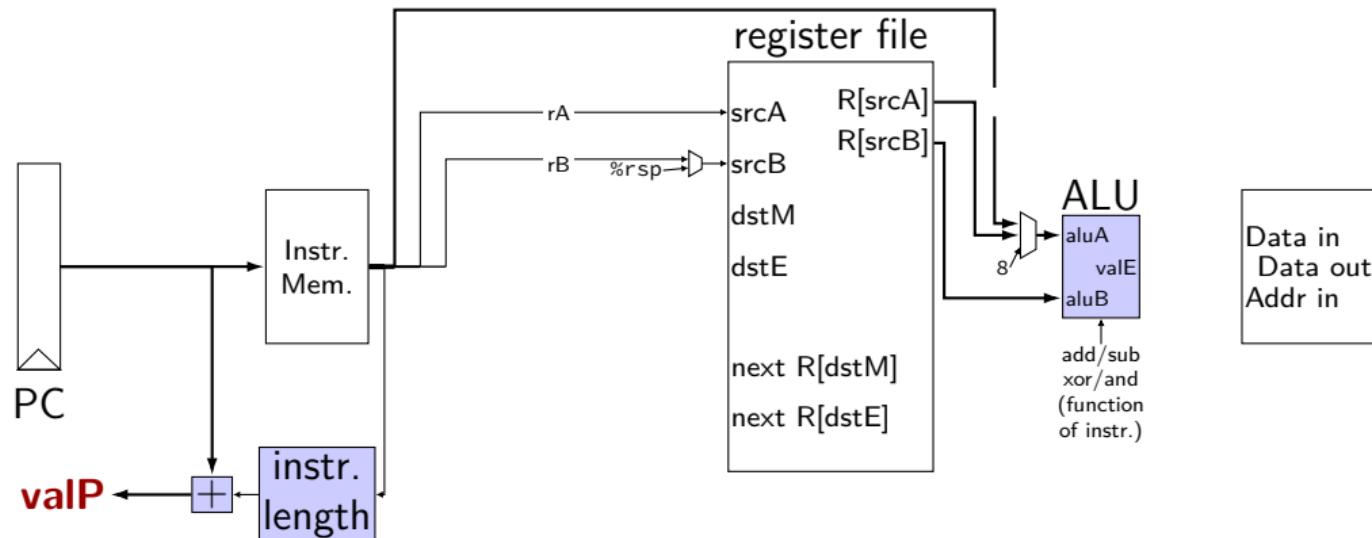


SEQ: Memory


read or write data memory

valM — value read from memory (if any)

memory (1)

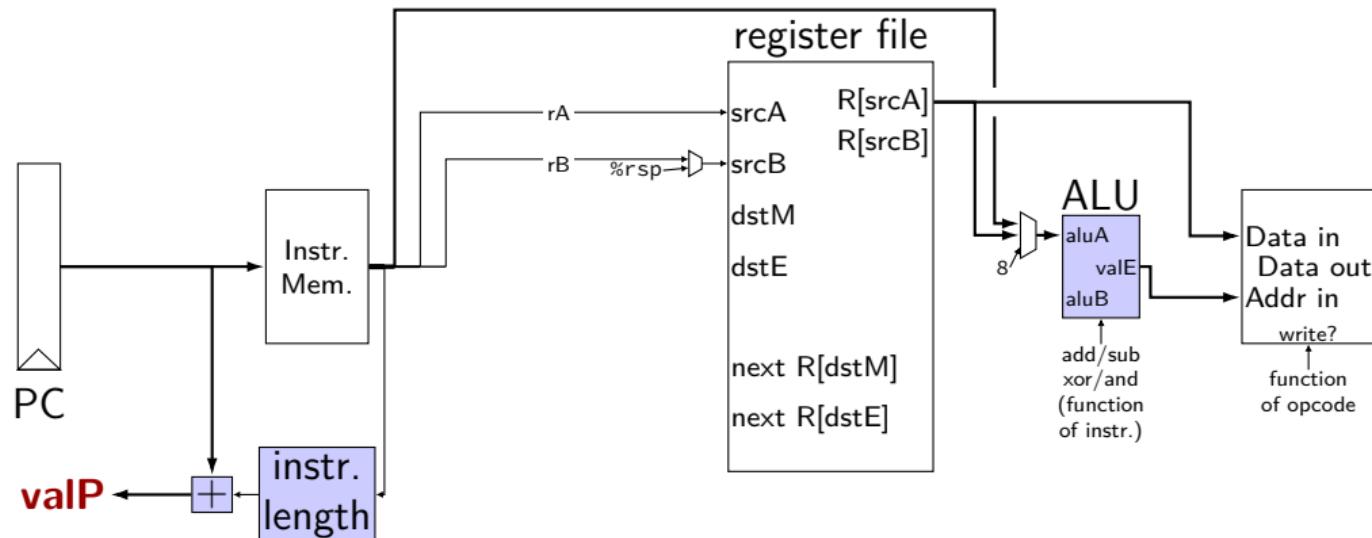

memory (1)

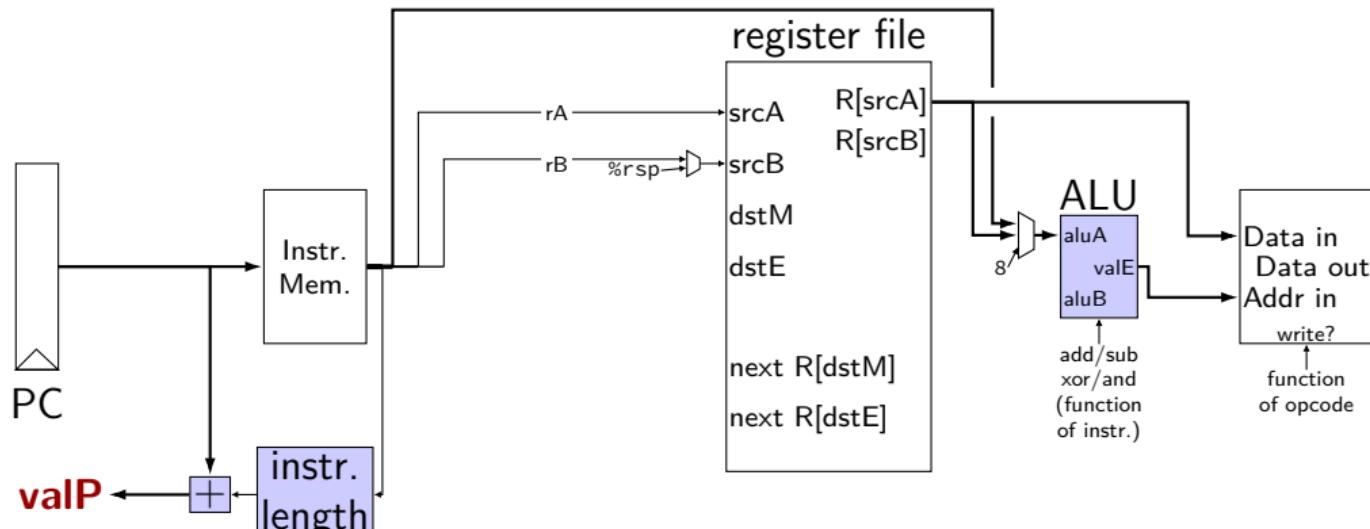

exercise: which of these instructions can this **not** work for?
nop, rmmovq, mrmovq, popq, call,

SEQ: control signals for memory

read/write — **read enable?** **write enable?**

Addr — address

mostly ALU output


tricky cases: **popq, ret**

Data — value to write

mostly valB

tricky cases: **call, push**


memory (2)

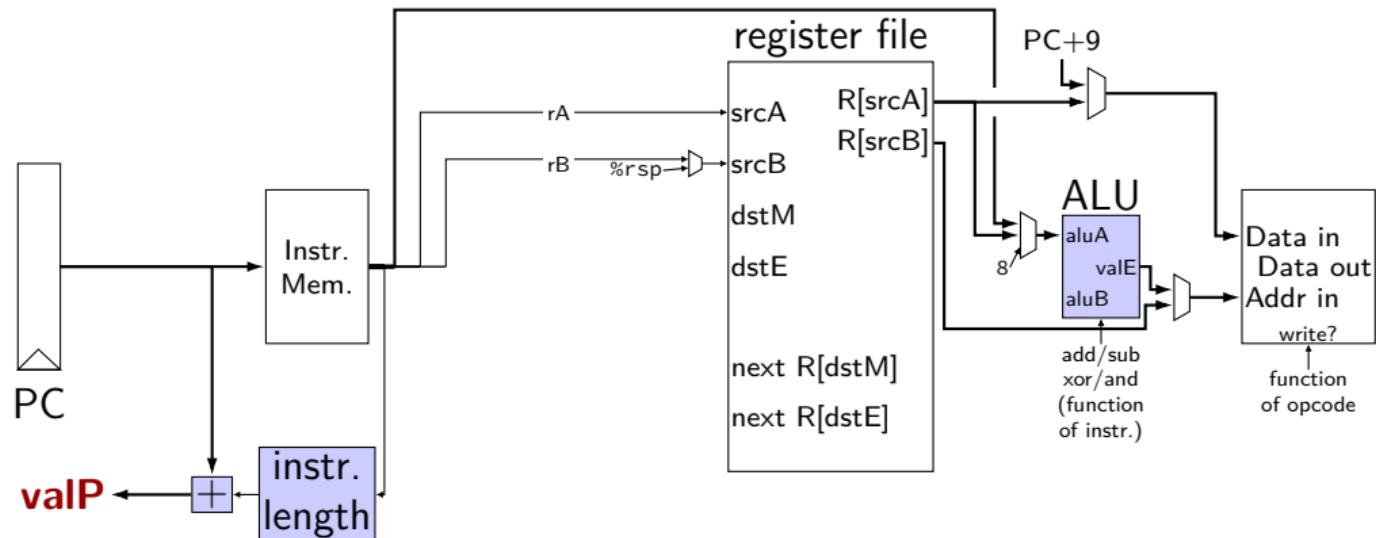


SEQ: write back

write registers

write back (1)

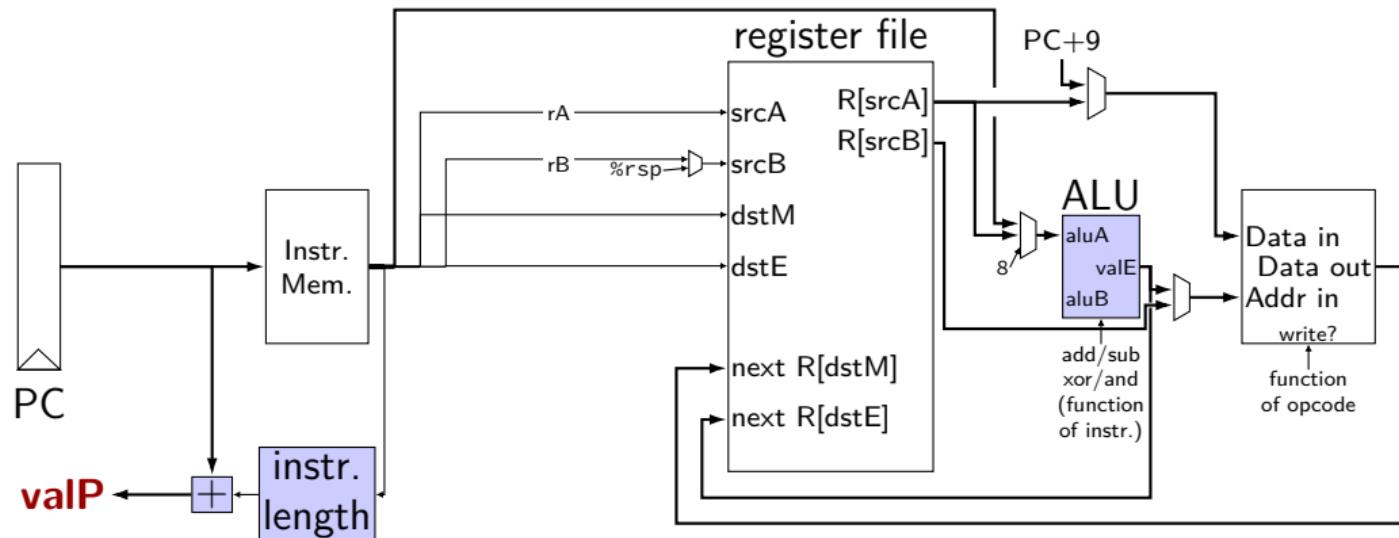

write back (1)

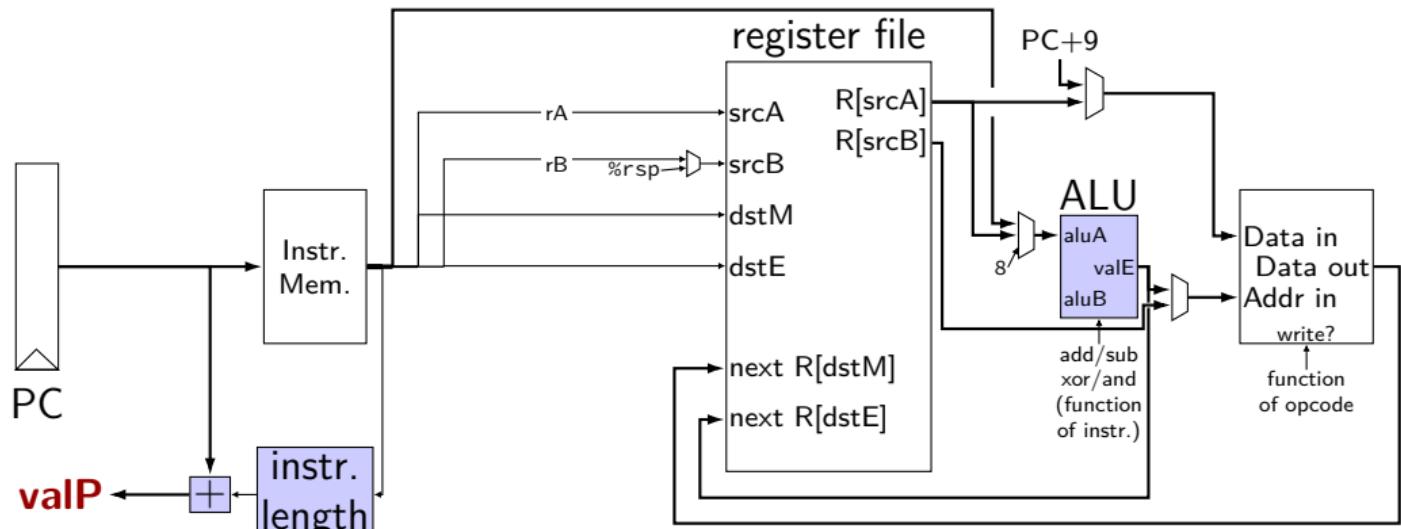


exercise: which of these instructions can this **not** work for?
nop, pushq, mrmovq, popq, call,

SEQ: control signals for WB


two write inputs — two needed by popq
valM (memory output), valE (ALU output)

two register numbers
dstM, dstE

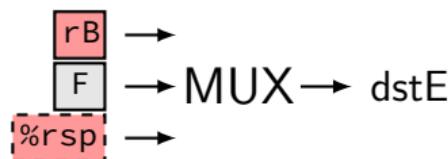
write disable — use dummy register number 0xF



write back (2a)

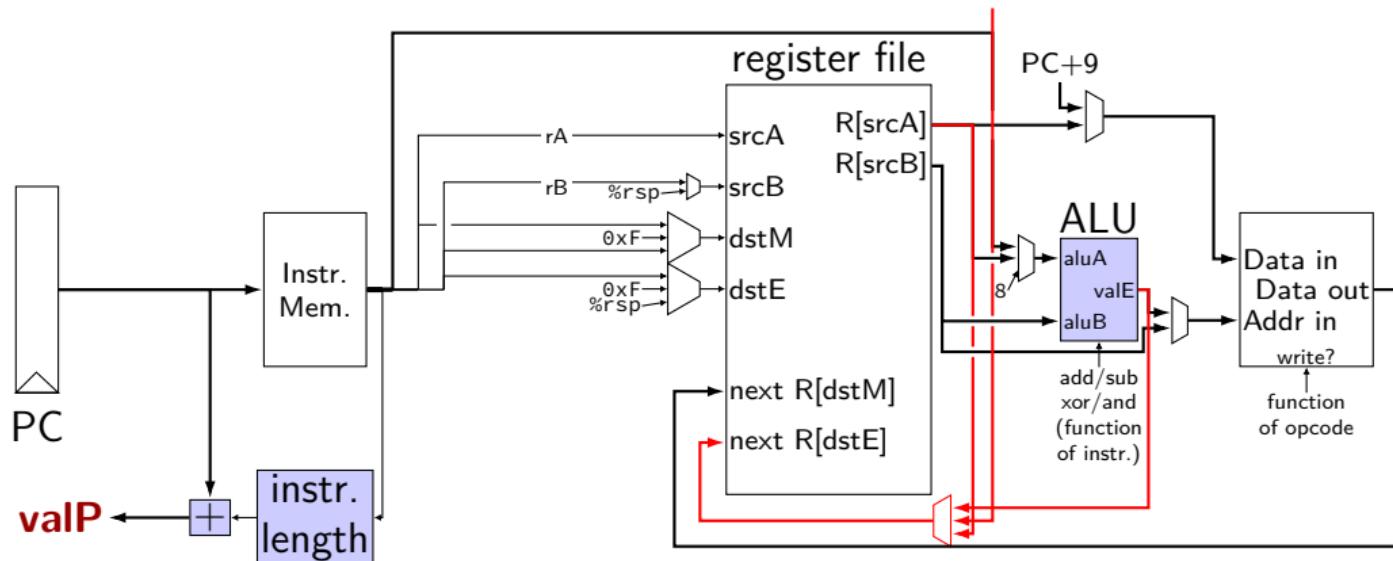

write back (2b)

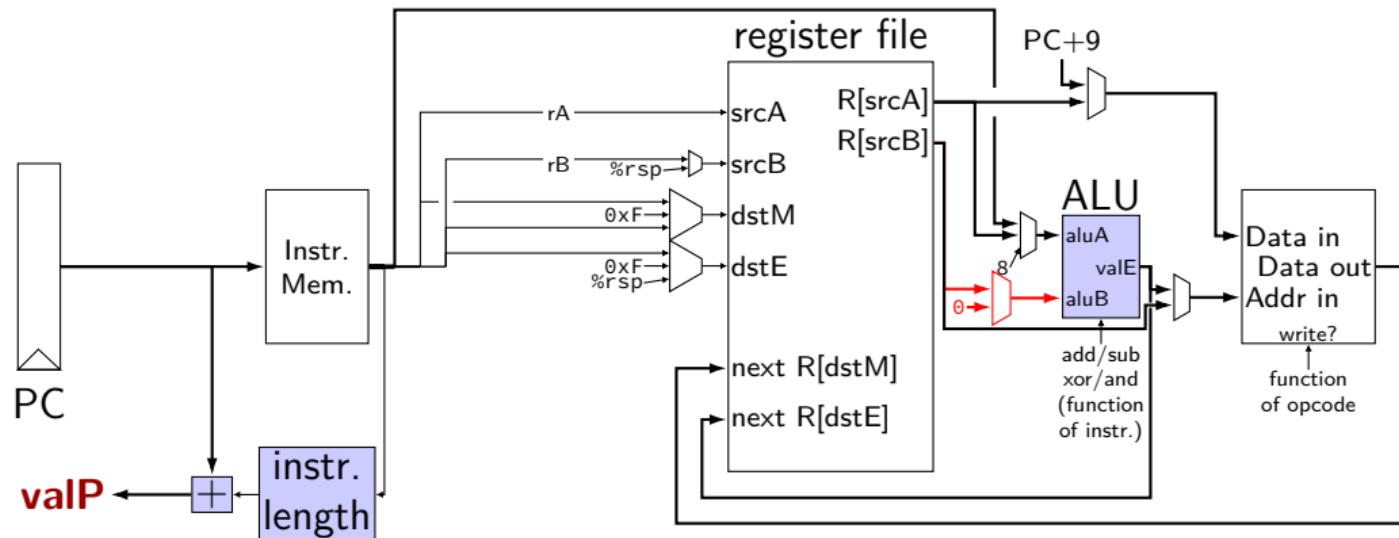


SEQ: Update PC

choose value for PC next cycle (input to PC register)


usually valP (following instruction)

exceptions: `call`, `jCC`, `ret`

PC update

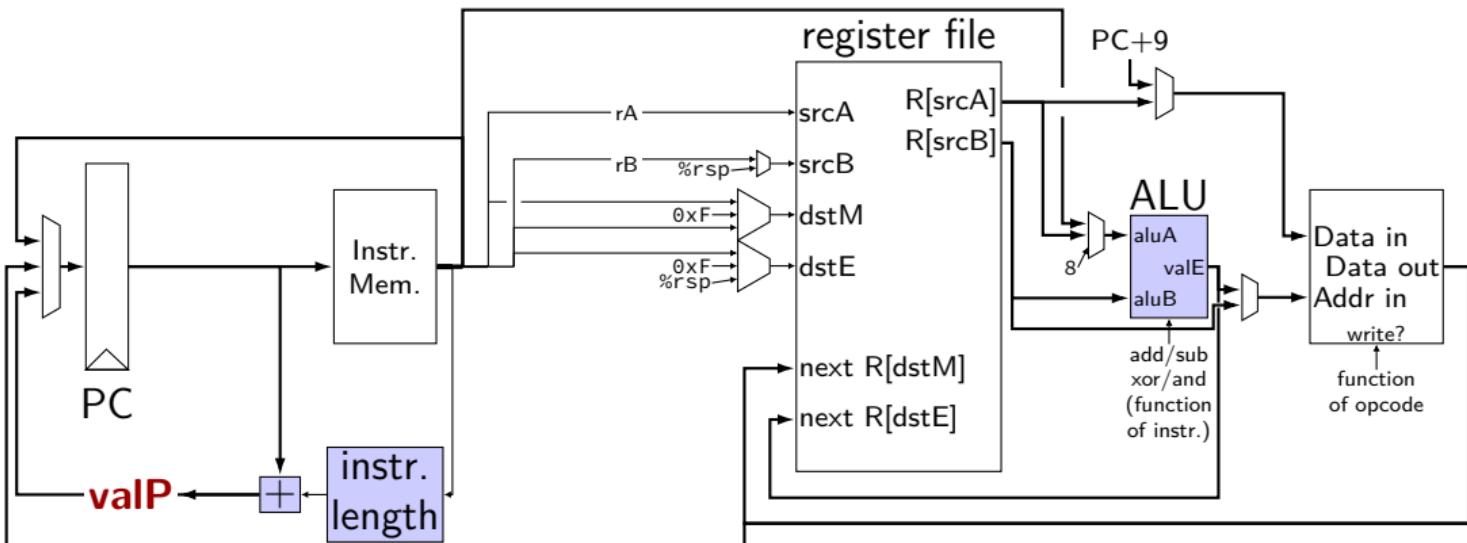


circuit: setting MUXes

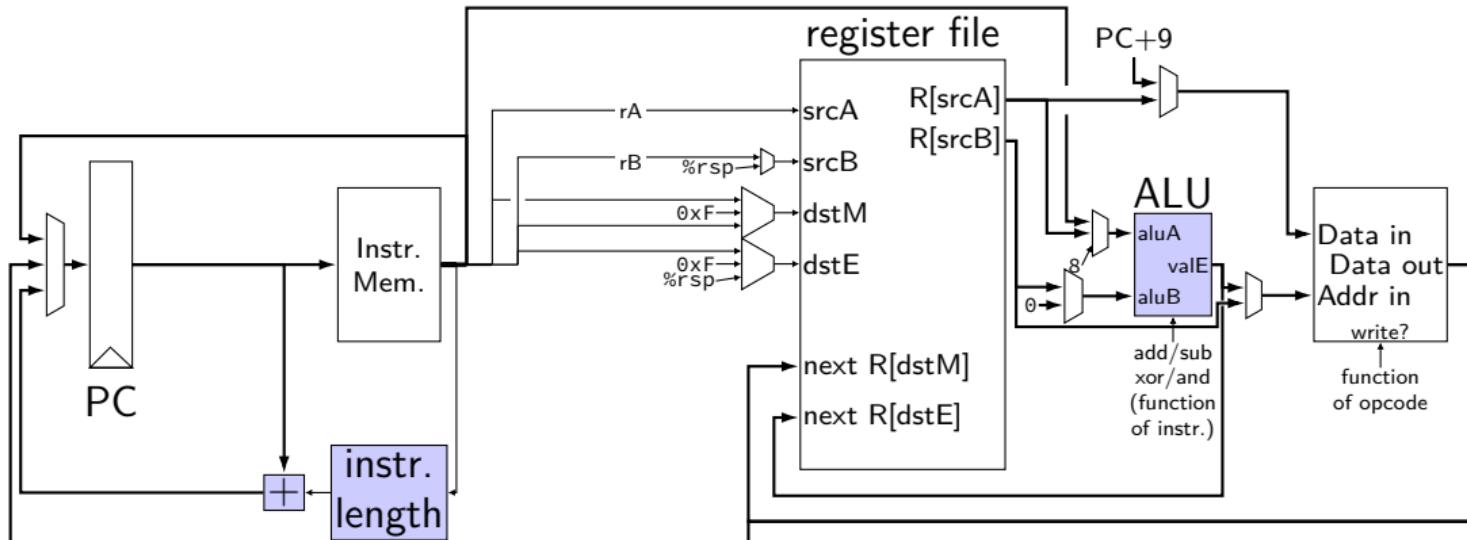


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running addq %r8, %r9?

circuit: setting MUXes

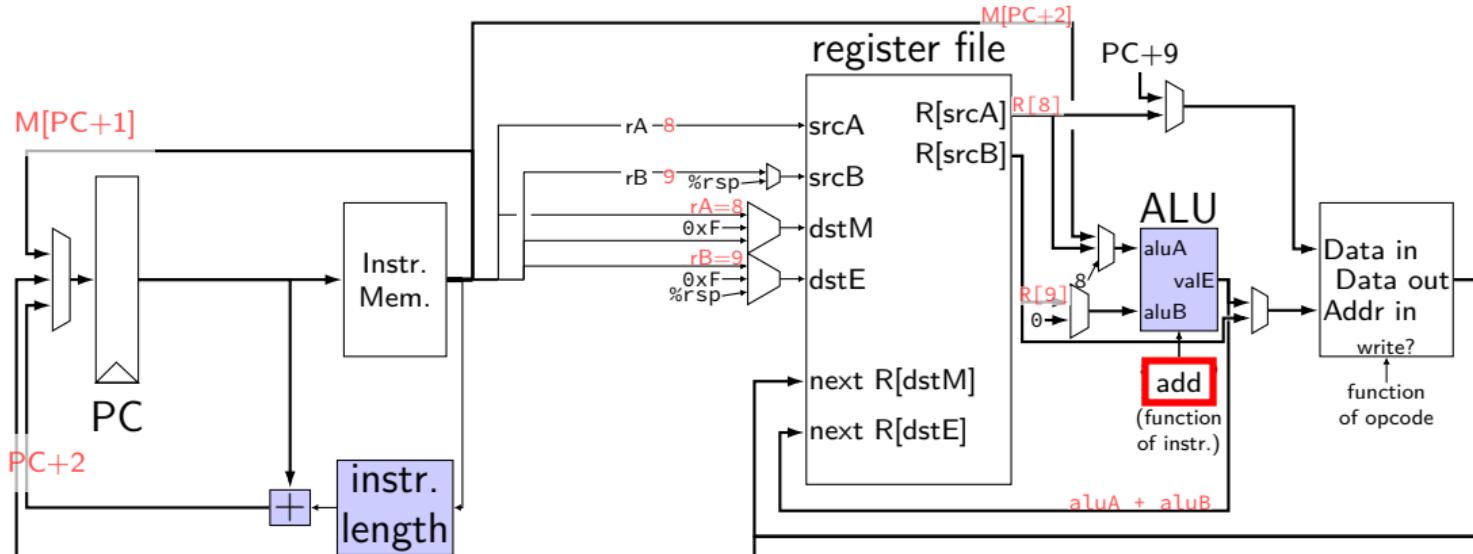


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running addq %r8, %r9?

circuit: setting MUXes

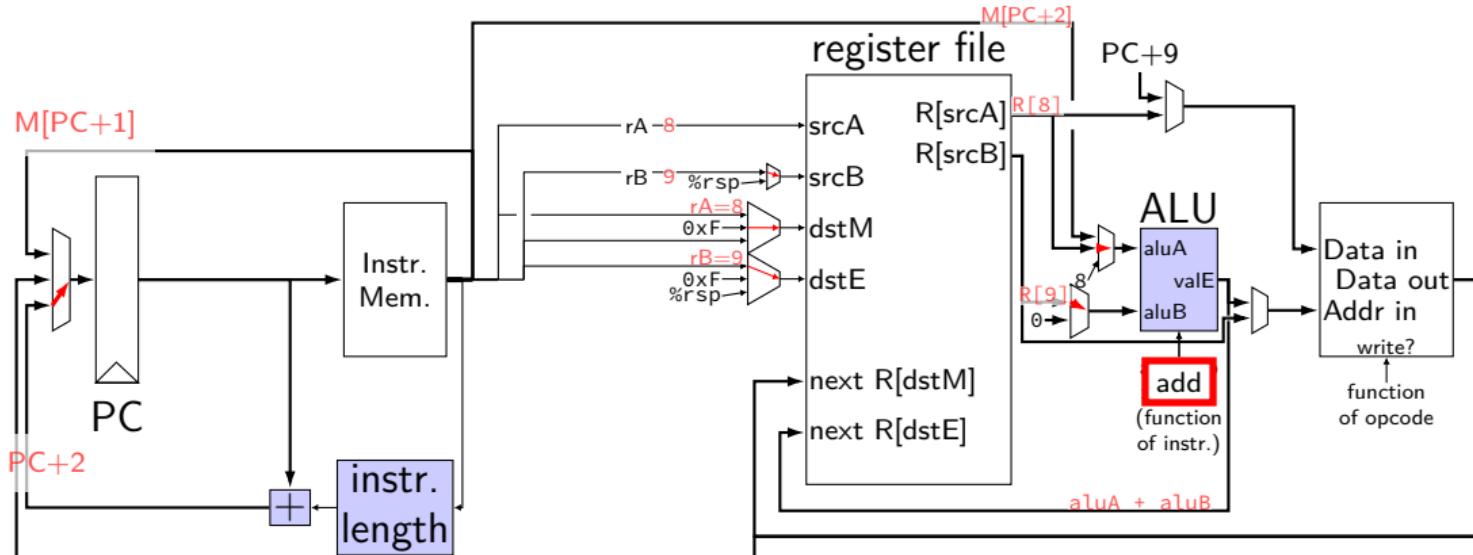


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running addq %r8, %r9?

circuit: setting MUXes

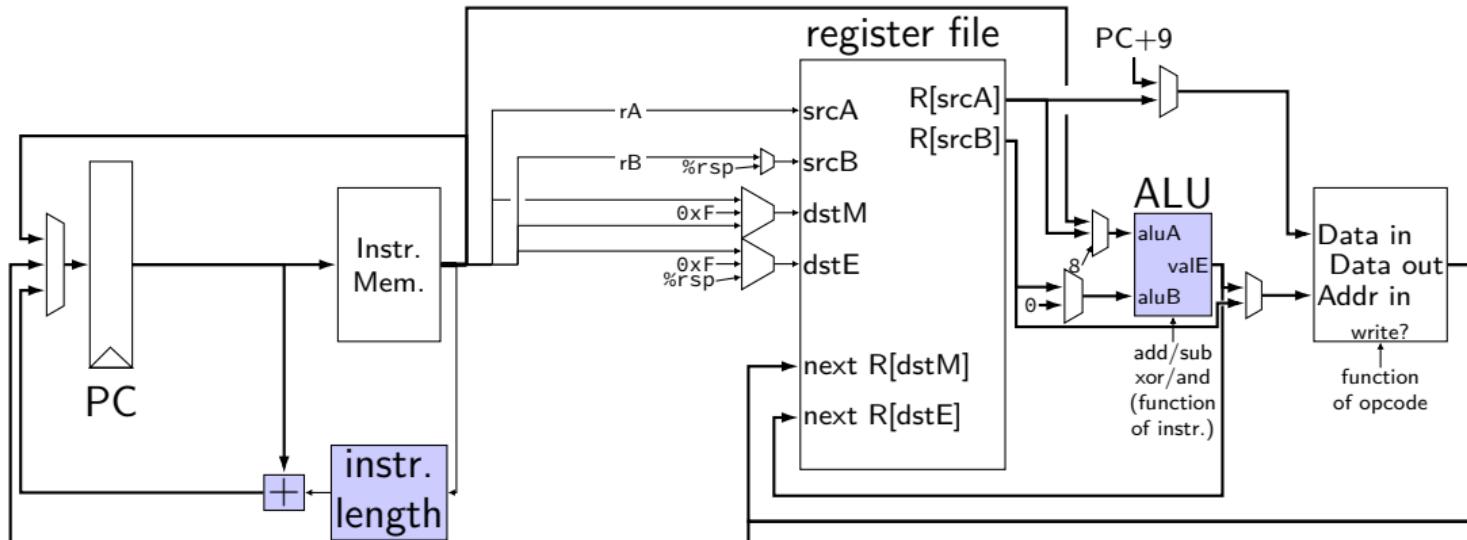


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `rmmovq`?

circuit: setting MUXes

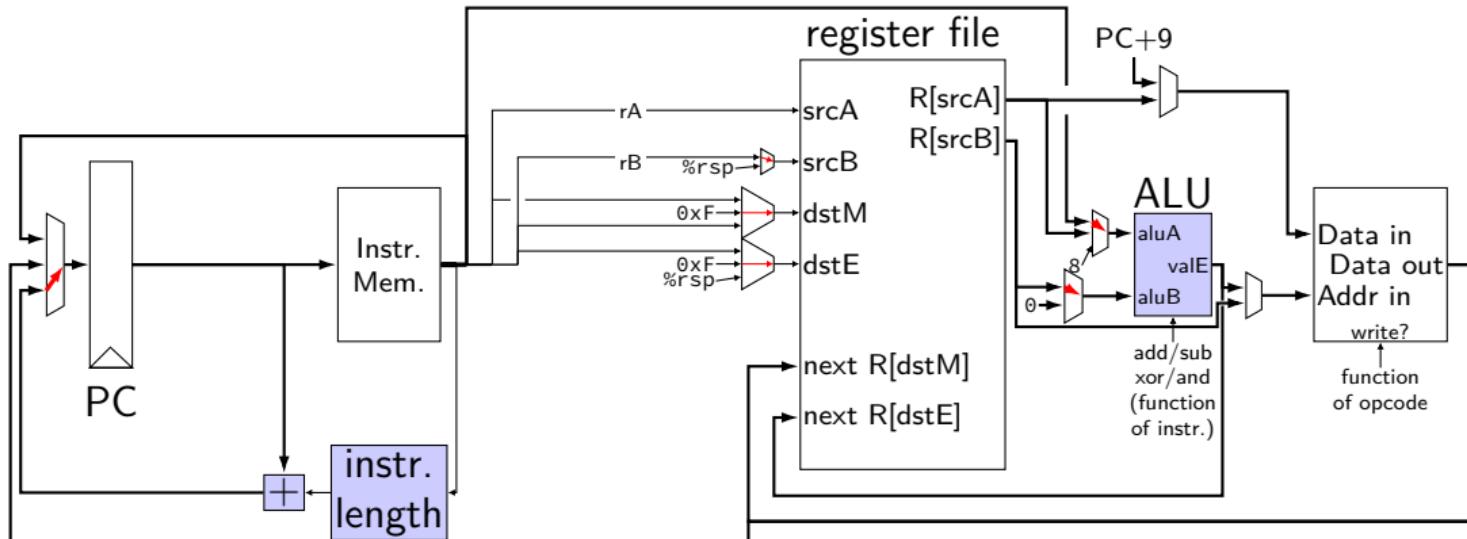


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `rmmovq`?

circuit: setting MUXes

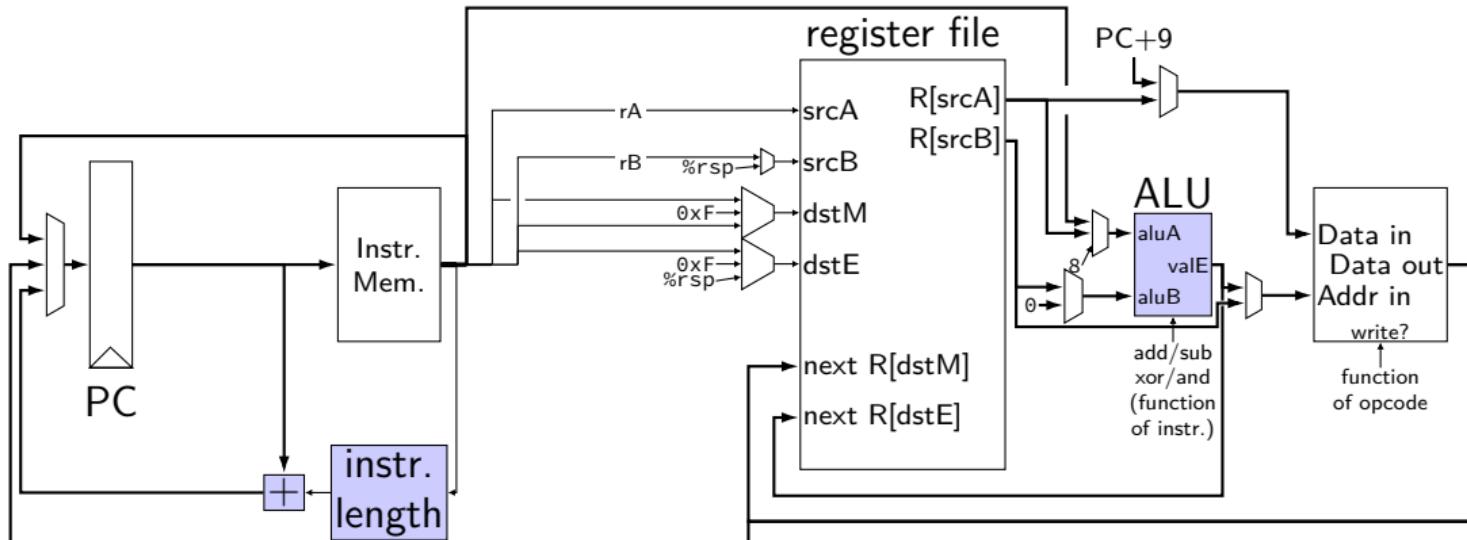


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **call**?

circuit: setting MUXes

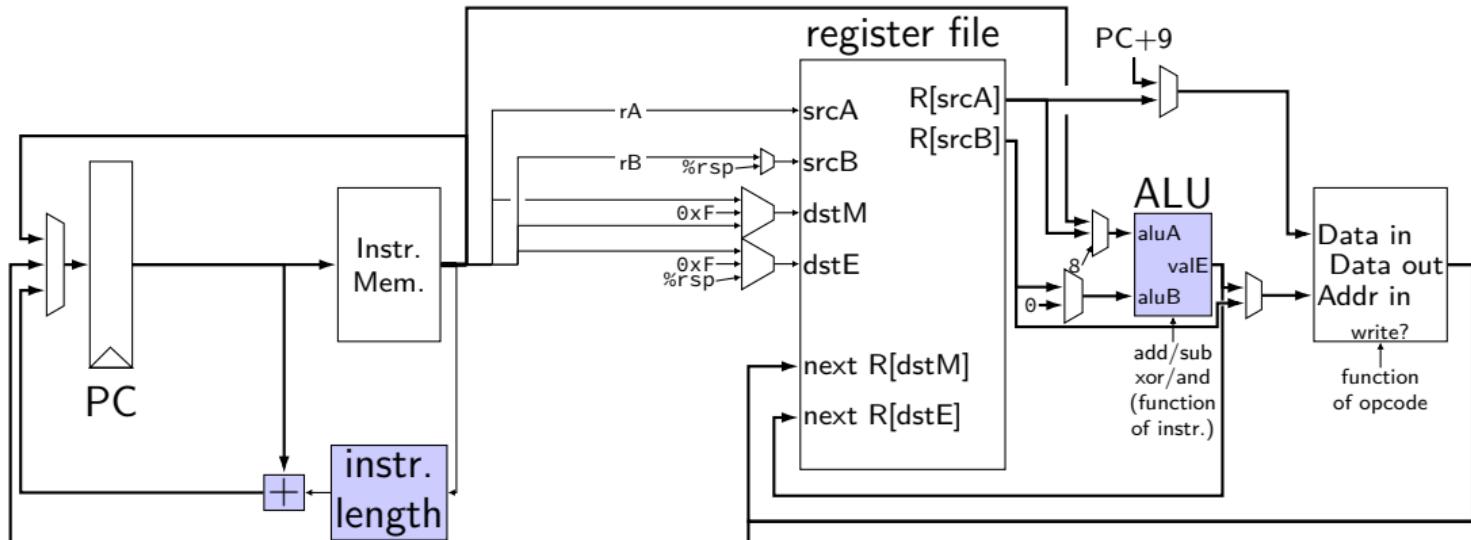


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **ret**?

circuit: setting MUXes

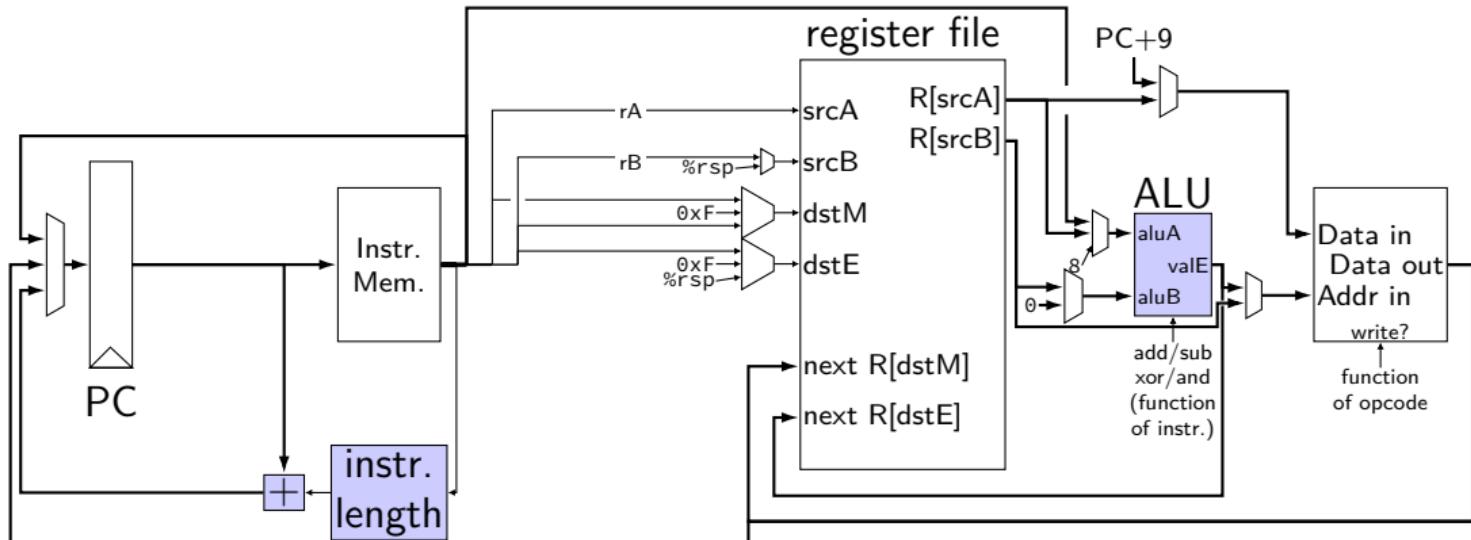


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `irmovq`?

circuit: setting MUXes


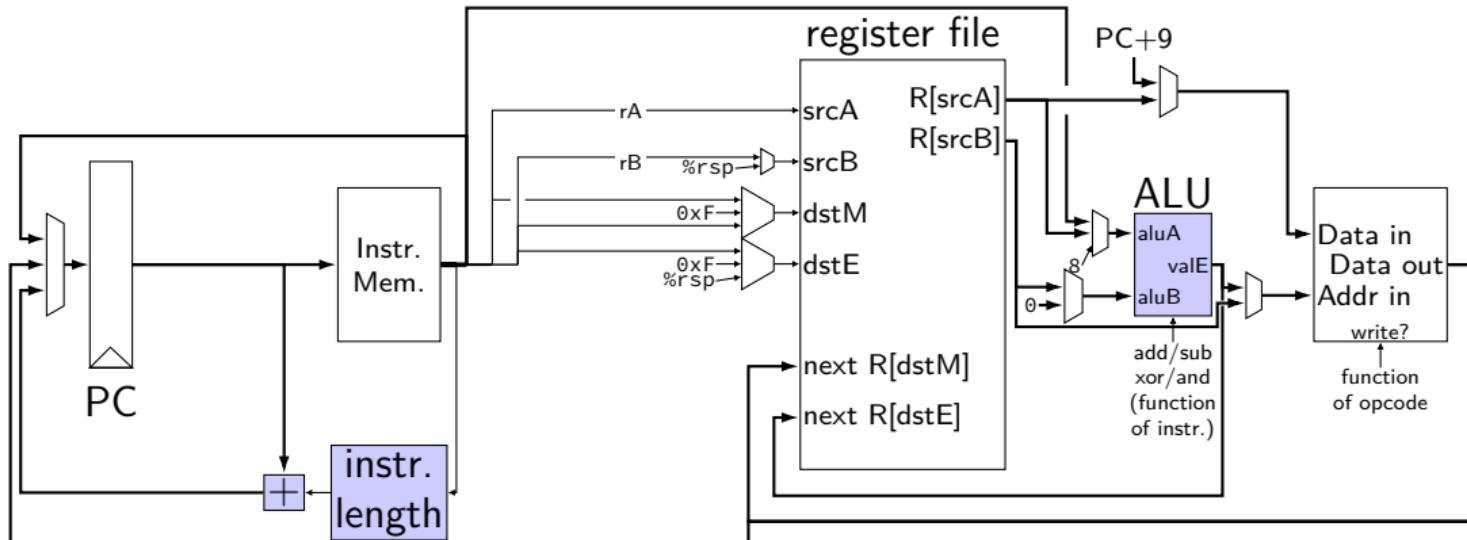


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **popq**?

Human pipeline: laundry

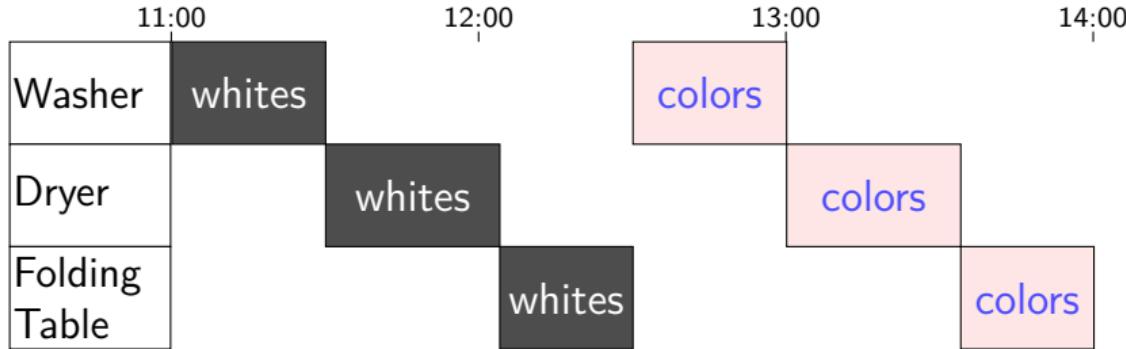


Human pipeline: laundry

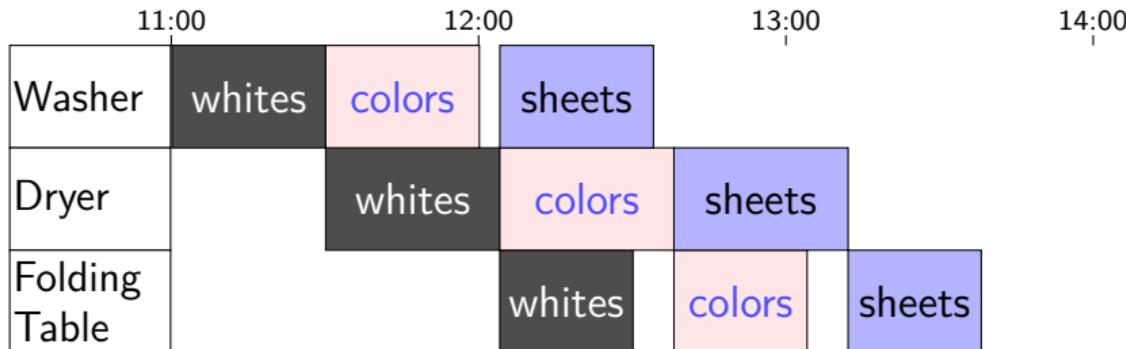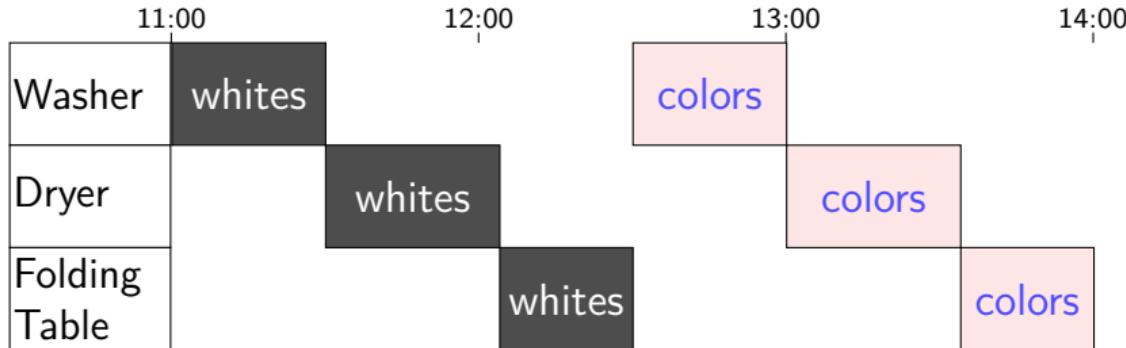


Waste (1)

	11:00	12:00	13:00	14:00
Washer	whites	colors	sheets	
Dryer		whites	colors	sheets
Folding Table		whites	colors	sheets

Waste (1)

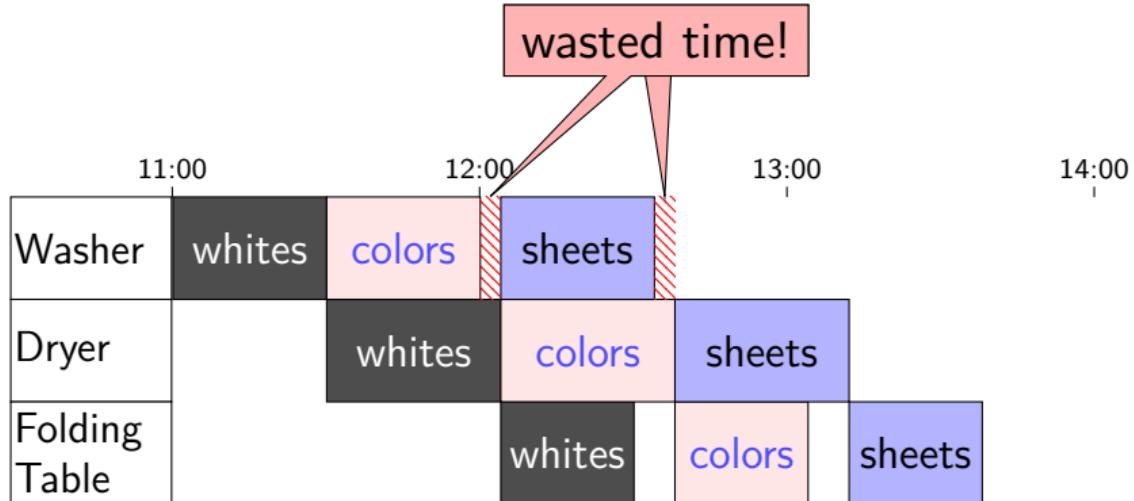


Waste (2)

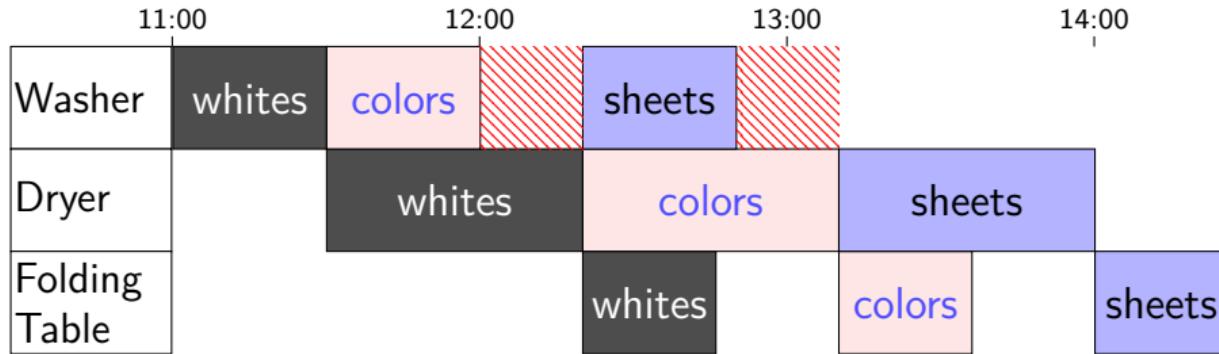


Latency — Time for One




Latency — Time for One

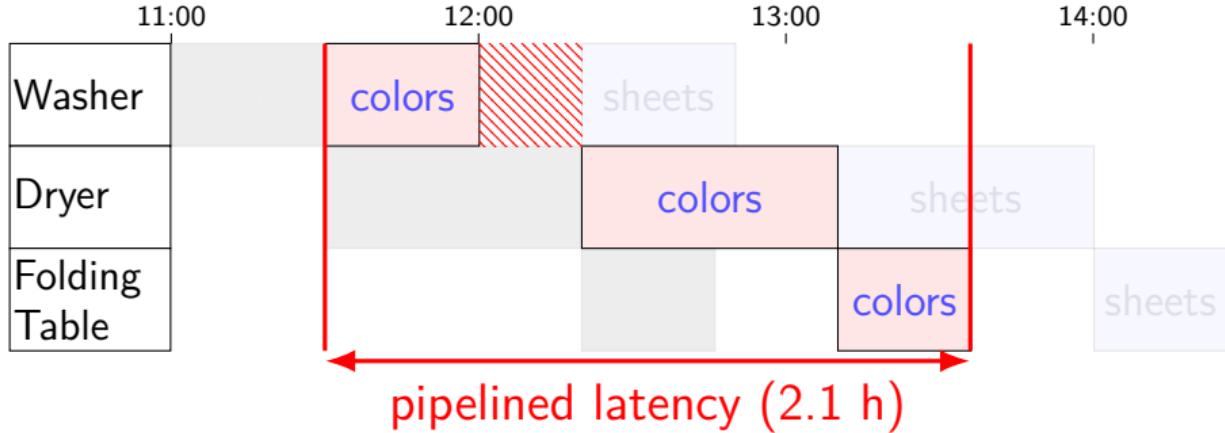


Latency — Time for One

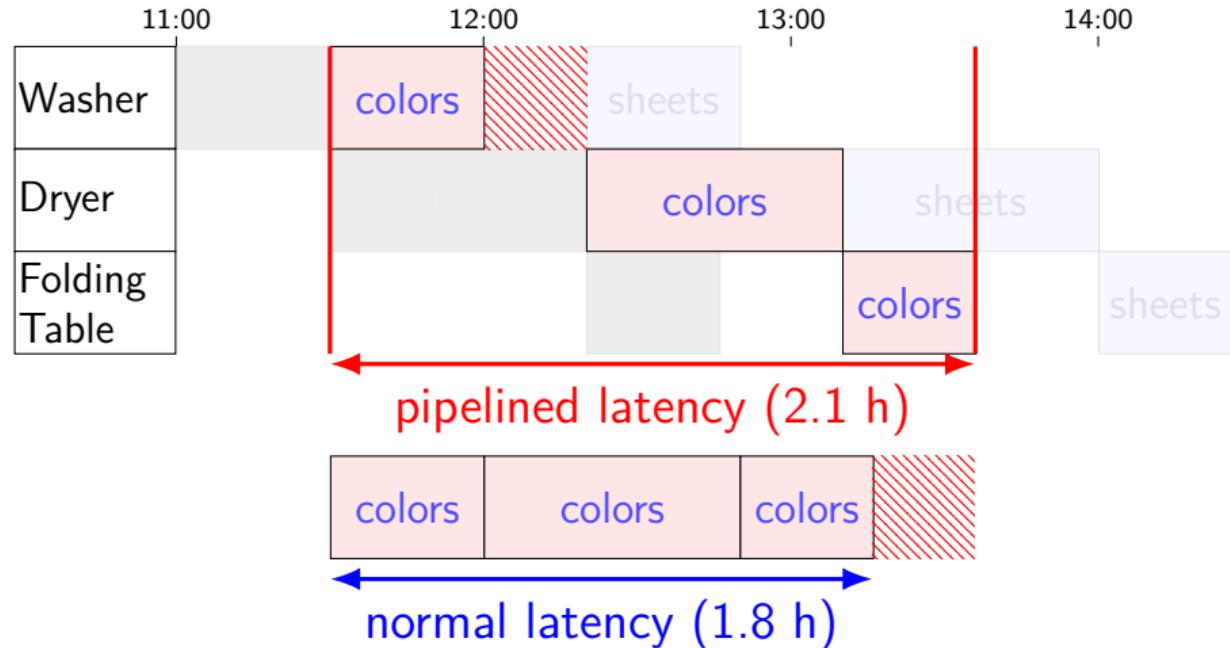

Throughput — Rate of Many

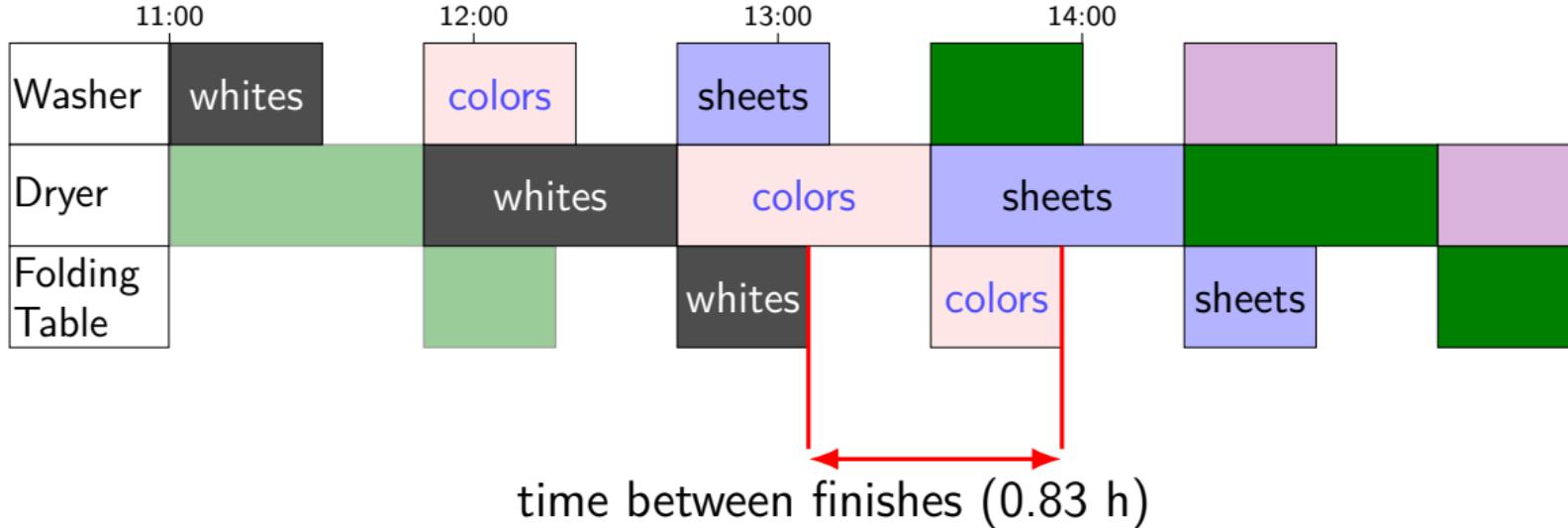


Throughput — Rate of Many

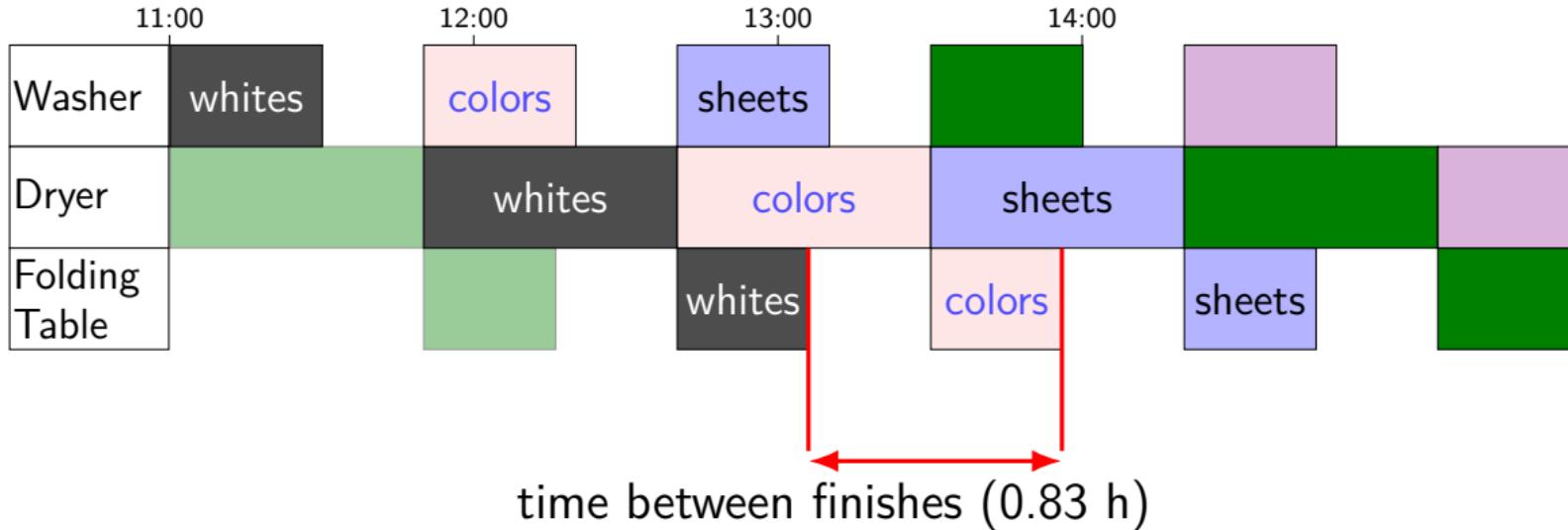


$$\frac{1 \text{ load}}{0.83\text{h}} = 1.2 \text{ loads/h}$$

Throughput — Rate of Many


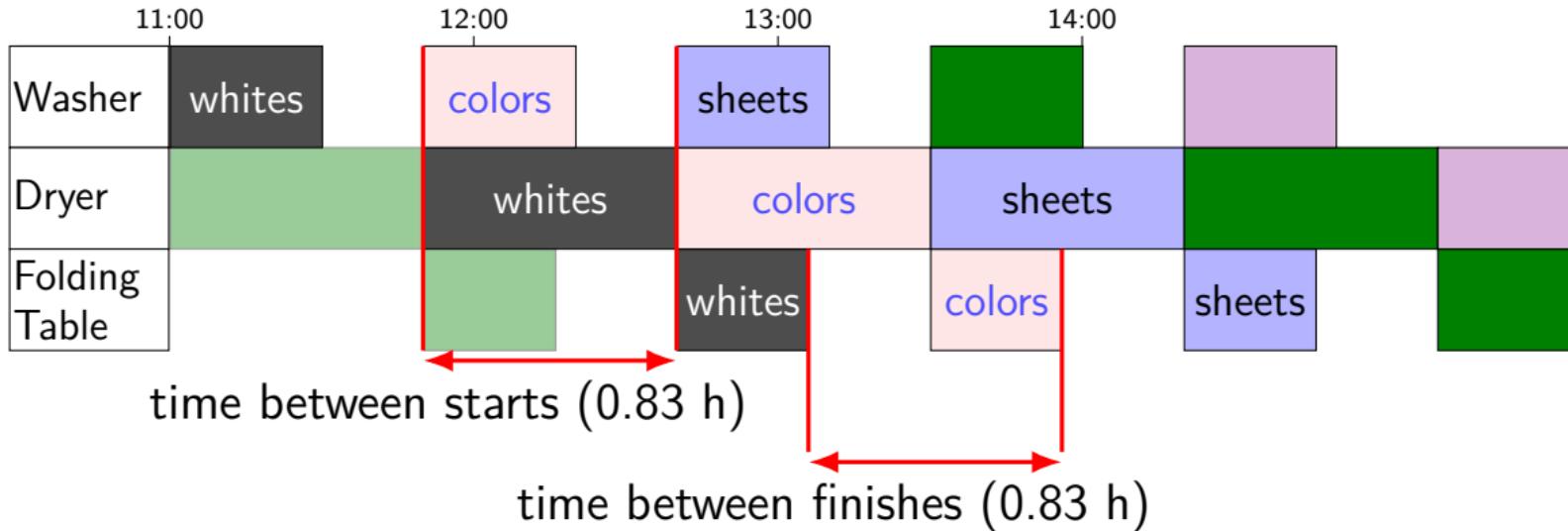


$$\frac{1 \text{ load}}{0.83\text{h}} = 1.2 \text{ loads/h}$$


times three circuit

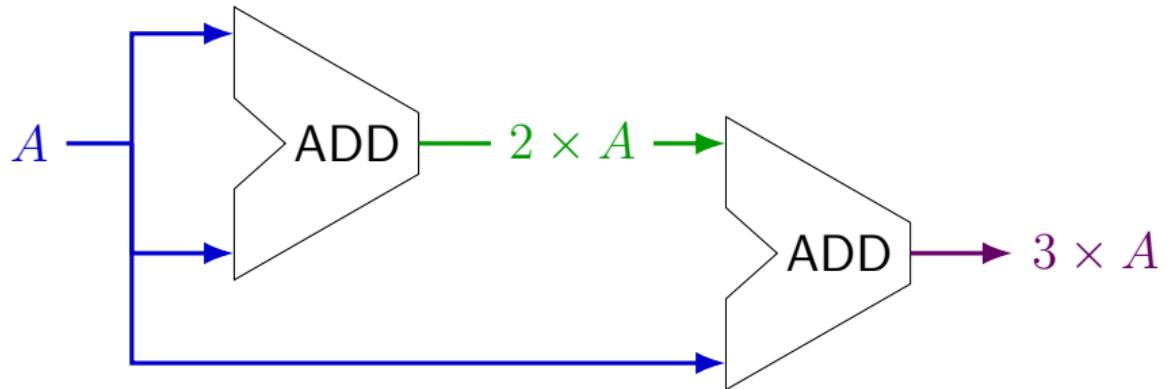


times three circuit

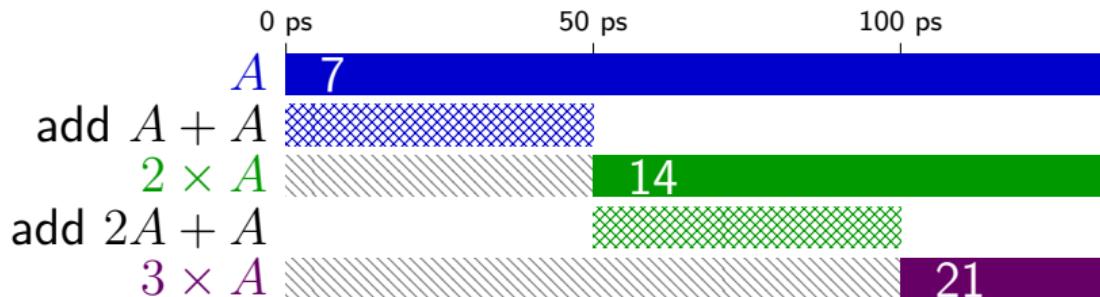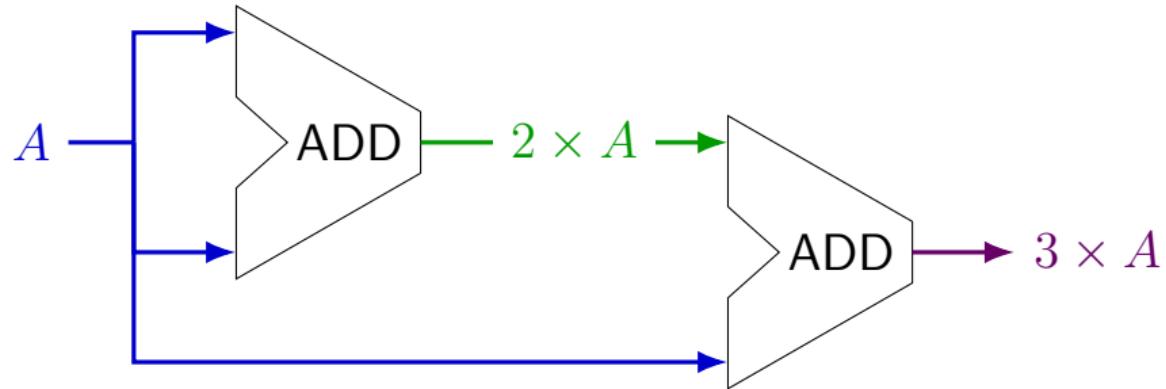


times three circuit

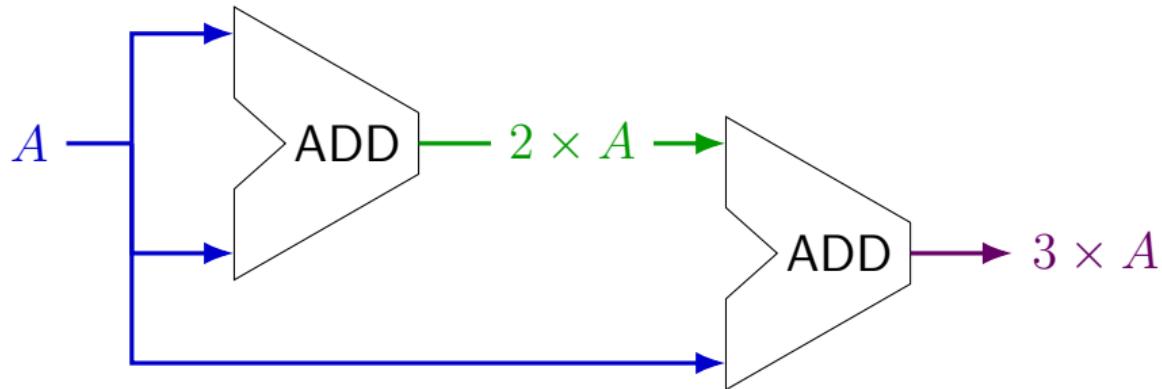


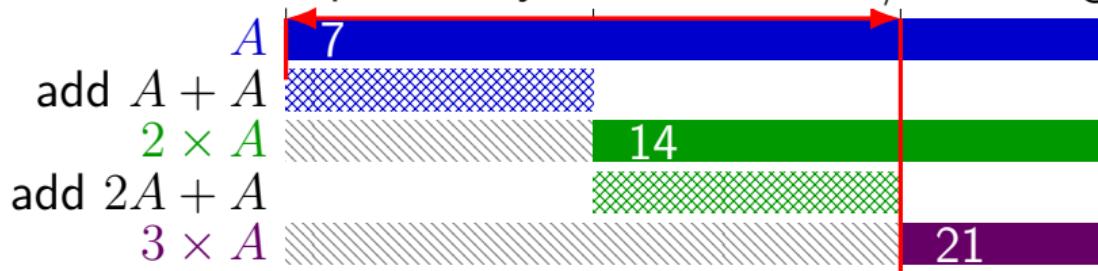
100 ps latency \Rightarrow 10 results/ns throughput




times three and repeat

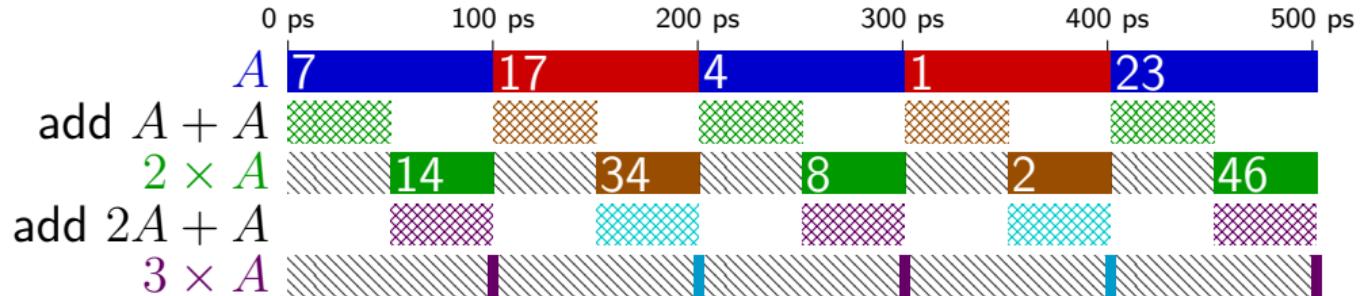


times three and repeat

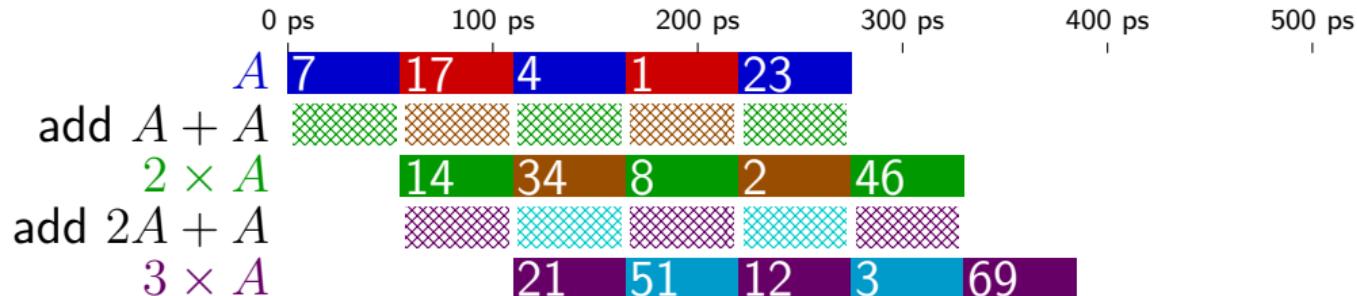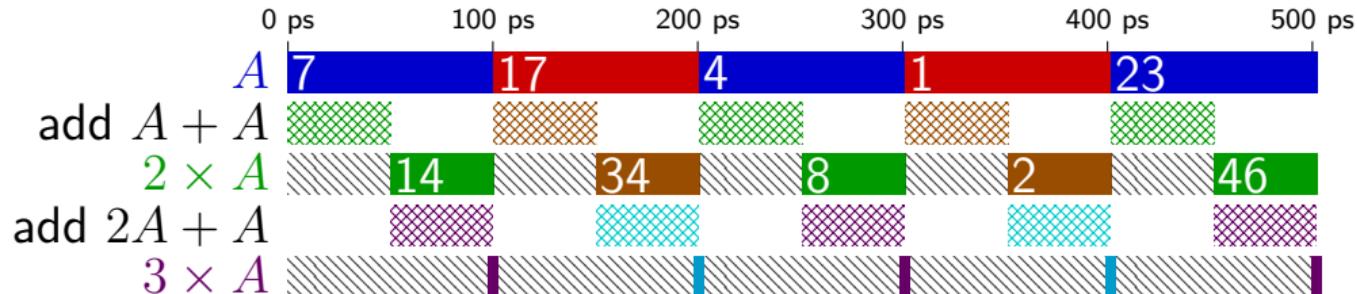

pipelined times three


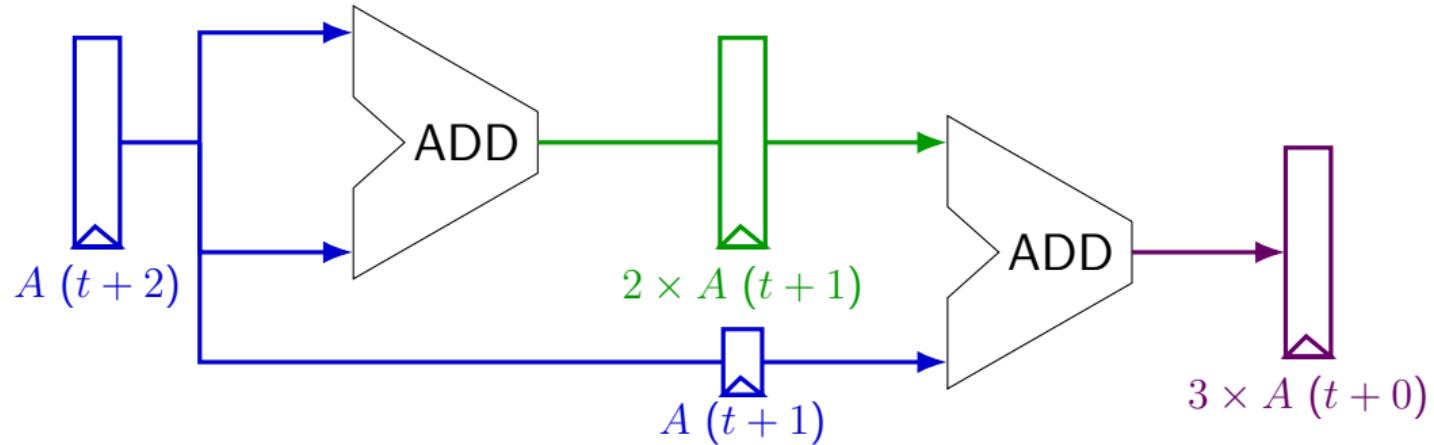


pipelined times three

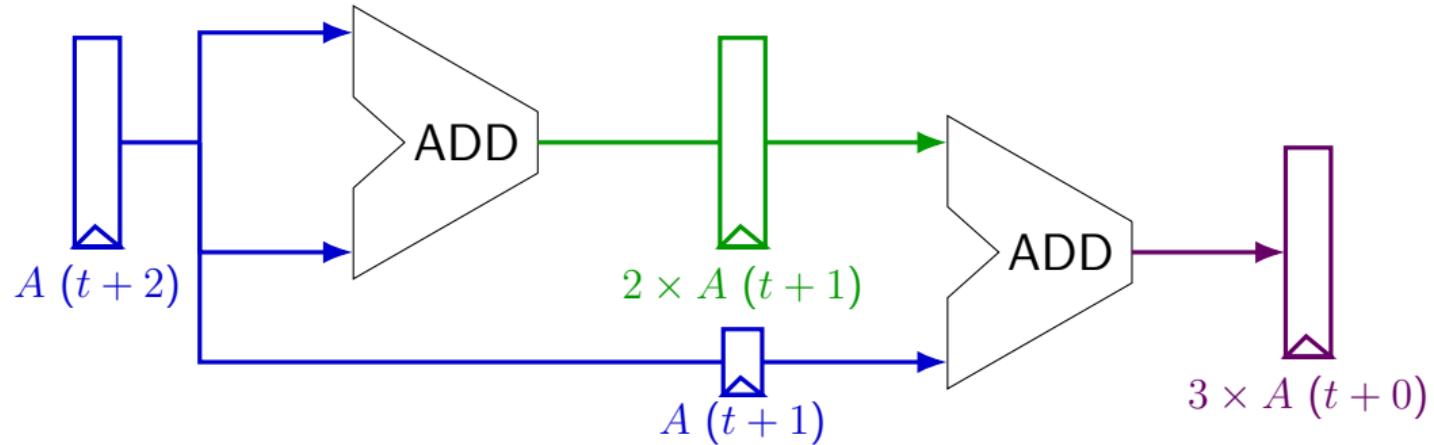


$A(t+2)$	7	17
$A(t+1)$	7	17
$2 \times A(t+1)$	14	34
$3 \times A(t+0)$		21


register tolerances

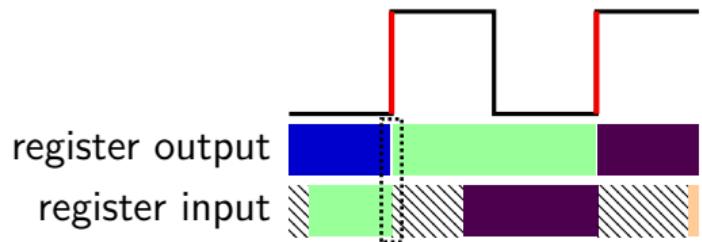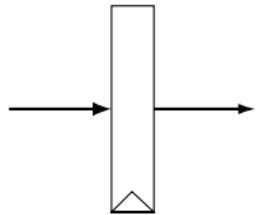


register tolerances

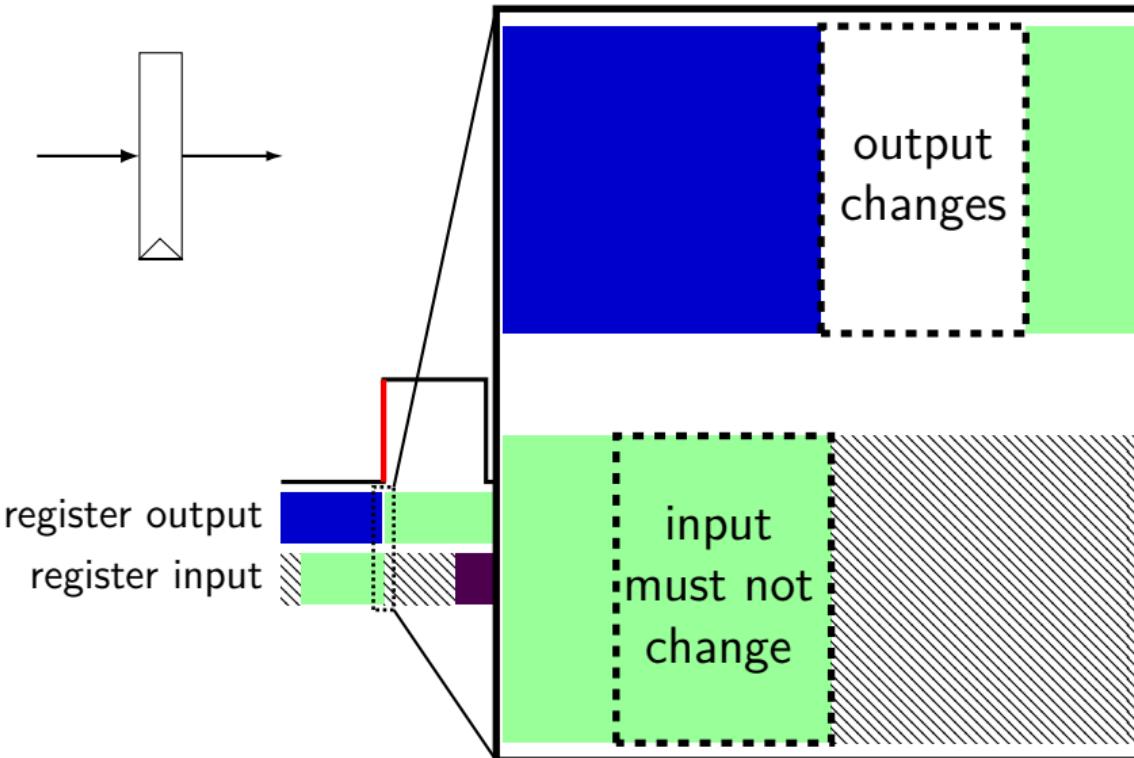


register tolerances

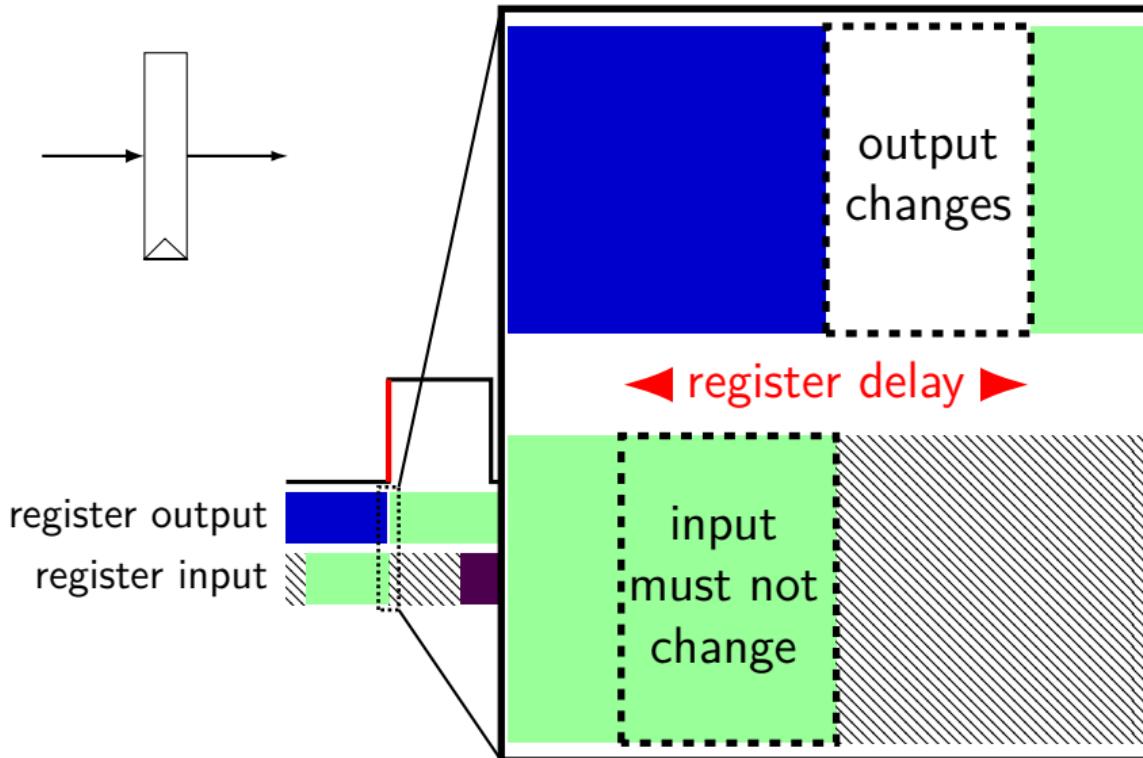

times three pipeline timing

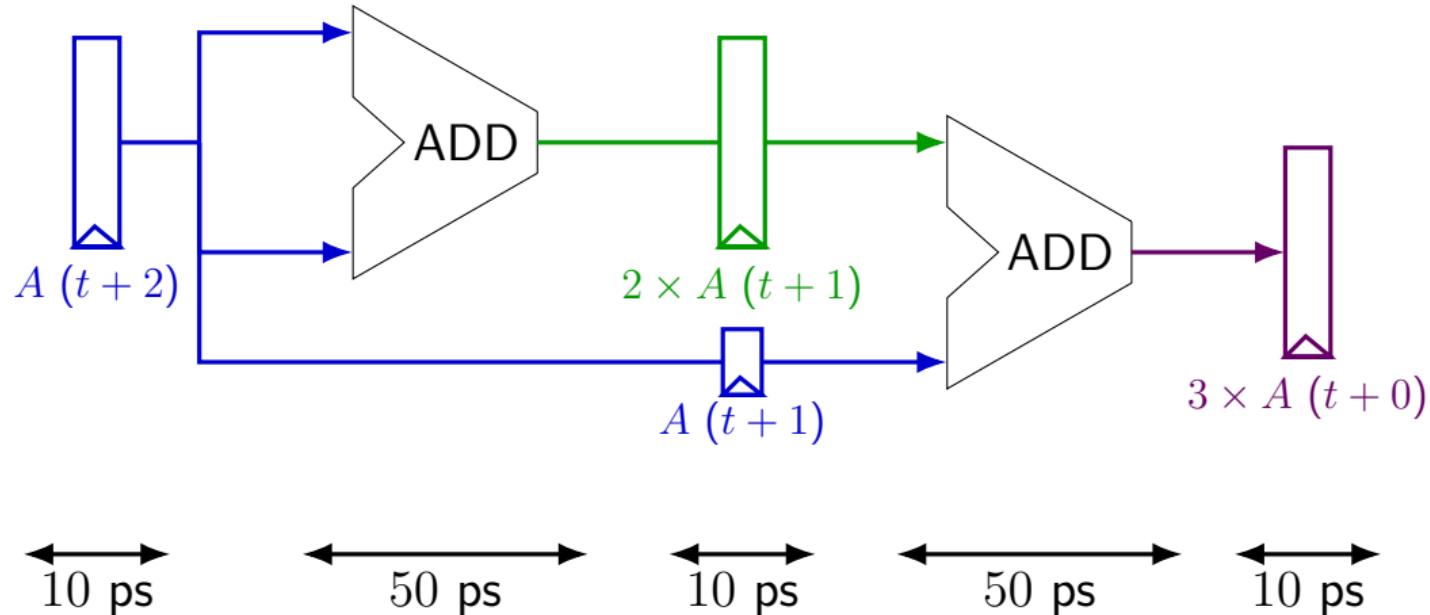

times three pipeline timing

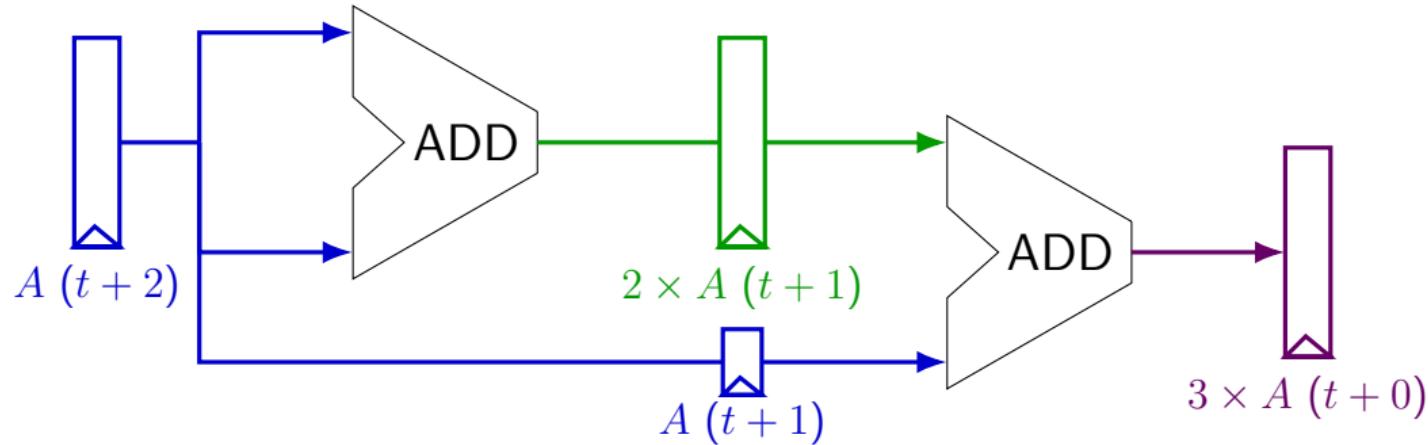


10 ps 50 ps 10 ps 50 ps 10 ps


10 ps

$$\text{throughput: } \frac{1}{60 \text{ ps}} \approx 16 \text{ G operations/sec}$$


deeper pipeline

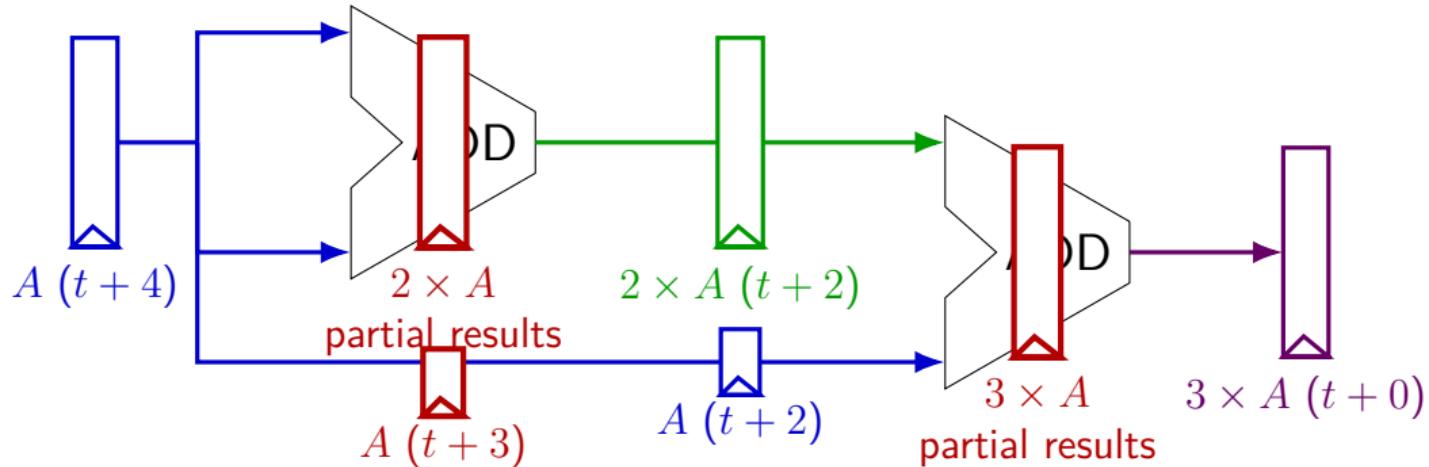

deeper pipeline

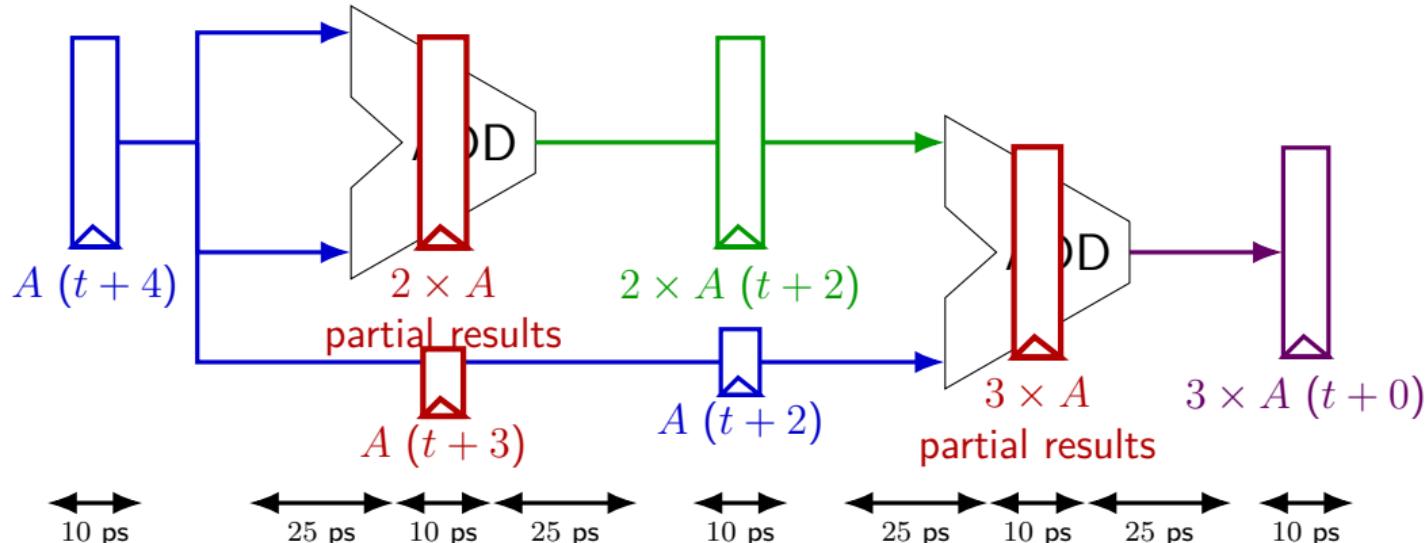


deeper pipeline

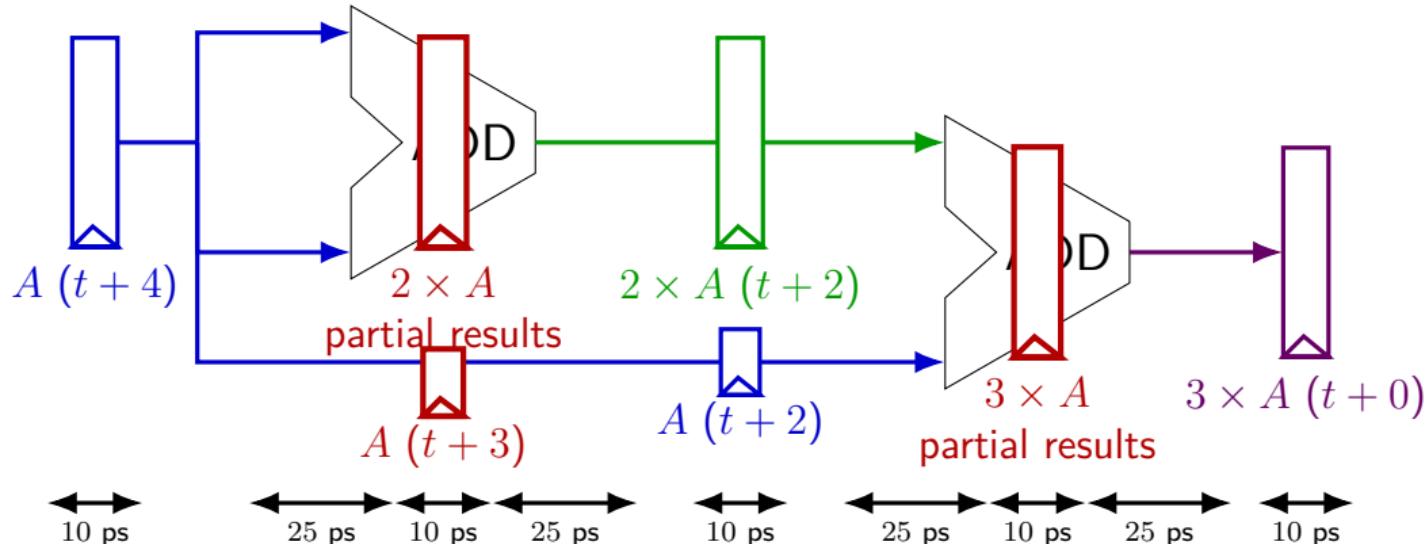


exercise: throughput now?

deeper pipeline

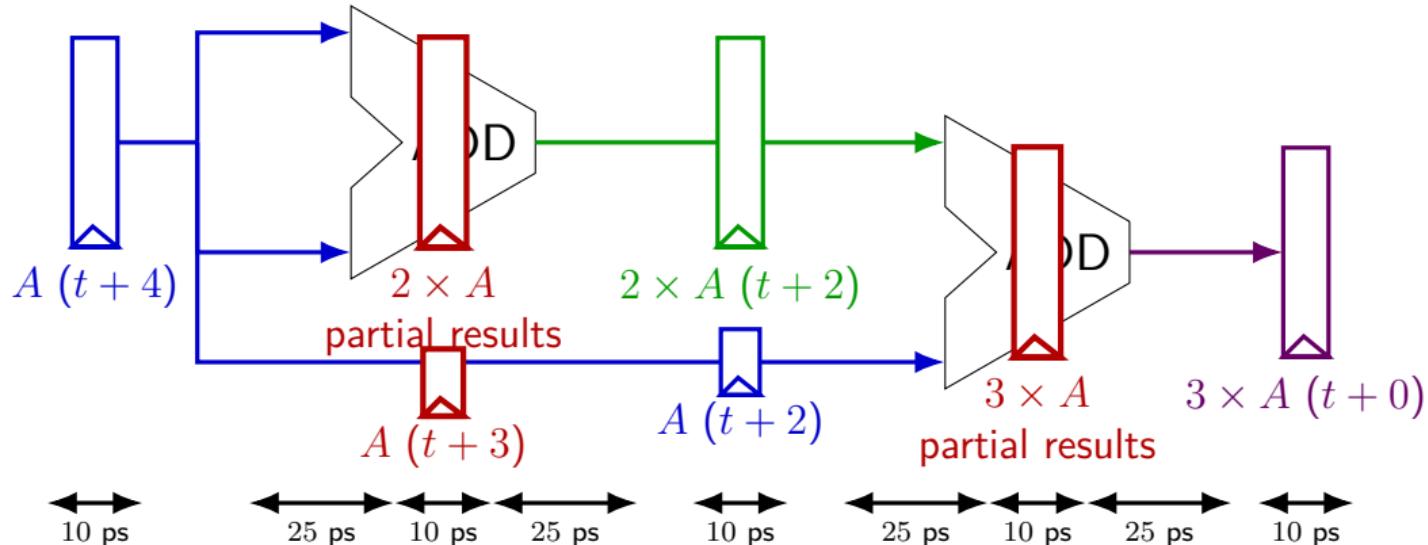


deeper pipeline

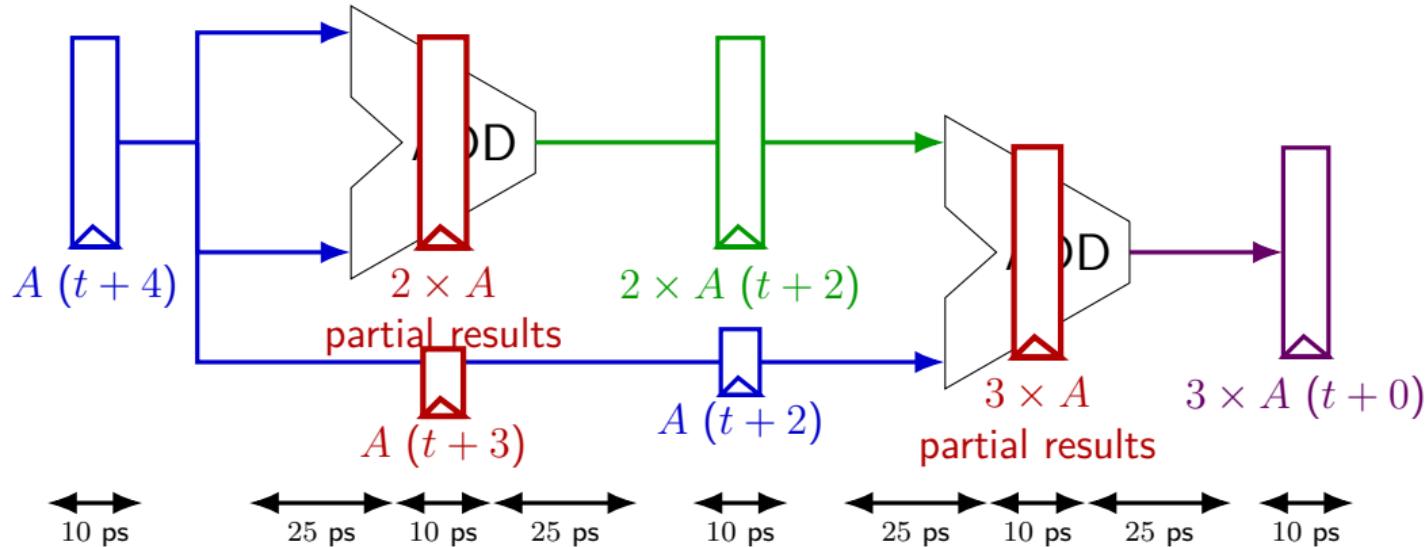


Problem: How much faster can we get?

Problem: Can we even do this?


diminishing returns: register delays

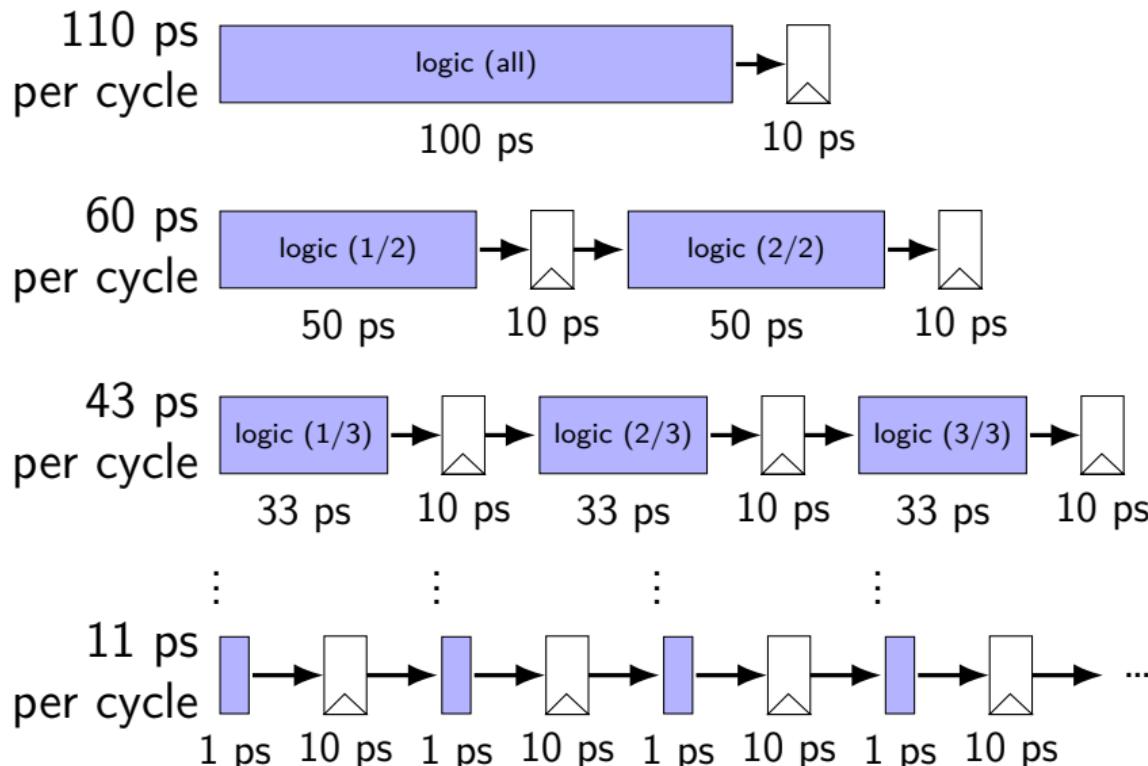


diminishing returns: register delays

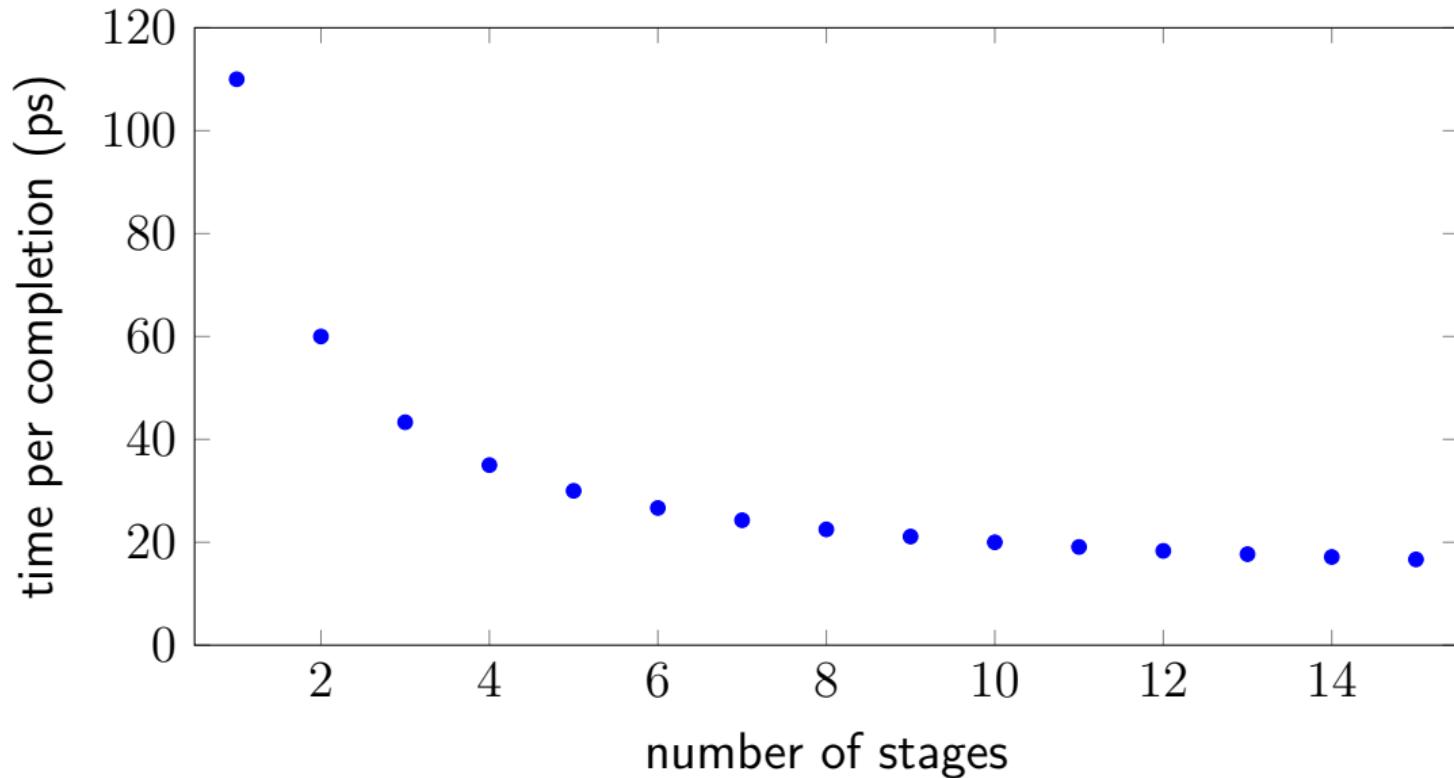


diminishing returns: register delays

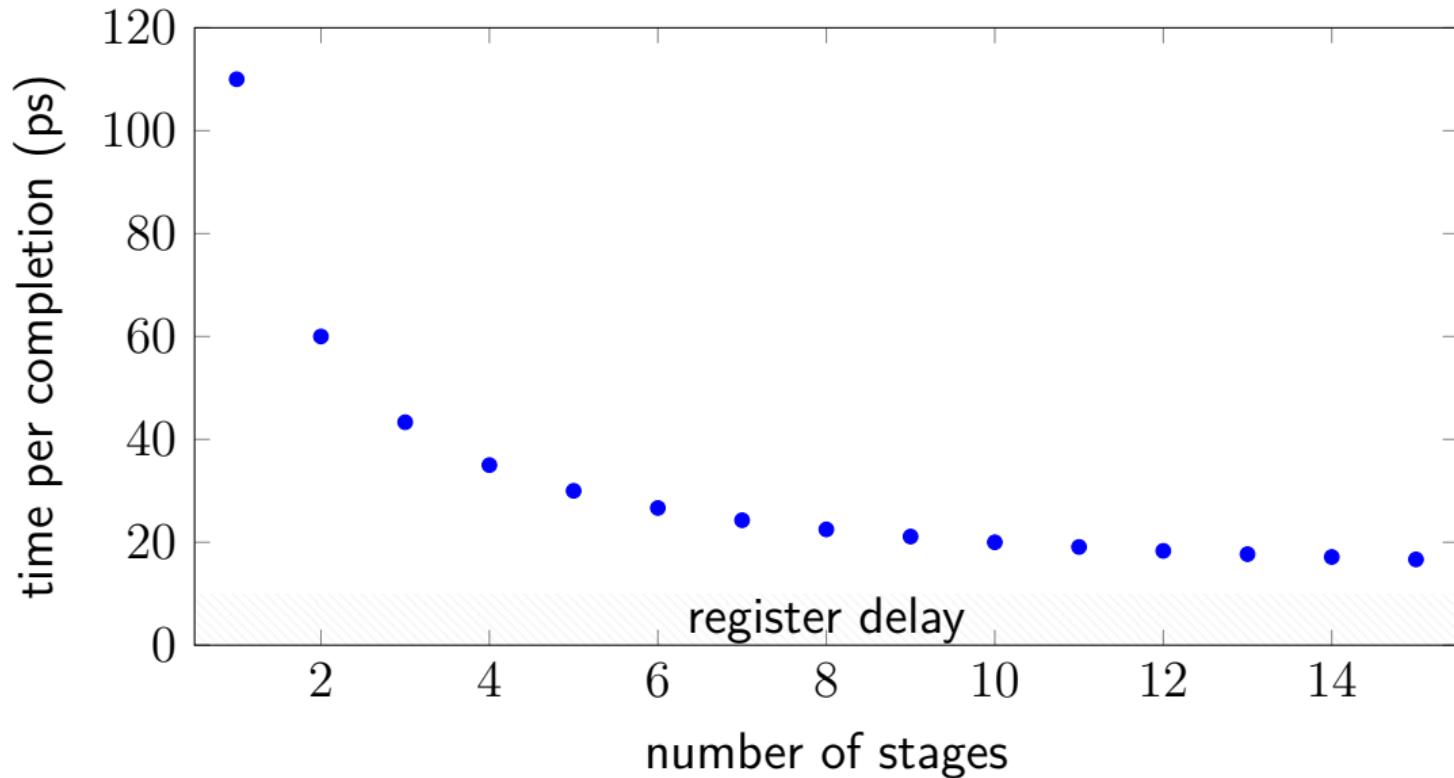


diminishing returns: register delays

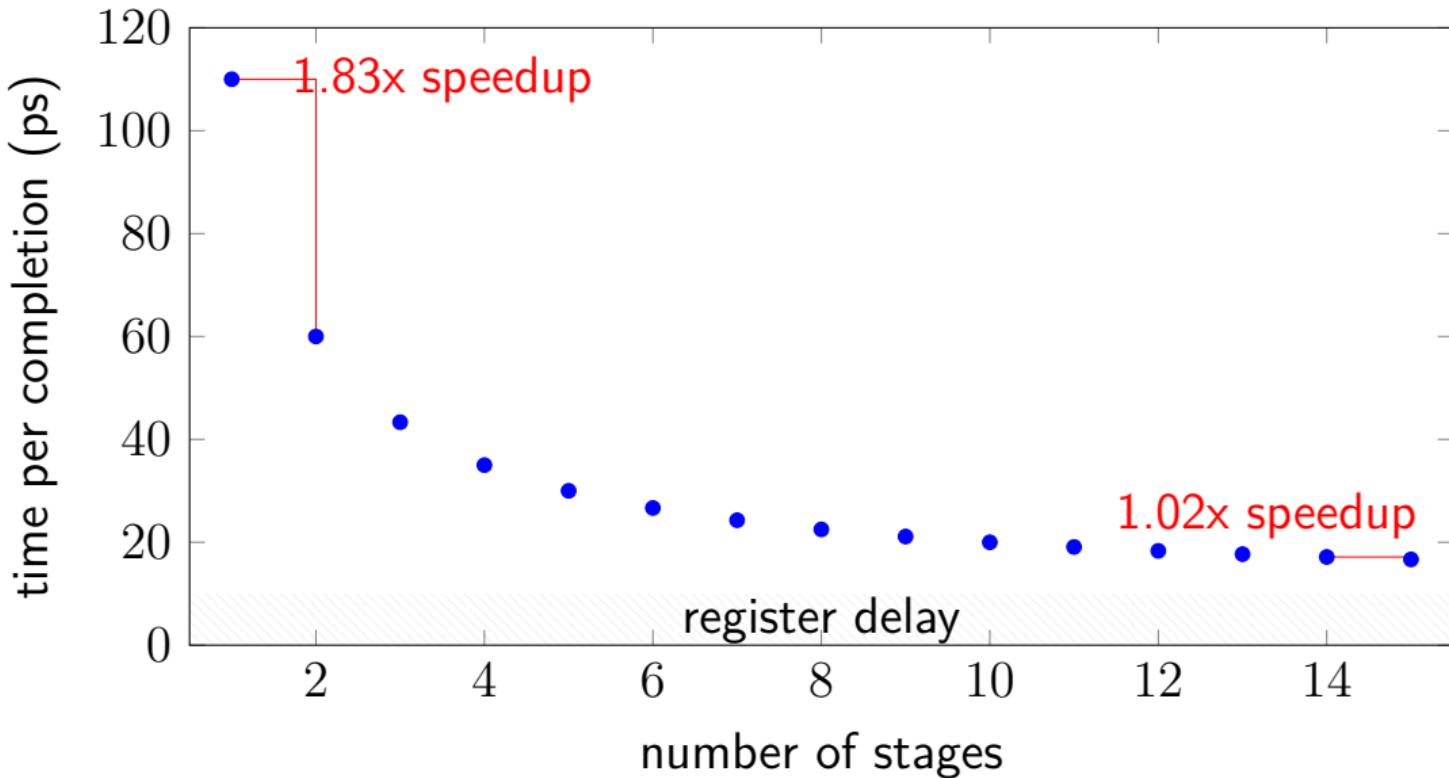


diminishing returns: register delays

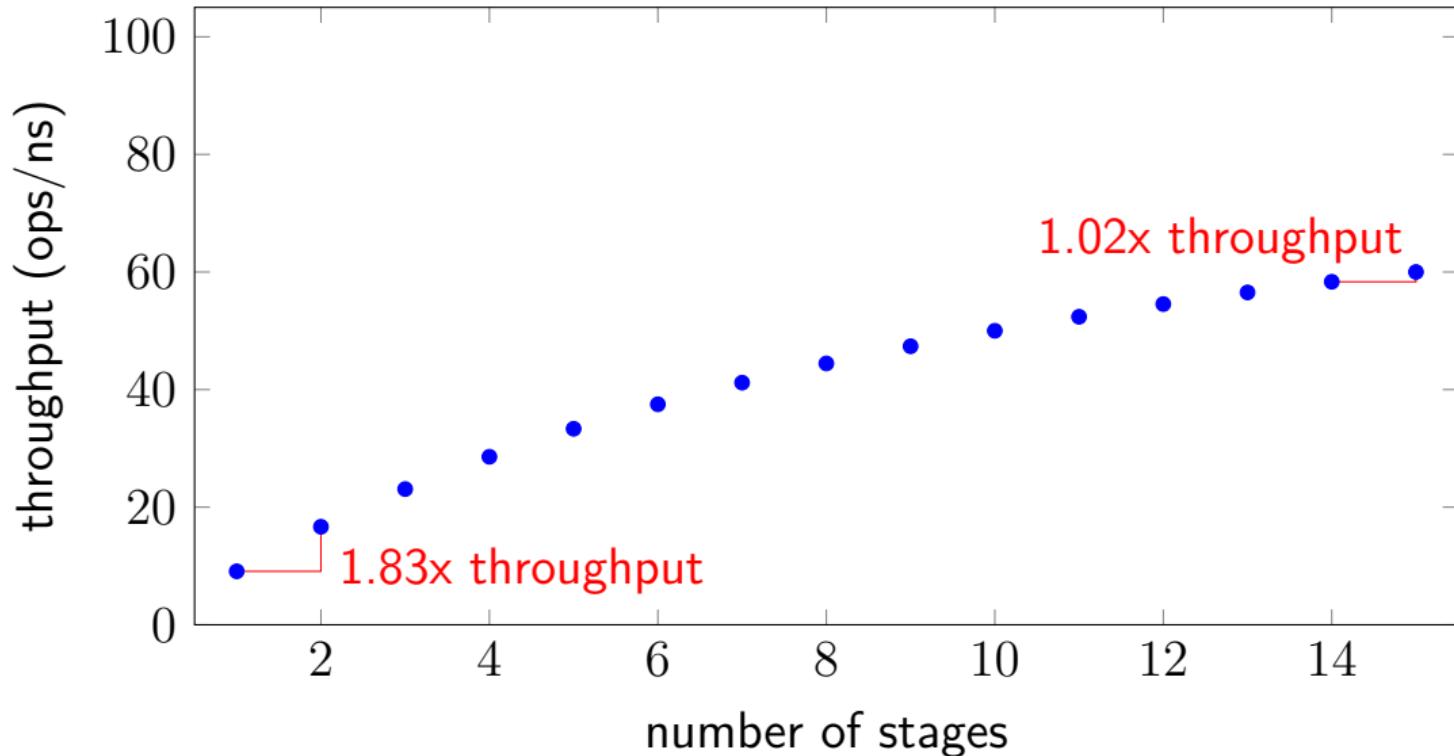

diminishing returns: register delays

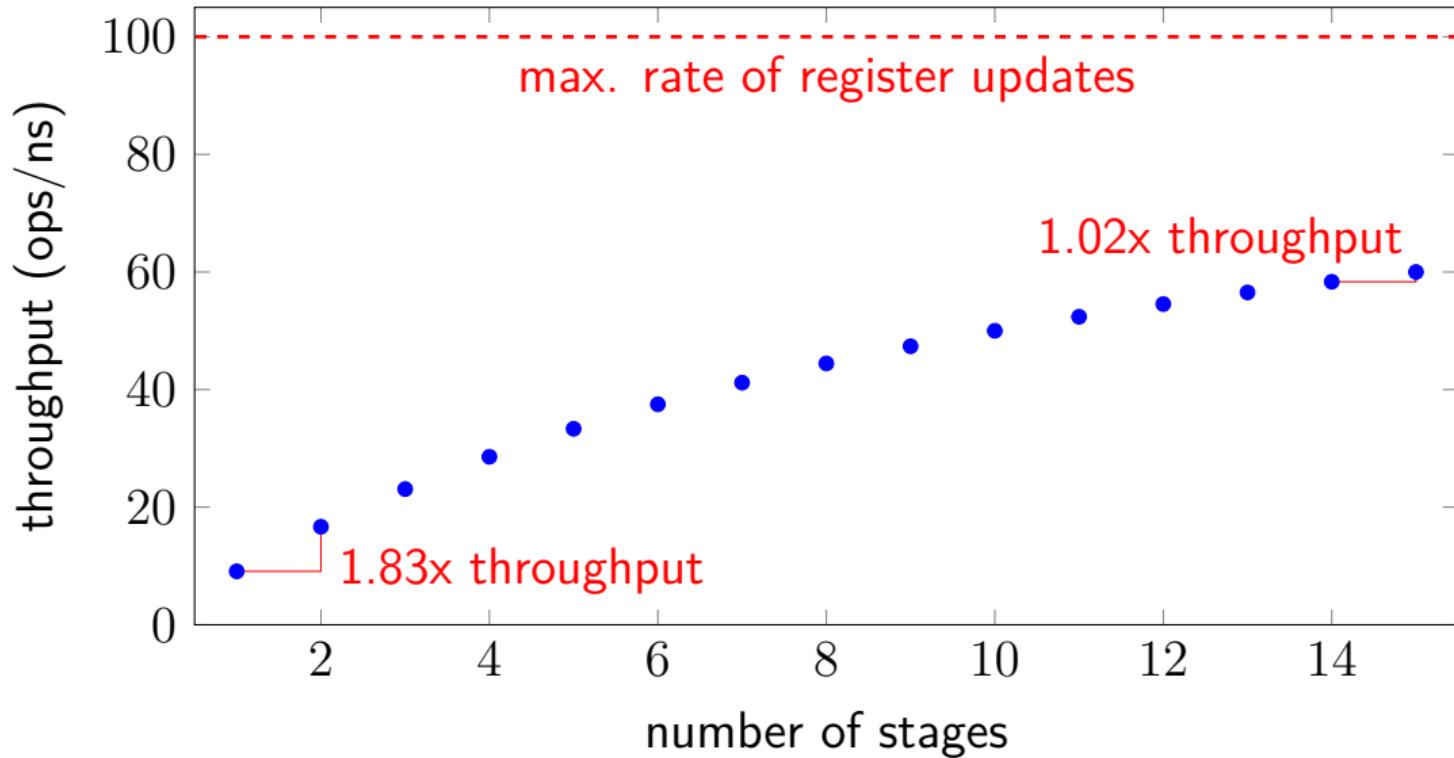


deeper pipeline

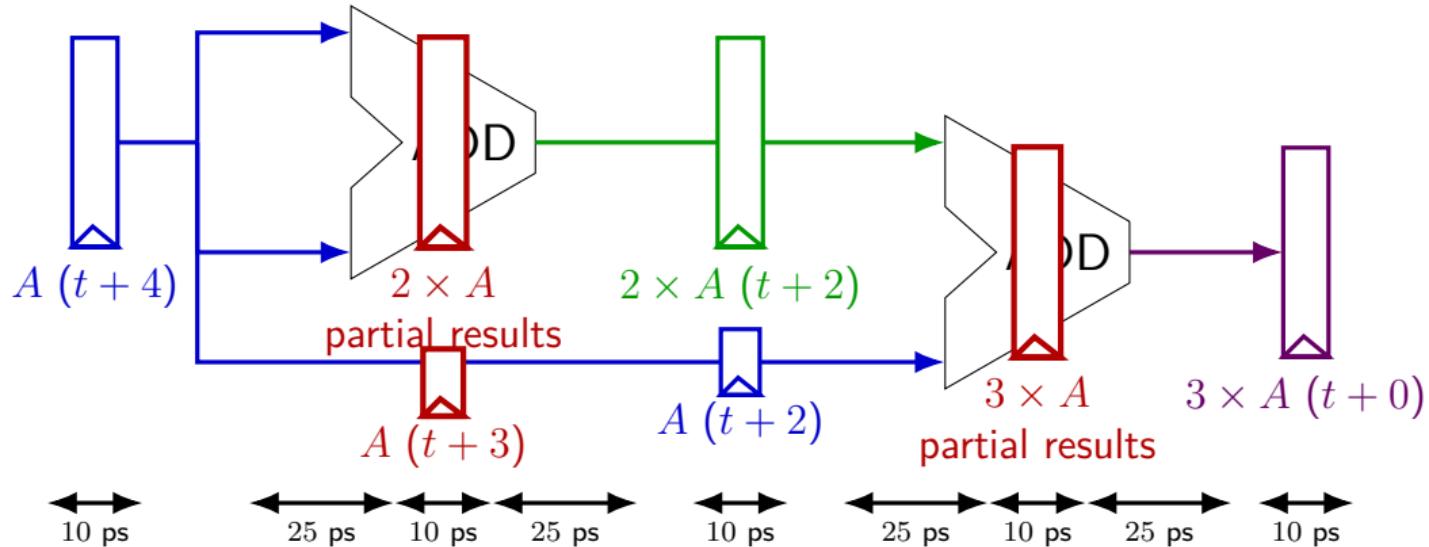

Problem: How much faster can we get?


Problem: Can we even do this?

deeper pipeline

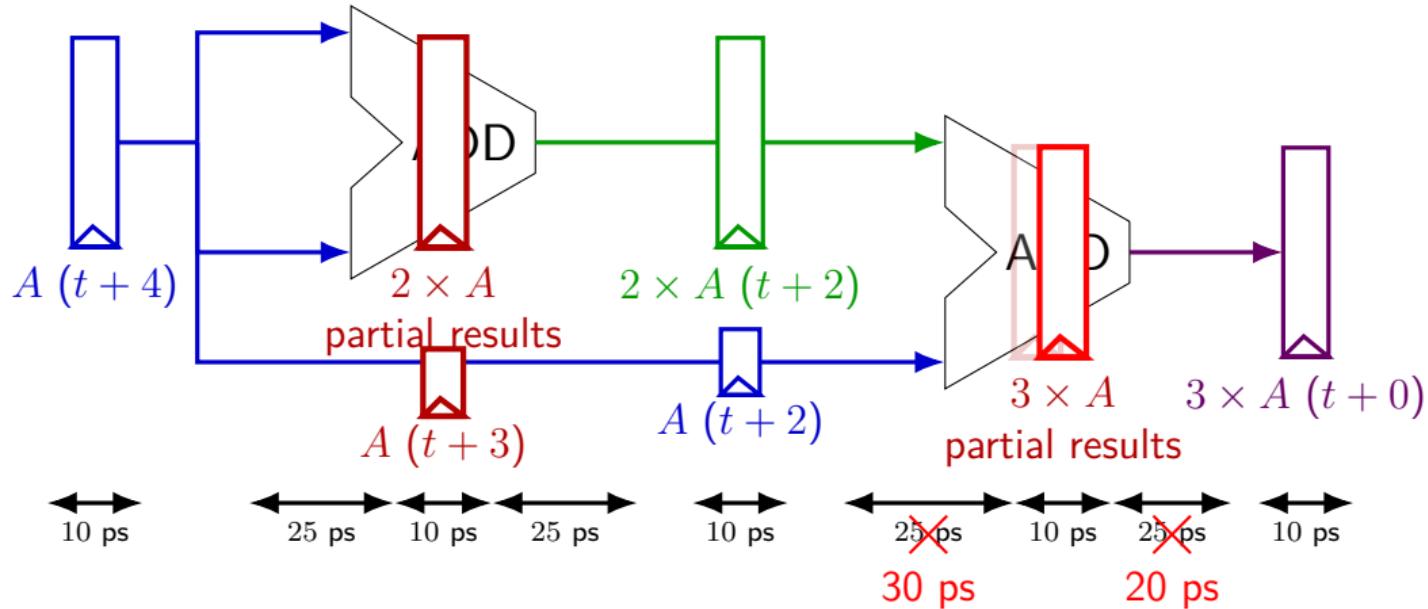

exercise: throughput now? (didn't split second add evenly)




deeper pipeline

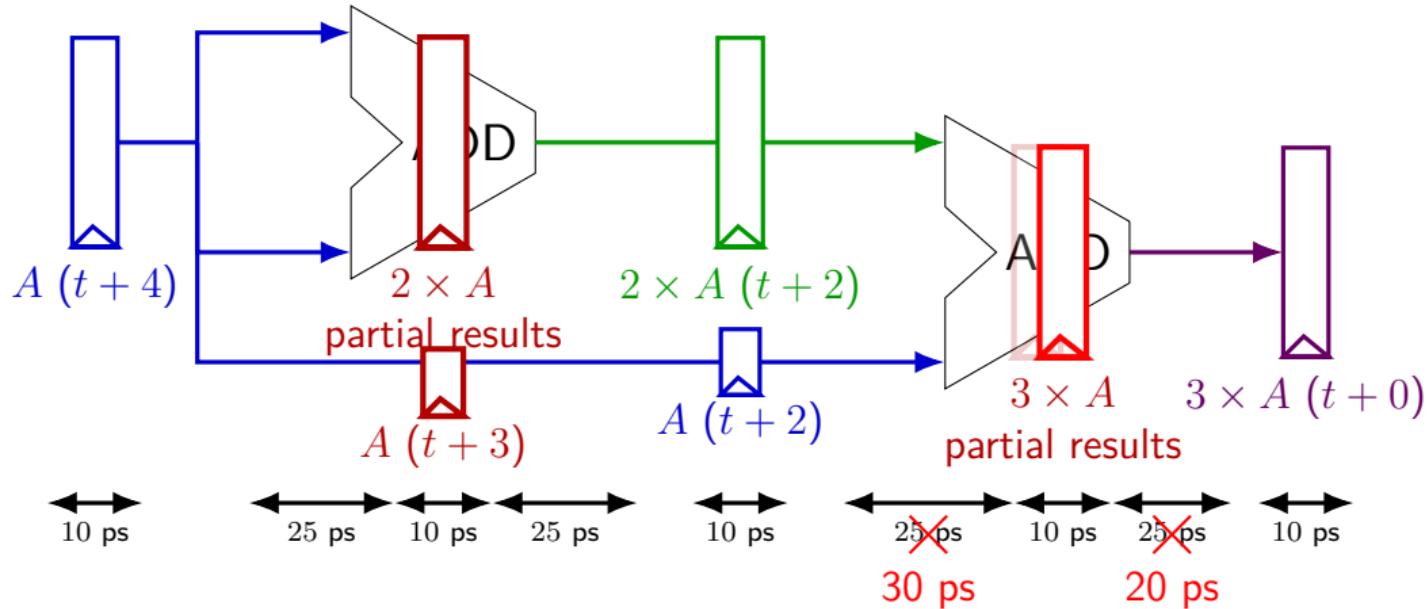

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?

Probably not...

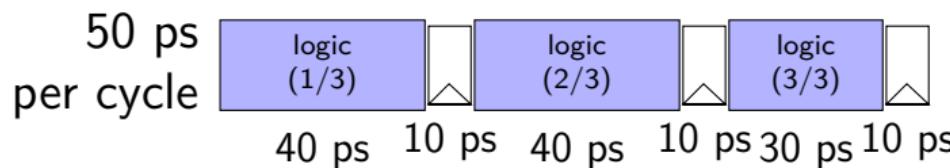
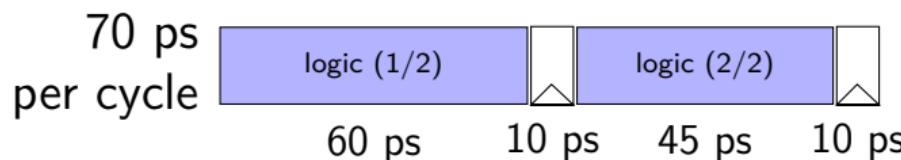
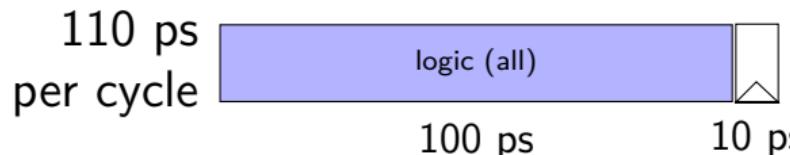


: : : :

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?

Probably not...

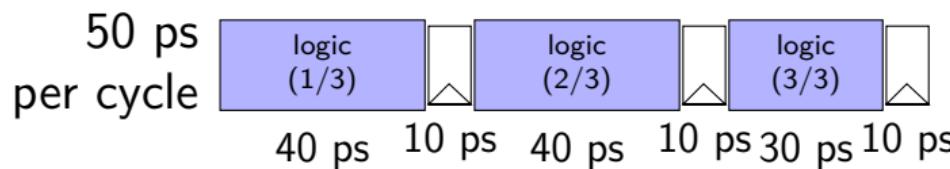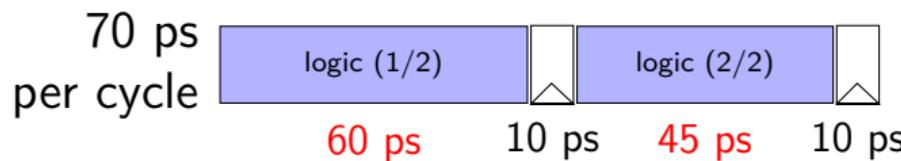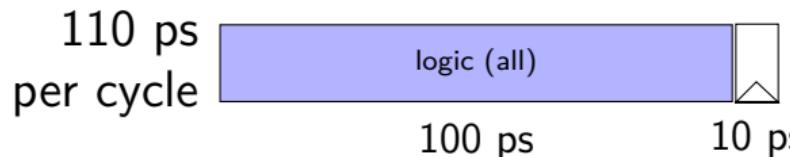

:

:




:

:

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?

Probably not...

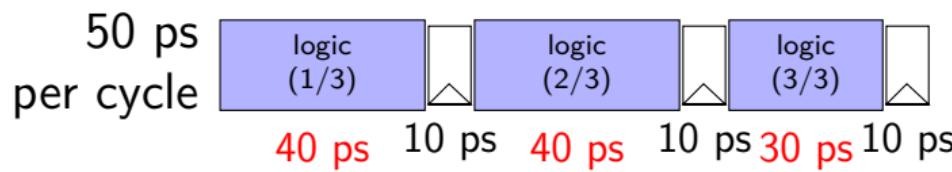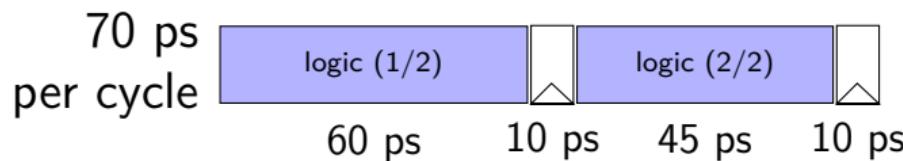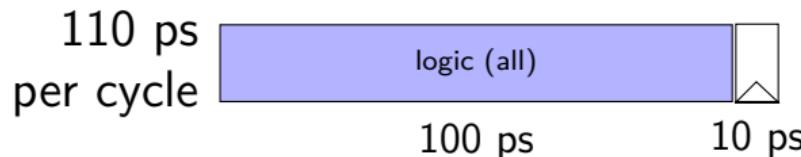

: : : :