

SEQ: instruction fetch

read instruction memory at PC

split into separate wires:

icode:ifun — opcode


rA, rB — register numbers

valC — call target or mov displacement

compute next instruction address:

valP — $PC + (\text{instr length})$

instruction fetch

 


SEQ: instruction “decode”


read registers

`valA`, `valB` — register values

instruction decode (1)

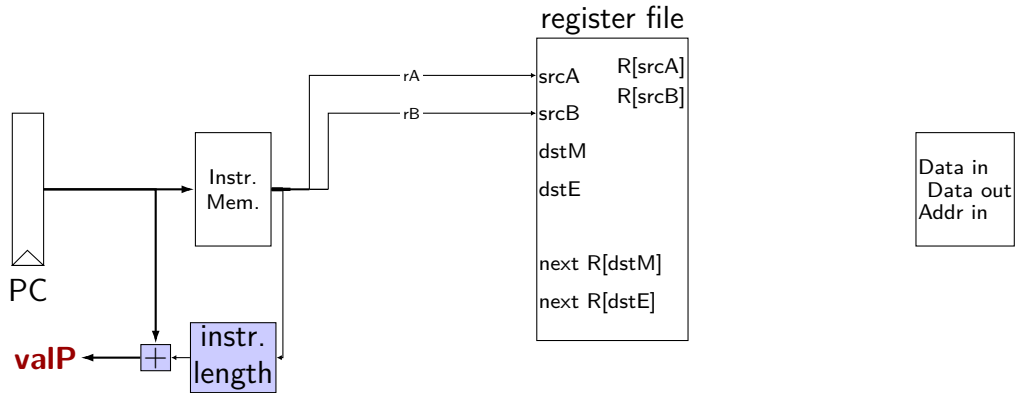

instruction decode (1)

 

exercise: which of these instructions can this **not** work for?
nop, addq, mrmovq, pushq, jmp,

SEQ: srcA, srcB

always read rA, rB?

Problems: (not planned to be included our assignments)

- push rA

- pop

- call


- ret

book: extra signals: srcA, srcB — computed input register

MUX controlled by icode


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 

instruction decode (2)

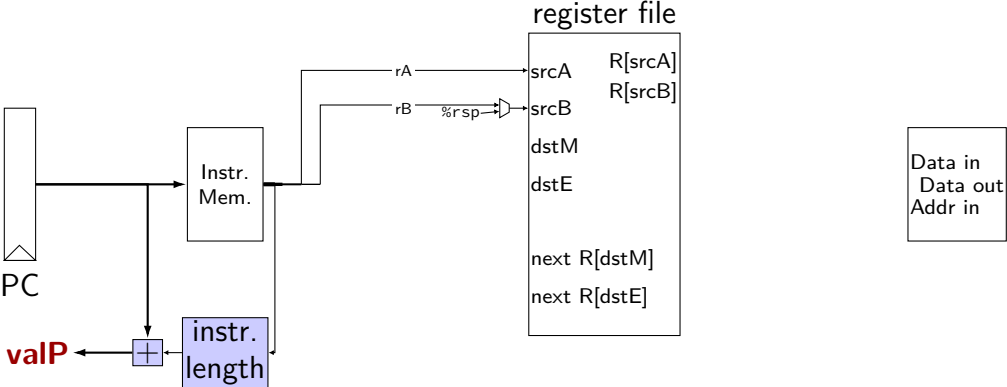

SEQ: execute

perform ALU operation (add, sub, xor, and)


valE — ALU output

read prior condition codes


Cnd — condition codes based on ifun (instruction type for jCC/cmouvCC)

write new condition codes


using condition codes: cmov

 

execute (1)

 

execute (1)

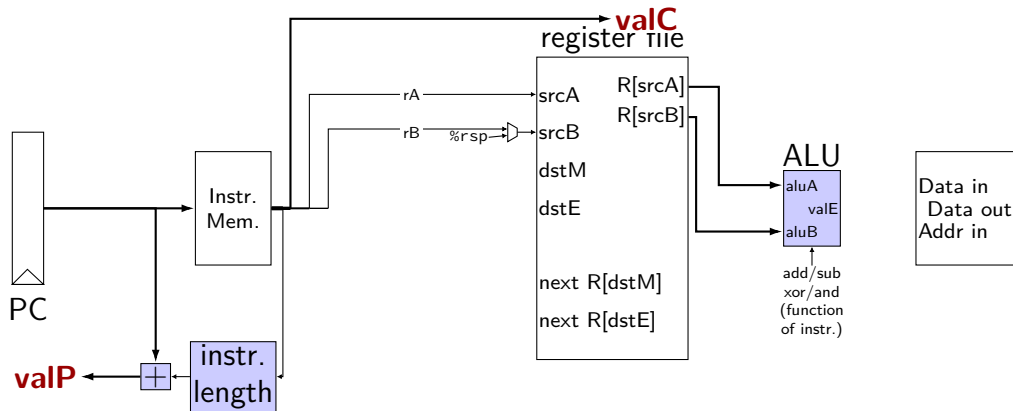


exercise: which of these instructions can this **not** work for?
nop, addq, mrmovq, popq, call,

SEQ: ALU operations?

ALU inputs always **valA**, **valB** (register values)?

no, inputs from instruction: (Displacement + rB)

`mrmovq`
`rmmovq`

 


no, constants: (`rsp +/- 8`) (not planned to be in assignments)

`pushq`
`popq`
`call`
`ret`

extra signals: **aluA**, **aluB**

computed ALU input values

execute (2)

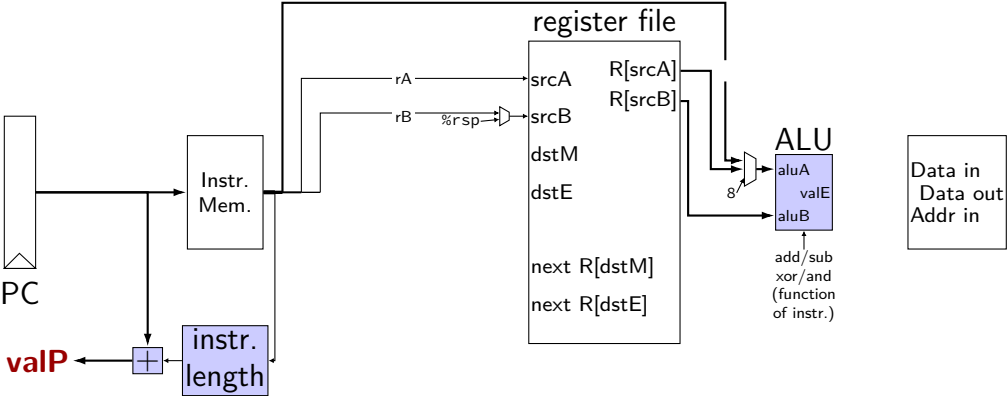


SEQ: Memory


read or write data memory

valM — value read from memory (if any)

memory (1)

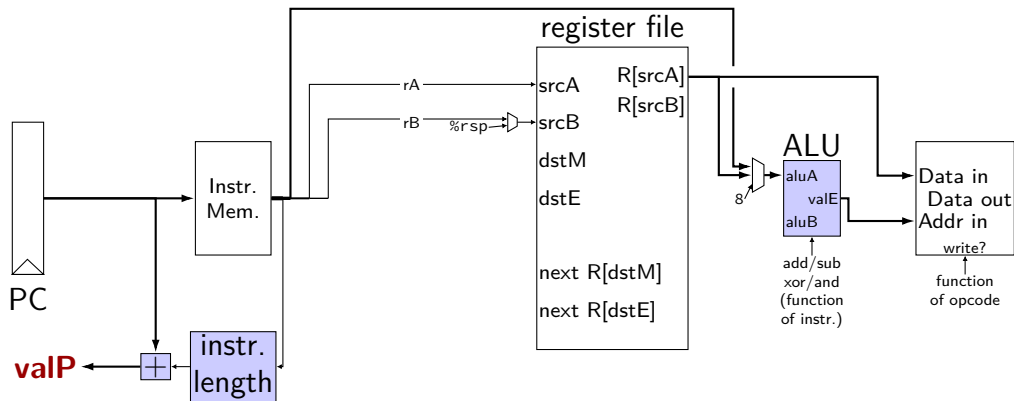

memory (1)

 

exercise: which of these instructions can this **not** work for?
nop, rmmovq, mrmovq, popq, call,

SEQ: control signals for memory

read/write — read enable? write enable?

Addr — address

mostly ALU output


special cases (need extra MUX): `popq`, `ret`

Data — value to write

mostly `valA`

special cases (need extra MUX): `call`


memory (2)

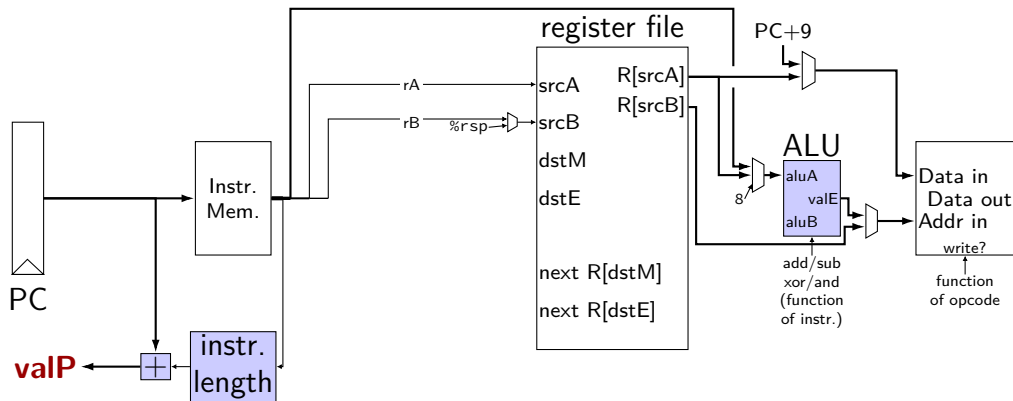


SEQ: write back

write registers


write back (1)

 

write back (1)

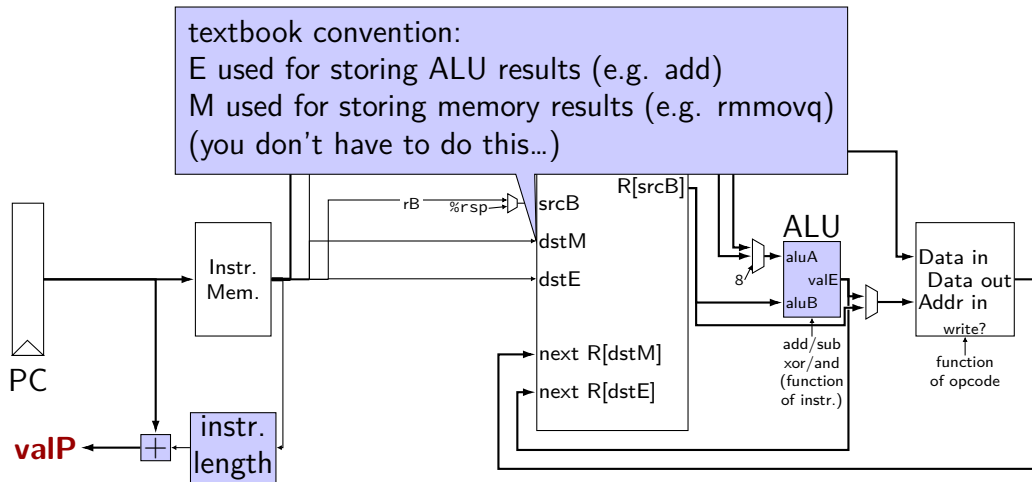

write back (1)

 


exercise: which of these instructions can this **not** work for?
nop, irmovq, mrmovq, pushq, addq

SEQ: control signals for WB


two write inputs — two needed by popq
valM (memory output), valE (ALU output)

two register numbers
dstM, dstE

 
write disable — use dummy register number 0xF



write back (2a)

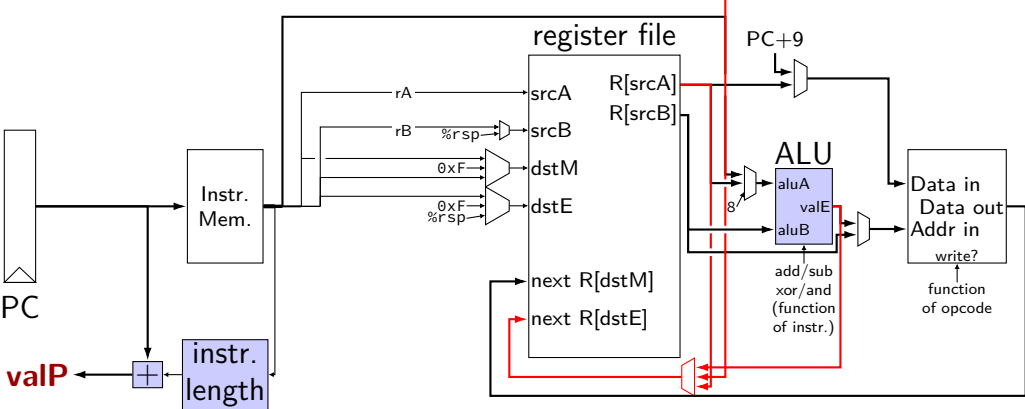

write back (2b)

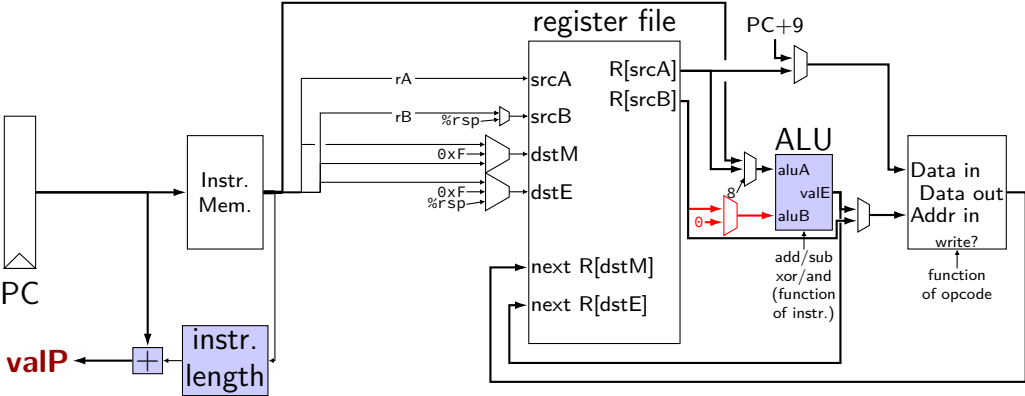


SEQ: Update PC

choose value for PC next cycle (input to PC register)


usually valP (following instruction)

exceptions: `call`, `jCC`, `ret`

PC update

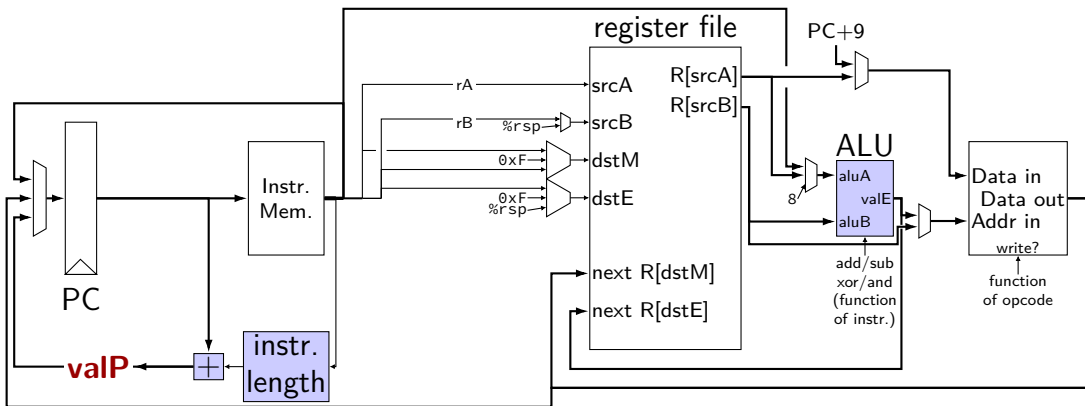


circuit: setting MUXEs

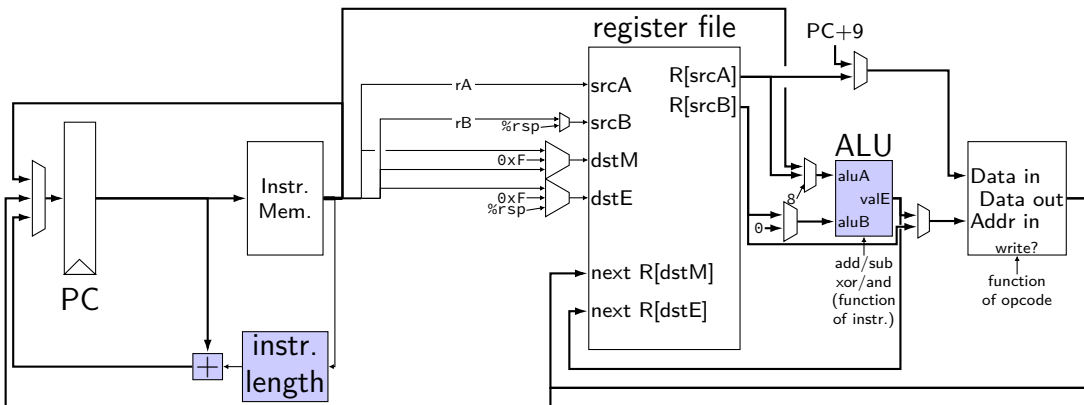


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXEs

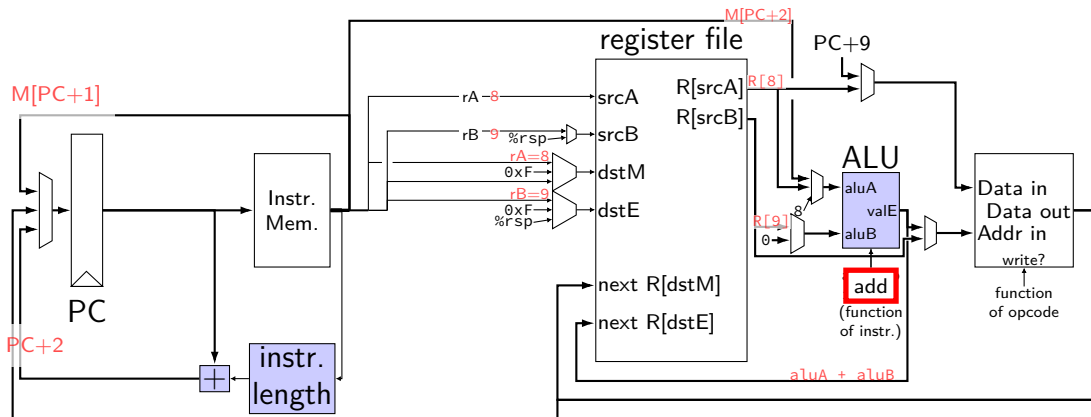


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXEs

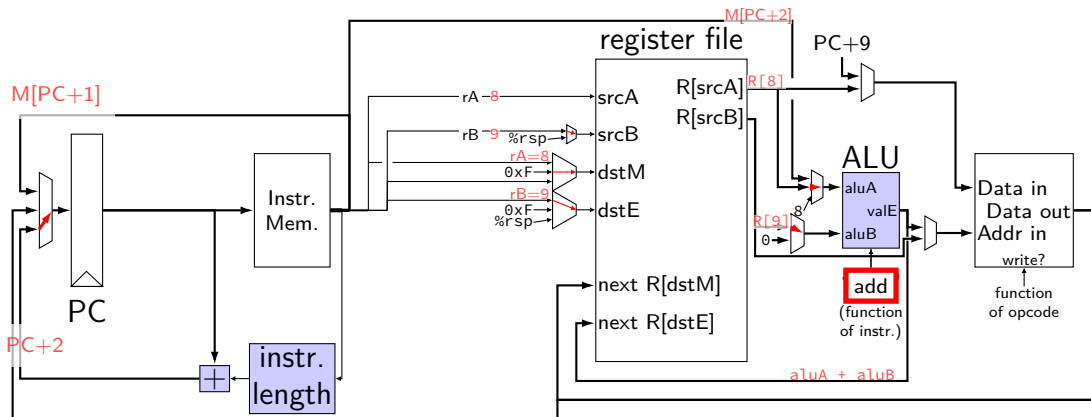


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXEs

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `rmmovq`?

circuit: setting MUXEs

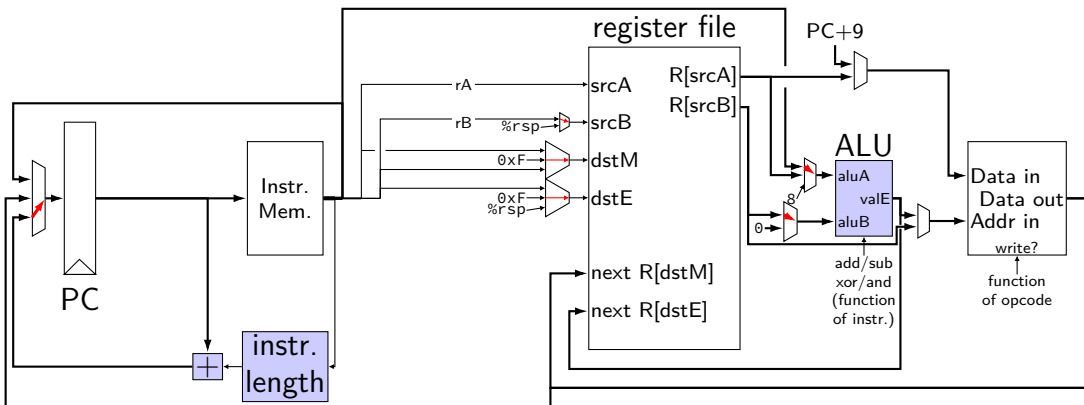


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `rmmovq`?

circuit: setting MUXEs

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `irmovq`?

circuit: setting MUXEs

 


MUXEs — PC, `dstM`, `dstE`, `aluA`, `aluB`, `dmemIn`, `dmemAddr`, ...
Exercise: what do they select for `mrmovq`?

circuit: setting MUXEs

 


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `jle`?

circuit: setting MUXEs

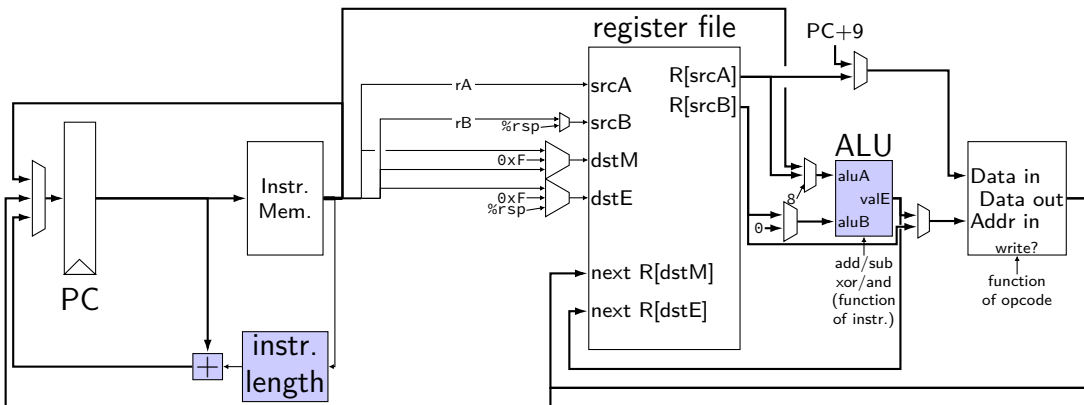


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **cmovle**?

circuit: setting MUXEs

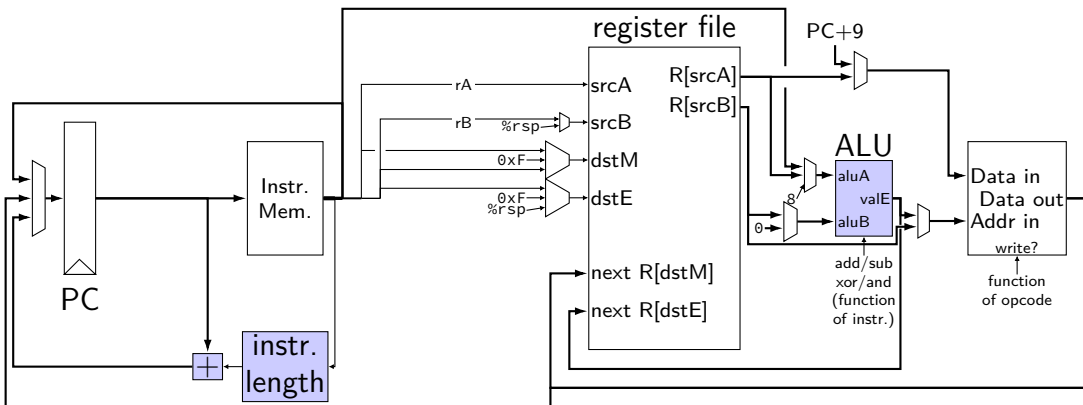


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **ret**?

circuit: setting MUXEs

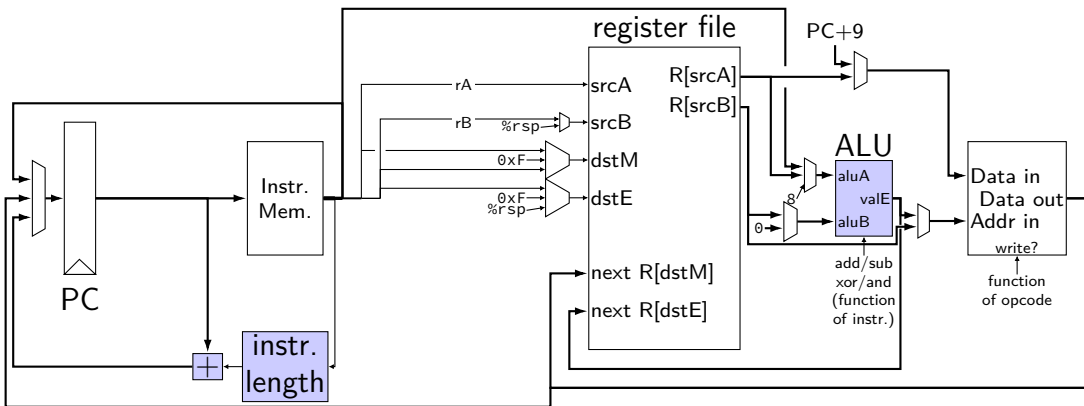


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **popq**?

circuit: setting MUXEs


 


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **call**?


Human pipeline: laundry

 


Human pipeline: laundry

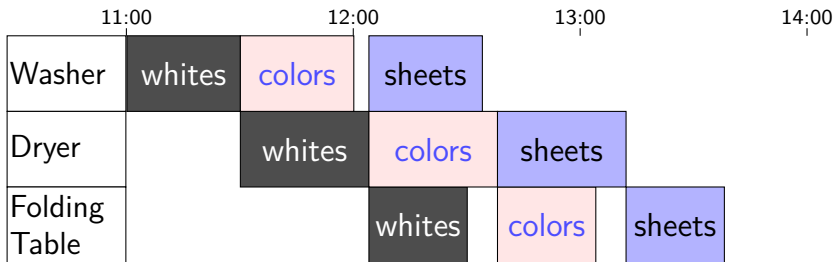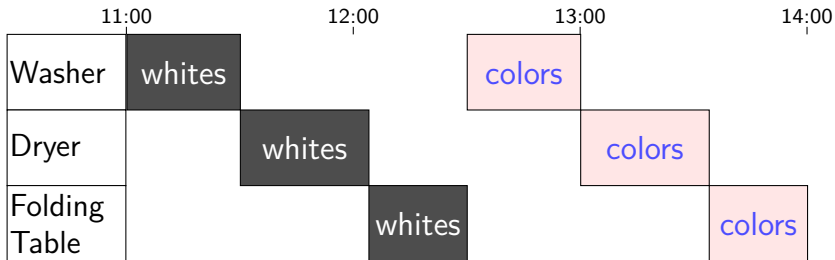


Waste (1)

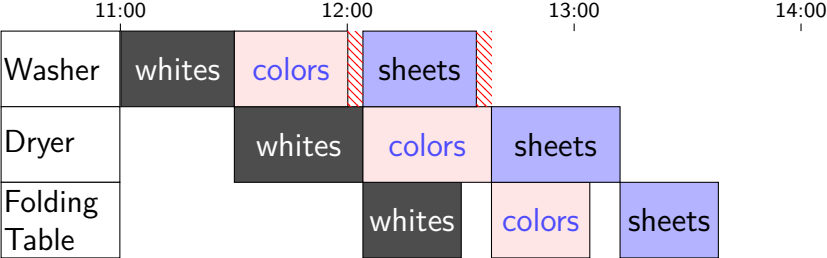


Waste (1)

 


Waste (2)

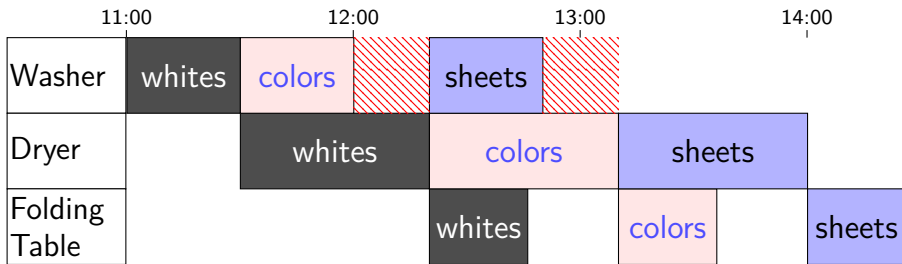


Latency — Time for One

 


Latency — Time for One

 


Latency — Time for One

 

Throughput — Rate of Many

 


Throughput — Rate of Many

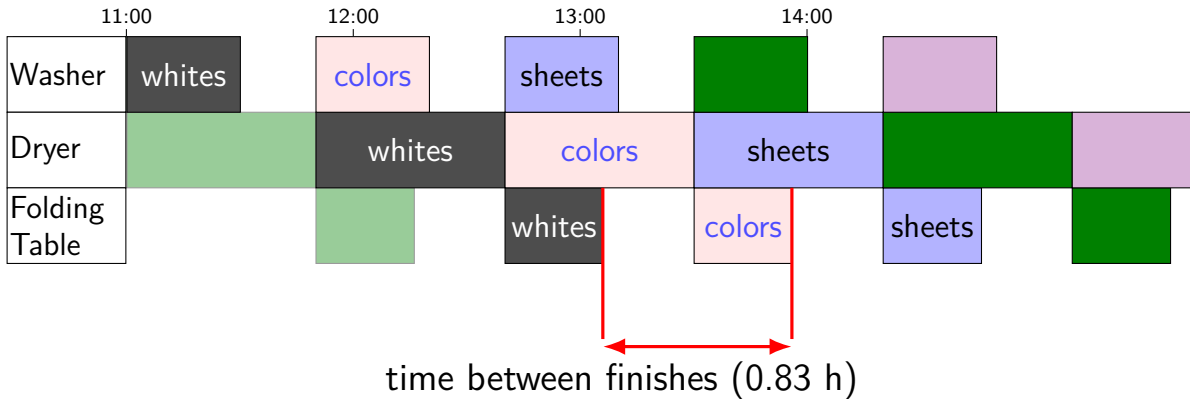


$$\frac{1 \text{ load}}{0.83\text{h}} = 1.2 \text{ loads/h}$$

Throughput — Rate of Many


 


$$\frac{1 \text{ load}}{0.83\text{h}} = 1.2 \text{ loads/h}$$


times three circuit

 


times three circuit

  


times three circuit

 


 
100 ps latency \Rightarrow 10 results/ns throughput




times three and repeat

 


times three and repeat

  

pipelined times three


 


pipelined times three

 


$A(t+2)$	7	17
$A(t+1)$	7	17
$2 \times A(t+1)$	14	34
$3 \times A(t+0)$		21


register tolerances

  


register tolerances

 



register tolerances

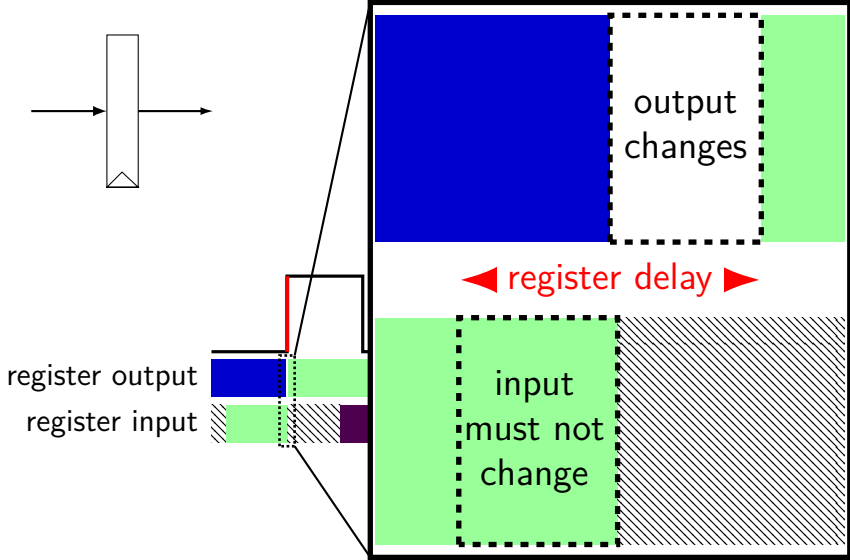

times three pipeline timing

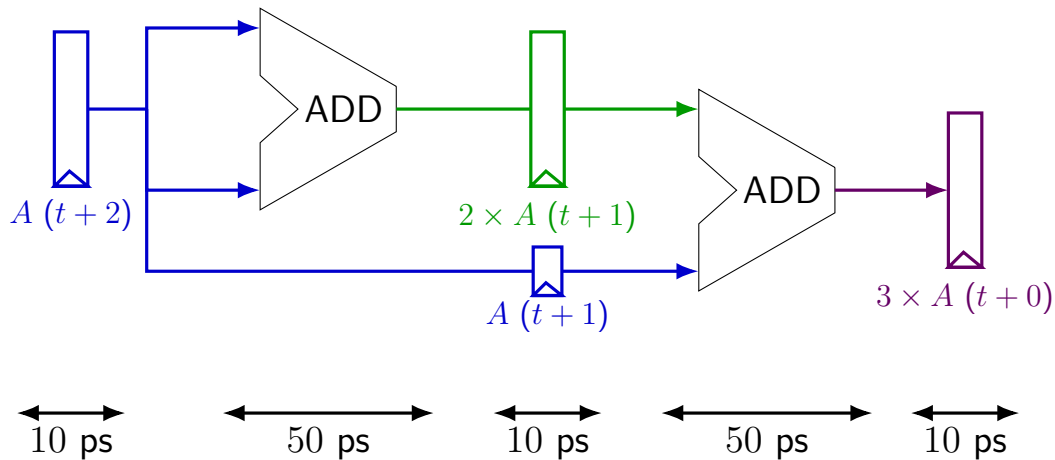


times three pipeline timing

  


throughput: $\frac{1}{60 \text{ ps}} \approx 16 \text{ G operations/sec}$


deeper pipeline

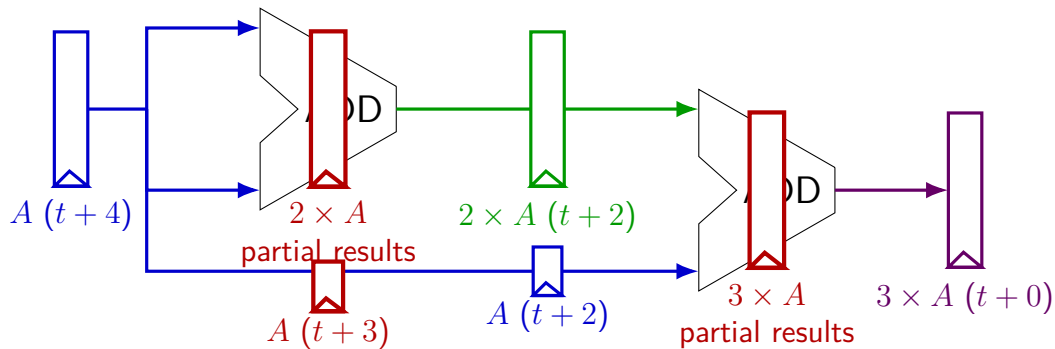

deeper pipeline

 


deeper pipeline

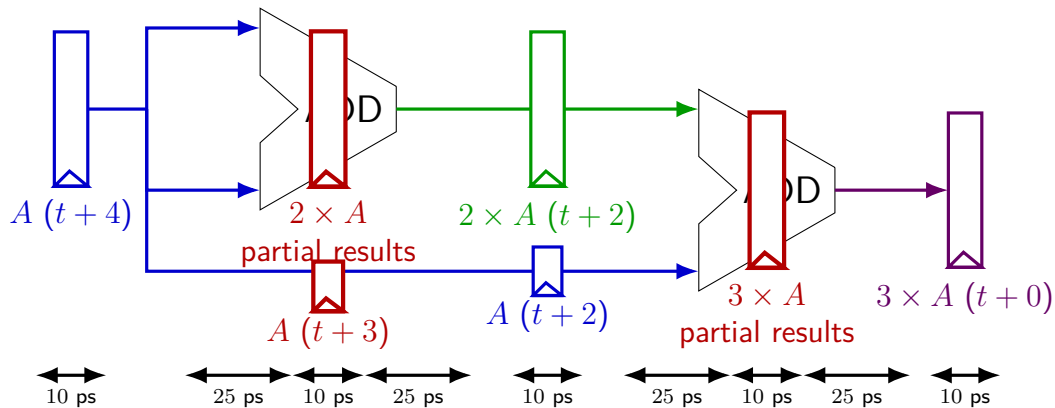


exercise: throughput now?

deeper pipeline

 


throughput: $\frac{1}{35 \text{ ps}} \approx 28 \text{ G ops/sec}$


diminishing returns: register delays

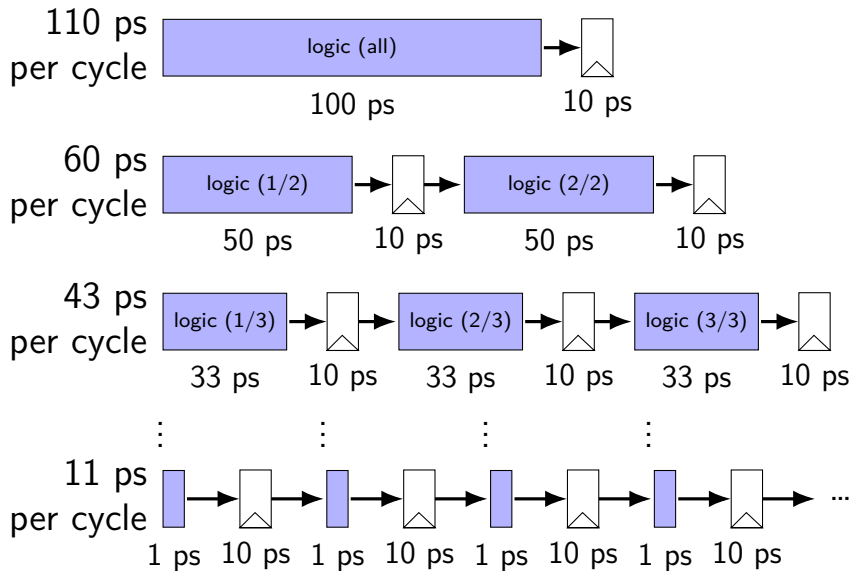


diminishing returns: register delays

 


diminishing returns: register delays

 


diminishing returns: register delays

 


diminishing returns: register delays

 

diminishing returns: register delays

 


deeper pipeline

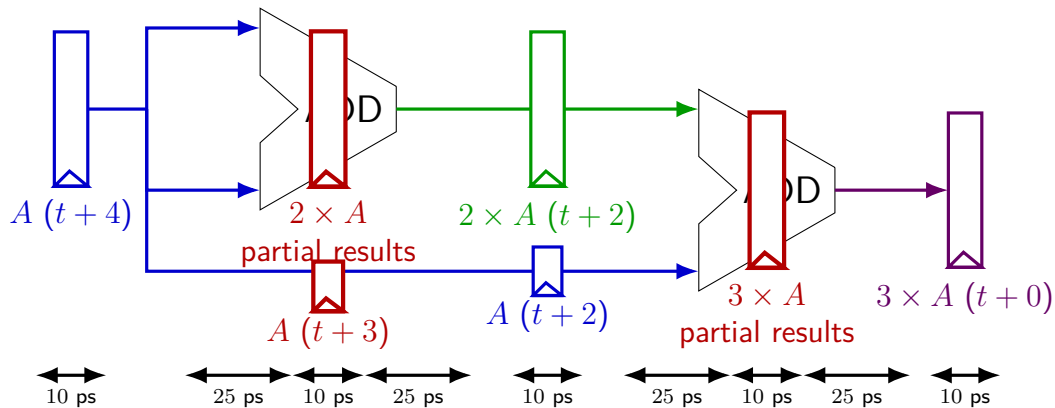

Problem: How much faster can we get?


Problem: **Can we even do this?**

deeper pipeline

 

exercise: throughput now? (didn't split second add evenly)


deeper pipeline

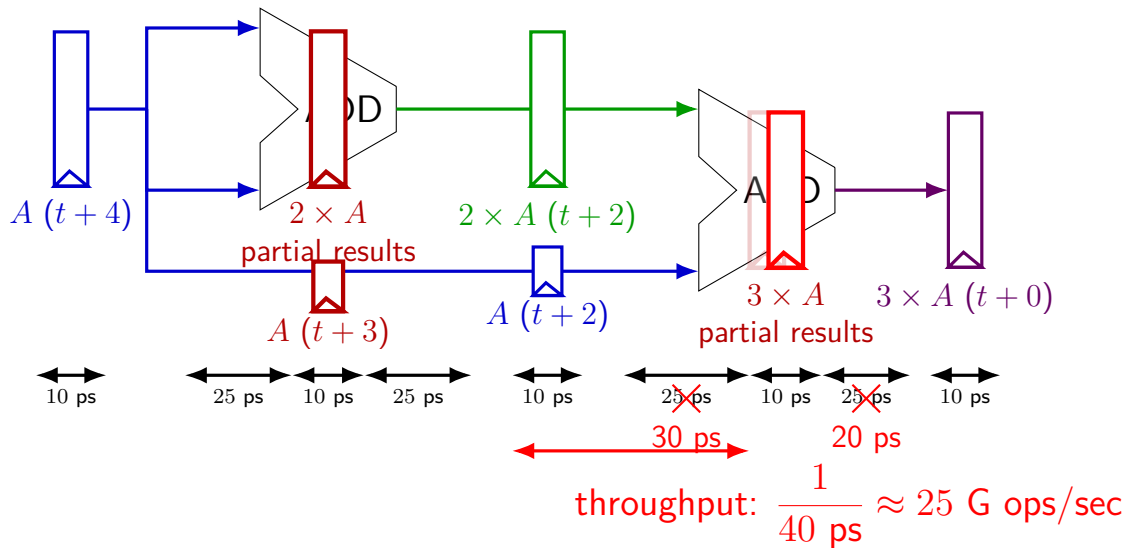

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?


Probably not...

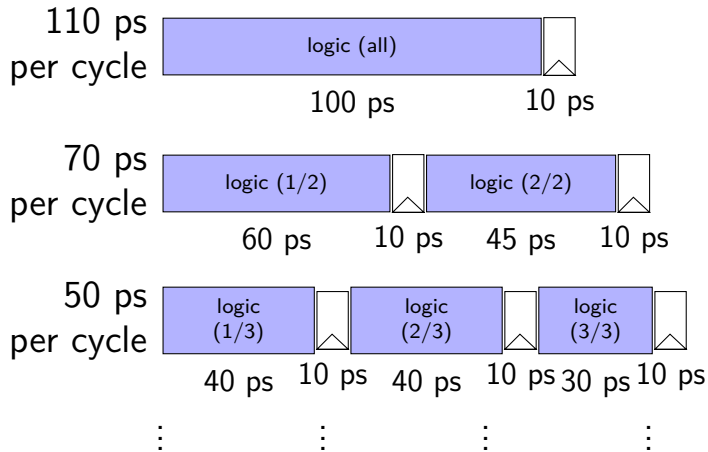

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?


Probably not...

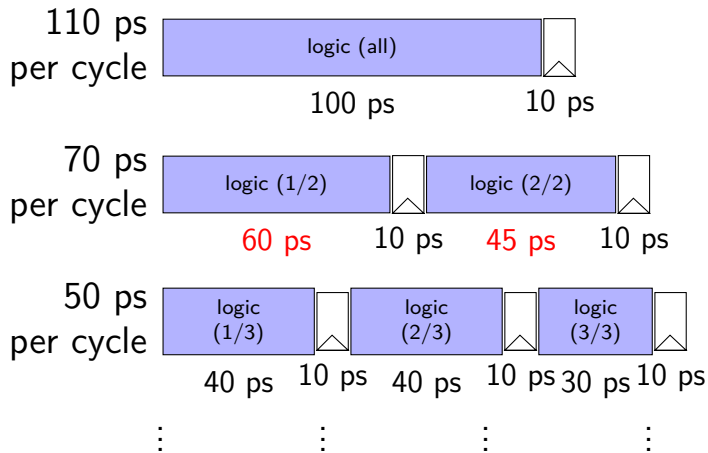

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?

Probably not...

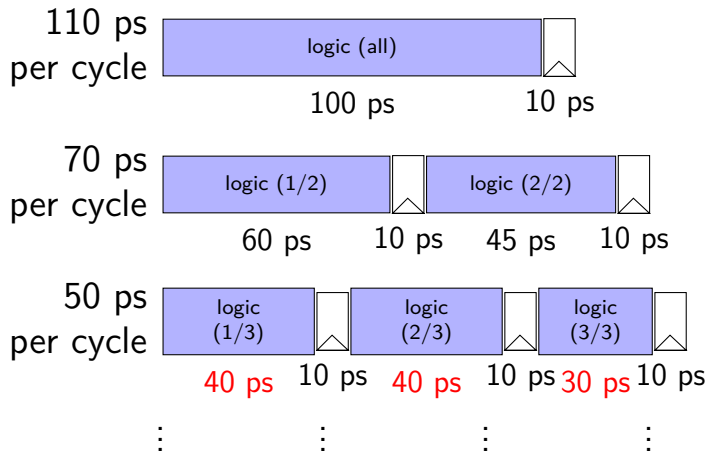

textbook SEQ 'stages'

conceptual order only

Fetch: read instruction memory

Decode: read register file

Execute: arithmetic (ALU)

Memory: read/write data memory

Writeback: write register file

PC Update: write PC register

textbook SEQ 'stages'

conceptual order only

Fetch: read instruction memory

Decode: read register file

Execute: arithmetic (ALU)

Memory: read/**write** data memory

Writeback: **write** register file

PC Update: **write** PC register

writes happen
at end of cycle

textbook SEQ 'stages'

conceptual order only

Fetch: **read** instruction memory

Decode: **read** register file

Execute: arithmetic (ALU)

Memory: **read**/write data memory

Writeback: write register file

PC Update: write PC register

reads — “magic”
like combinatorial logic
as values available

textbook stages

~~conceptual order only~~ pipeline stages

Fetch/PC Update: read instruction memory;
compute next PC

Decode: read register file

Execute: arithmetic (ALU)

Memory: read/write data memory

Writeback: write register file

textbook stages

conceptual order only pipeline stages

Fetch/PC Update: read instruction memory;
compute next PC

Decode: read register file

Execute: arithmetic (ALU)

Memory: read/write data memory


Writeback: write register file

5 stages


one instruction in each

compute next to start immediately

addq CPU

 


addq CPU

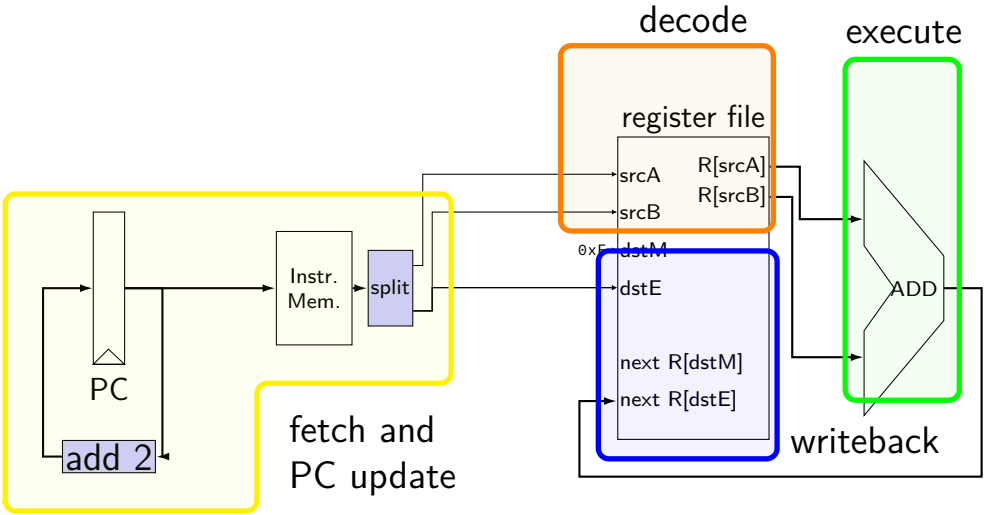


addq CPU


signal skips two stages

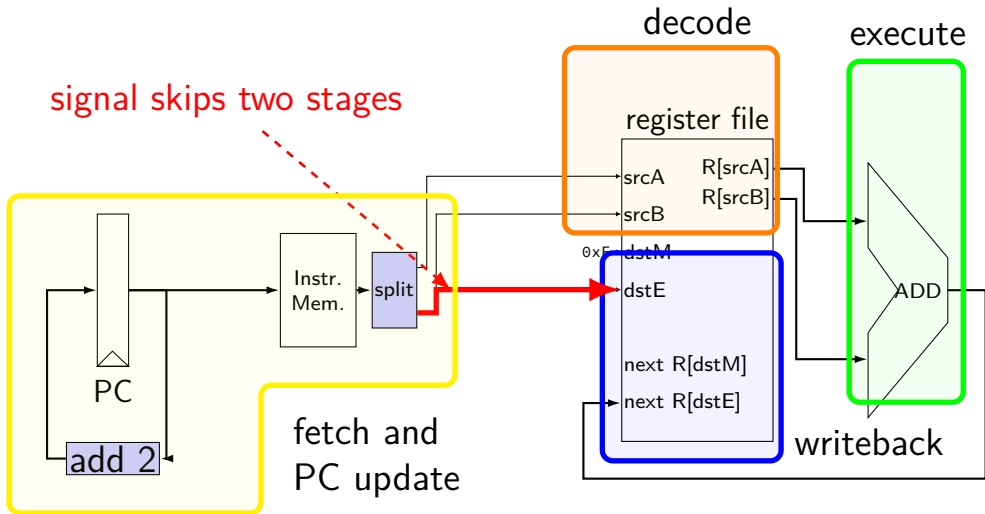


addq CPU

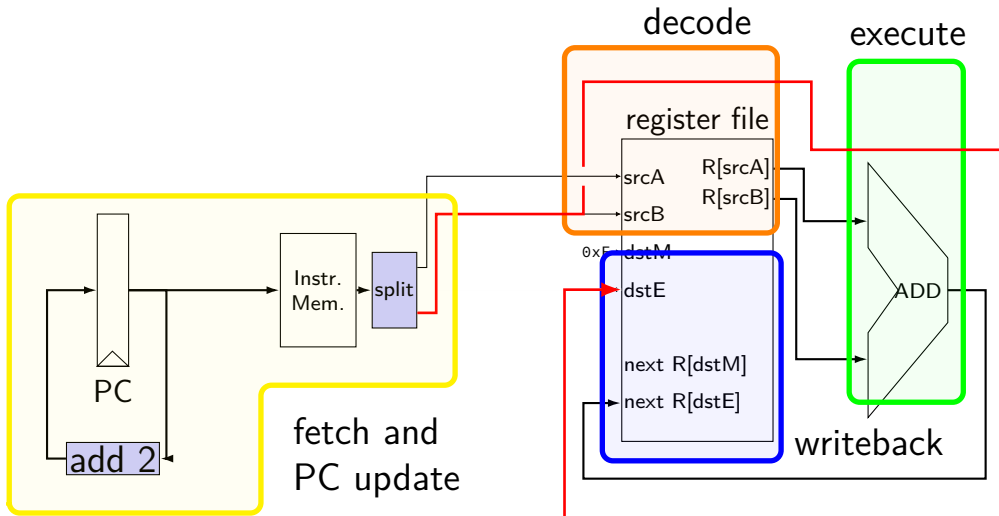


pipelined addq processor

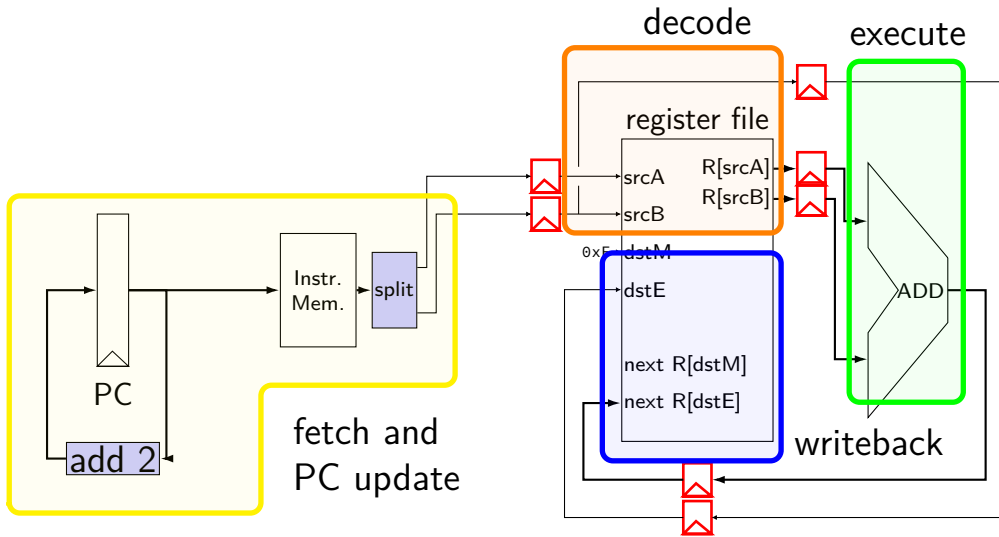


pipelined addq processor

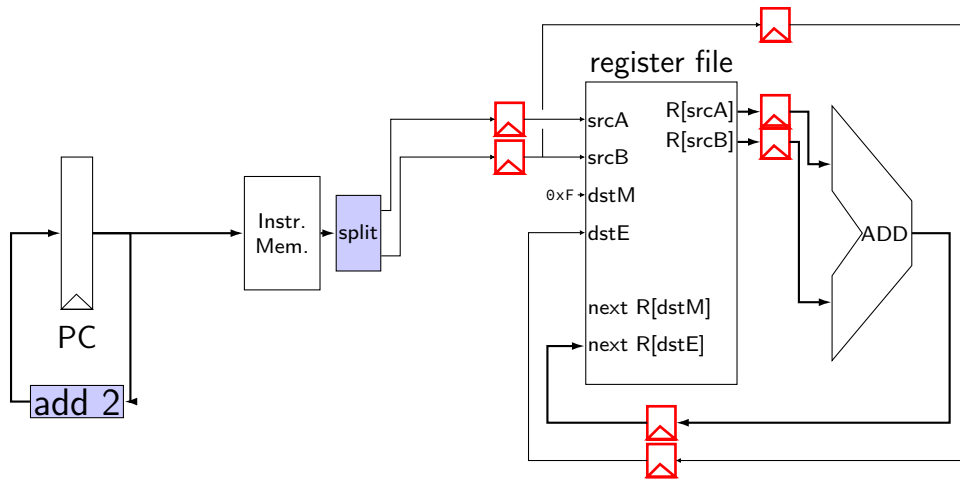

pipelined addq processor

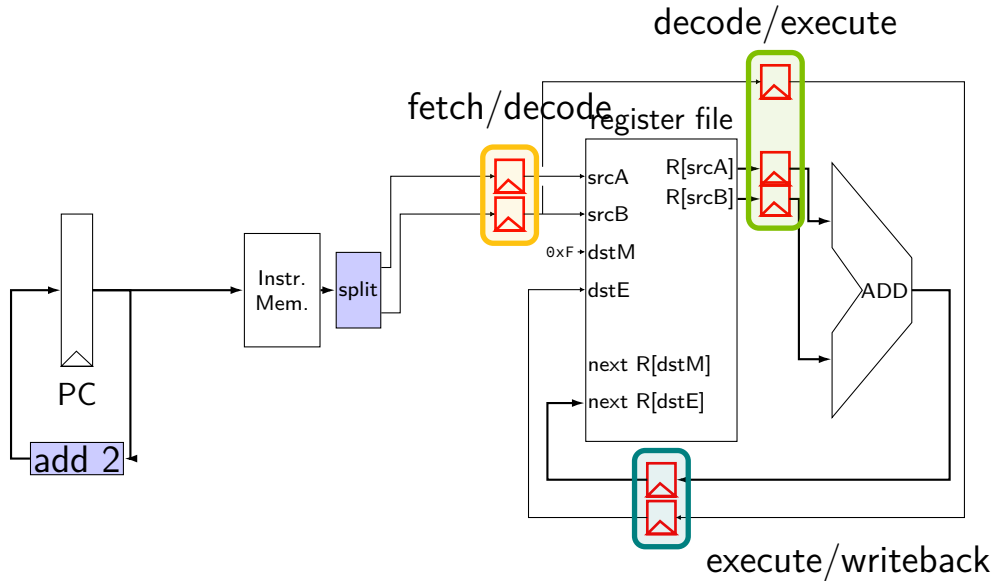


pipelined addq processor

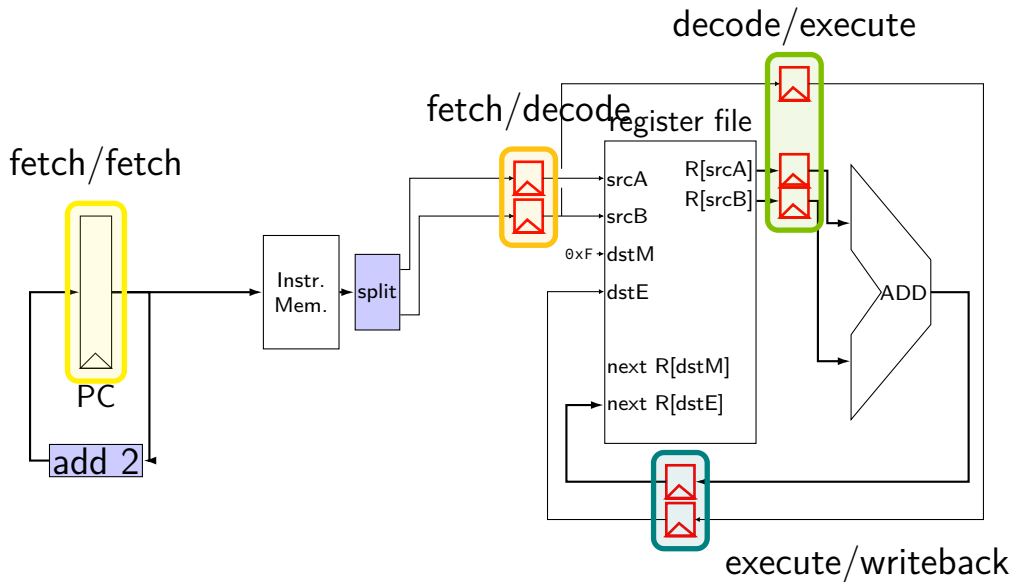


addq execution

```
addq %r8, %r9 // (1)  
addq %r10, %r11 // (2)
```


fetch/fetch

 

fetch/decode

 

decode/execute

 


execute/writeback

addq execution


```
addq %r8, %r9 // (1)  
addq %r10, %r11 // (2)
```

fetch/fetch

 


address of (2)

fetch/decode

 

decode/execute

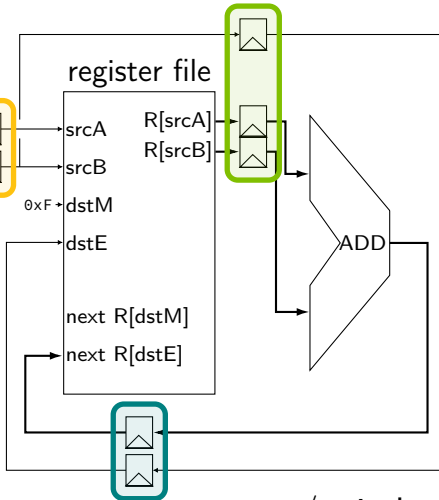


execute/writeback

addq execution

```
addq %r8, %r9 // (1)  
addq %r10, %r11 // (2)
```


fetch/fetch

 


reg #s 8, 9 from (1)

fetch/decode

addq %r10, %r11 // (2)

 


decode/execute

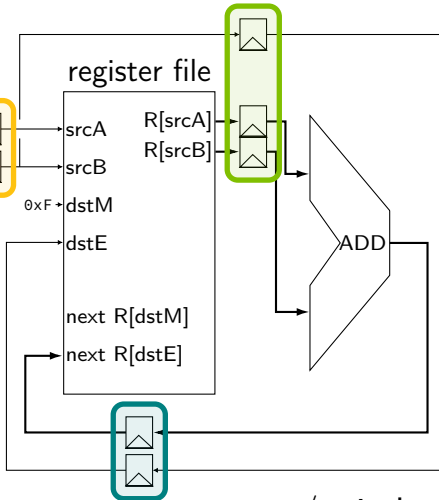

execute/writeback

addq execution

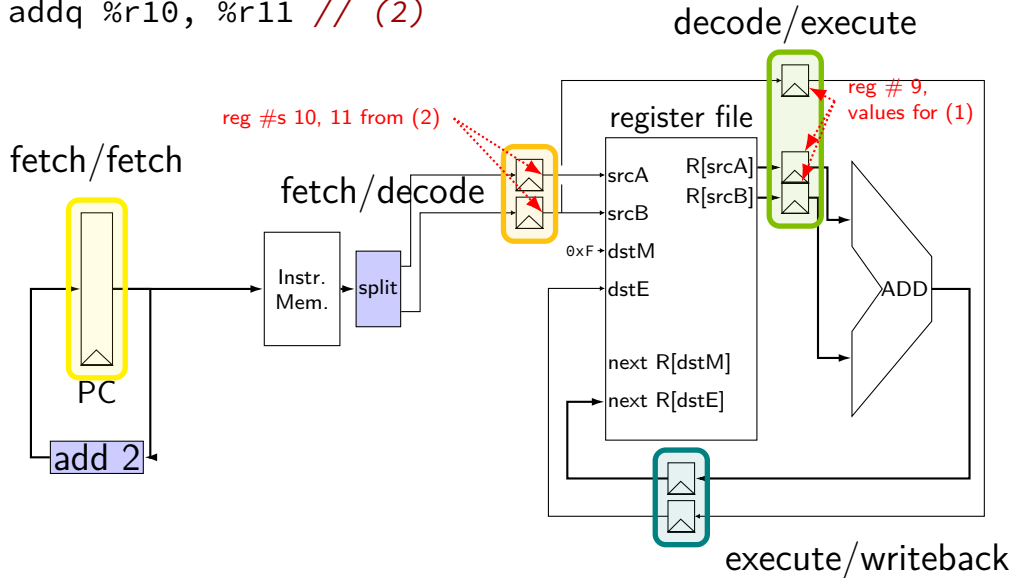
```
addq %r8, %r9 // (1)  
addq %r10, %r11 // (2)
```



addq processor timing

```
// initially %r8 = 800,
//           %r9 = 900, etc.
```
 
```
addq %r8, %r9
addq %r10, %r11
addq %r12, %r13
addq %r9, %r8
```




cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8

addq processor timing

```
// initially %r8 = 800,
//           %r9 = 900, etc.
```
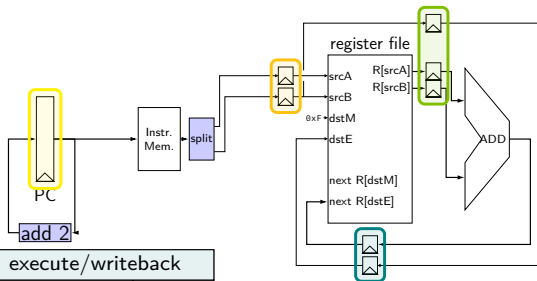
```
addq %r8, %r9
addq %r10, %r11
addq %r12, %r13
addq %r9, %r8
```




cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8

addq processor timing

```
// initially %r8 = 800,  
//           %r9 = 900, etc.
```
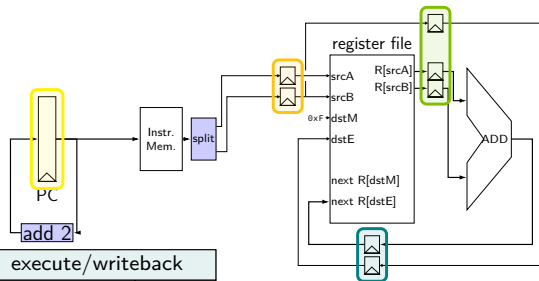
```
addq %r8, %r9  
addq %r10, %r11  
addq %r12, %r13  
addq %r9, %r8
```




cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8

addq processor timing

```
// initially %r8 = 800,  
//           %r9 = 900, etc.
```

```
addq %r8, %r9  
addq %r10, %r11  
addq %r12, %r13  
addq %r9, %r8
```


cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8

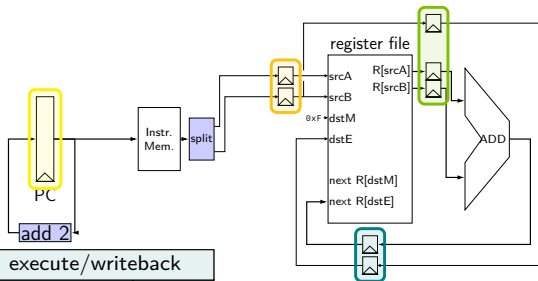

addq processor timing

```
// initially %r8 = 800,
//           %r9 = 900, etc.
```
 
```
addq %r8, %r9
addq %r10, %r11
addq %r12, %r13
addq %r9, %r8
```



cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8