

pipelining 1

last time

stages walkthrough

idea: table of what needs to happen for each instruction

special cases for stack instructions

book's strategy of adding zero

pipelining idea with laundry

higher *latency* — time from start to finish

higher *throughput* — work done per unit time

HCL4 aside

assignment: implement rest of single-cycle processor

includes push/pop/call/ret


HCLRS testing aside

test lists updated 14 Sep



a few may want to redownload

(but extra tests are basically subsets of other tests)


times three circuit

 


times three circuit

  


times three circuit

 


 
100 ps latency \implies 10 results/ns throughput




times three and repeat

 



times three and repeat

  



pipelined times three

 


pipelined times three

  


register tolerances

  


register tolerances

 


register tolerances

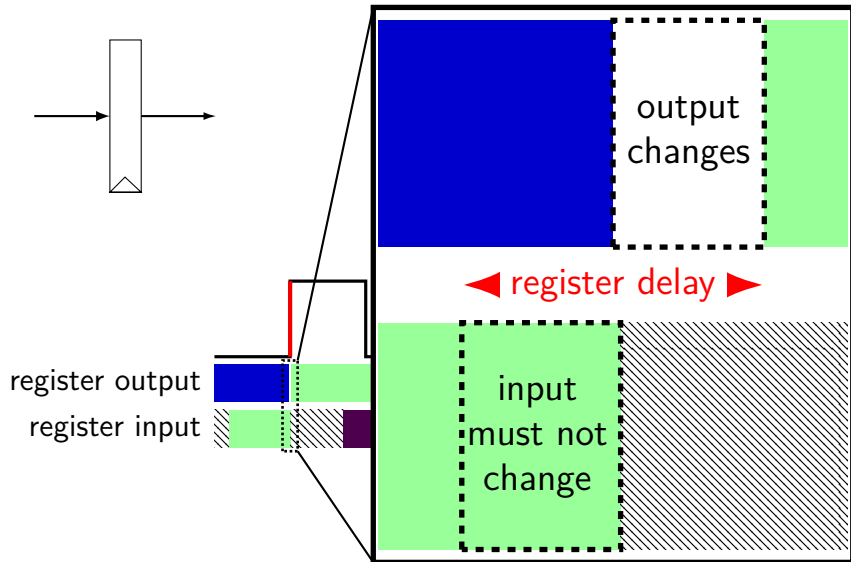

times three pipeline timing

 

times three pipeline timing

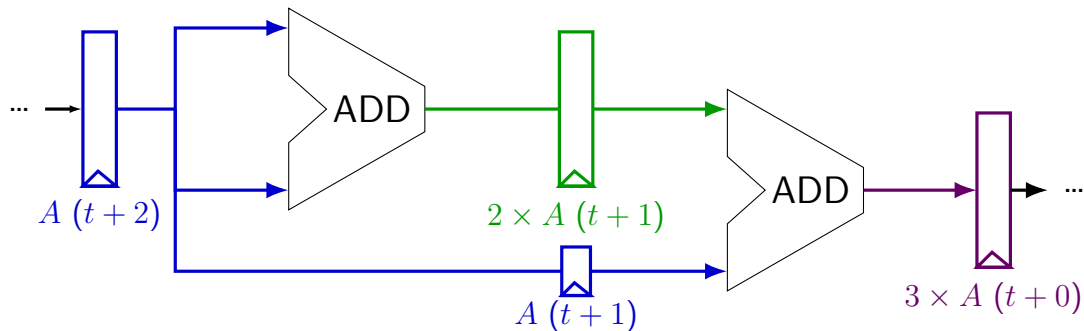

10 ps

50 ps

10 ps

50 ps

10 ps

exercise: minimum clock cycle time:

A. 50 ps



B. 60 ps

B. 65 ps

C. 70 ps


E. 130 ps

times three pipeline timing

  


throughput: $\frac{1}{60 \text{ ps}} \approx 16 \text{ G operations/sec}$


deeper pipeline

 

deeper pipeline

 


deeper pipeline

 

Problem: How much faster can we get?

Problem: Can we even do this?


deeper pipeline

 

exercise: throughput now?


- A. $1/(25 \text{ ps})$
- B. $1/(30 \text{ ps})$
- C. $1/(35 \text{ ps})$
- D. something else

deeper pipeline

 

throughput: $\frac{1}{35 \text{ ps}} \approx 28 \text{ G ops/sec}$


deeper pipeline

 


Problem: How much faster can we get?

Problem: Can we even do this?


diminishing returns: register delays

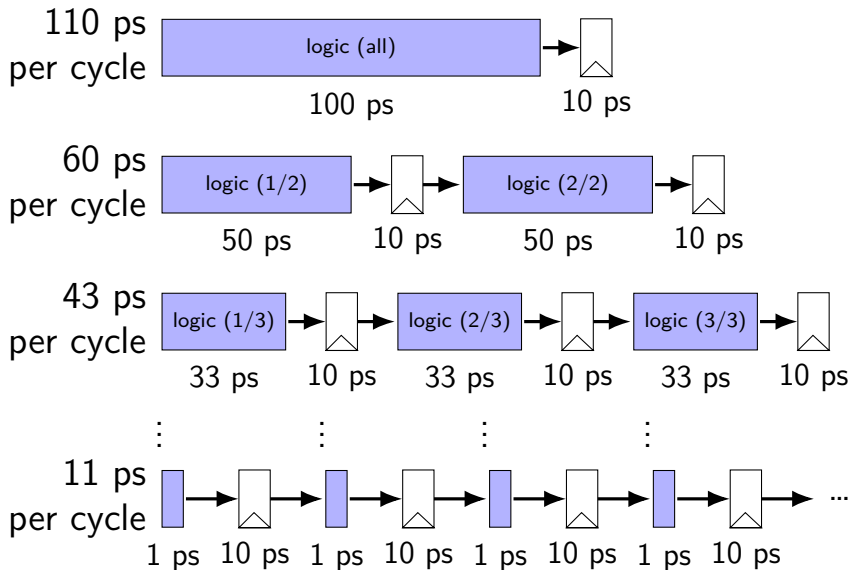


diminishing returns: register delays

 


diminishing returns: register delays

 


diminishing returns: register delays

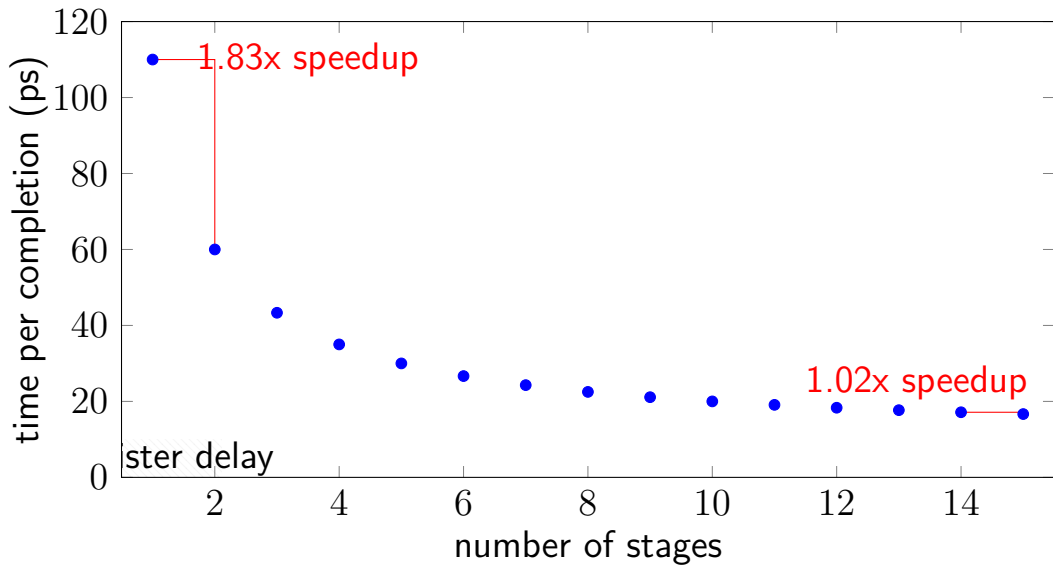


diminishing returns: register delays

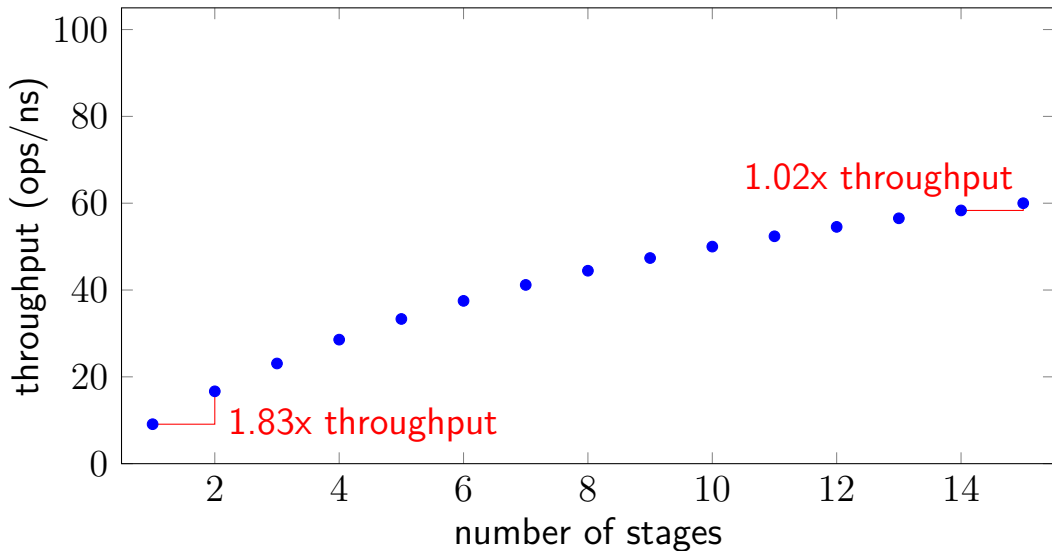

diminishing returns: register delays

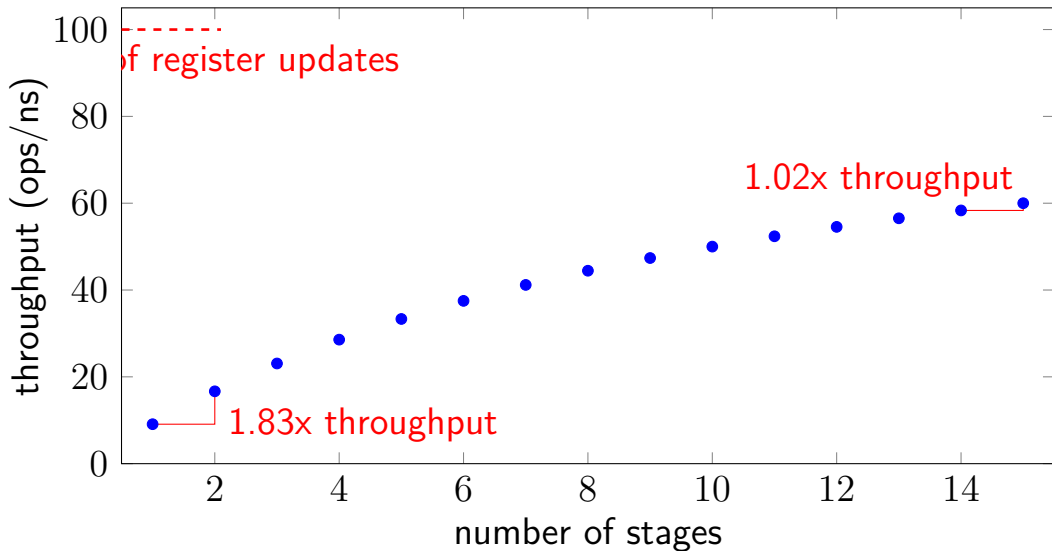


deeper pipeline

 

Problem: How much faster can we get?


Problem: **Can we even do this?**

deeper pipeline

 

exercise: throughput now? (didn't split second add evenly)

deeper pipeline

 

exercise: throughput now? (didn't split second add evenly)

A. $1/(25 \text{ ps})$


B. $1/(30 \text{ ps})$

C. $1/(35 \text{ ps})$

D. $1/(40 \text{ ps})$

E. something else


deeper pipeline

 

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?


Probably not...

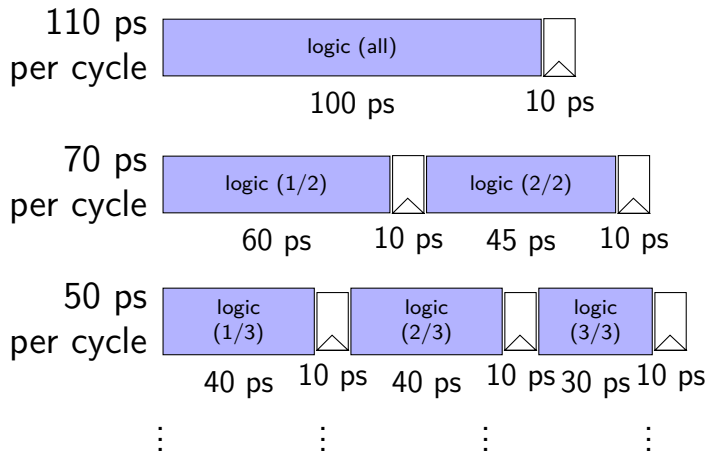

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?


Probably not...

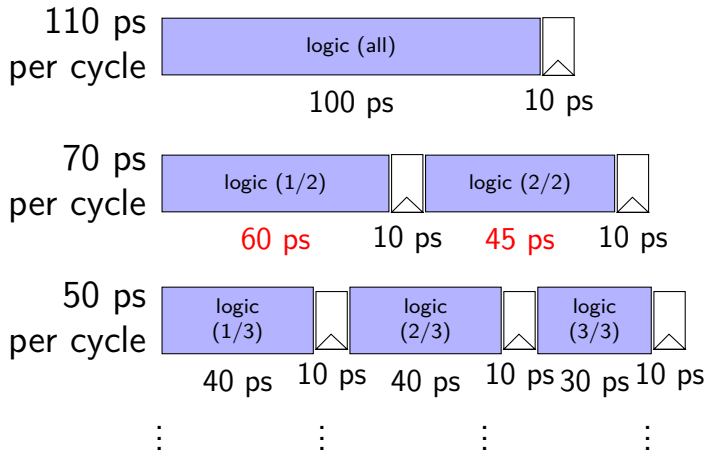

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?

Probably not...

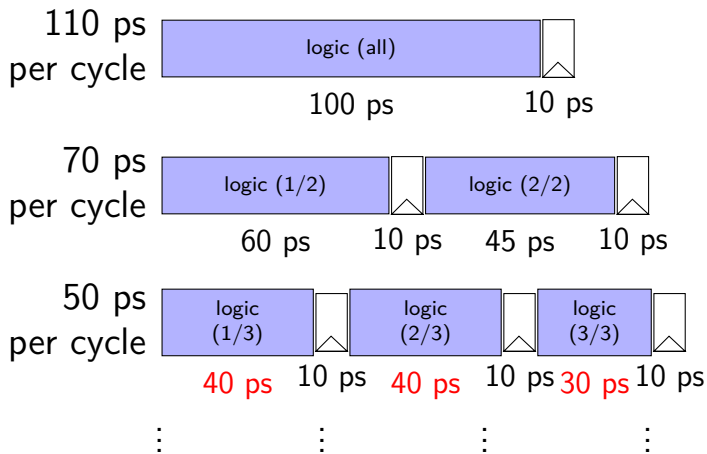

textbook SEQ 'stages'

conceptual order only

Fetch: read instruction memory

Decode: read register file

Execute: arithmetic (ALU)

Memory: read/write data memory

Writeback: write register file

PC Update: write PC register

textbook SEQ 'stages'

conceptual order only

Fetch: read instruction memory

Decode: read register file

Execute: arithmetic (ALU)

Memory: read/**write** data memory

Writeback: **write** register file

PC Update: **write** PC register

writes happen
at end of cycle

textbook SEQ 'stages'

conceptual order only

Fetch: **read** instruction memory

Decode: **read** register file

Execute: arithmetic (ALU)

Memory: **read**/write data memory

Writeback: write register file

PC Update: write PC register

reads — “magic”
like combinatorial logic
as values available

textbook stages

~~conceptual order only~~ pipeline stages

Fetch/PC Update: read instruction memory;
compute next PC

Decode: read register file

Execute: arithmetic (ALU)

Memory: read/write data memory

Writeback: write register file

textbook stages

conceptual order only pipeline stages

Fetch/PC Update: read instruction memory;
compute next PC

Decode: read register file


Execute: arithmetic (ALU)

Memory: read/write data memory


Writeback: write register file

5 stages
one instruction in each
compute next to start immediately

addq CPU

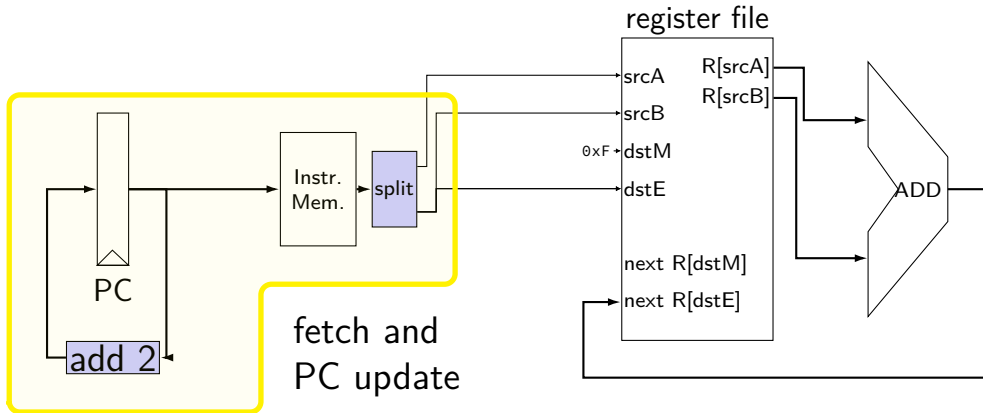


addq CPU

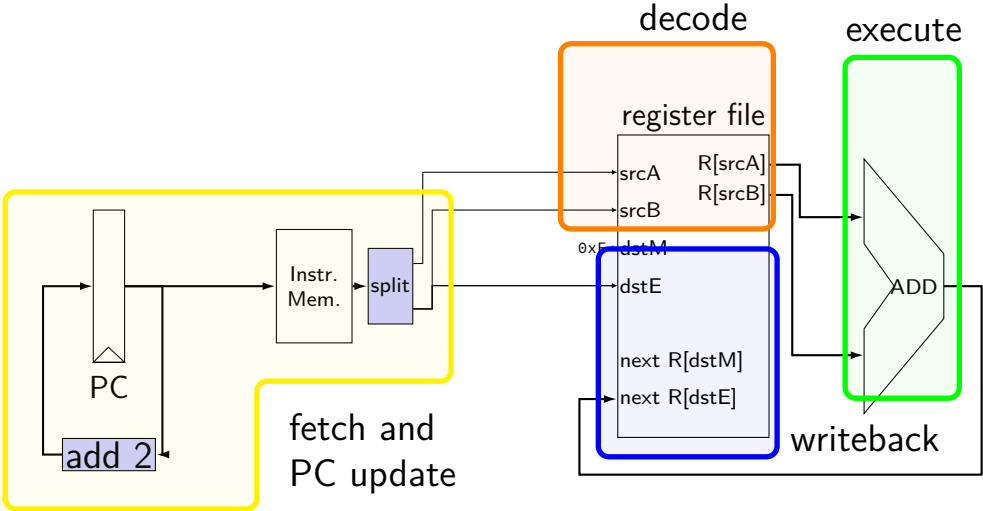


addq CPU


signal skips two stages

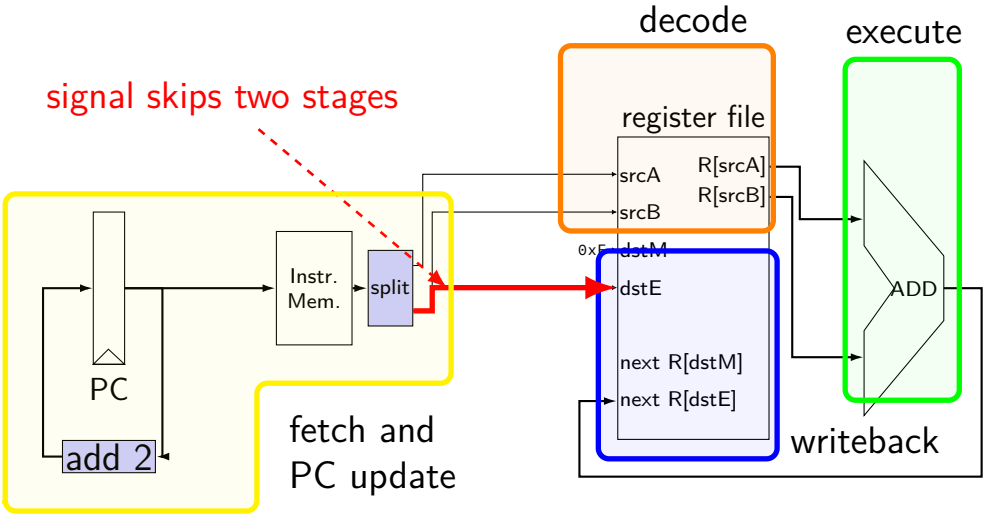


addq CPU

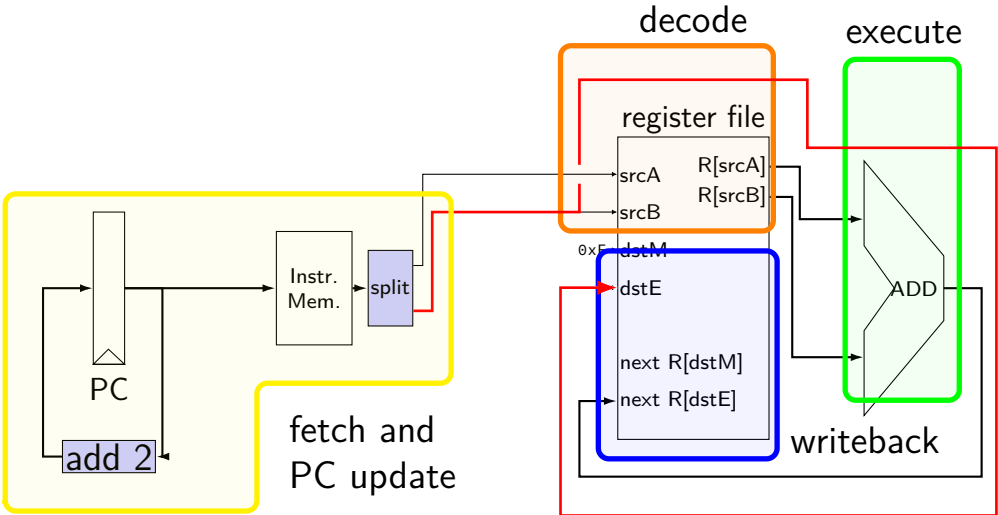


pipelined addq processor

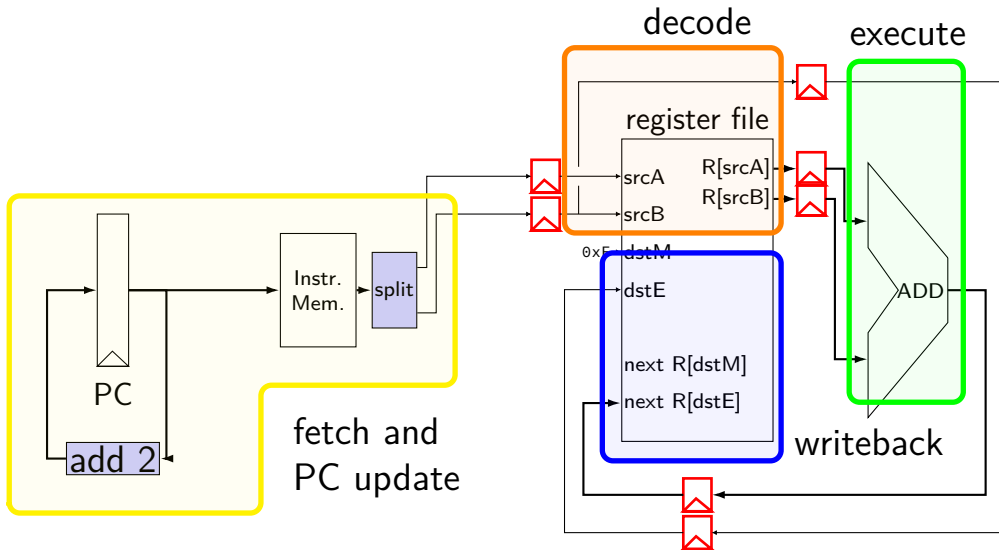


pipelined addq processor

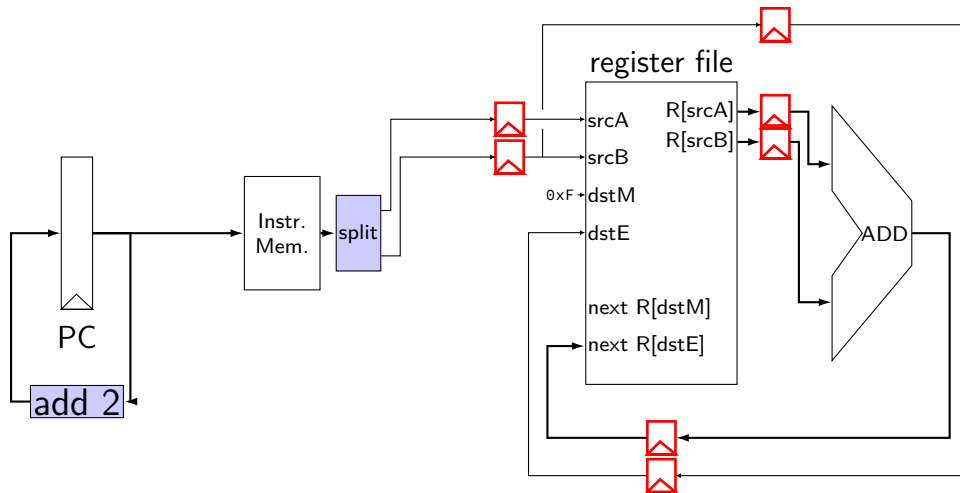

pipelined addq processor

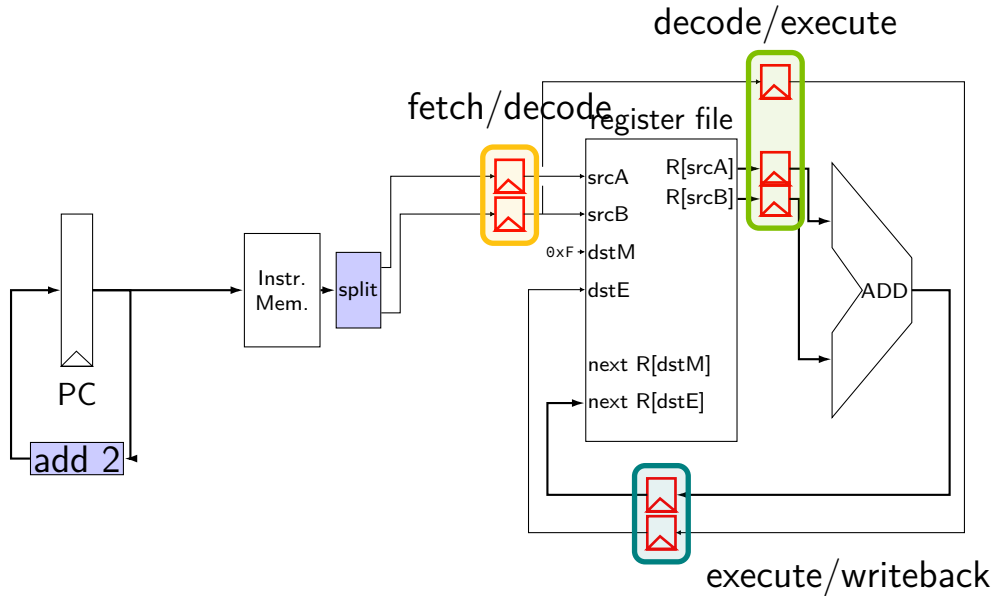


pipelined addq processor

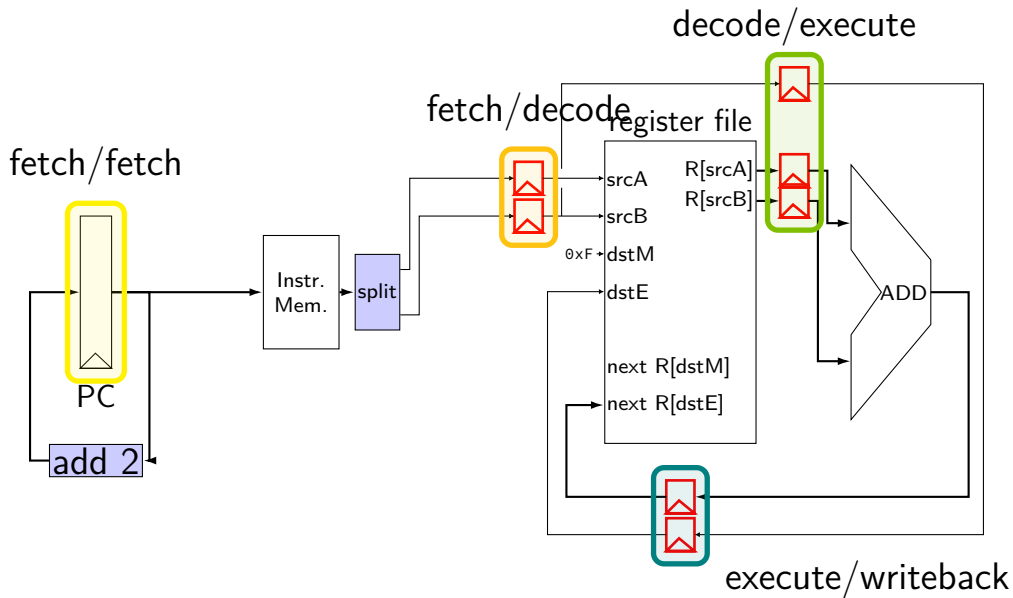


addq execution

```
addq %r8, %r9 // (1)  
addq %r10, %r11 // (2)
```


fetch/fetch

 

fetch/decode

 

decode/execute

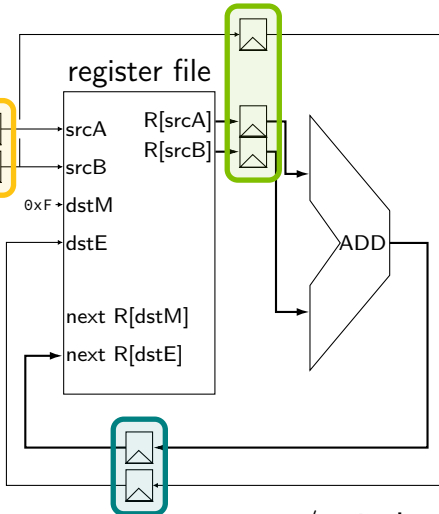


execute/writeback


addq execution

```
addq %r8, %r9 // (1)  
addq %r10, %r11 // (2)
```

fetch/fetch

 


fetch/decode

 

addq %r8, %r9 // (1)

decode/execute

 


execute/writeback

addq execution

```
addq %r8, %r9 // (1)  
addq %r10, %r11 // (2)
```


fetch/fetch

 


reg #s 8, 9 from (1)

fetch/decode

addq %r10, %r11 // (2)

 


decode/execute

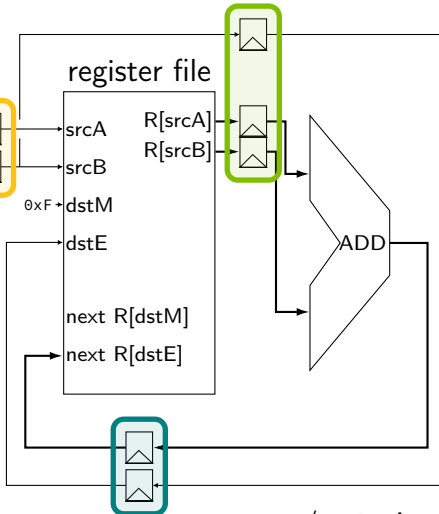

execute/writeback

addq execution
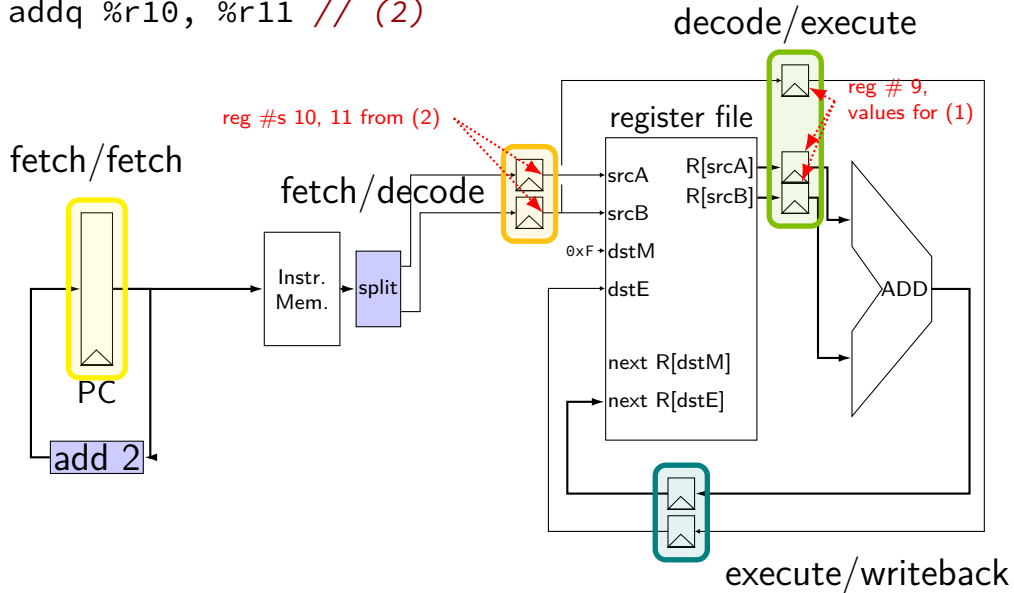
```
addq %r8, %r9 // (1)  
addq %r10, %r11 // (2)
```




addq processor timing

```
// initially %r8 = 800,  
//           %r9 = 900, etc.
```

```
addq %r8, %r9  
addq %r10, %r11  
addq %r12, %r13  
addq %r9, %r8
```

cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8

 


addq processor timing

```
// initially %r8 = 800,  
//           %r9 = 900, etc.
```

```
addq %r8, %r9  
addq %r10, %r11  
addq %r12, %r13  
addq %r9, %r8
```

cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8

 


addq processor timing

```
// initially %r8 = 800,  
//           %r9 = 900, etc.
```

```
addq %r8, %r9  
addq %r10, %r11  
addq %r12, %r13  
addq %r9, %r8
```

cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8

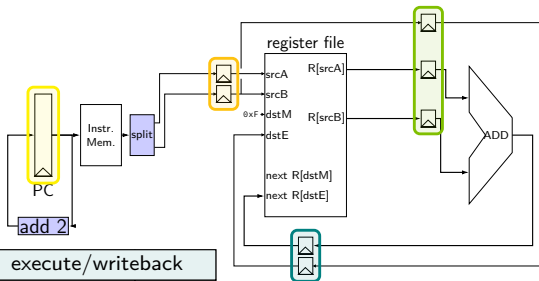


addq processor timing

```
// initially %r8 = 800,  
//           %r9 = 900, etc.
```

```
addq %r8, %r9  
addq %r10, %r11  
addq %r12, %r13  
addq %r9, %r8
```


cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8

 

addq processor timing

```
// initially %r8 = 800,  
//           %r9 = 900, etc.
```
 
```
addq %r8, %r9  
addq %r10, %r11  
addq %r12, %r13  
addq %r9, %r8
```



cycle	fetch	fetch/decode		decode/execute			execute/writeback	
	PC	rA	rB	R[srcA]	R[srcB]	dstE	next R[dstE]	dstE
0	0x0							
1	0x2	8	9					
2	0x4	10	11	800	900	9		
3	0x6	12	13	1000	1100	11	1700	9
4		9	8	1200	1300	13	2100	11
5				1700	800	8	2500	13
6							2500	8

critical path


every path from state output to state input needs enough time
output — may change on rising edge of clock
input — must be stable sufficiently before rising edge of clock

critical path: **slowest** of all these paths — determines cycle time
times three: slowest stage ended up mattering

have to choose *one* clock cycle length
can't vary clock depending on what instruction is running


matters with or without pipelining

SEQ paths

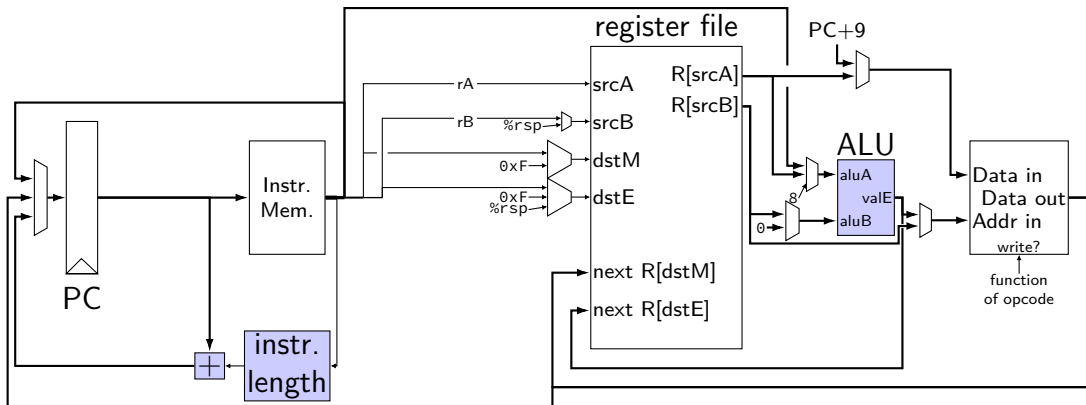

SEQ paths


path 1: 25 picoseconds

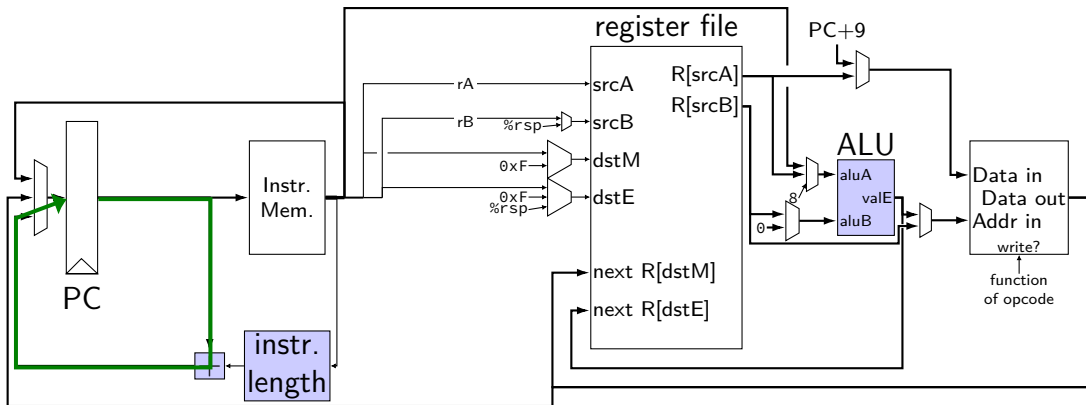

SEQ paths

path 1: 25 picoseconds

path 2: 50 picoseconds

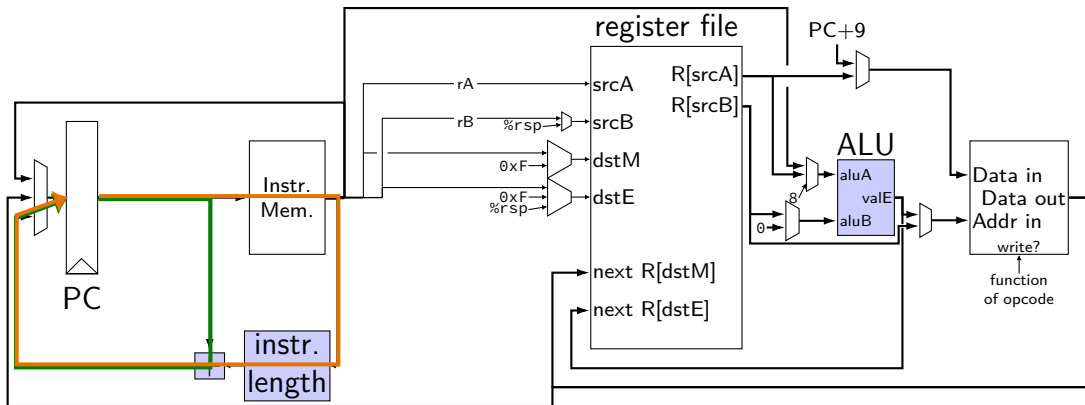


SEQ paths

path 1: 25 picoseconds

path 2: 50 picoseconds


path 3: 400 picoseconds

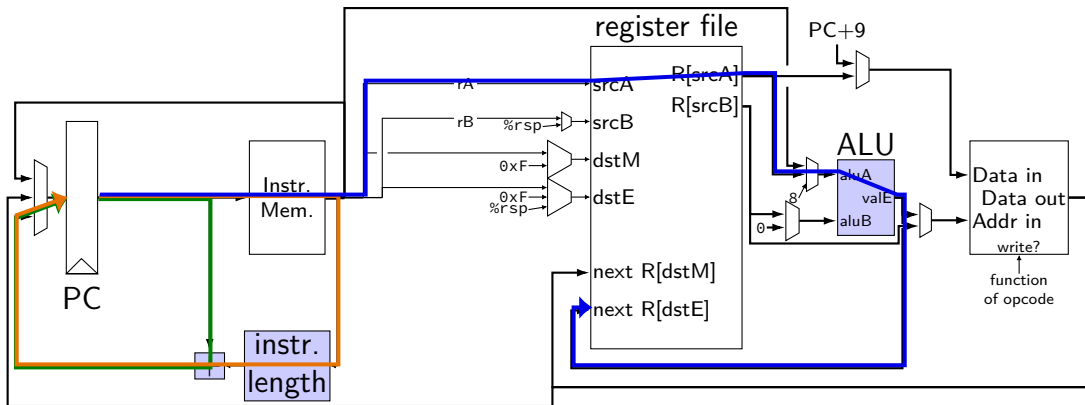

SEQ paths

path 1: 25 picoseconds
path 3: 400 picoseconds
...

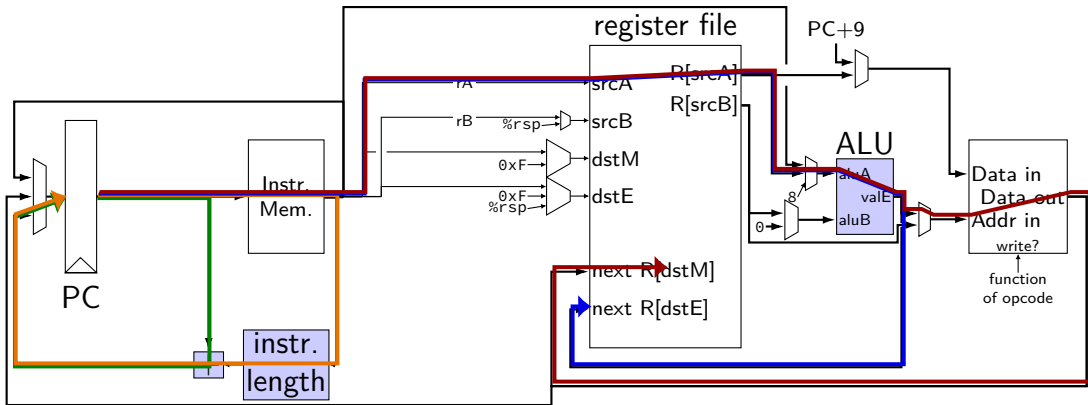path 2: 50 picoseconds
path 4: 900 picoseconds
...




SEQ paths

path 1: 25 picoseconds
path 3: 400 picoseconds


path 2: 50 picoseconds
path 4: 900 picoseconds

...

...

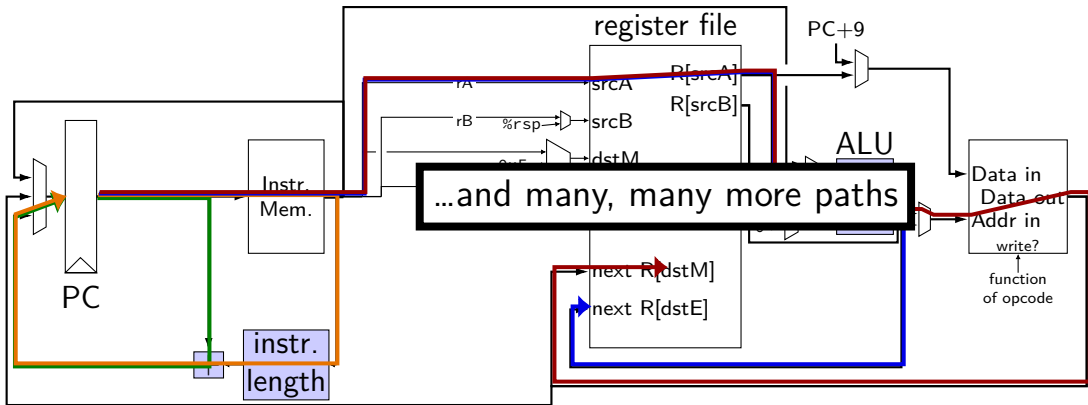


sequential addq paths

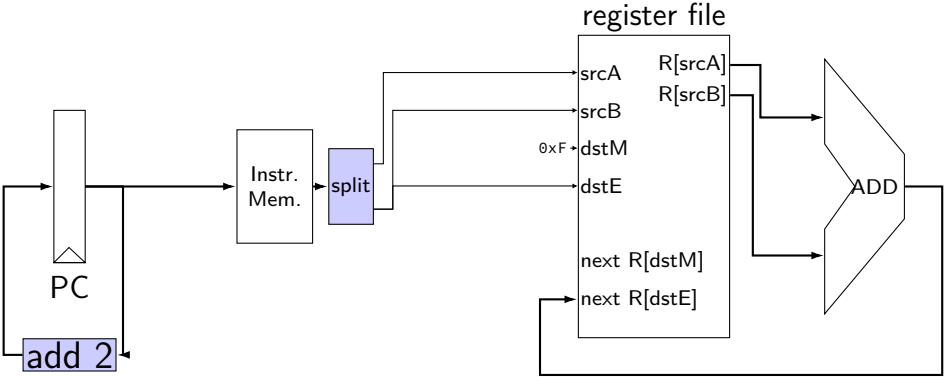

sequential addq paths


path 1: 25 picoseconds

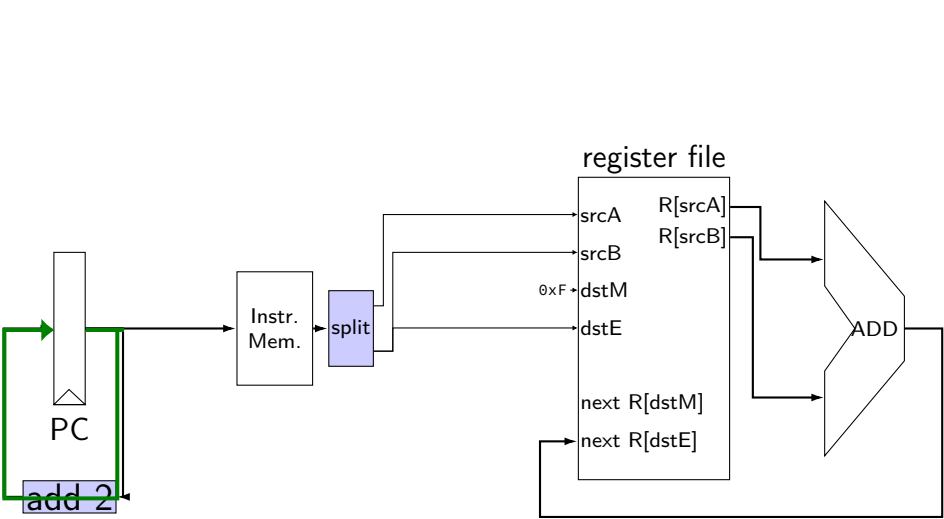

sequential addq paths


path 1: 25 picoseconds

path 2: 375 picoseconds

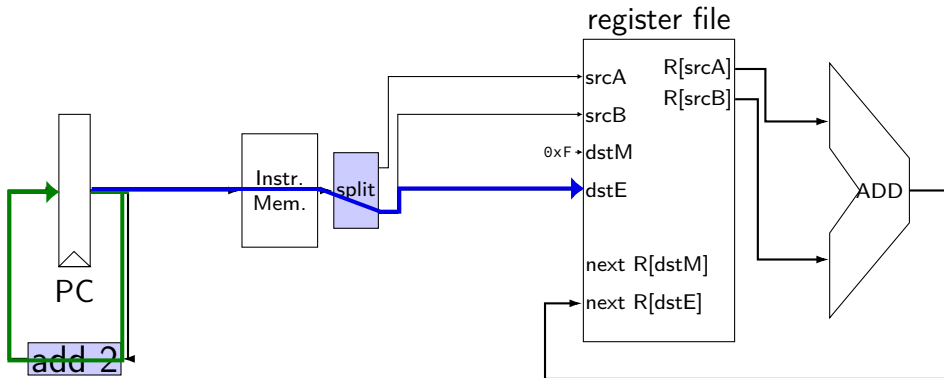


sequential addq paths

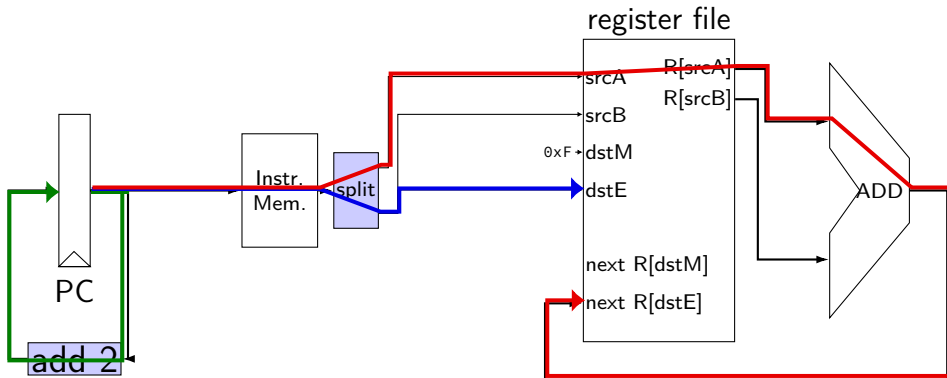- path 1: 25 picoseconds
- path 2: 375 picoseconds
- path 3: 500 picoseconds



sequential addq paths

 - path 1: 25 picoseconds
- path 2: 375 picoseconds
- path 3: 500 picoseconds
- path 4: 500 picoseconds



sequential addq paths


path 1: 25 picoseconds

path 2: 375 picoseconds


path 3: **500 picoseconds**

path 4: **500 picoseconds**

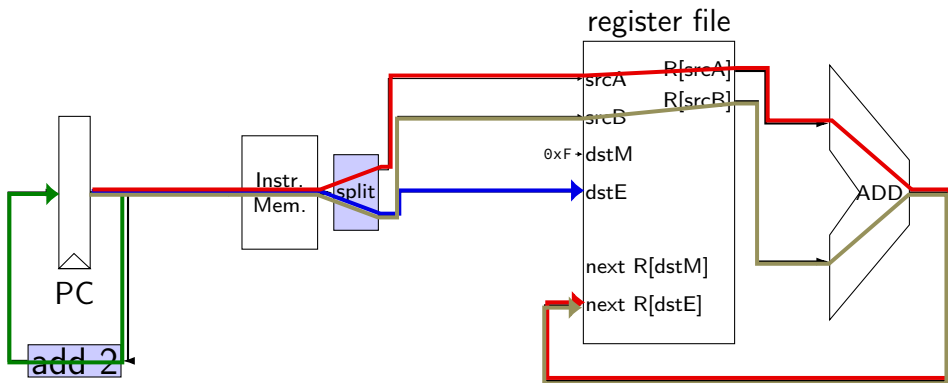overall cycle time: **500 picoseconds** (longest path)



pipelined addq paths

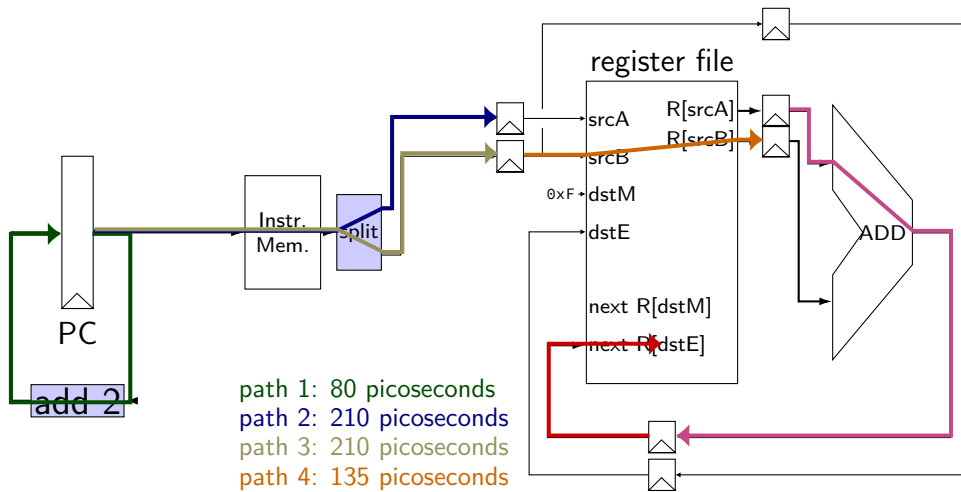


path 1: 80 picoseconds
path 2: 210 picoseconds
path 3: 210 picoseconds
path 4: 135 picoseconds
path 5: 110 picoseconds
path 6: 135 picoseconds

...

overall cycle time: 210 picoseconds

pipelined addq paths

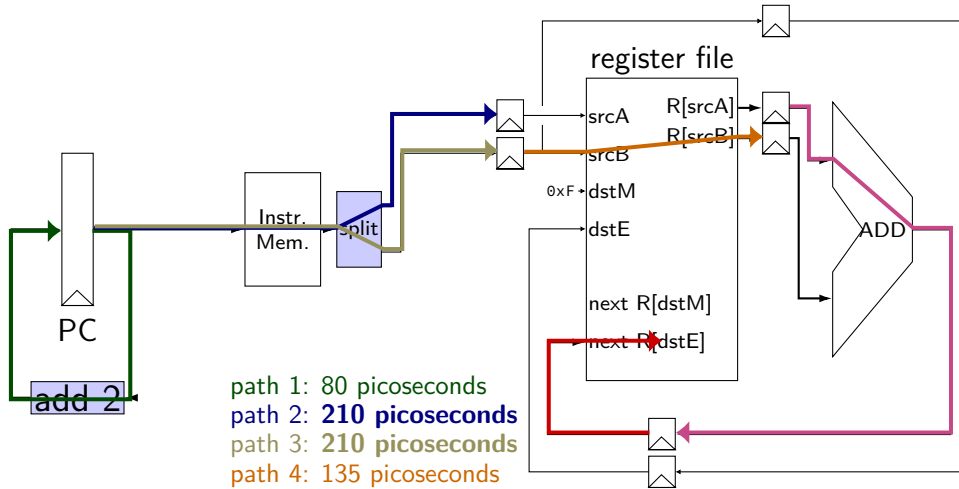


- path 1: 80 picoseconds
- path 2: **210 picoseconds**
- path 3: **210 picoseconds**
- path 4: 135 picoseconds
- path 5: 110 picoseconds
- path 6: 135 picoseconds

...
overall cycle time: **210 picoseconds**

addq processor performance

example delays:

path	time
add 2	80 ps
instruction memory	200 ps
register file read	125 ps
add	100 ps
register file write	125 ps

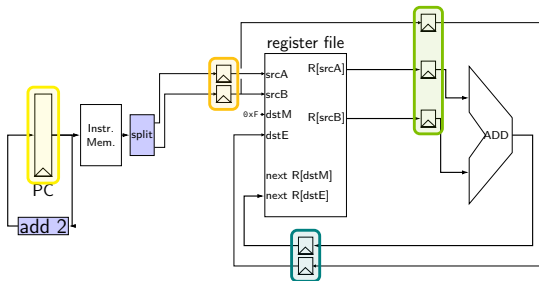

no pipelining: 1 instruction per 550 ps

add up everything but add 2 (**critical (slowest) path**)

pipelining: 1 instruction per 200 ps + pipeline register delays

slowest path through stage + pipeline register delays


latency: 800 ps + pipeline register delays (4 cycles)

addq processor performance exercise

example delays:

path	time
add 2	80 ps
instruction memory	200 ps
register file read	125 ps
add	100 ps
register file write	125 ps


now, cycle time = 200 ps + register delays per cycle

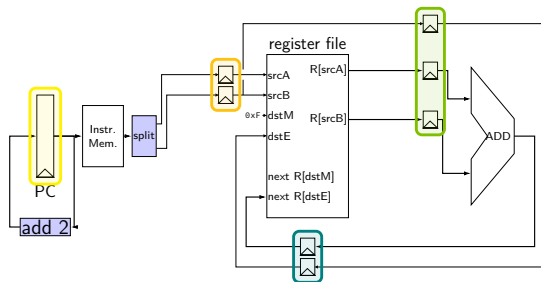

exercise 2:

suppose we combine add and register file read together — new cycle time?

pipeline register naming convention

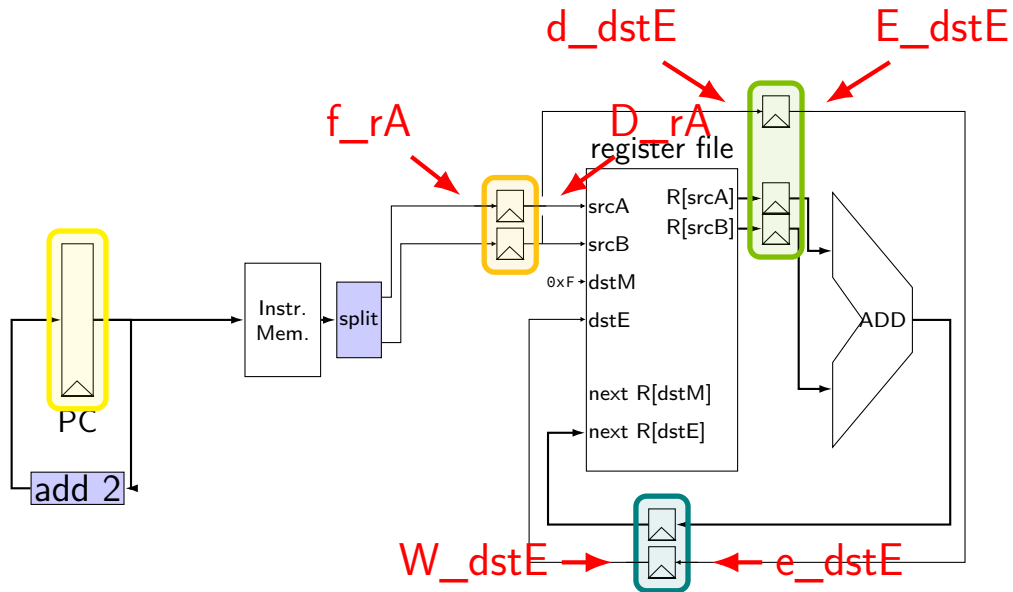

pipeline register naming convention

f — fetch sends values here

D — decode receives values here

d — decode sends values here

...

addq HCL

```
...
/* f: from fetch */
f_rA = i10bytes[12..16];
f_rB = i10bytes[8..12];

/* fetch to decode */
/* f_rA -> D_rA, etc. */
register fD {
    rA : 4 = REG_NONE;
    rB : 4 = REG_NONE;
}
```

```
/* D: to decode
   d: from decode */
d_dstE = D_rB;
/* use register file: */
reg_srcA = D_rA;
d_valA = reg_outputA;
...

/* decode to execute */
register dE {
    dstE : 4 = REG_NONE;
    valA : 64 = 0;
    valB : 64 = 0;
}
```

```
...
```

addq fetch/decode

unpipelined

```
/* Fetch+PC Update*/  
pc = P_pc;  
p_pc = pc + 2;  
rA = i10bytes[12..16];  
rB = i10bytes[8..12];  
/* Decode */  
reg_srcA = rA;  
reg_srcB = rB;  
reg_dstE = rB;  
valA = reg_outputA;  
valB = reg_outputB;
```


pipelined

```
/* Fetch+PC Update*/  
pc = P_pc;  
p_pc = pc + 2;  
f_rA = i10bytes[12..16];  
f_rB = i10bytes[8..12];  
/* Decode */  
reg_srcA = D_rA;  
reg_srcB = D_rB;  
d_dstE = D_rB;  
d_valA = reg_outputA;  
d_valB = reg_outputB;
```



addq pipeline registers

```
register pP {
    pc : 64 = 0;
};
/* Fetch+PC Update*/
register fD {
    rA : 4 = REG_NONE; rB : 4 = REG_NONE;
};
/* Decode */
register dE {
    valA : 64 = 0; valB : 64 = E; dstE : 4 = REG_NONE;
}
/* Execute */
register eW {
    valE : 64 = 0; dstE : 4 = REG_NONE;
}
/* Writeback */
```


SEQ without stages

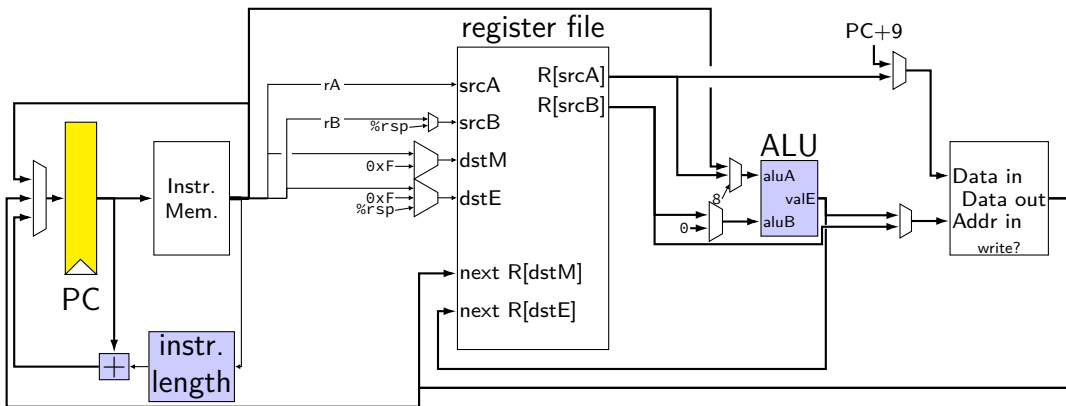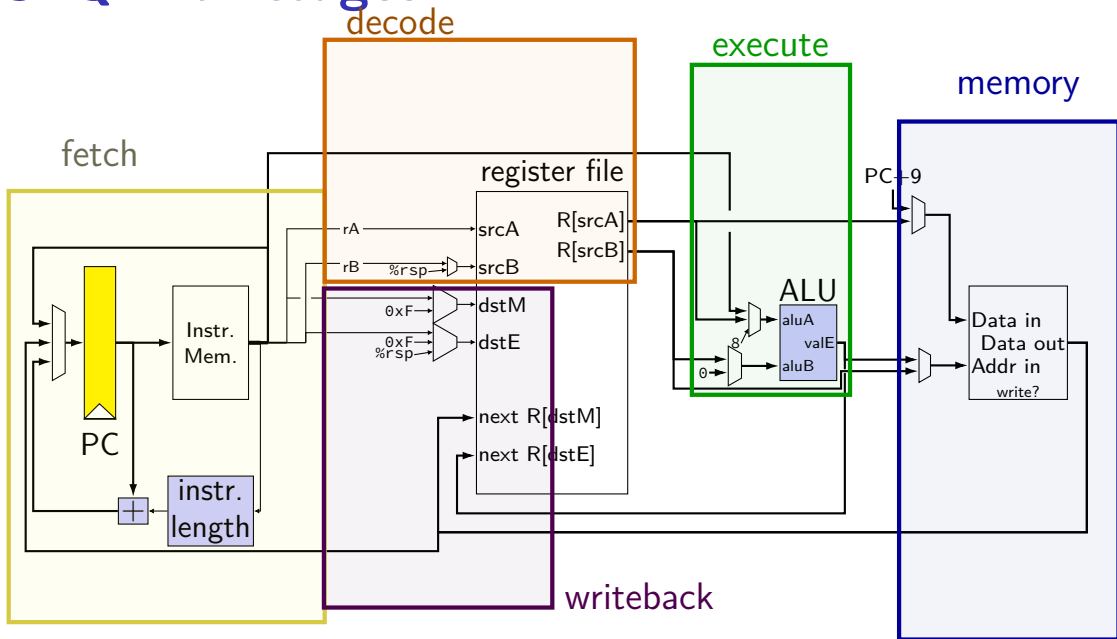


SEQ with stages




SEQ with stages

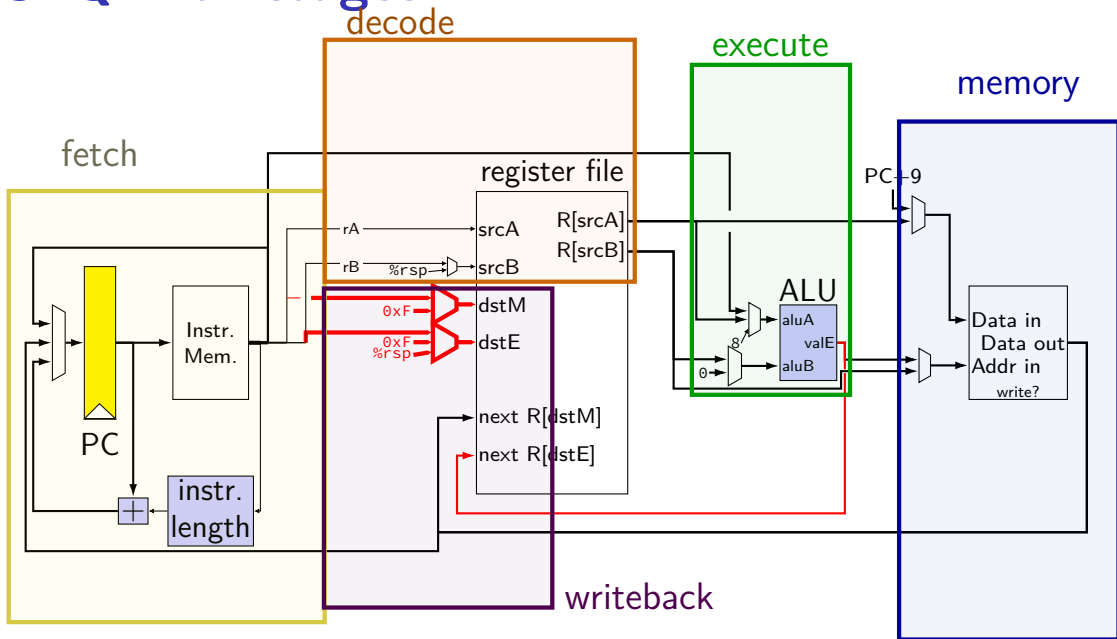


SEQ with stages

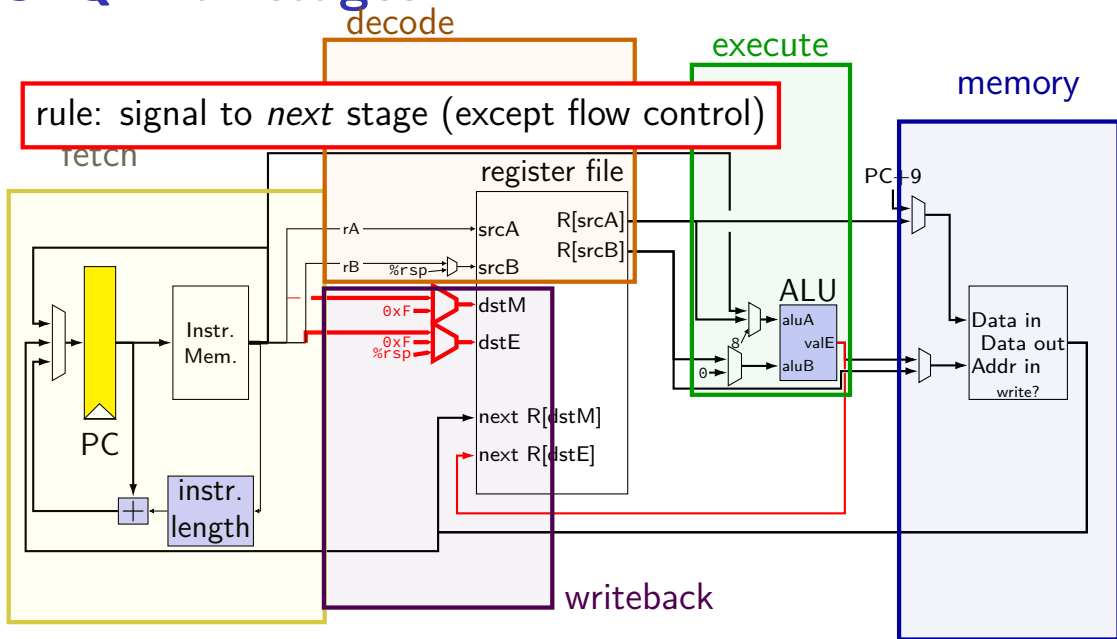


SEQ with stages (actually sequential)

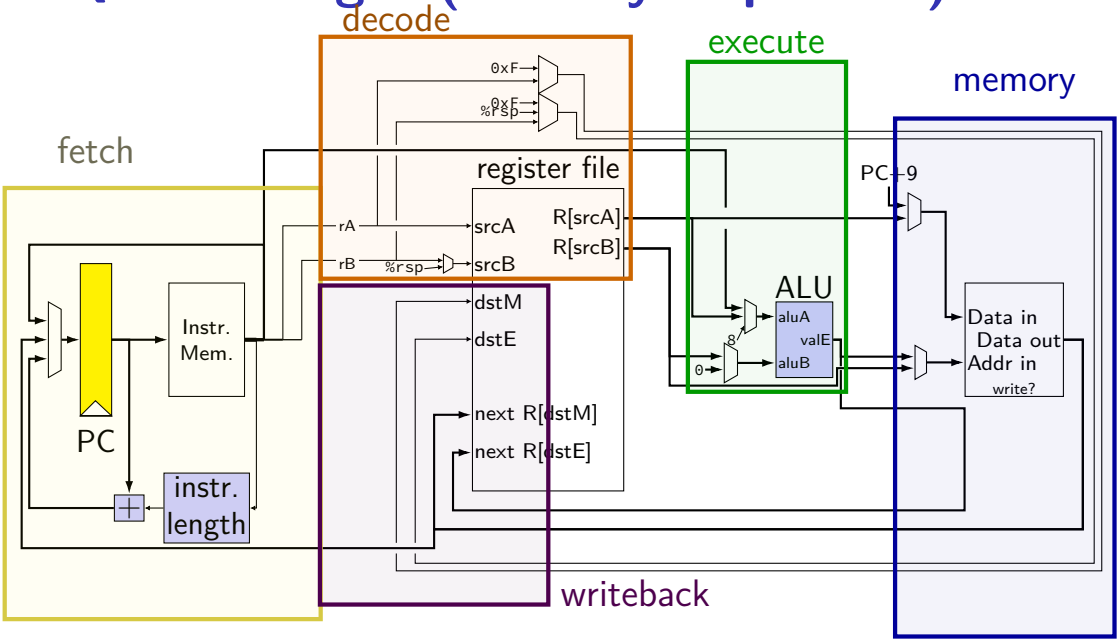

adding pipeline registers

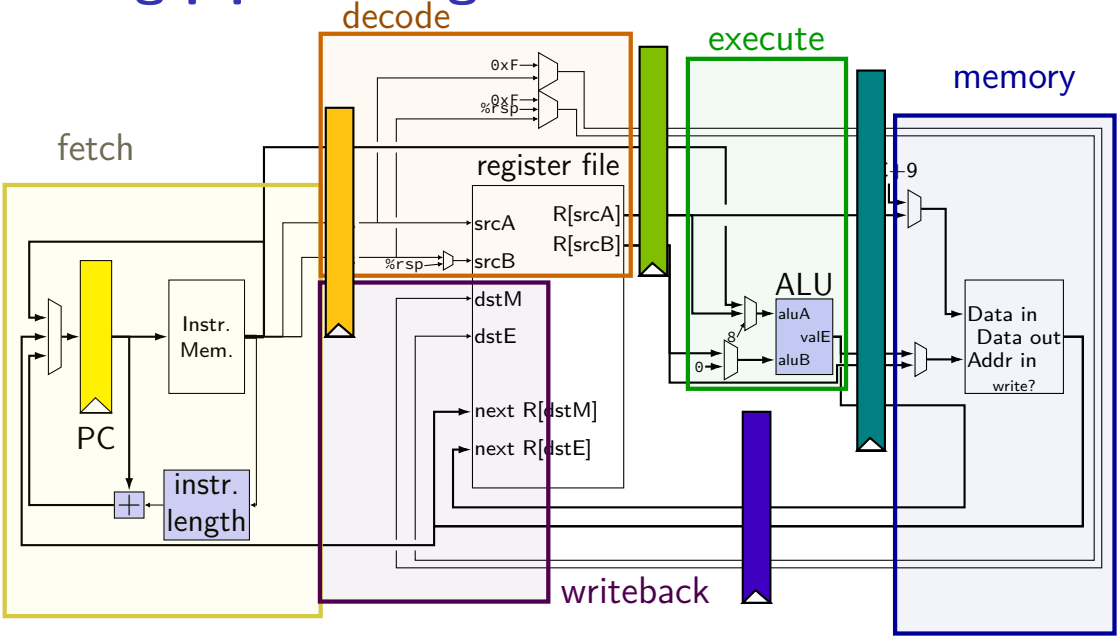

adding pipeline registers

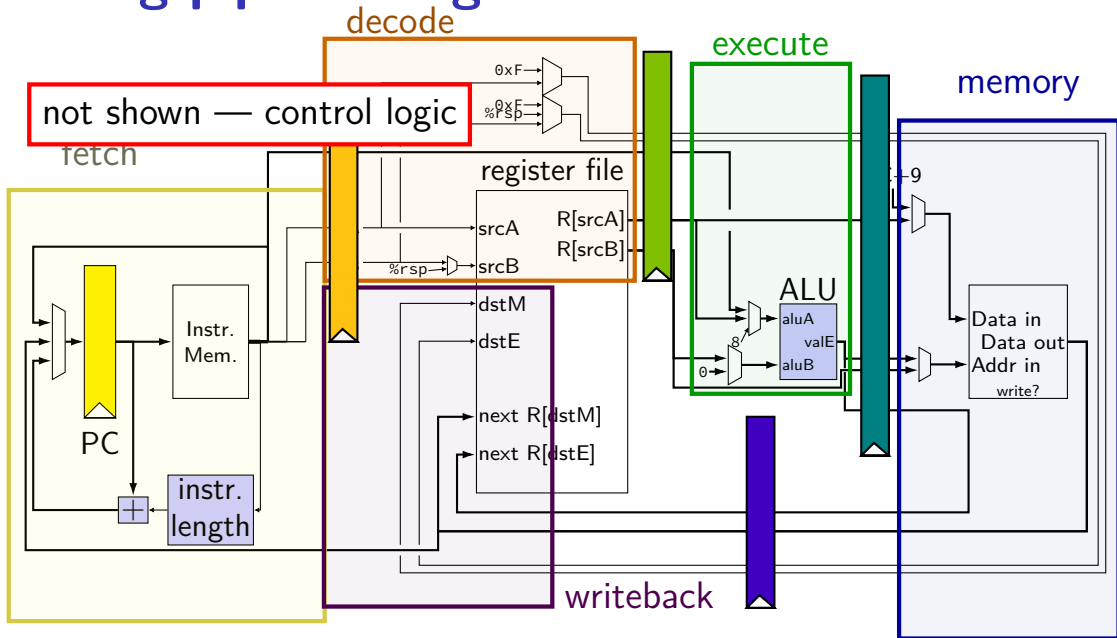

passing values in pipeline

read **prior stage's outputs**

e.g. decode: get from fetch via pipeline registers (D_icode, ...)

send **inputs for next stage**


e.g. decode: send to execute via pipeline registers (d_icode, ...)

exceptions: **deliberate sharing** between instructions


via register file/memory/etc.

via control flow instructions


memory read/write logic

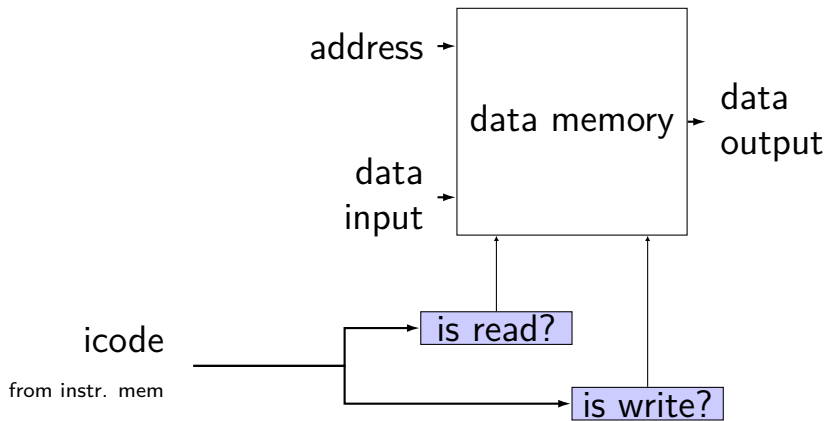

memory read/write logic

 

memory read/write logic

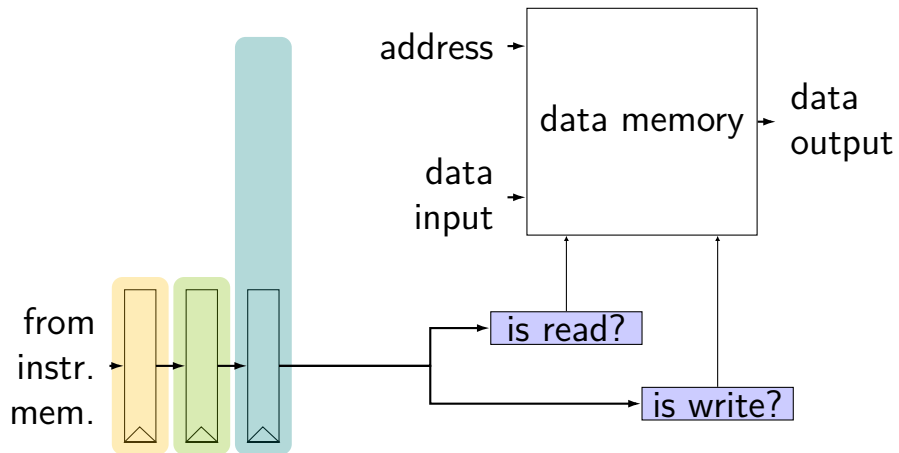

memory read/write: SEQ code

```
icode = i10bytes[4..8];  
mem_readbit = [  
    icode == MRMOVQ || ...: 1;  
    0;  
];
```

memory read/write: PIPE code

```
f_icode = i10bytes[4..8];
register fD { /* and dE and eM and mW */
    icode : 4 = NOP;
}
d_icode = D_icode;
...
e_icode = E_icode;
mem_readbit = [
    M_icode == MRMOVQ || ... : 1;
    0;
];
```

memory read/write: PIPE code

```
f_icode = i10bytes[4..8];
register fD { /* and dE and eM and mW */
    icode : 4 = NOP;
}
d_icode = D_icode;
...
e_icode = E_icode;
mem_readbit = [
    M_icode == MRMOVQ || ...: 1;
    0;
];
```