

SEQ part 4 / pipelining 0

last time

building processors: add MUX for each decision

single-cycle processor timing

storage (memory, registers, register file) write at rising edge

therefore, rising edge changes storage outputs = other circuit inputs

everything else adjusts as their inputs change

clock signal long enough to give storage stable inputs (at rising edge)

so-called “stages”

conceptual division of the processor (later: timing division)

fetch (read instruction; split into pieces; *compute next instruction addr*)

‘decode’ (read from register file)

execute (ALU operation; condition codes)

memory (setup data memory access)

writeback (setup write to register file)

PC update (setup next PC value)

SEQ: instruction fetch

read instruction memory at PC

split into separate wires:

`icode:ifun` — opcode


`rA, rB` — register numbers

`valC` — call target or mov displacement

compute next instruction address:

`valP` — $PC + (\text{instr length})$

instruction fetch

 


SEQ: instruction “decode”


read registers

valA, valB — register values

instruction decode (1)

 


instruction decode (1)

 

exercise: for which instructions would there be a problem ?
nop, addq, mrmovq, rmmovq, jmp, pushq

instruction decode (1)

 

SEQ: srcA, srcB

always read rA, rB?

Problems:

push rA

pop

call


ret

book: extra signals: srcA, srcB — computed input register

MUX controlled by icode


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmoveCC, rrmovq	rA	none
mrmmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmoveCC, rrmovq	rA	none
mrmmovq	none	rB
rrmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 

instruction decode (2)

 

SEQ: execute

perform ALU operation (add, sub, xor, and)


valE — ALU output

read prior condition codes


Cnd — condition codes based on ifun (instruction type for jCC/cmovCC)

write new condition codes


using condition codes: cmove

 

execute (1)

 

execute (1)

 


exercise: which of these instructions would there be a problem ?
nop, addq, mrmovq, popq, call,

SEQ: ALU operations?

ALU inputs always valA, valB (register values)?

no, inputs from instruction: (Displacement + rB)

`mrmovq`
`rmmovq`

 


no, constants: (rsp +/- 8)

`pushq`
`popq`
`call`
`ret`

extra signals: aluA, aluB

computed ALU input values

execute (2)

 


SEQ: Memory


read or write data memory

valM — value read from memory (if any)

memory (1)

 

memory (1)

 

exercise: which of these instructions would there be a problem ?
nop, rmmovq, mrmovq, popq, call,

SEQ: control signals for memory

read/write — **read enable?** **write enable?**

Addr — address

mostly ALU output


special cases (need extra MUX): **popq, ret**

Data — value to write

mostly valA

special cases (need extra MUX): **call**


memory (2)

 


SEQ: write back

write registers


write back (1)

 

write back (1)

 

write back (1)

 


exercise: which of these instructions would there be a problem ?
nop, irmovq, mrmovq, rmovq, addq, popq

SEQ: control signals for WB


two write inputs — two needed by popq
valM (memory output), valE (ALU output)

two register numbers
dstM, dstE

 
write disable — use dummy register number 0xF



write back (2a)

 

write back (2b)

 


SEQ: Update PC

choose value for PC next cycle (input to PC register)


usually valP (following instruction)

exceptions: `call`, `jCC`, `ret`

PC update

 


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select when running `addq %r8, %r9?`


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select when running `addq %r8, %r9?`


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select when running `addq %r8, %r9?`


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select for **rmmovq**?


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select for **rmmovq**?


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select for `irmovq`?


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select for **mrmovq**?


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select for **jle**?


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select for **cmovele**?


circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select for **ret**?


circuit: setting MUXes

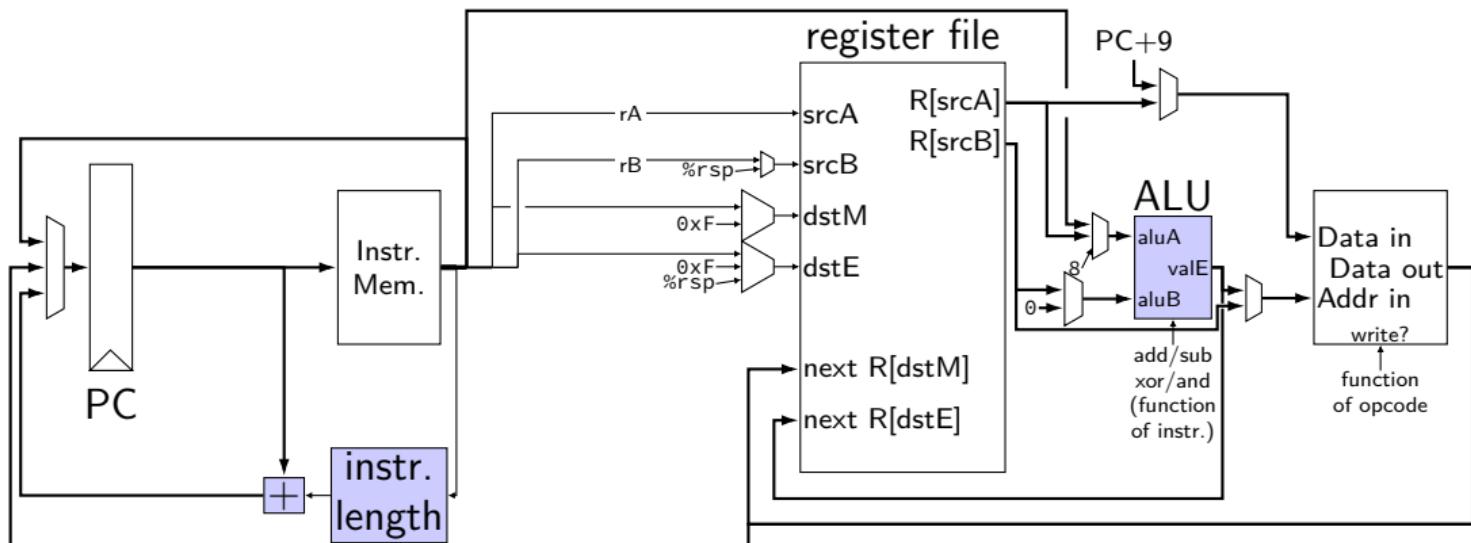

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select for **popq**?


circuit: setting MUXes

 



MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...

Exercise: what do they select for **call**?


Human pipeline: laundry

 


Human pipeline: laundry

  

Waste (1)

 

Waste (1)

 


Waste (2)

	11:00	12:00	13:00	14:00	
Washer	whites	colors	sheets		
Dryer		whites	colors	sheets	
Folding Table			whites	colors	sheets


Latency — Time for One




Latency — Time for One

 


Latency — Time for One

 

Throughput — Rate of Many

 


Throughput — Rate of Many

 


$$\frac{1 \text{ load}}{0.83\text{h}} = 1.2 \text{ loads/h}$$

Throughput — Rate of Many


 


$$\frac{1 \text{ load}}{0.83\text{h}} = 1.2 \text{ loads/h}$$


times three circuit

 


times three circuit

  


times three circuit

 


 
100 ps latency \Rightarrow 10 results/ns throughput



times three and repeat

 

times three and repeat

  

backup slides

comparing to yis

```
$ ./hclrs nopjmp_cpu.hcl nopjmp.yo
...
...
+----- (end of halted state) -----
Cycles run: 7
$ ./tools/yis nopjmp.yo
Stopped in 7 steps at PC = 0x1e. Status 'HLT', CC Z=1 S=0 O=0
Changes to registers:
Changes to memory:
```

HCLRS summary

declare/assign values to **wires**

MUXes with

```
[ test1: value1; test2: value2; 1: default; ]
```

register banks with **register i0**:

next value on **i_name**; current value on **0_name**

fixed functionality

register file (15 registers; 2 read + 2 write)

memories (data + instruction)

Stat register (start/stop/error)