 


# SEQUENTIAL Part 1


Samira Khan

The slides are prepared by Charles Reiss


# registers




updates every **clock cycle**

 


# state in Y86-64

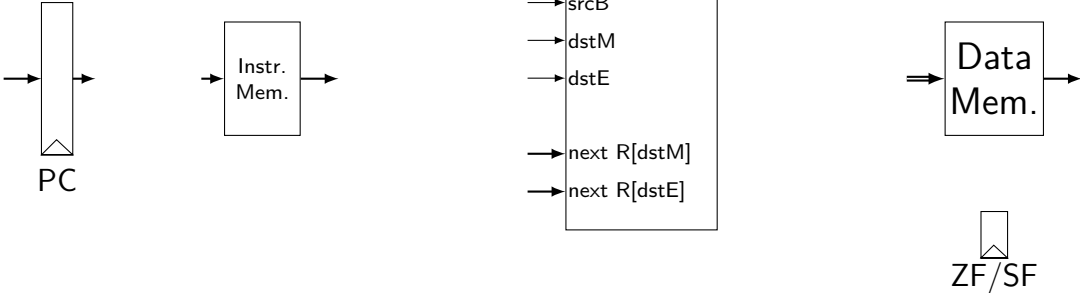


# state in Y86-64

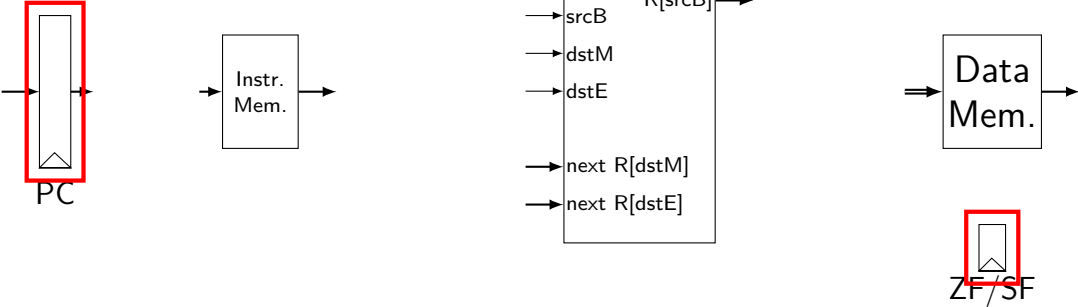


# state in Y86-64

 



# state in Y86-64

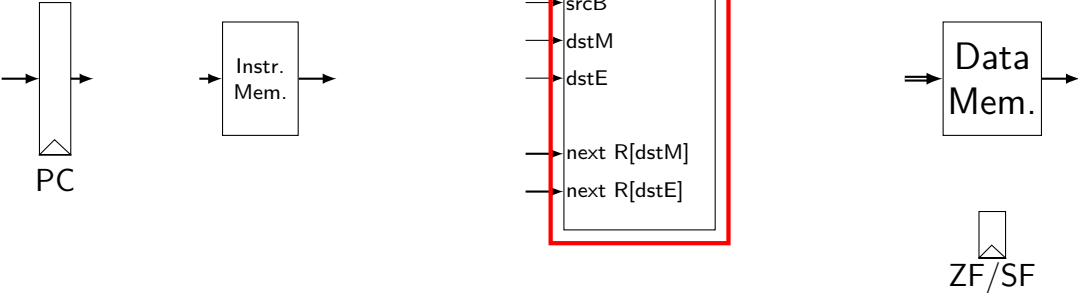

# state in Y86-64



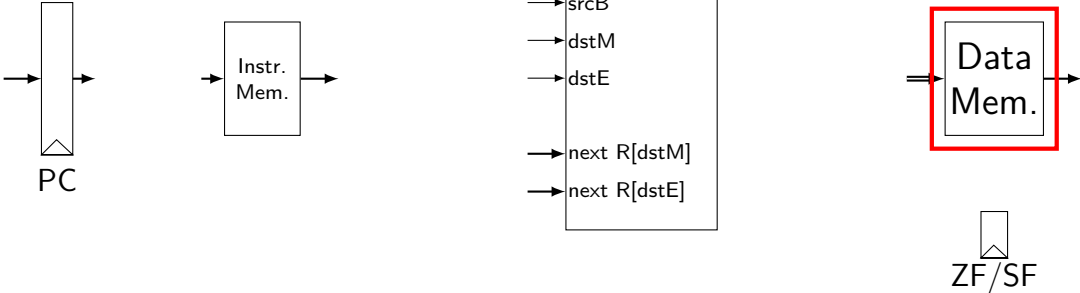


# memories



 
 





# memories

   



# memories

    




# register file

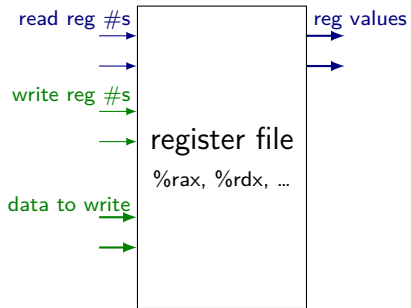


# register file

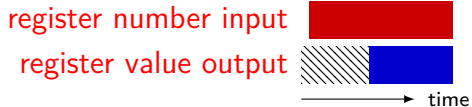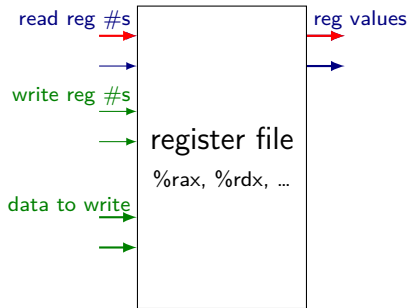



# register file

 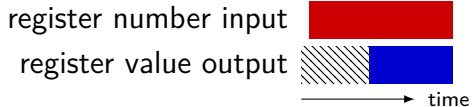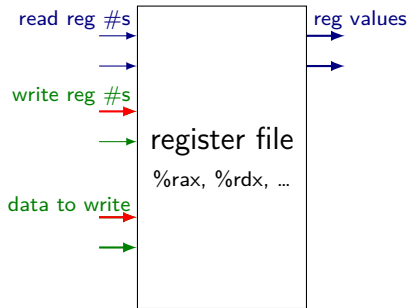


# register file

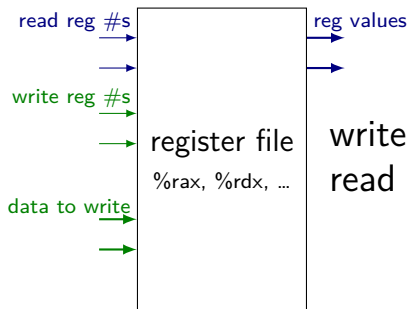

 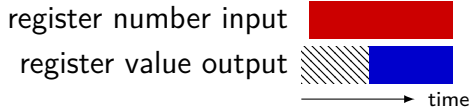write register #15: write is ignored  
read register #15: value is always 0



# ALUs

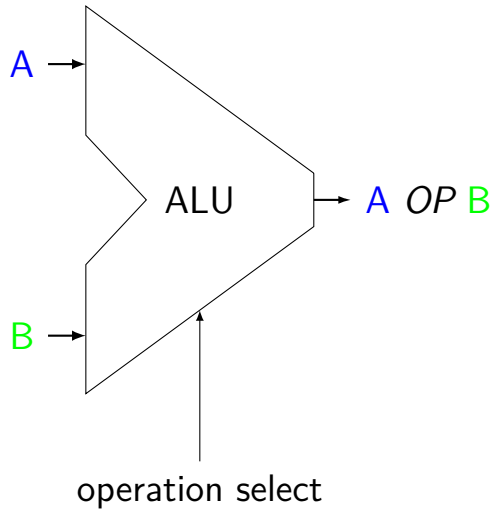

Operations needed:  
add — **addq**, addresses  
sub — **subq**  
xor — **xorq**  
and — **andq**  
more?

# simple ISA 1: addq

addq %rXX, %rYY



encoding: %rXX %rYY (two 4-bit register #s)

1 byte instructions, no opcode


no other instructions




# addq CPU

  


# addq CPU

 


# addq CPU

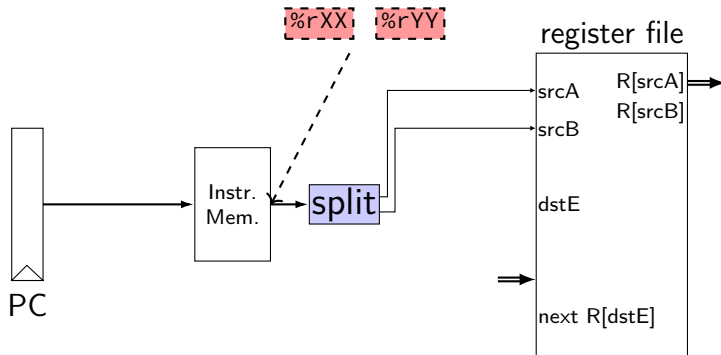


# addq CPU

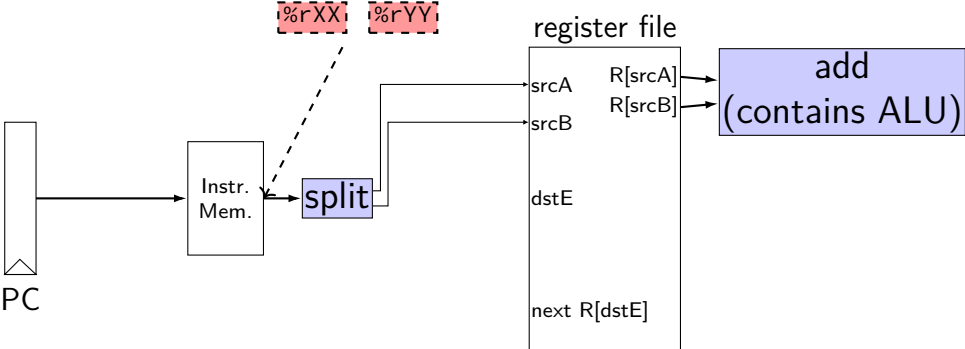

# addq CPU

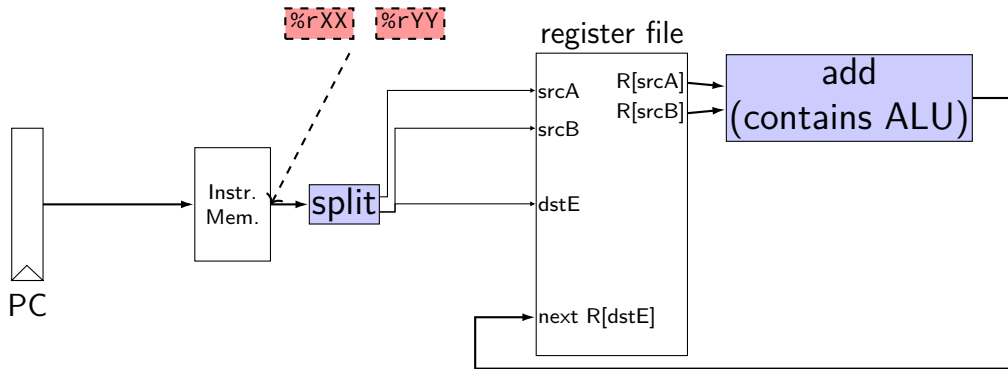

# addq CPU

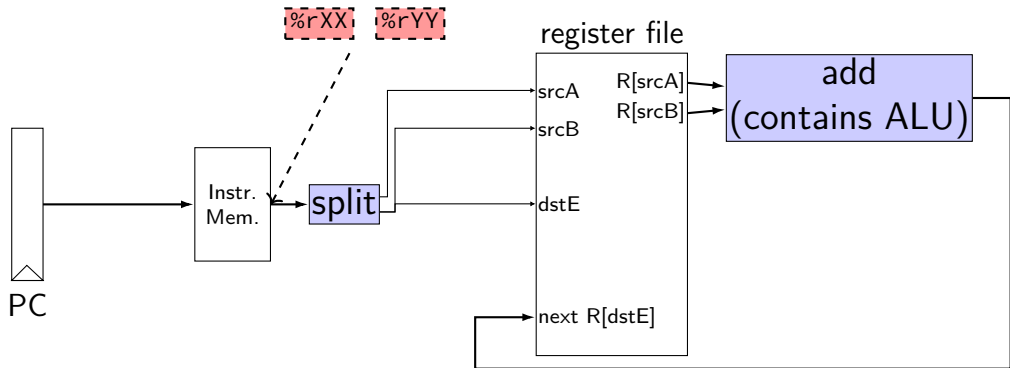

```
/* 0x00: */ addq %rax, %rdx
```


```
/* 0x01: */ addq %rbx, %rdx
```

initially: PC = 0x00, rax = 1, rbx = 2, rdx = 3


after cycle 1: PC = ????, rax = 1, rbx = 2, rdx = 4

after cycle 2: PC = ????, rax = ??, rbx = ??, rdx = ??

# addq CPU

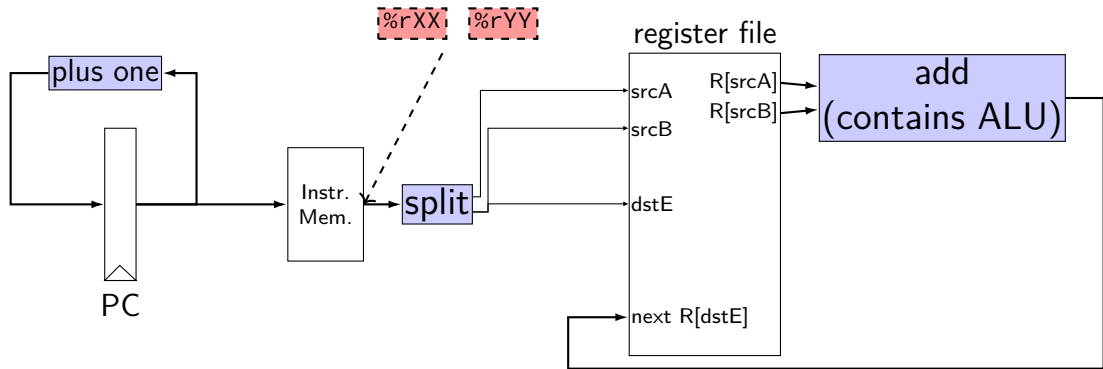

# addq CPU

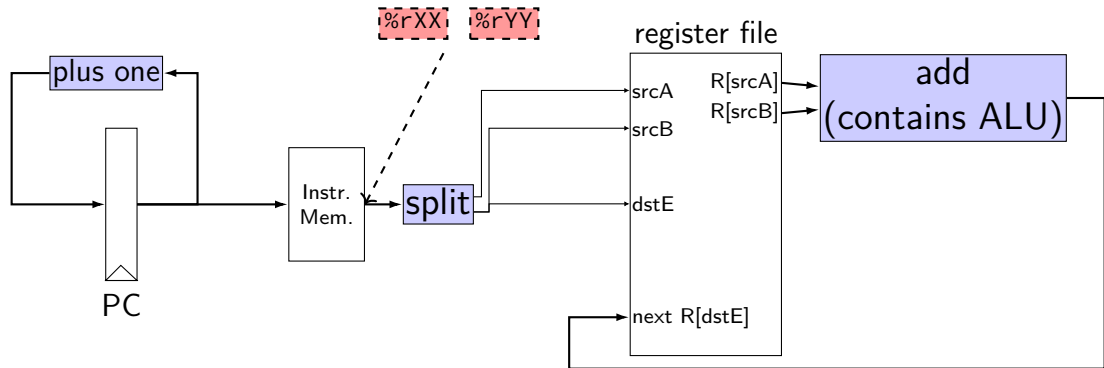

```
/* 0x00: */ addq %rax, %rdx
```

```
/* 0x01: */ addq %rbx, %rdx
```

initially: PC = 0x00, rax = 1, rbx = 2, rdx = 3

after cycle 1: PC = 0x01, rax = 1, rbx = 2, rdx = 4

after cycle 2: PC = 0x02, rax = 1, rbx = 2, rdx = 6




## Simple ISA 2: jmp

jmp label


encoding: *8-byte little-endian address*

8 byte instructions, no opcode


# jmp CPU

 

# jmp CPU

 

# jmp CPU

 

```
/* 0x00: */ jmp 0x10
```

```
/* 0x08: */ jmp 0x00
```

```
/* 0x10: */ jmp 0x08
```


initially: PC = 0x00

after cycle 1: PC = 0x10


after cycle 2: PC = 0x08

after cycle 3: PC = 0x00


# multiplexers

 

# multiplexers

 

# multiplexers

 

truth table:

select bit 1	select bit 0	output (many bits)
0	0	a
0	1	b
1	0	c
1	1	d

## Simple ISA 3: Jmp or No-Op


actual subset of Y86-64

`jmp LABEL` — encoded as `0x70` + address

`nop` — encoded as `0x10`




# jmp+nop CPU

 

**nop**  
**jmp** *Dest*




# jmp+nop CPU

 


nop



jmp Dest

 

# jmp+nop CPU

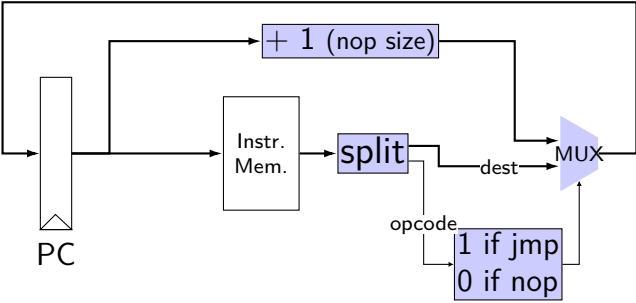


nop



jmp Dest




# jmp+nop CPU

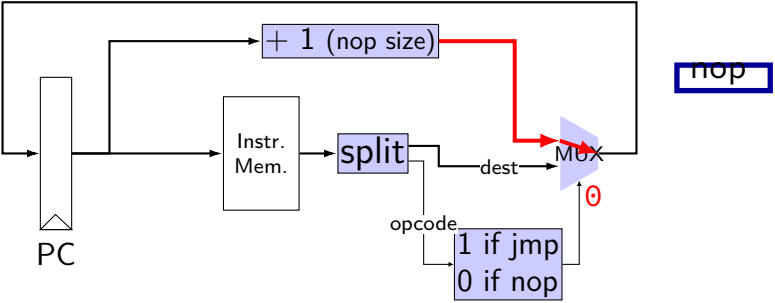


nop



jmp Dest

 


# jmp+nop CPU

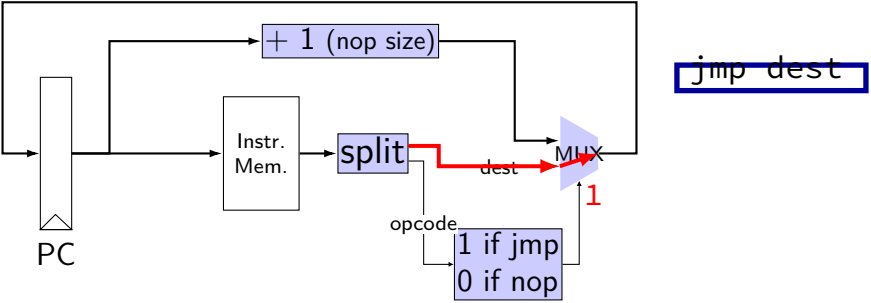

nop



jmp Dest

 

## exercise: nop/add CPU

Let's say we wanted to make **nop+add CPU**. Where would need MUXes?

- A. before one or both of the register file 'register number to read' inputs
- B. before the PC register's input
- C. before one of the register file 'register number to write' inputs
- D. before one of the register file 'register value to write' inputs
- E. before the instruction memory's address input

# Summary

each instruction takes one cycle

divided into stages for **design convenience**

read values **from previous cycle**

send **new values** to state components

control what is sent with **MUXes**

## simple ISA 4: mov-to-register


`irmovq $constant, %rYY`

`rrmovq %rXX, %rYY`

`mrmovq 10(%rXX), %rYY`




# mov-to-register CPU

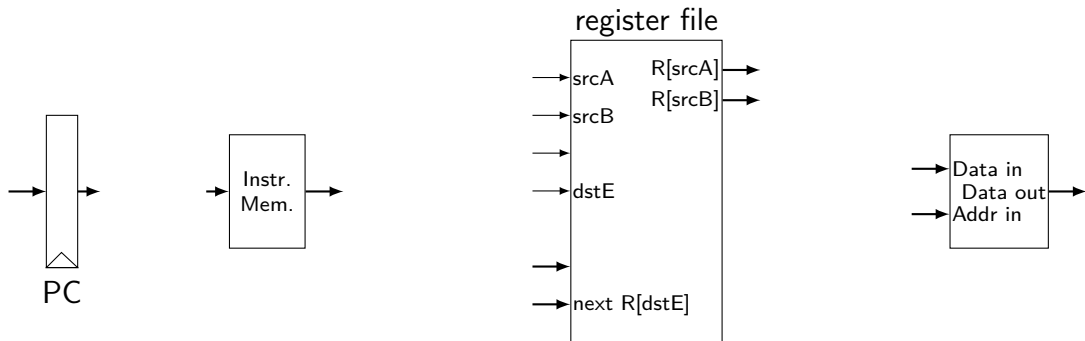


`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 


# mov-to-register CPU

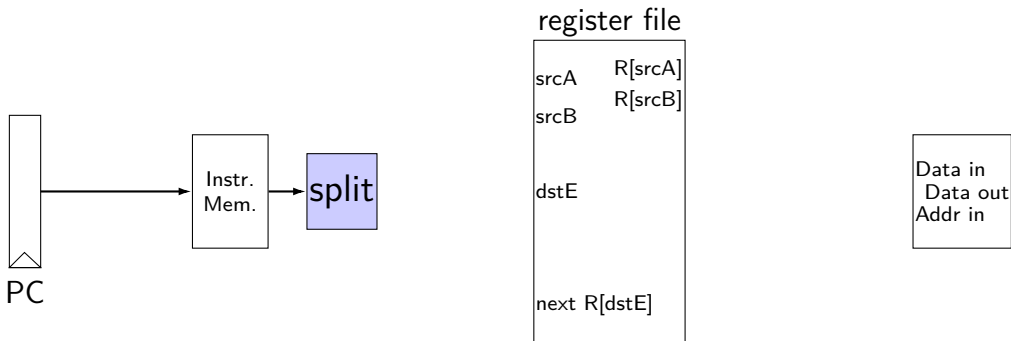


`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 


# mov-to-register CPU

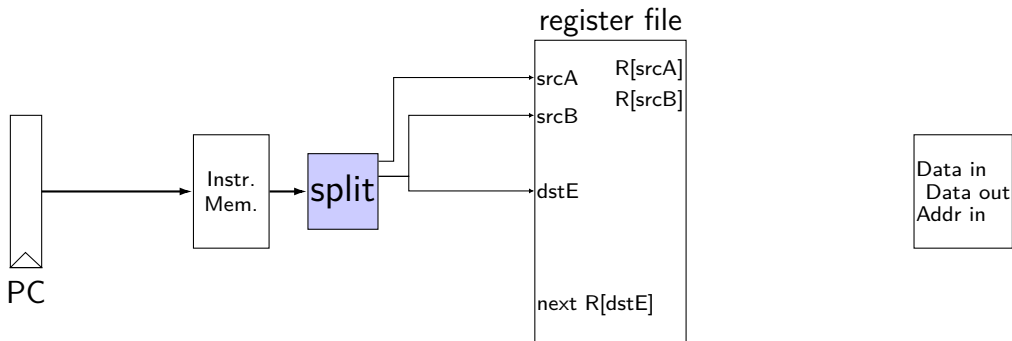

`rrmovq rA, rB`


`irmovq V, rB`

`mrmovq D(rB), rA`

 



# mov-to-register CPU

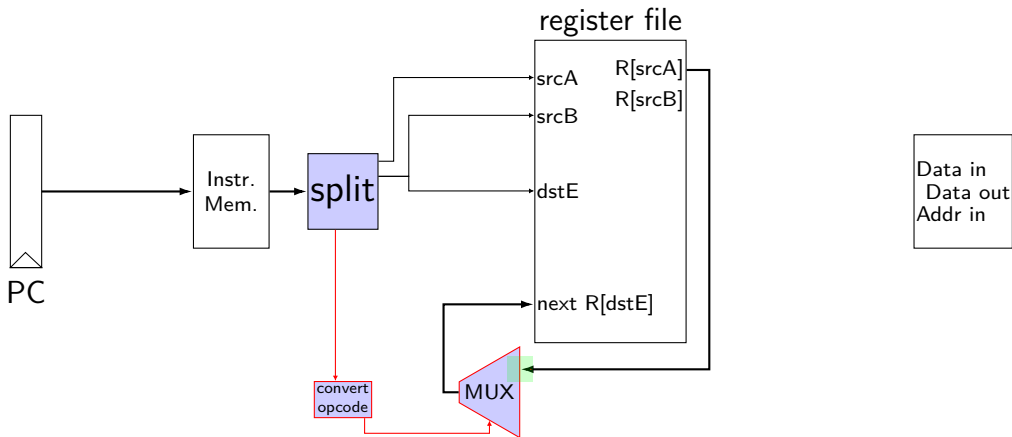

`rrmovq rA, rB`




`irmovq V, rB`



`mrmovq D(rB), rA`



# mov-to-register CPU

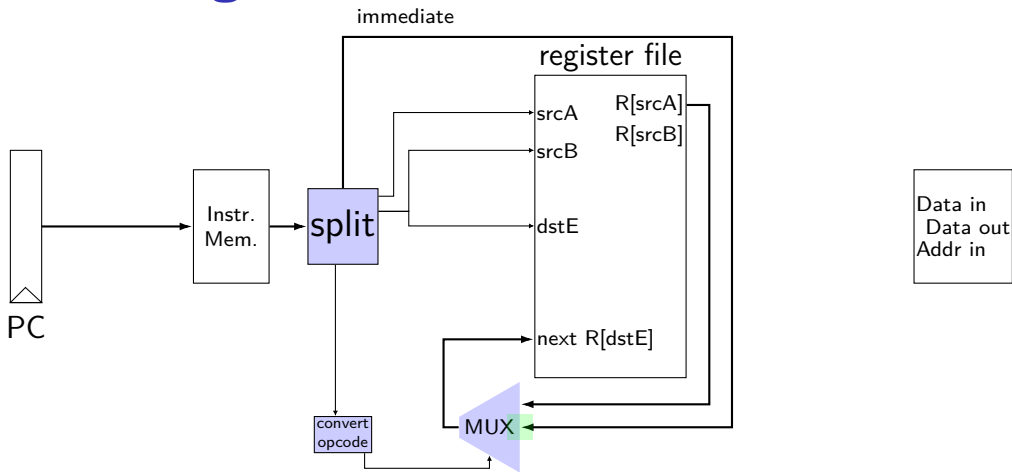

`rrmovq rA, rB`




`irmovq V, rB`



`mrmovq D(rB), rA`



# mov-to-register CPU

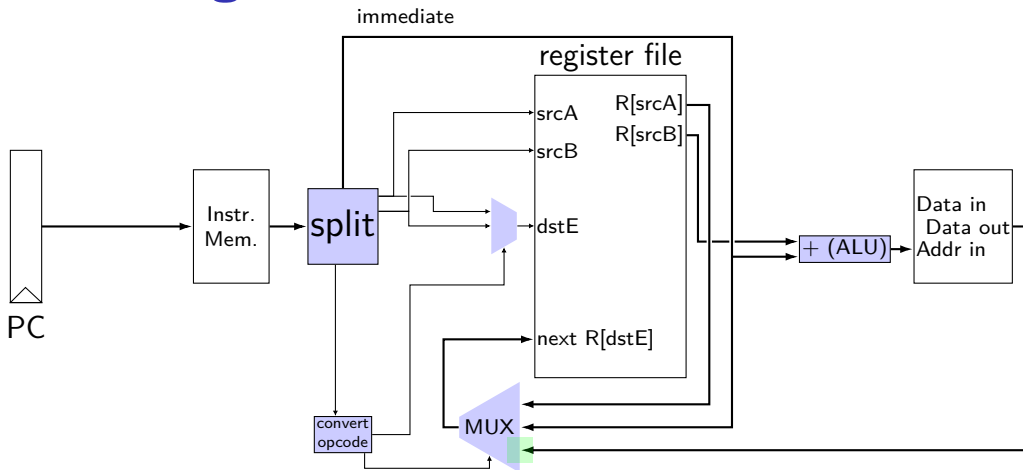

`rrmovq rA, rB`




`irmovq V, rB`



`mrmovq D(rB), rA`



# mov-to-register CPU

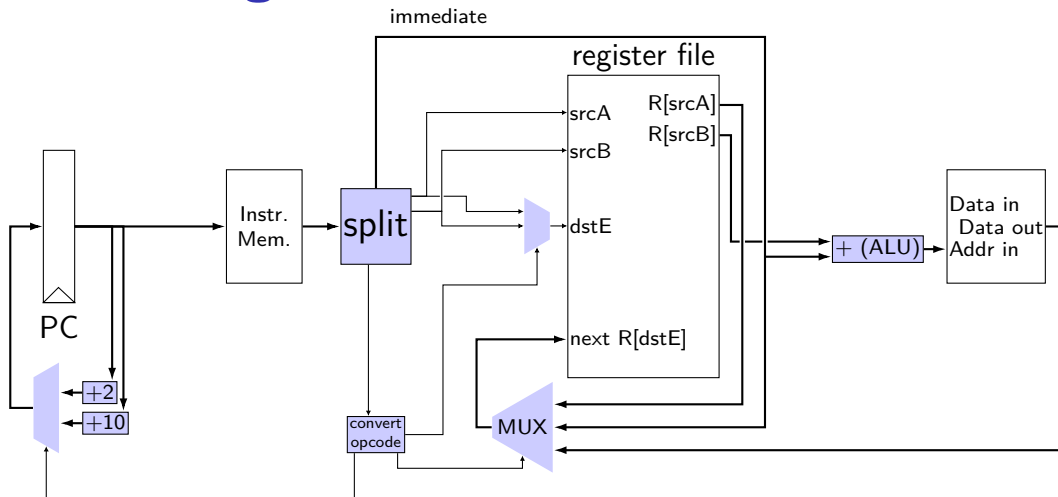

`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

