

representing HW

# last time

## RISC

efficient, simple hardware  
expose what hardware can do well

## CISC

convenience of compiler/assembly programmer

## Y86-64

movq  $\rightarrow$  {irmovq, rrmovq, mrmovq, rmmovq}  
cmovXX


one set of operand types per item

## Y86-64 encoding table

# describing hardware

how do we describe hardware?

pictures?

 

# circuits with pictures?

yes, something you can do

such commercial tools exist, but...

not commonly used for processors

# hardware description language

programming language for hardware

(typically) text-based representation of circuit

often abstracts away details like:

- how to build arithmetic operations from gates

- how to build registers from transistors

- how to build memories from transistors

- how to build MUXes from gates

...

those details also not a topic in this course


# our tool: HCLRS

built for this course


assumes you're making a processor

somewhat different from textbook's HCL

# circuits: wires

 


## circuits: wires

 

binary value — actually voltage




## circuits: wires

 

value propagates to rest of wire (small delay)  
binary value — actually voltage


# circuits: wire bundles

 

# circuits: wire bundles




same as

 

$$11010 = 26$$


# circuits: wire bundles

 

same as




same as

 

$$11010 = 26$$


# circuits: wire bundles

 

same as




same as

 

$$11010 = 26$$


# circuits: wire bundles

 

same as







same as

 

$$11010 = 26$$


## circuits: gates

    

# circuits: logic

want to do calculations?

generalize gates:

 




# circuits: logic

want to do calculations?

generalize gates:

 output wires contain result of function on input  
changes as input changes (with delay)




# circuits: logic

want to do calculations?



generalize gates:

output wires contain result of function on input  
changes as input changes (with delay)

need not be same width as output

 

## HCLRS: wire (bundle)s

  


`wire foo : 5; foo = 0b11010;`      *OR*

`wire foo : 5; foo = 26;`              *OR*

`wire foo : 5; foo = 0x1a;`

# HCLRS: wire (bundle)s

 

wire `foo` : 5; foo = 0b11010;     *OR*

wire `foo` : 5; foo = 26;             *OR*

wire `foo` : 5; foo = 0x1a;

*name*

# HCLRS: wire (bundle)s



wire foo : 5; foo = 0b11010;    *OR*

wire foo : 5; foo = 26;        *OR*

wire foo : 5; foo = 0x1a;

*width* (in bits)

# HCLRS: wire (bundle)s



wire foo : 5; foo = 0b11010; *OR*

wire foo : 5; foo = 26; *OR*


wire foo : 5; foo = 0x1a;

*assignment*

indicates wire is *connected* to value
 
# HCLRS: gates + calculations (1)


```
wire a : 2; wire b : 2; wire c : 2;  
c = b & a;  
a = 0b10;  
b = 0b11;
```


 
# HCLRS: gates + calculations (1)

```
wire a : 2; wire b : 2; wire c : 2;  
c = b & a; }  
a = 0b10; } same as { a = 0b10;  
b = 0b11; }          { b = 0b11;  
                   { c = b & a;
```

**order doesn't matter**  
connected or not





# HCLRS: gates + calculations (1)

```
wire a : 2; wire b : 2; wire c : 2;
```


```
c = b & a;
```

```
a = 0b10;
```

```
b = 0b11;
```

C-like expressions supported

$0b10 \ \& \ 0b11 = 0b10$

 

## HCLRS: gates + calculations (2)


```
wire a : 2; wire b : 2; wire c : 2;
```

```
c = b + a; /* was b & a */
```


```
a = 0b10;
```

```
b = 0b11;
```

 
more than bitwise operators supported  
 $0b10 + 0b11 = 0b101 \rightarrow 0b01$  (extra bits lost)



## example: (broken) counter circuit (1)

 


## example: (broken) counter circuit (1)

 


```
wire x : 3;  
x = x + 1;
```

## example: (broken) counter circuit (1)

 

```
wire x : 3;  
x = x + 1;
```


## example: (broken) counter circuit (1)

 

time 0: 000 ← set how???

```
wire x : 3;  
x = x + 1;
```


## example: (broken) counter circuit (1)

 

time 0: 000  
time 1: 001?  
time 2: 010?  
time 3: 011?

```
wire x : 3;  
x = x + 1;
```

## example: (broken) counter circuit (2)

 


```
wire x : 3;  
x = x + 1;
```

HCLRS: compile error

“Circular dependency detected:  
x depends on x”



## example: (broken) counter circuit (3)

 

time 0: 000

time 1: 001?

time 2: 010?


time 3: 011?

```
wire x : 3;
```

```
x = x + 1;
```



## example: (broken) counter circuit (3)

 

time 0: 000


time 1: 001?

time 2: 010?

time 3: 011?


```
wire x : 3;
```

```
x = x + 1;
```

 

problem 1: how will "add 1" react to this value?  
(not zero or one) ...

# example: (broken) counter circuit (3)

 


time 0: 000  
time 1: 001?  
time 2: 010?  
time 3: 011?

```
wire x : 3;  
x = x + 1;
```




## example: (broken) counter circuit (3)

 


time 0: 000  
time 1: 001?  
time 2: 010?  
time 3: 011?

```
wire x : 3;  
x = x + 1;
```

 

problem 2: changes not in sync?

## example: (broken) counter circuit (4)

 

```
wire x : 3;  
x = x + 1;
```

~~time 0: 000  
time 1: 001?  
time 2: 010?  
time 3: 011?~~

circuit is **not stable**  
**transient values** during changes  
hard to predict behavior


## circuits: state

logic performs calculations all the time


never stores values!

need **extra elements** to store values  
registers, memory

# example: counter circuit (corrected)

 

## example: counter circuit (corrected)

 

time 0: 000


time 1: 001

time 2: 010

time 3: 011



## example: counter circuit (corrected)

 

time 0: 000


time 1: 001

time 2: 010


time 3: 011

add **register** to store current count  
updates based on “clock signal” (not shown)  
avoids intermediate updates


# registers

 


updates every **clock cycle**

 

## example: counter circuit (real HCLRS)

 


## example: counter circuit (real HCLRS)

 

```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```


## example: counter circuit (real HCLRS)

 

```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```

register "bank"  
can have multiple (related) registers


## example: counter circuit (real HCLRS)

 

```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```

label for left/right side of registers  
x: label for input side (always lowercase)  
Y: label for output side (always uppercase)


## example: counter circuit (real HCLRS)

 

```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```

register "name"  
input/output = *prefix\_name*

## example: counter circuit (real HCLRS)

 


```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```

input wire to register




## example: counter circuit (real HCLRS)

 

```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```

output wire of register


## example: counter circuit (real HCLRS)

 

initial value of register  
first value for output wire (Y\_count)


```
register xY {  
    count : 3 = 0b000;  
}  
x_count = Y_count + 0b001;
```

## example: counter circuit

 

```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```


## example: counter circuit

 

```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```

time	Y_count	x_count
start	000	001
start + 1 rising edge	001	010
start + 2 rising edges	010	011
start + 3 rising edges	011	100
...	...	...

# example: counter circuit

 

```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```

time	Y_count	x_count
start	000	001
start + 1 rising edge	001	010
start + 2 rising edges	010	011
start + 3 rising edges	011	100
...	...	...

# HCL circuit with registers

```
register xY {  
    a : 4 = 1; /* <-- initial Y_a */  
    b : 4 = 1; /* <-- initial Y_b */  
}
```



$x_b = x_a + Y_a;$

$x_a = Y_a + Y_b;$

exercise: value of  $Y_a$ ,  $Y_b$  after two rising edges of clock?

- A.  $Y_a = 2, Y_b = 3$
- B.  $Y_a = 2, Y_b = 2$
- C.  $Y_a = 3, Y_b = 5$
- D.  $Y_a = 3, Y_b = 7$
- E.  $Y_a = 3, Y_b = 11$
- F.  $Y_a = 5, Y_b = 7$
- G.  $Y_a = 7, Y_b = 11$
- H. none of the above

# instruction memory

  

# Stat signal

how do we stop the simulated machine?

hard-wired mechanism — Stat wire

possible values:

STAT\_AOK — keep going

STAT\_HLT — stop, normal shutdown

STAT\_INS — invalid instruction

...(and more errors)

(predefined 3-bit constants)

must be set

determines if **simulator** keeps going