 


SEQ Continued

February 21, 2023

quiz Q1

```
register xY {  
    a : 64 = 2;  
    b : 64 = ???;  
}
```



→ $x_a = Y_a + Y_a;$
 $x_b = Y_b + x_a;$

clk	x_a	x_b	Y_a	Y_b
0	4	$4+w$	2	w
1	8	$8+4+w$	4	$4+w$
2			8	$8 + 4+w = 1024$ $w = 1024-12=1012$

quiz Q2


PC set to 0x101

i10bytes[0..80] = 0x33221100DEBC9A785634


i10bytes[0..8] = 0x34

i10bytes[8..12] = 0x6

i10bytes[12..20] = 0x85

 

recap: register, logic, counter circuit

 


```
register xY {  
    count : 3 = 0b000 ;  
}  
x_count = Y_count + 0b001;
```

time	Y_count	x_count
start	000	001
start + 1 rising edge	001	010
start + 2 rising edges	010	011
start + 3 rising edges	011	100
...

program counter, simplest CPU

recap: Instr. Mem., pc, nop CPU, Stat

“pc” “i10bytes”

 

```
register pF {  
  thePc : 64 = 0;  
}  
p_thePc = F_thePc + 1;  
pc = F_thePc;  
Stat = STAT_AOK;
```

→ 0 0

0

-06


hop

op

0x46

x0b

recap: MUX, opcode, nop/halt CPU

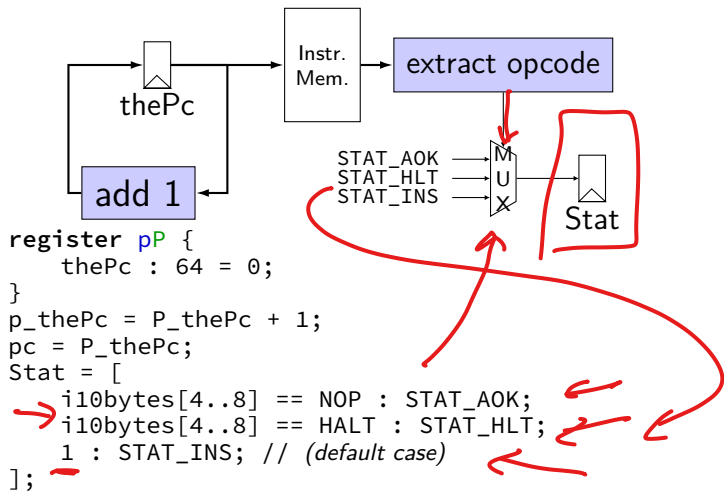

nop/jmp CPU, register file, addq CPU, build a processor

simple ISA: addq

addq %rXX, %rYY

encoding:


6	0	%rXX	%rYY
---	---	------	------

 (two 4-bit register #s)
2 byte instructions, no opcode



for now: no other instructions

later: adding support for nop+halt




register file

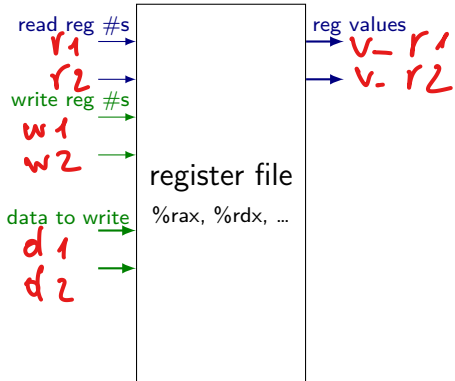


register file

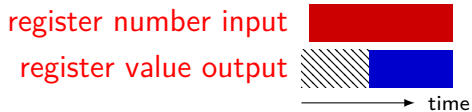 

register file

 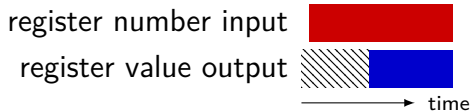
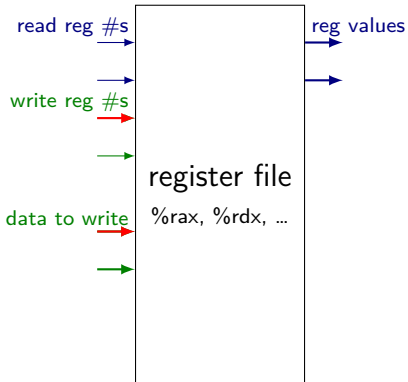


register file



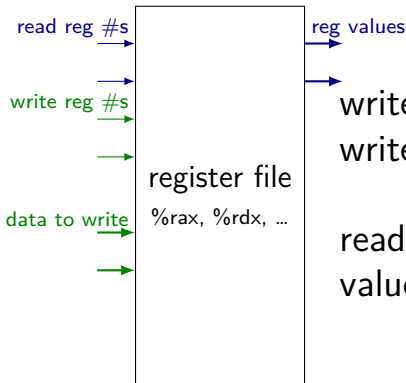


write register #15 (REG_NONE):
write is ignored

 
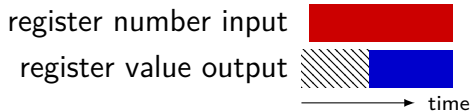
read register #15 (REG_NONE):
value is always 0




register file

 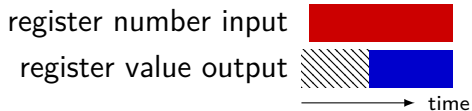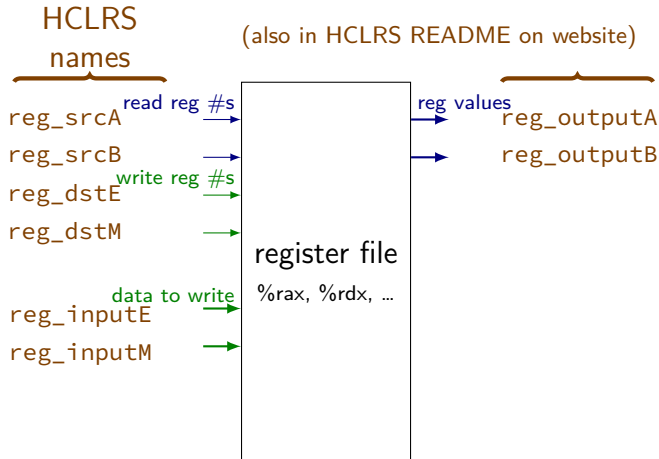


addq CPU

 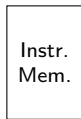


addq CPU

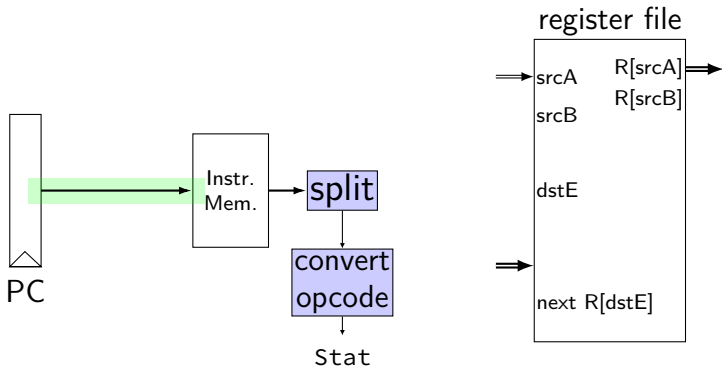


addq CPU

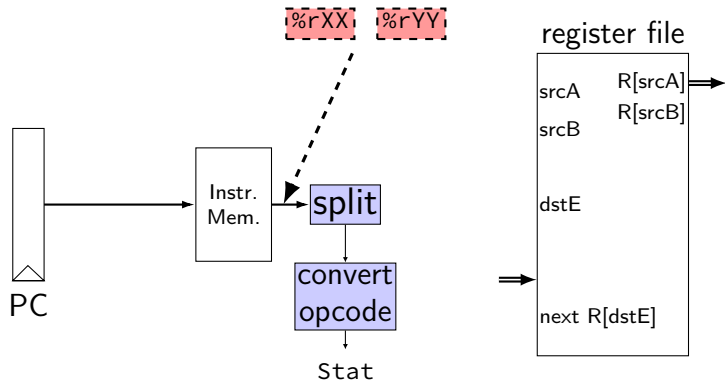


addq CPU

 


addq CPU

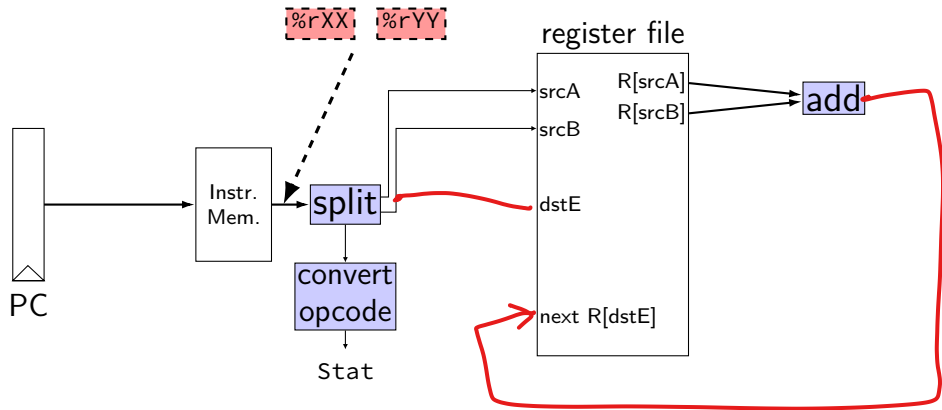

addq CPU

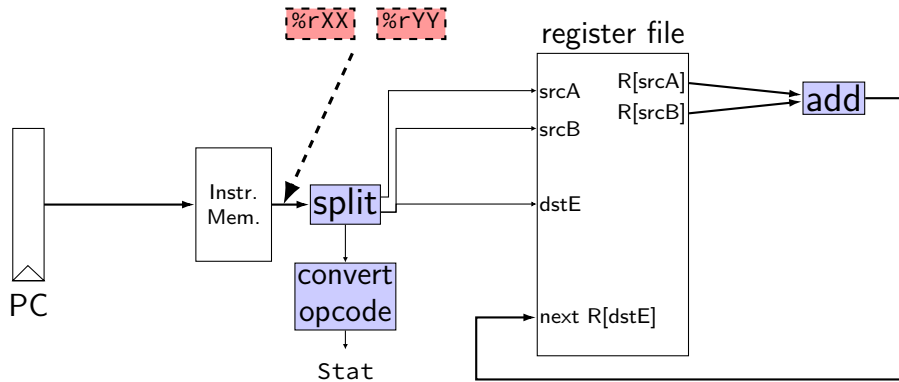

addq CPU

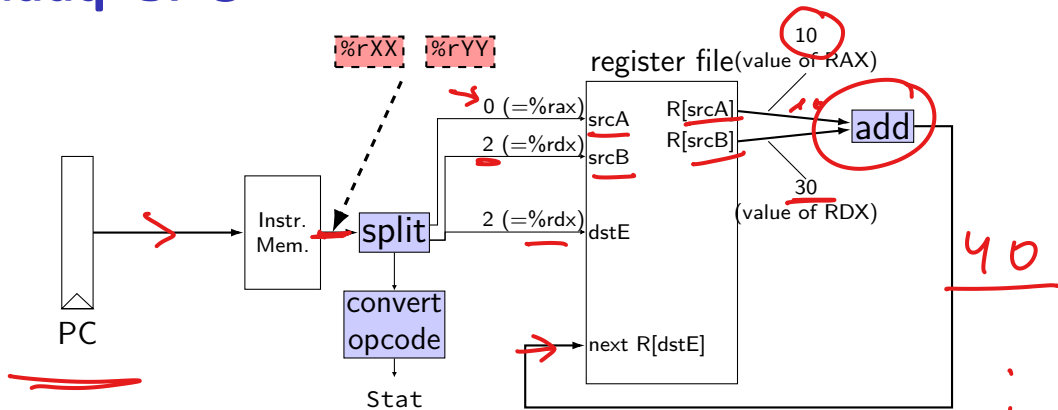

`/* 0x00: */ addq %rax, %rdx`


`/* 0x02: */ addq %rbx, %rdx`

initially: PC = 0x00, rax = 10, rbx = 20, rdx = 30

after cycle 1: PC = ????, rax = 10, rbx = 20, rdx = 40



addq CPU

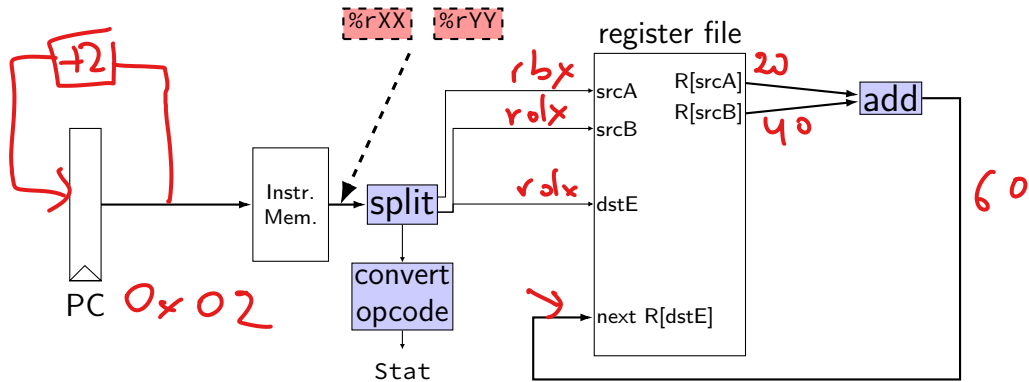


→ `/* 0x00: */ addq %rax, %rdx`
 → `/* 0x02: */ addq %rbx, %rdx`

initially: PC = 0x00, rax = 10, rbx = 20, rdx = 30


after cycle 1: PC = ????, rax = 10, rbx = 20, rdx = 40

after cycle 2: PC = ????, rax = ??, rbx = ??, rdx = ??


10 20 60

 

addq CPU

 

addq CPU

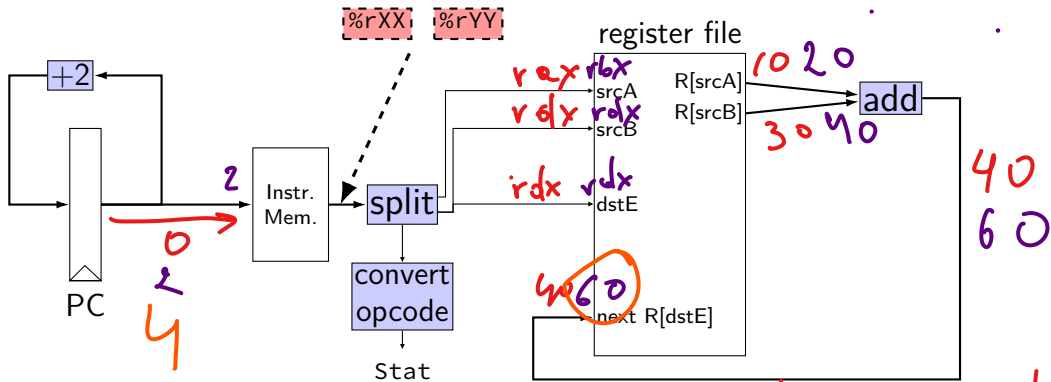

```

→ /* 0x00: */ addq %rax, %rdx
→ /* 0x02: */ addq %rbx, %rdx


```

$$\Rightarrow \begin{aligned} rdx &= rax + rdx \\ rdx &= rbx + rdx \end{aligned}$$


- initially: PC = 0x00, rax = 10, rbx = 20, rdx = 30
- after cycle 1: PC = 0x02, rax = 10, rbx = 20, rdx = 40
- after cycle 2: PC = 0x04, rax = 10, rbx = 20, rdx = 60

4

addq CPU: HCL

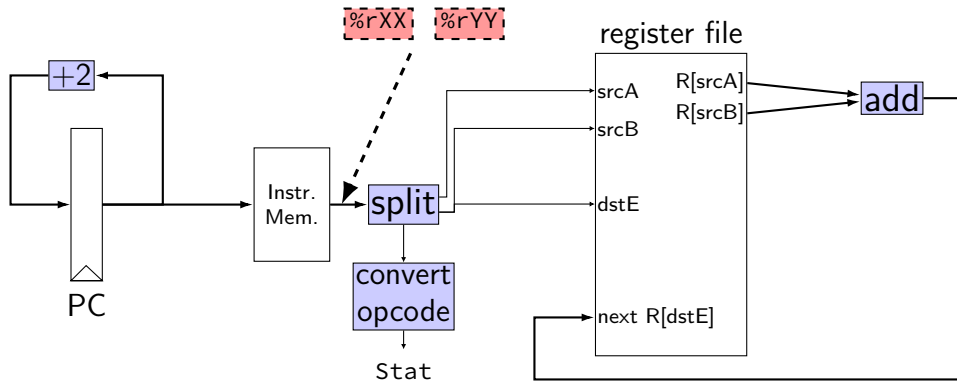

addq CPU: HCL

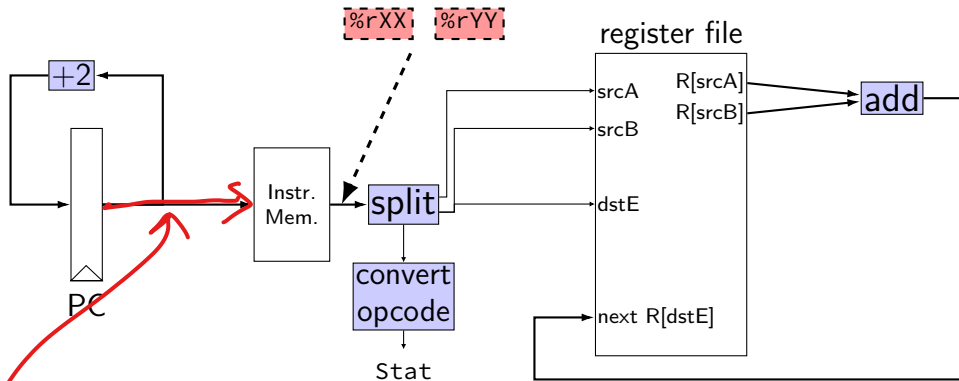

```

register pP {
  pc : 64 = 0;
}
p_pc = P_pc + 2;
pc = P_pc;

```

```

wire opcode : 4;
wire rA : 4, rB : 4;
opcode = i10bytes[4..8];
rA = i10bytes[12..16];
rB = i10bytes[8..12];


```

```

reg_srcA = rA;
reg_srcB = rB;
reg_dstE = rB;
reg_inputE =
  reg_outputA +
  reg_outputB;

```


addq CPU: HCL

 


```
register pP {  
  pc : 64 = 0;  
}
```

```
p_pc = P_pc + 2;  
pc = P_pc;
```

```
wire opcode : 4;  
wire rA : 4, rB : 4;  
opcode = i10bytes[4..8];  
rA = i10bytes[12..16];  
rB = i10bytes[8..12];
```

```
reg_srcA = rA;  
reg_srcB = rB;  
reg_dstE = rB;  
reg_inputE =  
  reg_outputA +  
  reg_outputB;
```

addq CPU: HCL

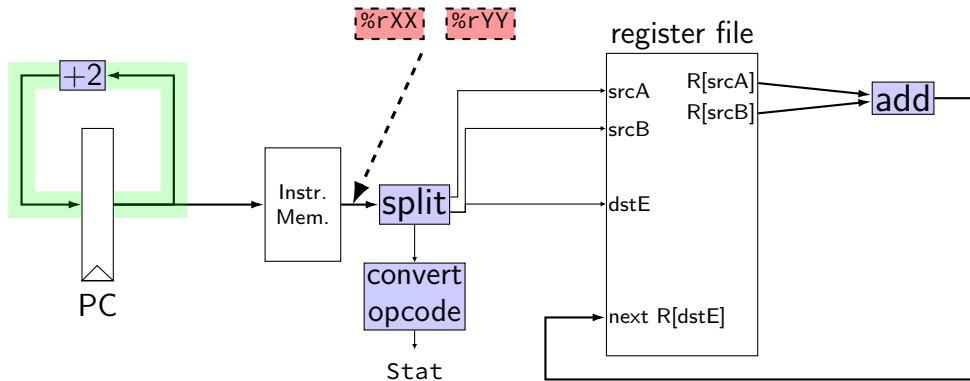


```
register pP {  
    pc : 64 = 0;  
}  
p_pc = P_pc + 2;  
pc = P_pc;
```

```
wire opcode : 4;  
wire rA : 4, rB : 4;  
opcode = i10bytes[4..8];  
rA = i10bytes[12..16];  
rB = i10bytes[8..12];
```

```
reg_srcA = rA;  
reg_srcB = rB;  
reg_dstE = rB;  
reg_inputE =  
    reg_outputA +  
    reg_outputB;
```

addq CPU: HCL

 


```
register pP {  
    pc : 64 = 0;  
}  
p_pc = P_pc + 2;  
pc = P_pc;
```

```
wire opcode : 4;  
wire rA : 4, rB : 4;  
opcode = i10bytes[4..8];  
rA = i10bytes[12..16];  
rB = i10bytes[8..12];
```

```
reg_srcA = rA;  
reg_srcB = rB;  
reg_dstE = rB;  
reg_inputE =  
    reg_outputA +  
    reg_outputB;
```

addq CPU: HCL

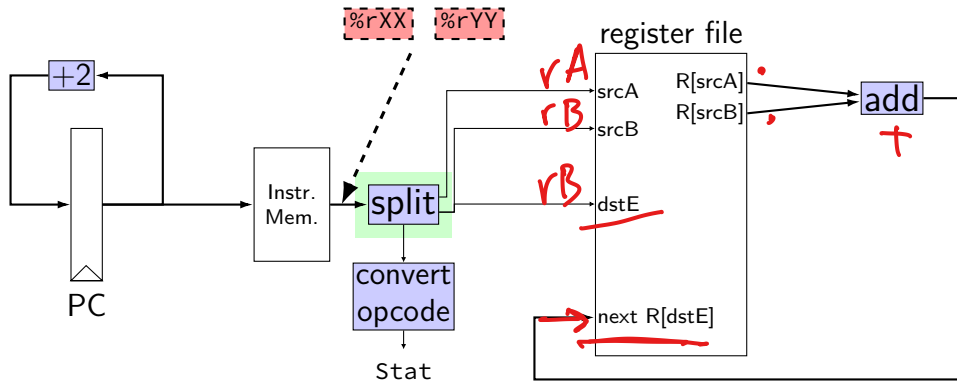


```
register pP {  
    pc : 64 = 0;  
}  
p_pc = P_pc + 2;  
pc = P_pc;
```

```
wire opcode : 4;  
wire rA : 4, rB : 4;  
opcode = i10bytes[4..8];  
rA = i10bytes[12..16];  
rB = i10bytes[8..12];
```

```
reg_srcA = rA;  
reg_srcB = rB;  
reg_dstE = rB;  
reg_inputE =  
    reg_outputA +  
    reg_outputB;
```

addq CPU: HCL

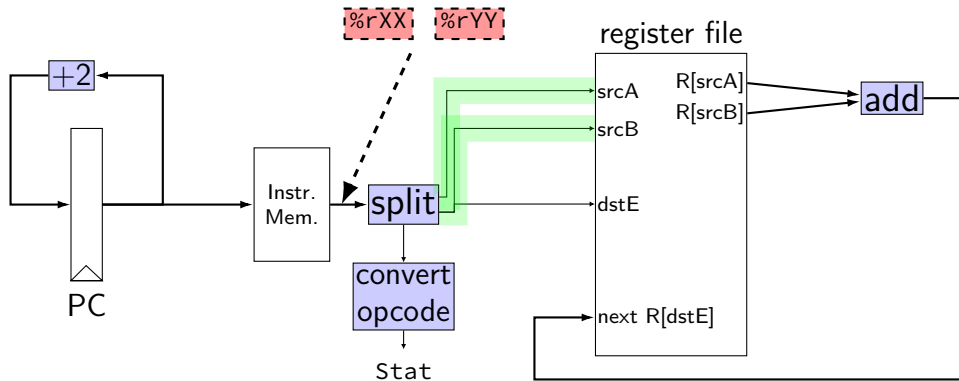


```
register pP {  
  pc : 64 = 0;  
}  
p_pc = P_pc + 2;  
pc = P_pc;
```

```
wire opcode : 4;  
wire rA : 4, rB : 4;  
opcode = i10bytes[4..8];  
rA = i10bytes[12..16];  
rB = i10bytes[8..12];
```

```
reg_srcA = rA;  
reg_srcB = rB;  
reg_dstE = rB;  
reg_inputE =  
  reg_outputA +  
  reg_outputB;
```

addq CPU: HCL

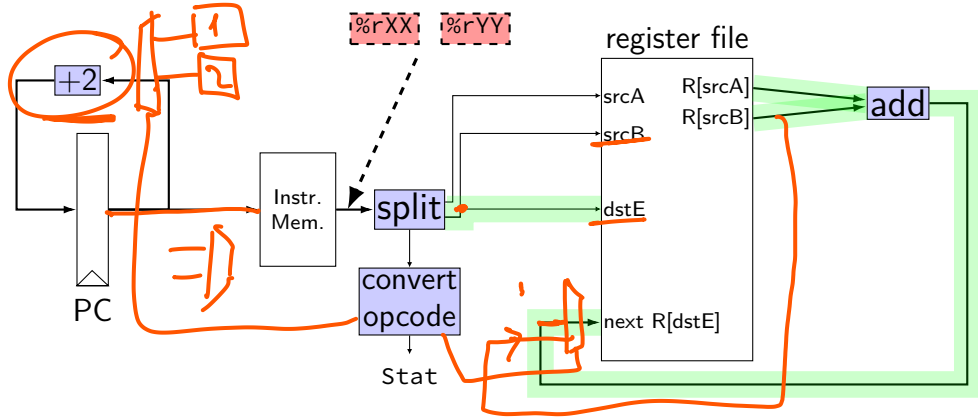

```

register pP {
  pc : 64 = 0;
}
p_pc = P_pc + 2;
pc = P_pc;

```

```

wire opcode : 4;
wire rA : 4, rB : 4;
opcode = i10bytes[4..8];
rA = i10bytes[12..16];
rB = i10bytes[8..12];

```

```

reg_srcA = rA;
reg_srcB = rB;
reg_dstE = rB;
reg_inputE =
  reg_outputA +
  reg_outputB;

```

differences from book

wire not **bool** or **int**

book uses names like `valC` — not required!

author's environment limited adding new wires

MUXes must have default (`1 : something`) case

implement your own ALU

differences from book

wire not **bool** or **int**

book uses names like `valC` — not required!

author's environment limited adding new wires

MUXes must have default (1 : something) case

implement your own ALU

differences from book

wire not **bool** or **int**


book uses names like `valC` — not required!

author's environment limited adding new wires

MUXes must have default (`1 : something`) case

implement your own ALU

ALUs (Arithmetic Logic Unit)

 

Operations needed:
add — **addq**, addresses
sub — **subq**
xor — **xorq**
and — **andq**
more?

ALUs not for PC increment

our processor will have one ALU

not used for PC increment (computing next instruction address)

need to do other computation in same cycle

don't need a general circuit for it

i) ALU 1 operation
1 clk

ALUs in HCLRS

HCLRS doesn't supply an ALU

the HCL the textbook authors use does

...but you can build one yourself

not required — we check functionality

exercise: nop/add CPU


Let's say we wanted to make a add+nop CPU. Where would we need MUXes? Before...

(modify add CPU to also support the nop instruction)

ok

A. one or both of the register file 'register number to read' inputs (reg_src...)

✓ B. the PC register's input (p_pc)

 

✓ C. one of the register file 'register number to write' inputs (reg_dst...)

✓ D. one of the register file 'register value to write' inputs (reg_input...)

✗ E. the instruction memory's address input (pc)



simple ISA: mov-to-register

```
irmovq $constant, %rYY
```



```
rrmovq %rXX, %rYY
```

```
mrmovq 10(%rXX), %rYY
```

two memories

  


two memories

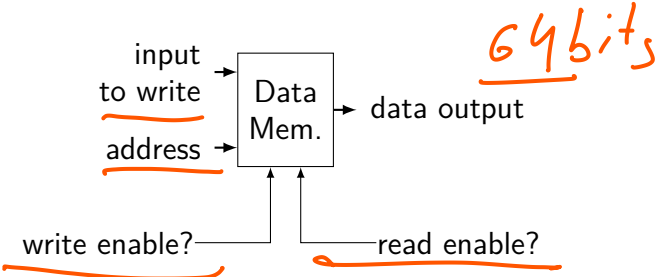 



data mem. in **read** mode

—or—

instr. mem:

 


two memories

  


data mem. in **read** mode

—or—



instr. mem:

 

data mem.
in **write** mode:


 


two memories

  


data mem. in **read** mode

data mem. in **write** mode:

  

two memories? (read + write)

 

really two memories??

in Y86-64 (and many real CPUs):

writing to address X in data memory:

changes address X in instruction memory

really two memories??

in Y86-64 (and many real CPUs):
writing to address X in data memory:
changes address X in instruction memory

so really just one memory??

we'll explain when we talk about *caches*

exercise: mov-to-register

irmovq \$constant, %rYY

rrmovq %rXX, %rYY 2

mrmovq 10(%rXX), %rYY

for which of these are we going to need MUXes? before...


A. register file's register number (index) inputs (reg_srcA, reg_srcB, reg_dstE, ...)

B. register file's value inputs (reg_inputE/M)

C. PC register's input +2 +10

D. instruction memory's address input (pc)


mov-to-register CPU

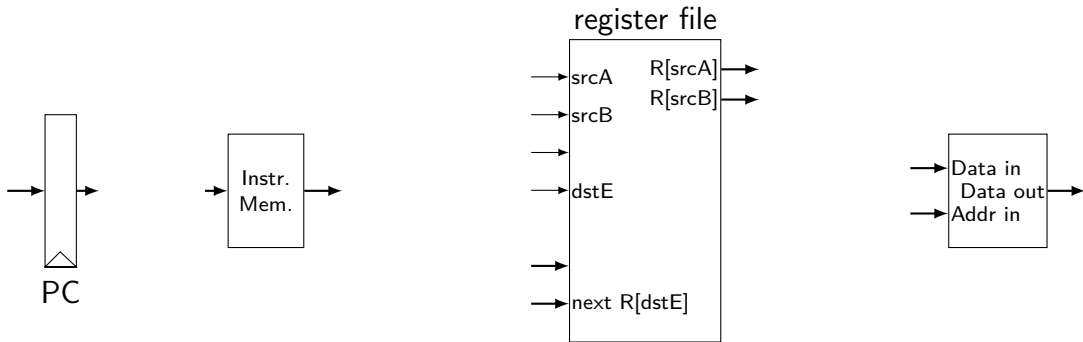


`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 


mov-to-register CPU

 


`rrmovq rA, rB`

`irmovq V, rB`

`rrmovq D(rB), rA`

 

mov-to-register CPU

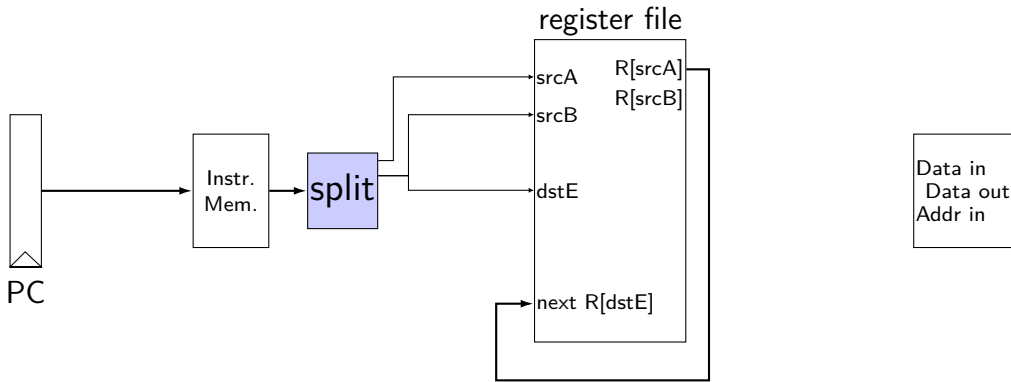

`rrmovq rA, rB`




`irmovq V, rB`



`rrmovq D(rB), rA`




mov-to-register CPU

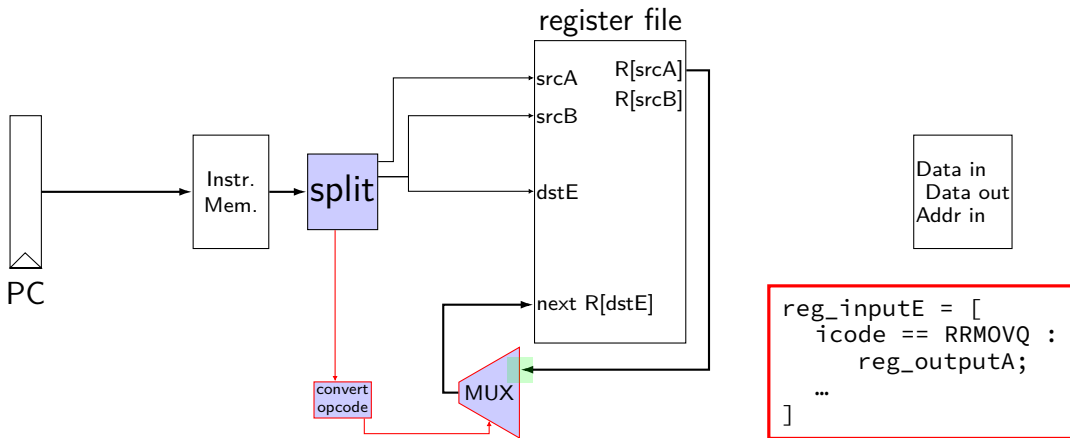


`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 

mov-to-register CPU

 


Data in
Data out
Addr in


`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 

mov-to-register CPU

 


`rrmovq rA, rB`




`irmovq V, rB`



`mrmovq D(rB), rA`

 

mov-to-register CPU

 

`rrmovq rA, rB`




`irmovq V, rB`



`mrmovq D(rB), rA`




mov-to-register CPU

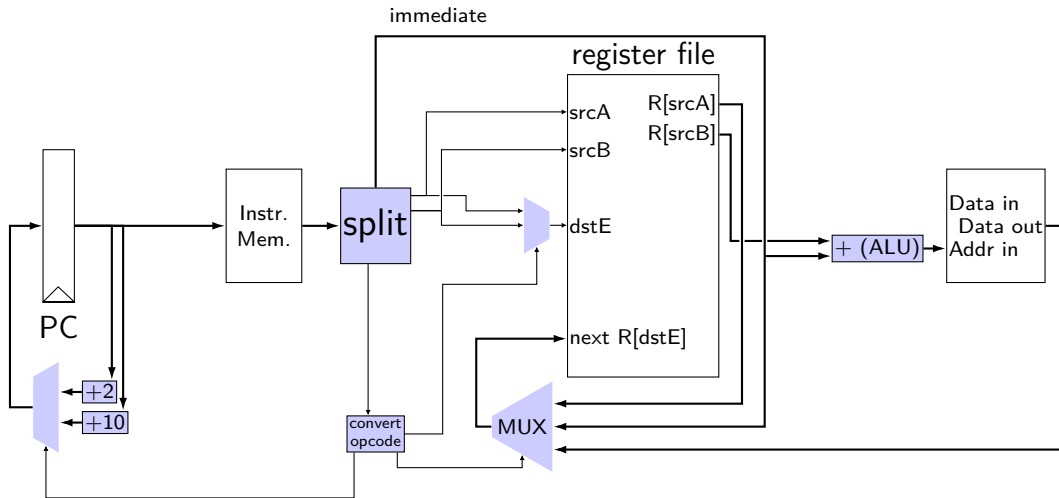

`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 

simple ISA: mov (all cases)


`irmovq $constant, %rYY`

`rrmovq %rXX, %rYY`

`mrmovq 10(%rXX), %rYY`

`rmmovq %rXX, 10(%rYY)`

mov CPU

 

`rrmovq rA, rB`

2	0	rA	rB
---	---	----	----

`irmovq V, rB`

3	0	F	rB
---	---	---	----


`rrmovq D(rB), rA`

5	0	rA	rB
---	---	----	----

`rmmovq rA, D(rB)`

4	0	rA	rB
---	---	----	----

mov CPU

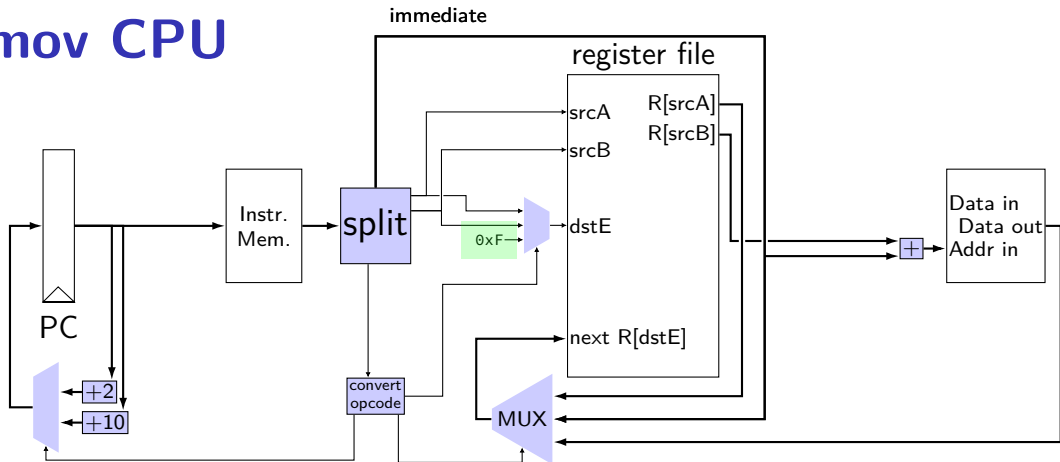

`rrmovq rA, rB`



`irmovq V, rB`




`rrmovq D(rB), rA`



`rmmovq rA, D(rB)`



mov CPU

 

`rrmovq rA, rB`



`irmovq V, rB`



`rrmovq D(rB), rA`



`rmmovq rA, D(rB)`



data path versus control path


data path — signals carrying “actual data”

control path — signals that control MUXes, etc.

fuzzy line: e.g. are condition codes part of control path?

we will often omit parts of the control path in drawings, etc.

mov CPU

 

`rrmovq rA, rB`



`irmovq V, rB`




`rrmovq D(rB), rA`




`rmmovq rA, D(rB)`



mov CPU

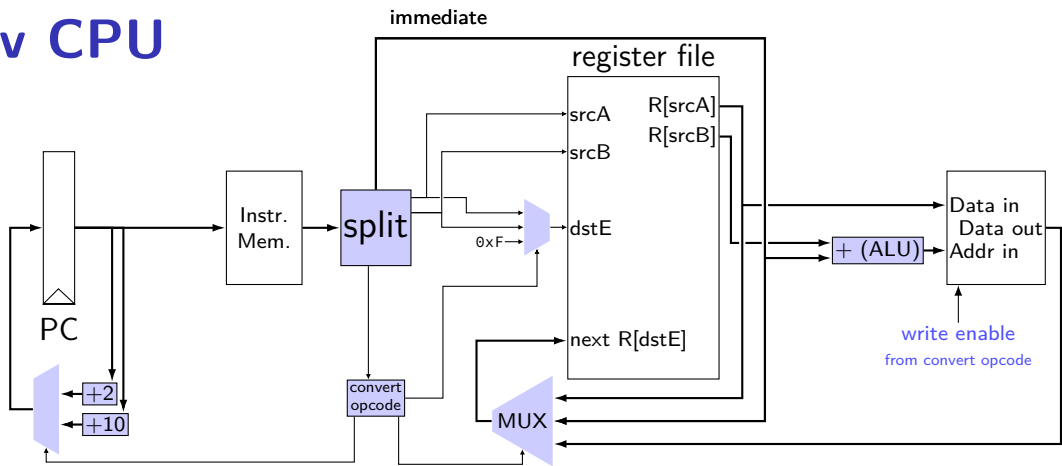

mov CPU

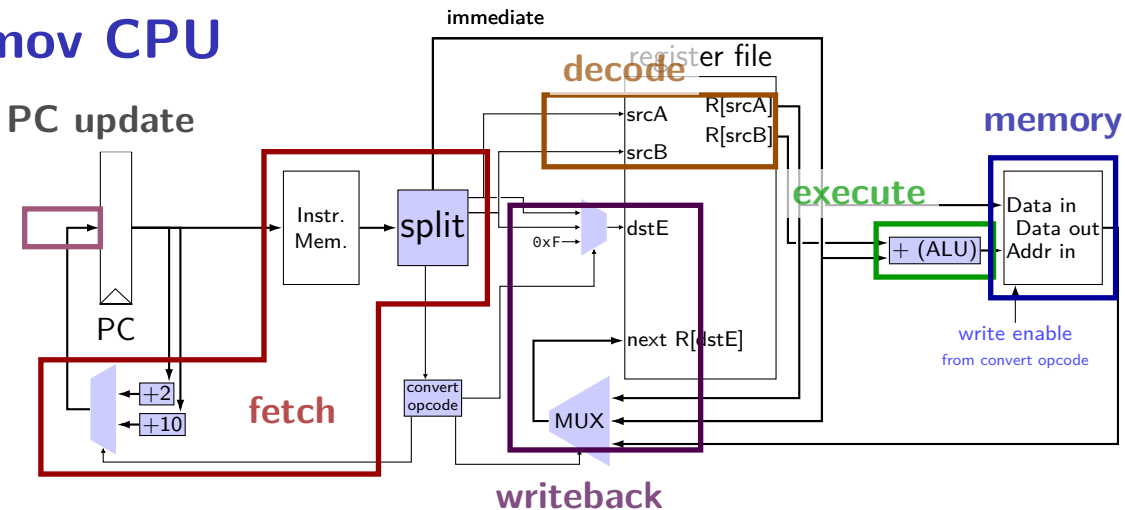

Stages

conceptual division of instruction:

fetch — read instruction memory, split instruction, compute length

decode — read register file

execute — arithmetic (including of addresses)

memory — read or write data memory

write back — write to register file

PC update — compute next value of PC

stages and time

fetch / decode / execute / memory / write back / PC update

Order when these events happen pushq %rax instruction:

1. instruction read
2. memory changes
3. %rsp changes
4. PC changes

Hint: recall how registers, register files, memory works

- a. 1; then 2, 3, and 4 in any order
- b. 1; then 2, 3, and 4 at almost the same time
- c. 1; then 2; then 3; then 4
- d. 1; then 3; then 2; then 4
- e. 1; then 2; then 3 and 4 at almost the same time
- f. something else

SEQ: instruction fetch

read instruction memory at PC

split into separate wires:

icode:ifun — opcode


rA, rB — register numbers

valC — call target or mov displacement

compute next instruction address:

valP — $PC + (\text{instr length})$

instruction fetch

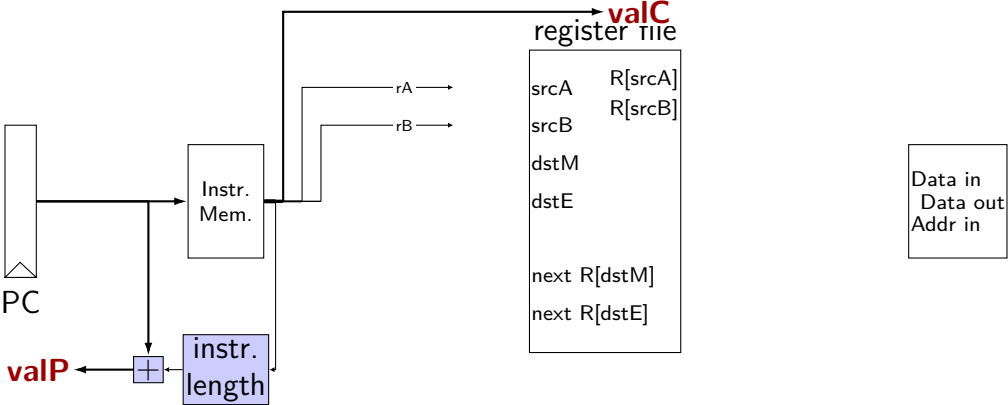


SEQ: instruction “decode”


read registers

`valA`, `valB` — register values

instruction decode (1)

 


instruction decode (1)

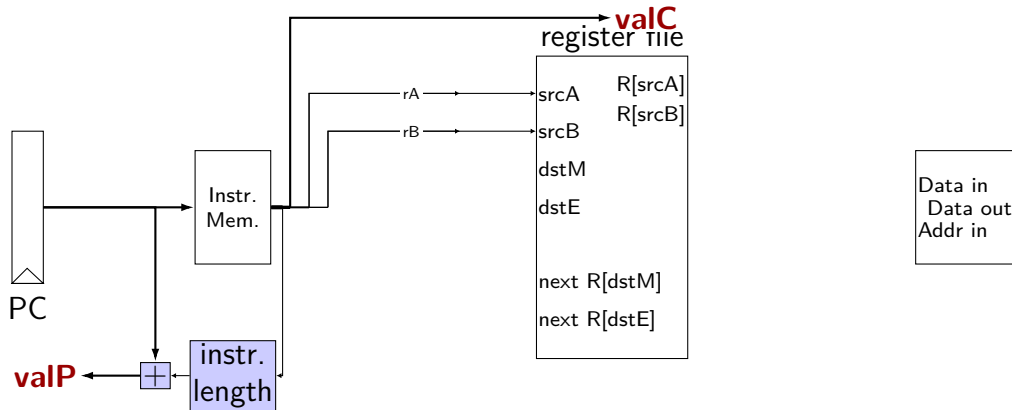

exercise: for which instructions would there be a problem ?
nop, addq, mrmovq, rmmovq, jmp, pushq

instruction decode (1)

 

SEQ: srcA, srcB

always read rA, rB?

Problems:

- push rA

- pop

- call


- ret

book: extra signals: srcA, srcB — computed input register

MUX controlled by icode


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 

instruction decode (2)

 

SEQ: execute

perform ALU operation (add, sub, xor, and)


valE — ALU output

read prior condition codes


Cnd — condition codes based on ifun (instruction type for jCC/cmouvCC)

write new condition codes


using condition codes: cmov

 

execute (1)

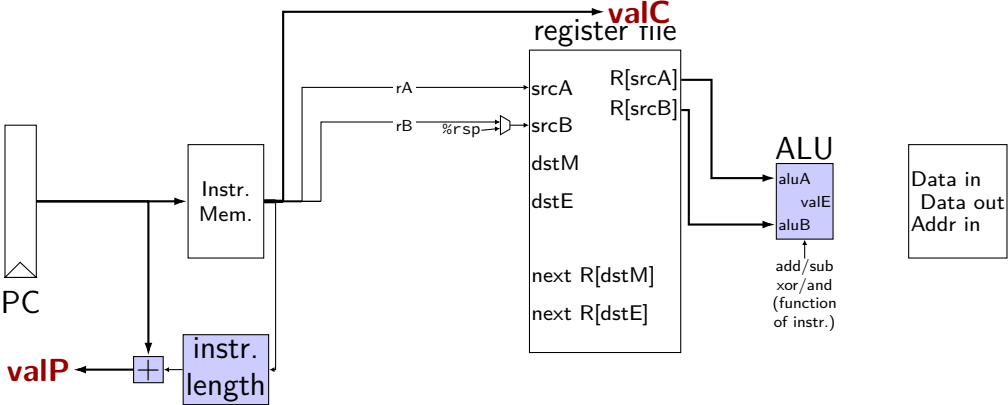

execute (1)

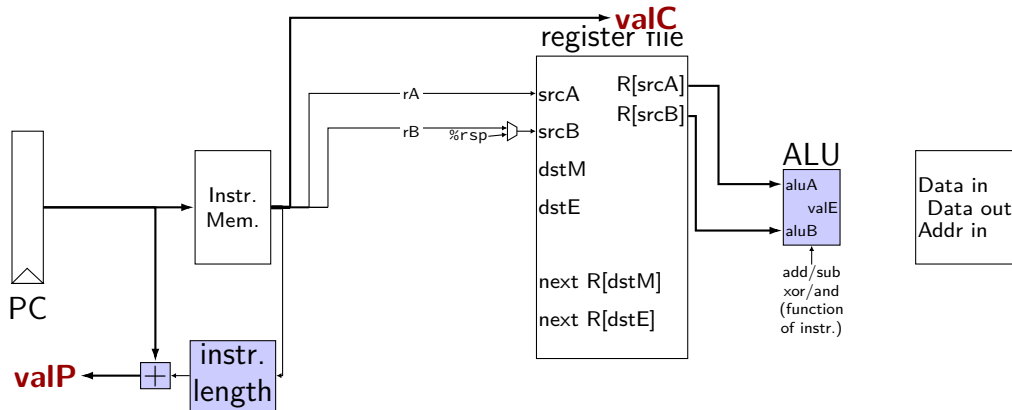


exercise: which of these instructions would there be a problem ?
nop, addq, mrmovq, popq, call,

SEQ: ALU operations?

ALU inputs always **valA**, **valB** (register values)?

no, inputs from instruction: (Displacement + rB)

`mrmovq`
`rmmovq`

 


no, constants: (rsp +/- 8)

`pushq`
`popq`
`call`
`ret`

extra signals: **aluA**, **aluB**

computed ALU input values

execute (2)

 


SEQ: Memory


read or write data memory

valM — value read from memory (if any)

memory (1)

 

memory (1)

 

exercise: which of these instructions would there be a problem ?
nop, rmmovq, mrmovq, popq, call,

SEQ: control signals for memory

read/write — read enable? write enable?

Addr — address

mostly ALU output


special cases (need extra MUX): `popq`, `ret`

Data — value to write

mostly `valA`

special cases (need extra MUX): `call`


memory (2)

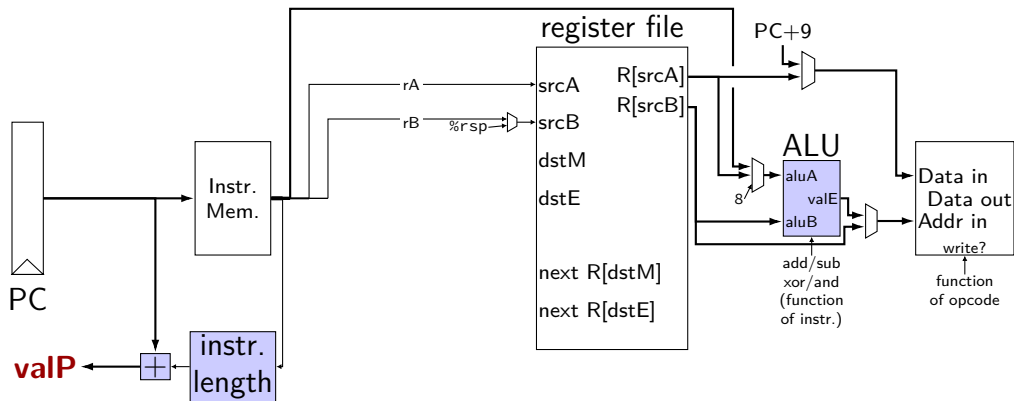

SEQ: write back


write registers

write back (1)

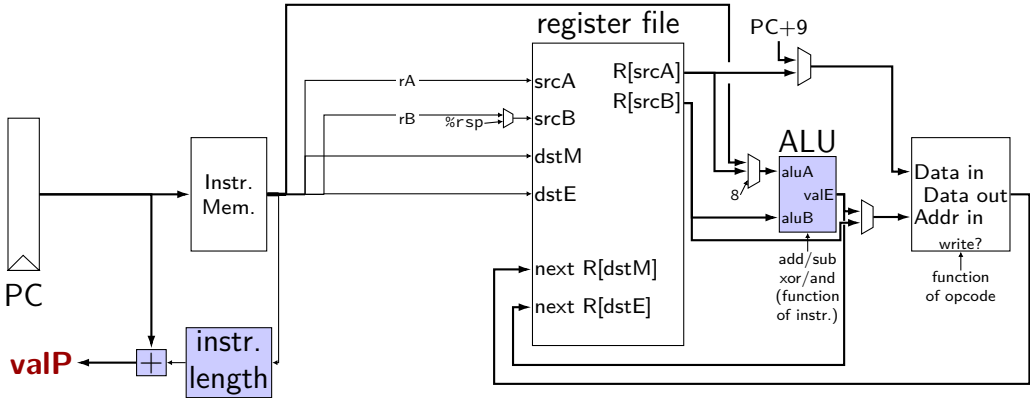


write back (1)

 textbook convention:
E used for storing ALU results (e.g. add)
M used for storing memory results (e.g. rmmovq)
(you don't have to do this...)



write back (1)

 


exercise: which of these instructions would there be a problem ?
nop, irmovq, mrmovq, rmmovq, addq, popq

SEQ: control signals for WB


two write inputs — two needed by popq
valM (memory output), valE (ALU output)

two register numbers
dstM, dstE

 
write disable — use dummy register number 0xF



write back (2a)

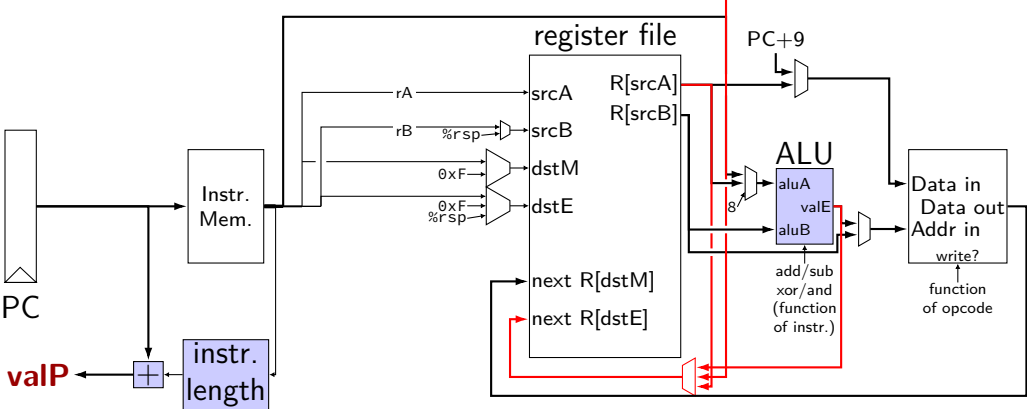

write back (2b)

 


SEQ: Update PC

choose value for PC next cycle (input to PC register)


usually valP (following instruction)

exceptions: `call`, `jCC`, `ret`

PC update

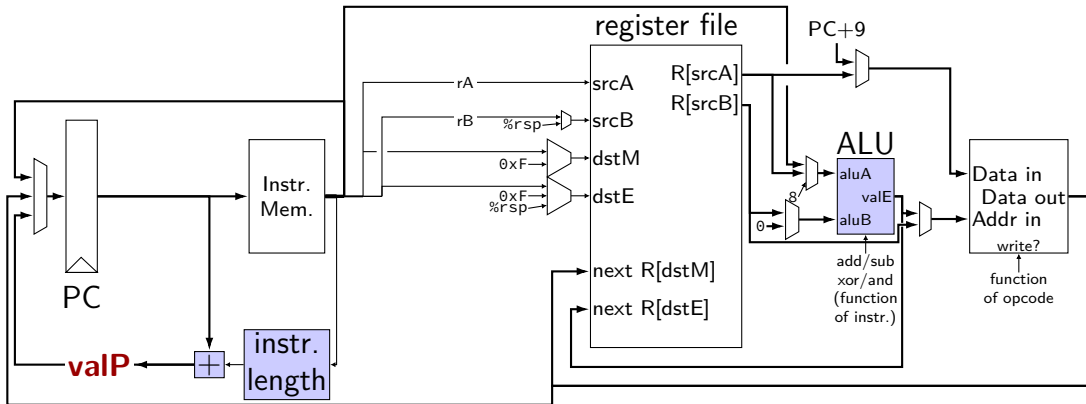


circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXEs

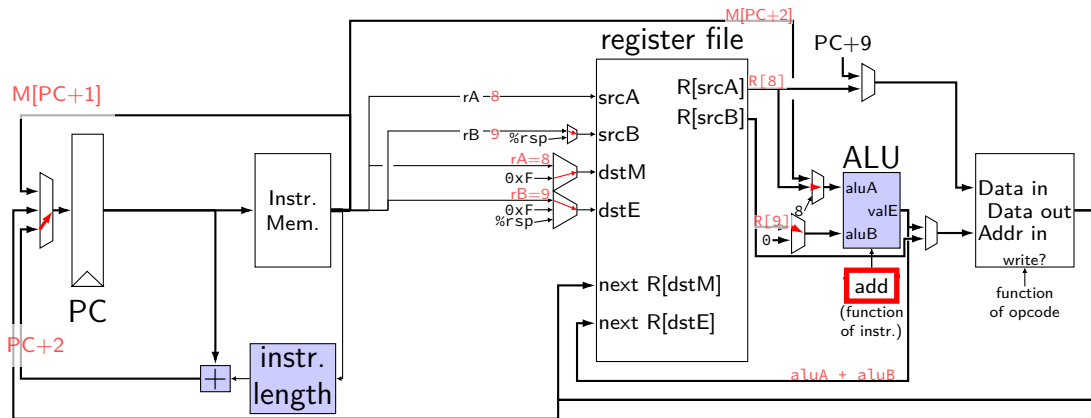


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `rmmovq`?

circuit: setting MUXes

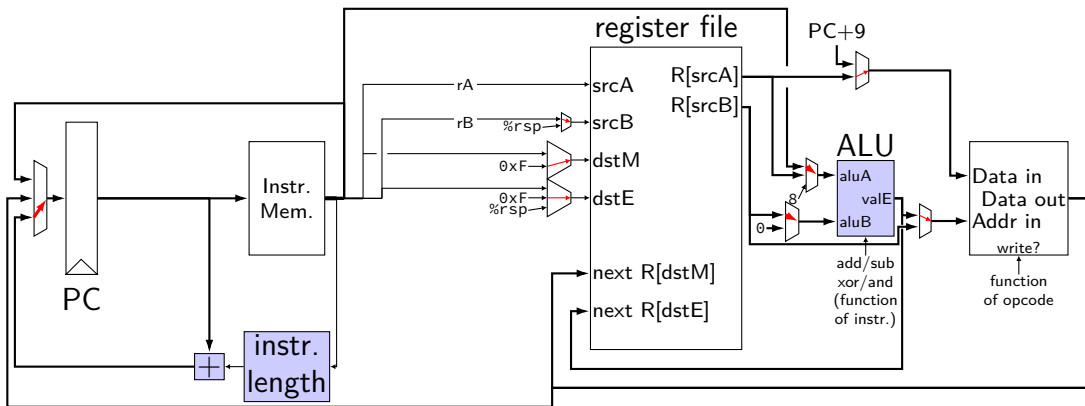


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **rmmovq**?

circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `irmovq`?

circuit: setting MUXes

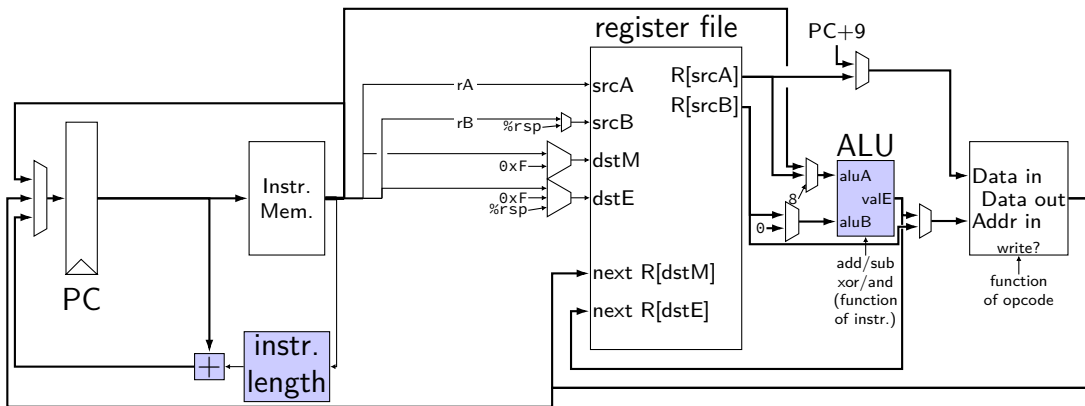


MUXes — PC, $dstM$, $dstE$, $aluA$, $aluB$, $dmemIn$, $dmemAddr$, ...
Exercise: what do they select for `mrmovq`?

circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **jle**?

circuit: setting MUXes

 


MUXes — PC, $dstM$, $dstE$, $aluA$, $aluB$, $dmemIn$, $dmemAddr$, ...
Exercise: what do they select for **ret**?

circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **popq**?

circuit: setting MUXEs

 

MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **call**?

backup slides

comparing to yis

```
$ ./hclrs nopjmp_cpu.hcl nopjmp.yo
```

```
...  
...
```

```
+----- (end of halted state) -----+
```

```
Cycles run: 7
```

```
$ ./tools/yis nopjmp.yo
```

```
Stopped in 7 steps at PC = 0x1e.  Status 'HLT', CC Z=1 S=0 O=0
```

```
Changes to registers:
```

```
Changes to memory:
```

HCLRS summary

declare/assign values to **wires**

MUXes with

```
[ test1: value1; test2: value2; 1: default; ]
```

register banks with **register** i0:

next value on i_name; current value on O_name

fixed functionality

register file (15 registers; 2 read + 2 write)

memories (data + instruction)

Stat register (start/stop/error)