

SEQ Continued


February 23, 2023

exercise: mov-to-register

irmovq \$constant, %rYY


rrmovq %rXX, %rYY

mrmovq 10(%rXX), %rYY

 


for which of these are we going to need MUXes? before...

 - A. register file's register number (index) inputs (reg_srcA, reg_srcB, reg_dstE, ...)
- ✓ B. register file's value inputs (reg_inputE/M)
- ✓ C. PC register's input +2, +10
- ~~✗~~ D. instruction memory's address input (pc)



mov-to-register CPU

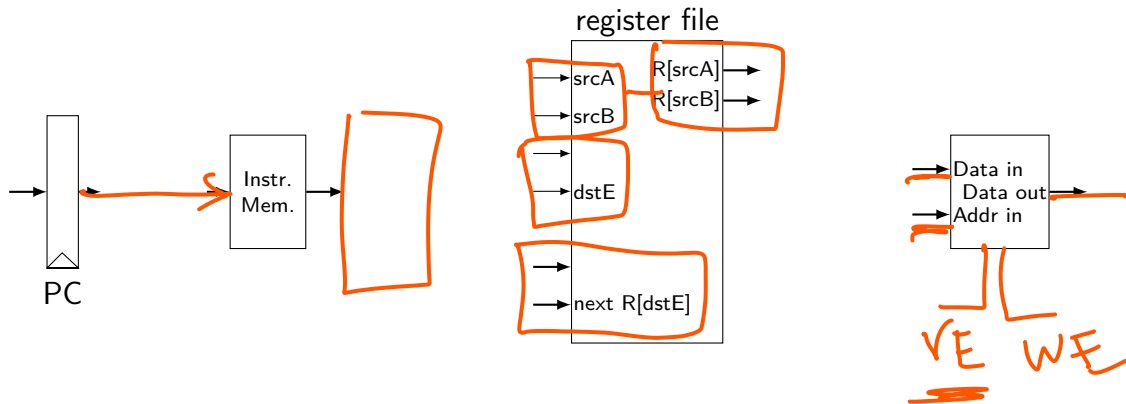

`rrmovq rA, rB`




`irmovq V, rB`



`mrmovq D(rB), rA`




mov-to-register CPU

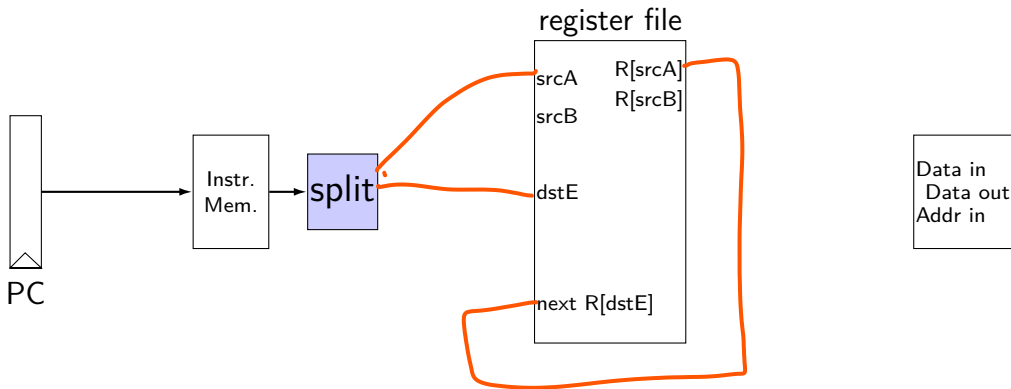


`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 


mov-to-register CPU

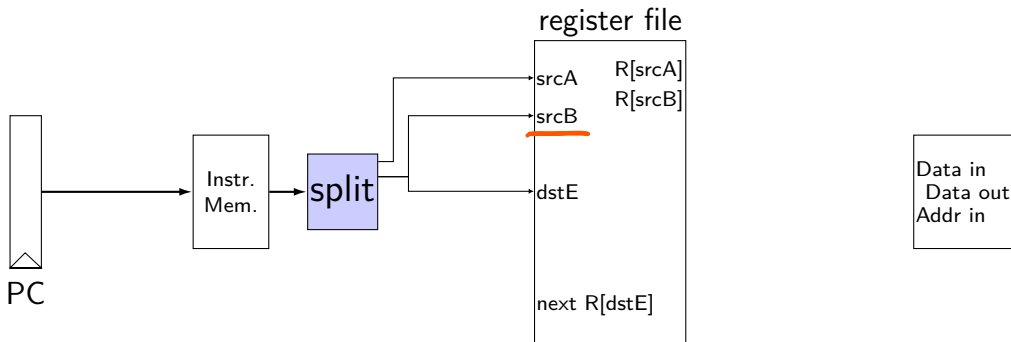


`rrmovq rA, rB`

`irmovq V, rB`

`rrmovq D(rB), rA`

 

mov-to-register CPU

 

`rrmovq rA, rB`




`irmovq V, rB`



`rrmovq D(rB), rA`



mov-to-register CPU

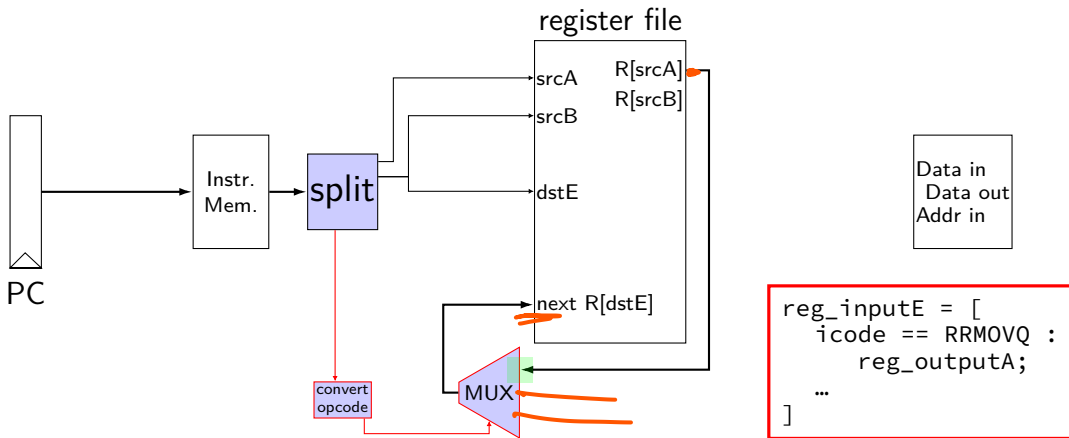

rrmovq rA, rB



irmovq V, rB




rrmovq D(rB), rA



mov-to-register CPU

$D + rB$

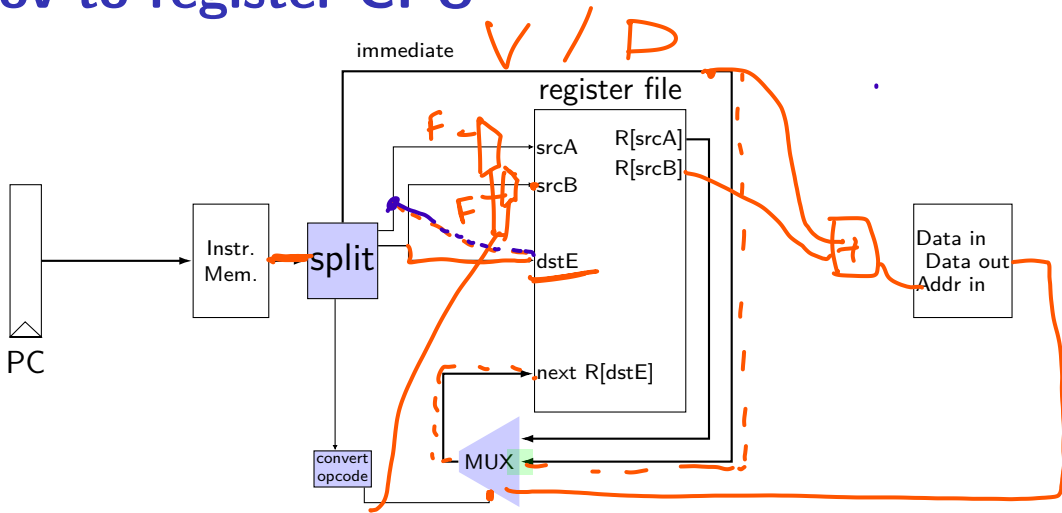


`rrmovq rA, rB`

`irmovq V, rB`

`rrmovq D(rB), rA`

2	0	rA	rB	
3	0	F	rB	V
5	0	rA	rB	D


mov-to-register CPU

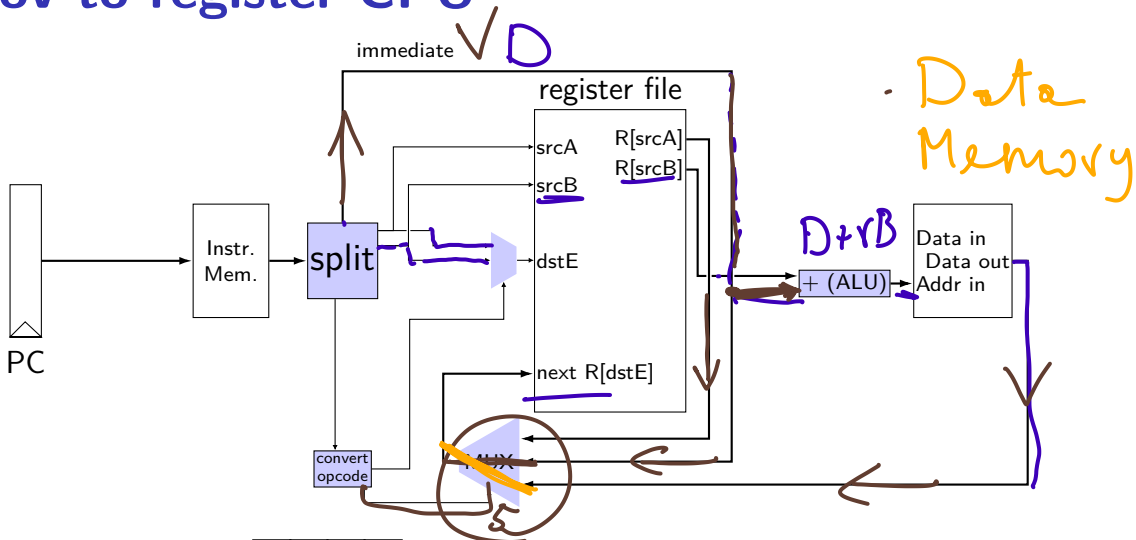


`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 


mov-to-register CPU

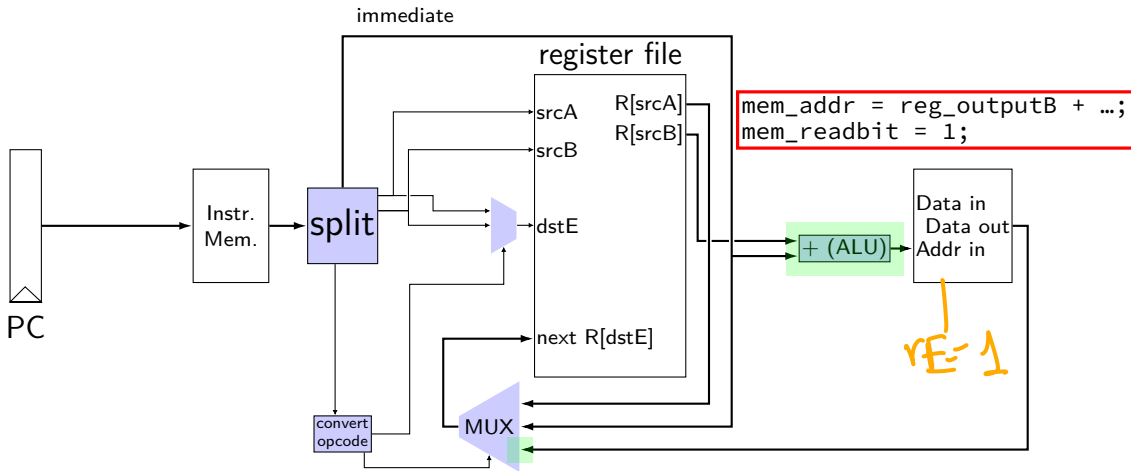


`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 


mov-to-register CPU

 

`rrmovq rA, rB`

`irmovq V, rB`

`mrmovq D(rB), rA`

 

simple ISA: mov (all cases)


`irmovq $constant, %rYY`

`rrmovq %rXX, %rYY`

`mrmovq 10(%rXX), %rYY`

`rmmovq %rXX, 10(%rYY)`

mov CPU

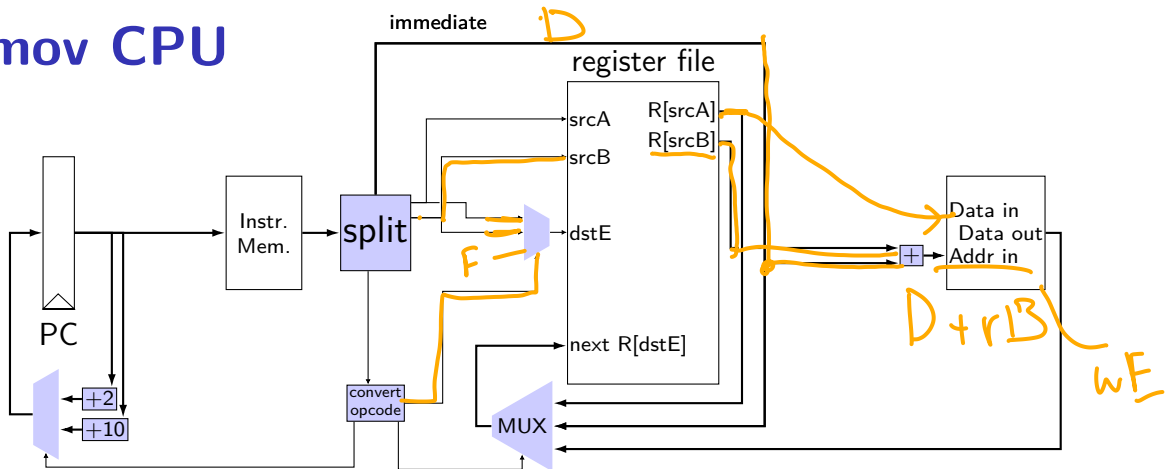

`rrmovq rA, rB`



`irmovq V, rB`




`rrmovq D(rB), rA`



`rmmovq rA, D(rB)`



mov CPU

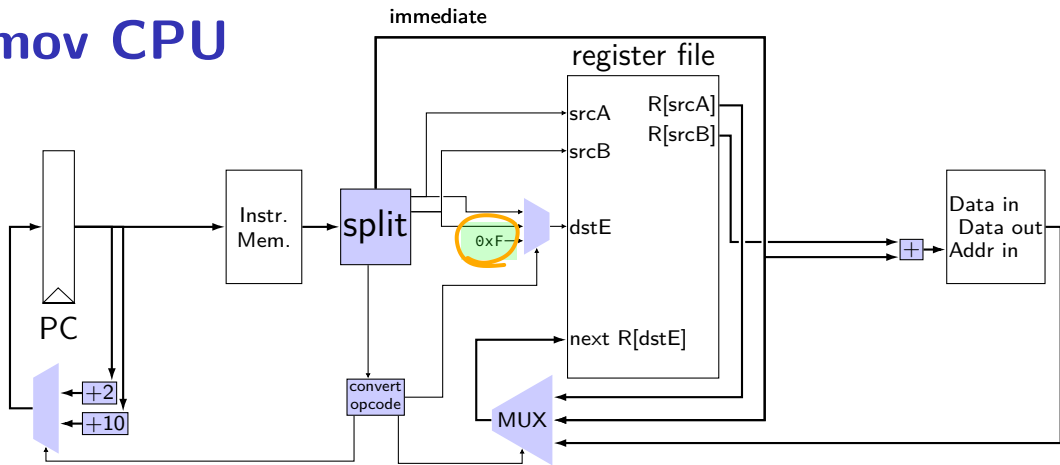

`rrmovq rA, rB`

2	0	rA	rB
---	---	----	----

`irmovq V, rB`

3	0	F	rB
---	---	---	----


`rrmovq D(rB), rA`

5	0	rA	rB
---	---	----	----

`rmmovq rA, D(rB)`

4	0	rA	rB
---	---	----	----

mov CPU

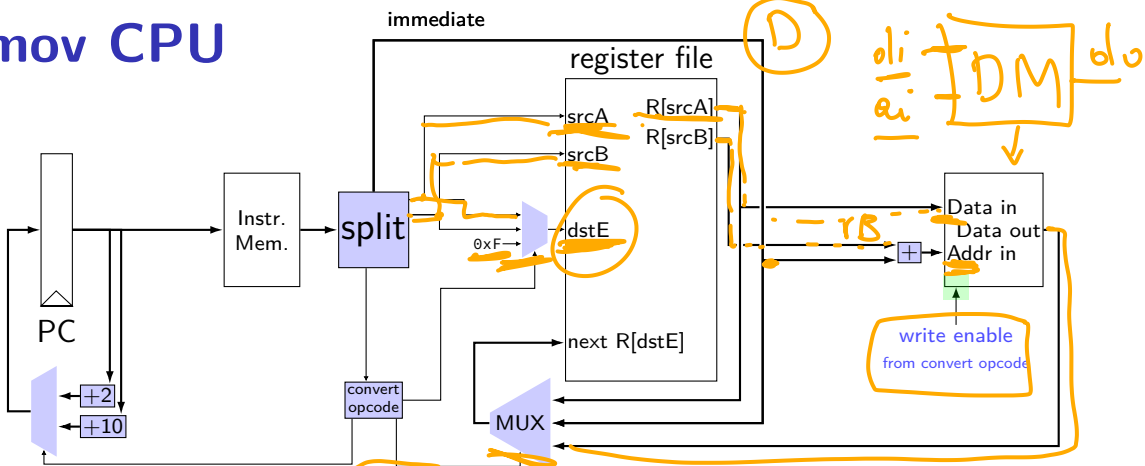

`rrmovq rA, rB`

`irmovq V, rB`


`mrmovq D(rB), rA`

`rmmovq rA, D(rB)`

2	0	rA	rB	
3	0	F	rB	V
5	0	rA	rB	D
4	0	rA	rB	D

D + rB ↓ ↓


mov CPU

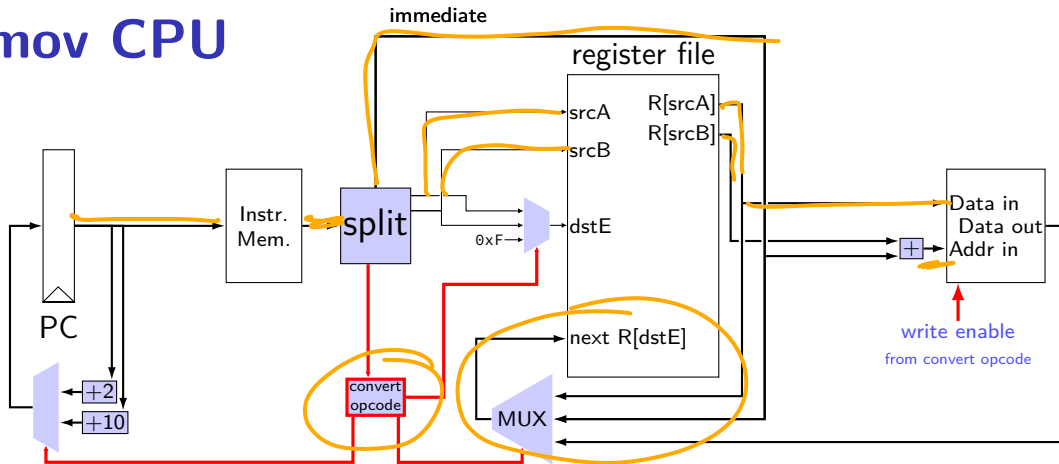

`rrmovq rA, rB`



`irmovq V, rB`

 


`rrmovq D(rB), rA`



`rmmovq rA, D(rB)`




mov CPU


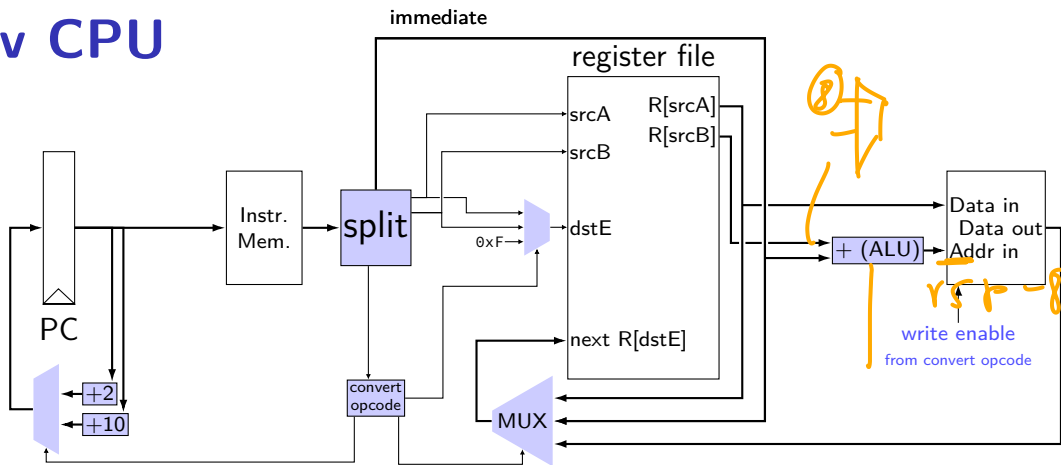


mov CPU


PC update

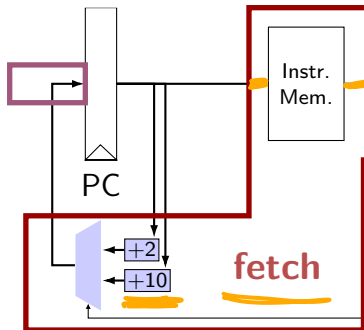

immediate

  


register file

 


writeback

execute

 

memory

 

write enable
from convert opcode

Stages

conceptual division of instruction:

fetch — read instruction memory, split instruction, compute length

decode — read register file

execute — arithmetic (including of addresses)

memory — read or write data memory

write back — write to register file

PC update — compute next value of PC

stages and time

fetch / decode / execute / memory / write back / PC update

Order when these events happen `pushq %rax` instruction:

1. instruction read
2. memory changes ✓
3. %rsp changes ✓
4. PC changes ✓

Hint: recall how registers, register files, memory works

- a. 1; then 2, 3, and 4 in any order
- b. 1; then 2, 3, and 4 at almost the same time
- c. 1; then 2; then 3; then 4
- d. 1; then 3; then 2; then 4
- e. 1; then 2; then 3 and 4 at almost the same time
- f. something else

SEQ: instruction fetch

read instruction memory at PC

split into separate wires:

icode:ifun — opcode


rA, rB — register numbers

valC — call target or mov displacement

compute next instruction address:

valP — $PC + (\text{instr length})$

instruction fetch

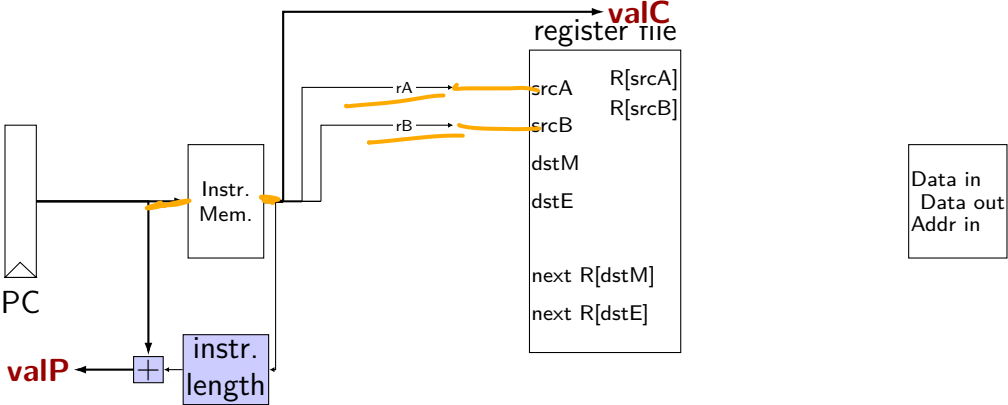


SEQ: instruction “decode”

read registers


`valA`, `valB` — register values

instruction decode (1)

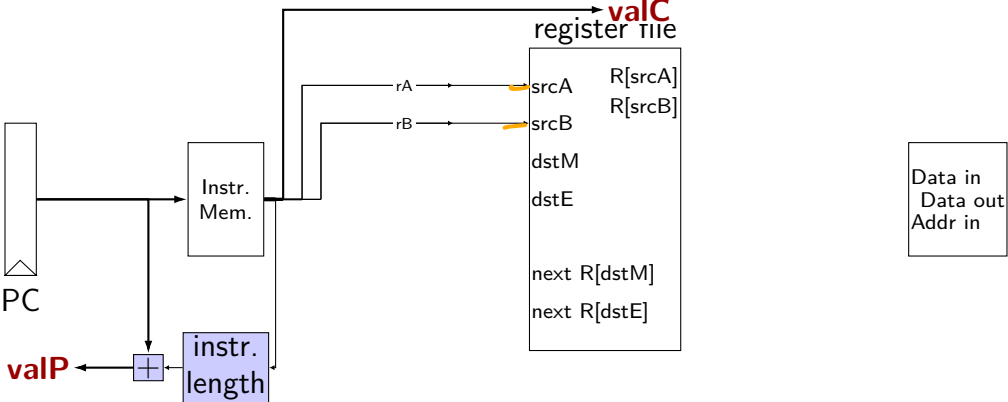

instruction decode (1)


nop *addq*
□ □
pushq *rax*
rsp

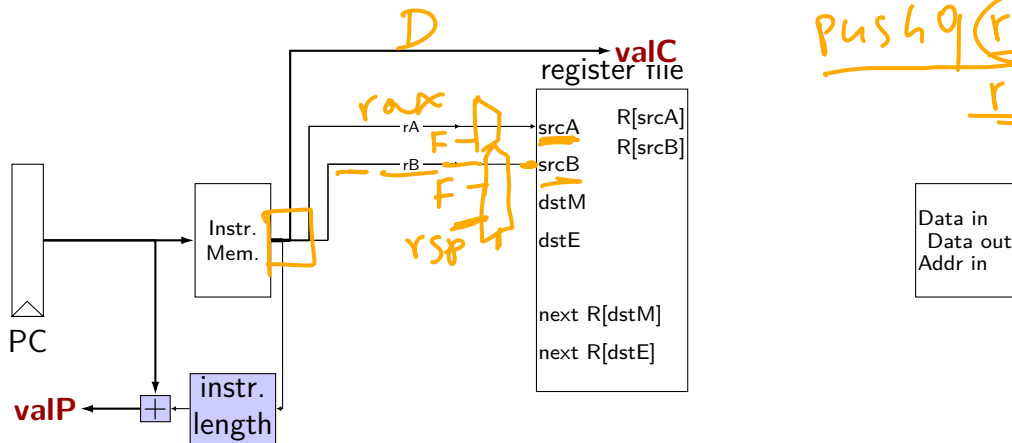

exercise: for which instructions would there be a problem ?

nop, *addq*, *mrmovq*, *rmmovq*, *jmp*, *pushq*

instruction decode (1)

 

SEQ: srcA, srcB

always read rA, rB?

Problems:

- push rA

- pop

- call


- ret

book: extra signals: srcA, srcB — computed input register

MUX controlled by icode


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 

instruction decode (2)

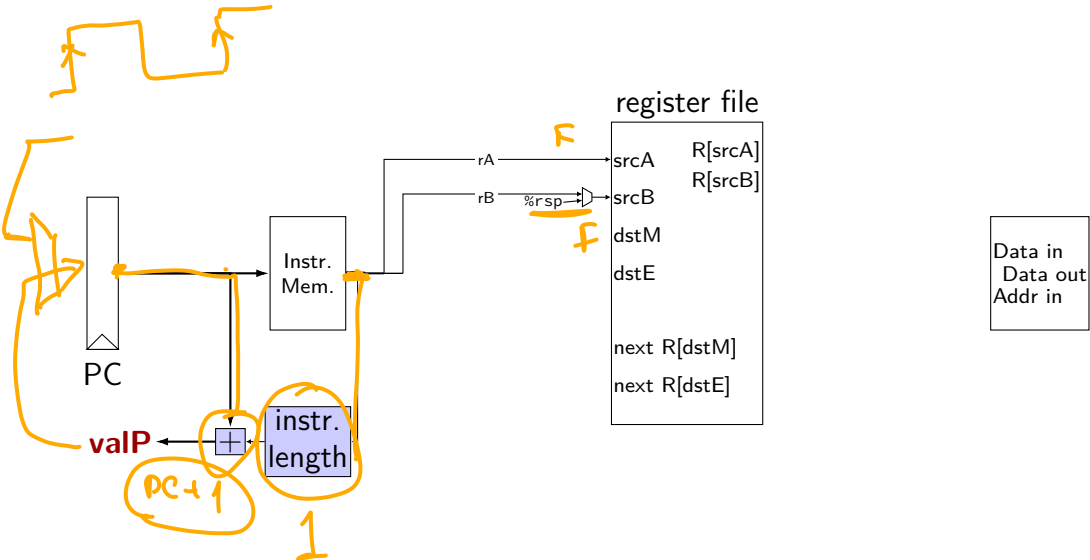

SEQ: execute

perform ALU operation (add, sub, xor, and)


valE — ALU output

read prior condition codes


Cnd — condition codes based on ifun (instruction type for jCC/cmouvCC)

write new condition codes

using condition codes: cmov

 


execute (1)

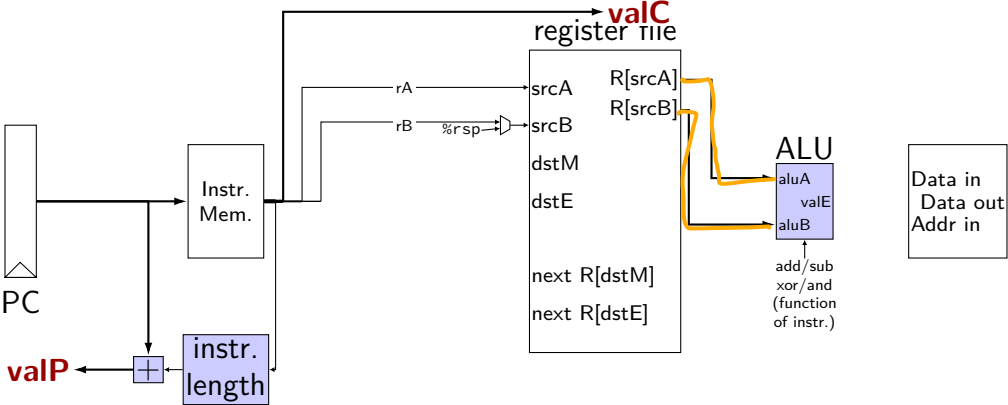

execute (1)

$$\underline{D + r_b \rightarrow r_a}$$

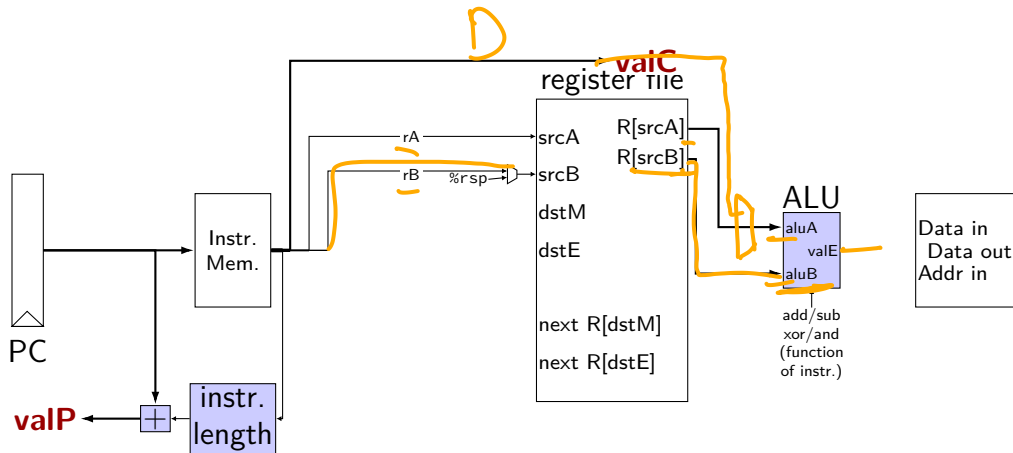


exercise: which of these instructions would there be a problem ?
nop, addq, mrmovq, popq, call,

SEQ: ALU operations?

ALU inputs always **valA**, **valB** (register values)?

no, inputs from instruction: (Displacement + rB)

`mrmovq`
`rmmovq`

 


no, constants: (rsp +/- 8)

`pushq`
`popq`
`call`
`ret`

extra signals: **aluA**, **aluB**

computed ALU input values

execute (2)

 


SEQ: Memory


read or write data memory

valM — value read from memory (if any)

memory (1)

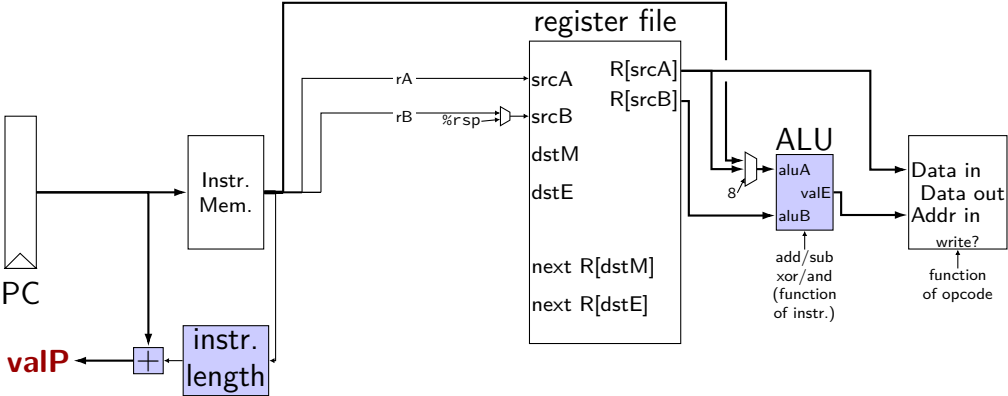

memory (1)

 

exercise: which of these instructions would there be a problem ?
nop, rmmovq, mrmovq, popq, call,

SEQ: control signals for memory

read/write — read enable? write enable?

Addr — address

mostly ALU output


special cases (need extra MUX): `popq`, `ret`

Data — value to write

mostly `valA`

special cases (need extra MUX): `call`


memory (2)

 

SEQ: write back


write registers

write back (1)

 


write back (1)

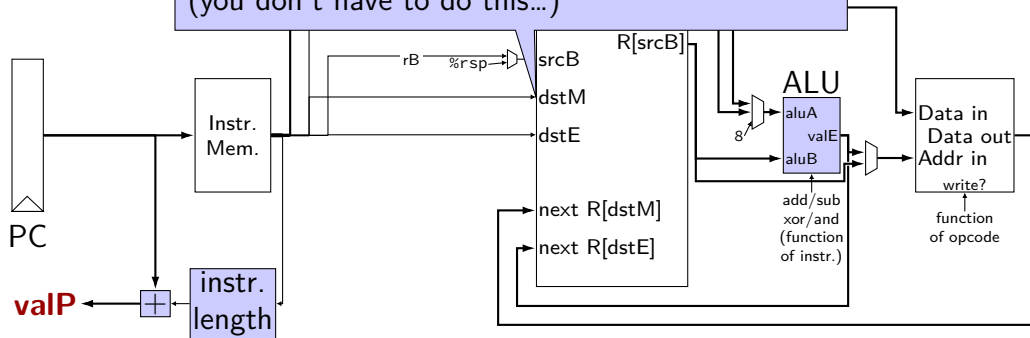textbook convention:
E used for storing ALU results (e.g. add)
M used for storing memory results (e.g. rmmovq)
(you don't have to do this...)



write back (1)

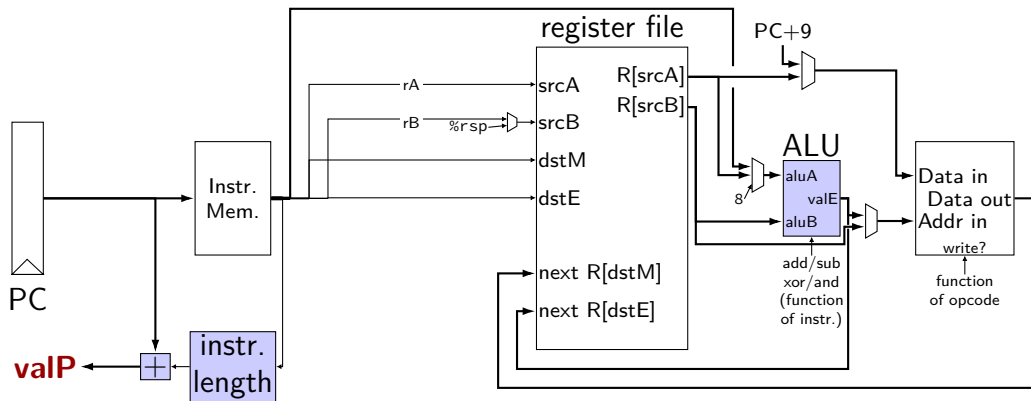


exercise: which of these instructions would there be a problem ?
nop, irmovq, mrmovq, rmmovq, addq, popq

SEQ: control signals for WB


two write inputs — two needed by popq
valM (memory output), valE (ALU output)

two register numbers
dstM, dstE

 
write disable — use dummy register number 0xF



write back (2a)

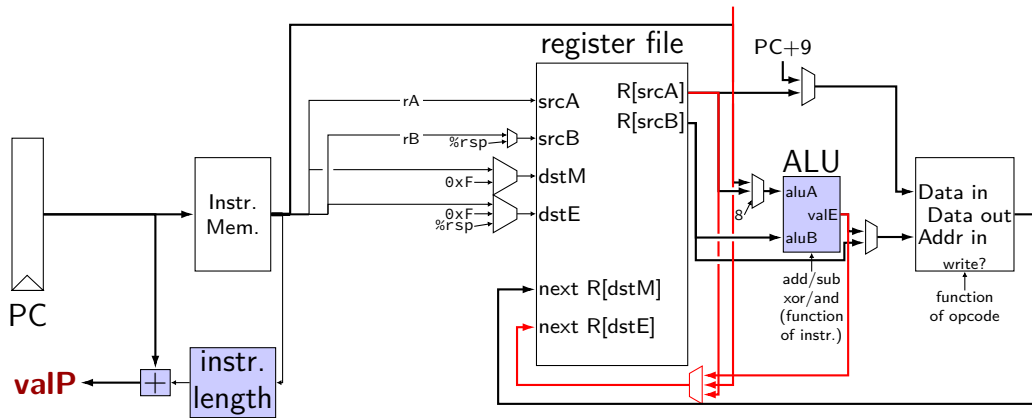

write back (2b)

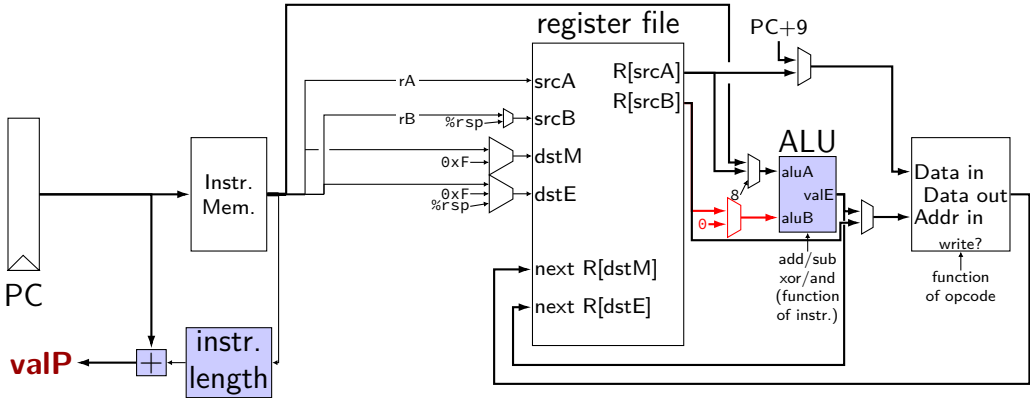


SEQ: Update PC

choose value for PC next cycle (input to PC register)


usually valP (following instruction)

exceptions: `call`, `jCC`, `ret`

PC update

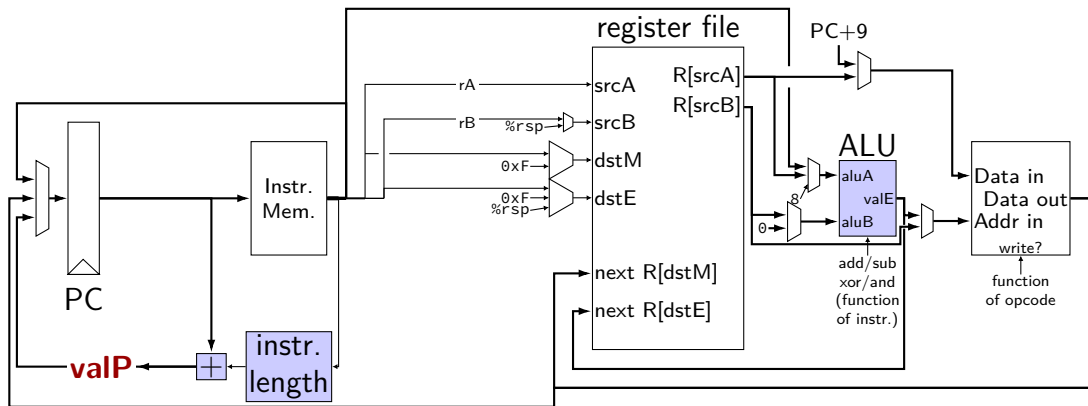


circuit: setting MUXes

 


MUXes — PC, $dstM$, $dstE$, $aluA$, $aluB$, $dmemIn$, $dmemAddr$, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXes

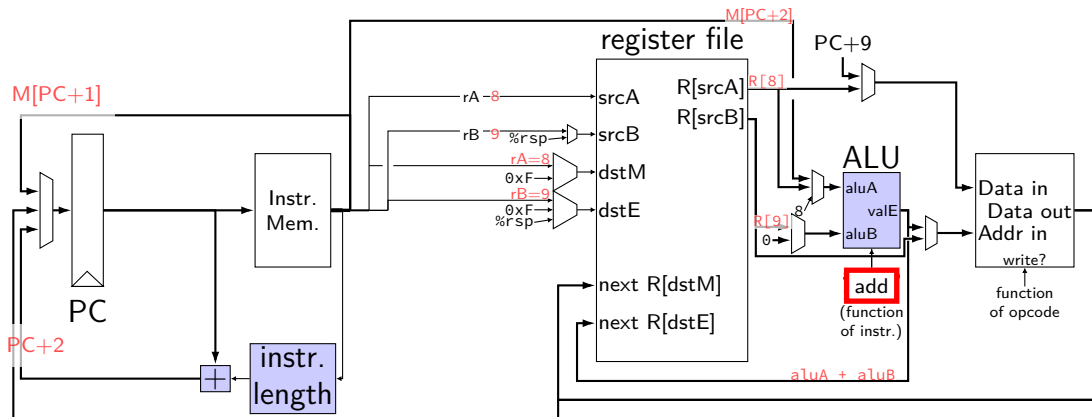


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXEs

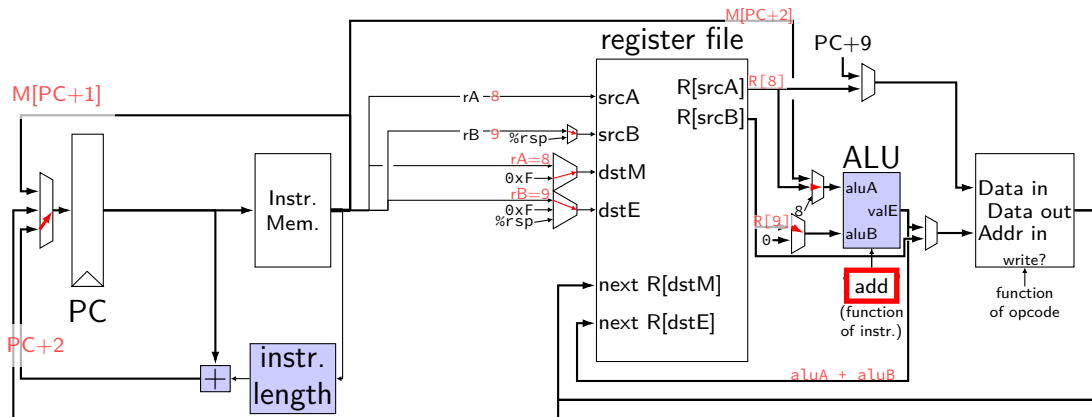


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXEs

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **rmmovq**?

circuit: setting MUXes

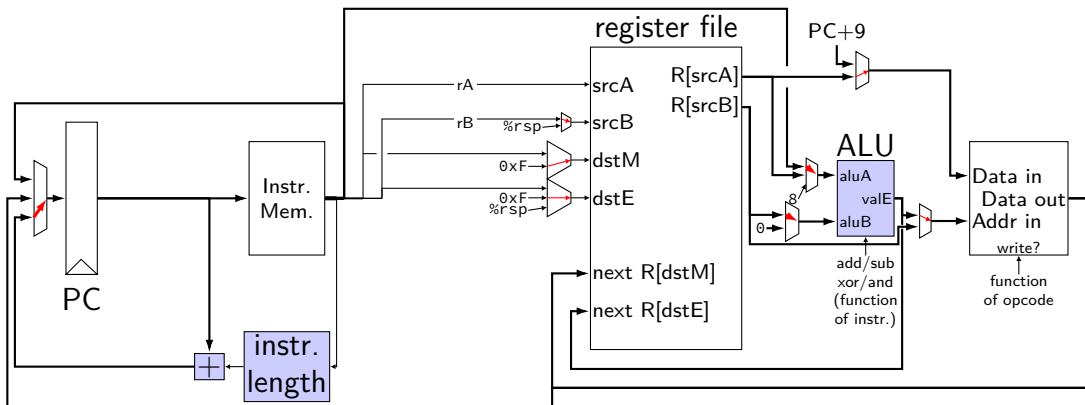


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **rmmovq**?

circuit: setting MUXes

 


MUXes — PC, `dstM`, `dstE`, `aluA`, `aluB`, `dmemIn`, `dmemAddr`, ...
Exercise: what do they select for `irmovq`?

circuit: setting MUXes

 


MUXes — PC, `dstM`, `dstE`, `aluA`, `aluB`, `dmemIn`, `dmemAddr`, ...
Exercise: what do they select for `mrmovq`?

circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **jle**?

circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `cmovle`?

circuit: setting MUXEs

 


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **ret**?

circuit: setting MUXes

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **popq**?

circuit: setting MUXEs

 

MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **call**?

backup slides

comparing to yis

```
$ ./hclrs nopjmp_cpu.hcl nopjmp.yo
```

```
...  
...
```

```
+----- (end of halted state) -----+
```

```
Cycles run: 7
```

```
$ ./tools/yis nopjmp.yo
```

```
Stopped in 7 steps at PC = 0x1e.  Status 'HLT', CC Z=1 S=0 O=0
```

```
Changes to registers:
```

```
Changes to memory:
```

HCLRS summary

declare/assign values to **wires**

MUXes with

```
[ test1: value1; test2: value2; 1: default; ]
```

register banks with **register** `i0`:

next value on `i_name`; current value on `O_name`

fixed functionality

register file (15 registers; 2 read + 2 write)

memories (data + instruction)

Stat register (start/stop/error)