

last time

timing on our processor

changing stored values: triggered by rising clock edge

other things: computed as inputs change

current design: one instruction per cycle

data memory / write enable

implementing movs, etc.

“stages”

fetch / decode [reg read] / execute [ALU] / memory / write back [reg write]

quiz Q1

adding incq: what encoding?

want: distinct, so we won't confuse it with others

$0x60$, $0x1[rX]$ — already used for `addq %rcx, rX`

$[rX]0xF$ — if $rX = \%rcx$, shares icode with `nop` (technically not already used, but ...)

want: fields in same place as other instructions to simplify logic

$[rX]0xF$ and $0xE[rX]$ — rX not in second byte like other instructions

quiz Q2

adding incq: new MUX to control?

address input to instruction memory — no, still from PC register
out

register value input — no, still comes from ALU
add MUX controlling ALU inputs instead

quiz Q3

rjmq %r?? — machine code format

- one field for register index

- icode, but different than others

most similar to popq — just change icode

others required changing length/removing fields/etc.

quiz Q4

rjmq %r?? — PC register input

needs to be address of next instruction

= address stored in %r??

≠ index of %r?? in register file

address stored in %r?? will be output from register file

quiz Q5

rjmq %r??

need to read register %r??

so, need to pass register index from instruction to register file

SEQ: instruction fetch

read instruction memory at PC

split into separate wires:

icode:ifun — opcode


rA, rB — register numbers

valC — call target or mov displacement

compute next instruction address:

valP — $PC + (\text{instr length})$

instruction fetch

 


SEQ: instruction “decode”


read registers

`valA`, `valB` — register values

instruction decode (1)

 


instruction decode (1)

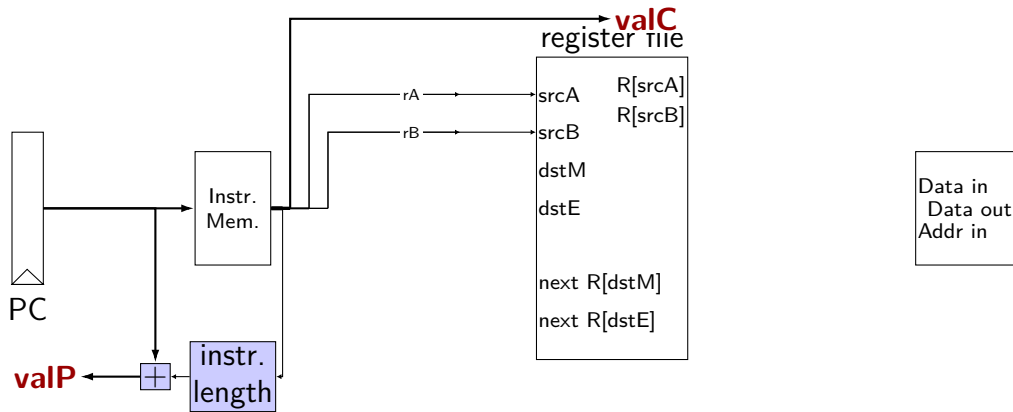

exercise: for which instructions would there be a problem ?
nop, addq, mrmovq, rmmovq, jmp, pushq

instruction decode (1)

 

SEQ: srcA, srcB

always read rA, rB?

Problems:

- push rA

- pop

- call


- ret

book: extra signals: srcA, srcB — computed input register

MUX controlled by icode


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 


SEQ: possible registers to read

instruction	srcA	srcB
halt, nop, jCC, irmovq	none	none
cmovCC, rrmovq	rA	none
mrmovq	none	rB
rmmovq, OPq	rA	rB
call, ret	none?	%rsp
pushq, popq	rA	%rsp

 

instruction decode (2)

 

SEQ: execute

perform ALU operation (add, sub, xor, and)


valE — ALU output

read prior condition codes


Cnd — condition codes based on ifun (instruction type for jCC/cmouvCC)

write new condition codes


using condition codes: cmov

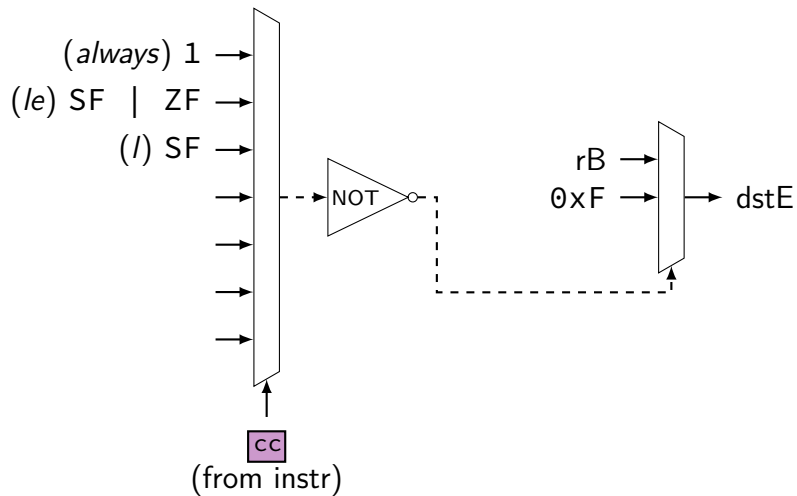

execute (1)

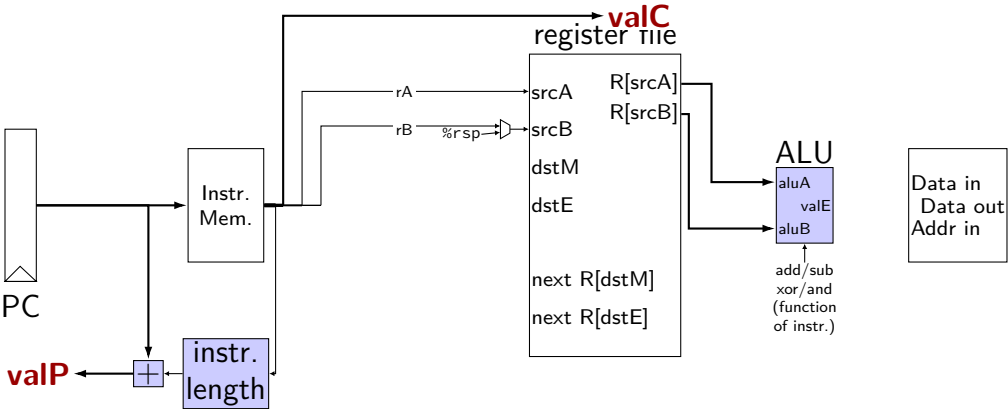

execute (1)

 


exercise: which of these instructions would there be a problem ?
nop, addq, mrmovq, popq, call,

SEQ: ALU operations?

ALU inputs always **valA**, **valB** (register values)?

no, inputs from instruction: (Displacement + rB)

`mrmovq`
`rmmovq`

 


no, constants: (rsp +/- 8)

`pushq`
`popq`
`call`
`ret`

extra signals: **aluA**, **aluB**

computed ALU input values

execute (2)

 


SEQ: Memory


read or write data memory

valM — value read from memory (if any)

memory (1)

 

memory (1)

 

exercise: which of these instructions would there be a problem ?
nop, rmmovq, mrmovq, popq, call,

SEQ: control signals for memory

read/write — read enable? write enable?

Addr — address

mostly ALU output


special cases (need extra MUX): `popq`, `ret`

Data — value to write

mostly `valA`

special cases (need extra MUX): `call`


memory (2)

 

SEQ: write back

write registers

write back (1)

 


write back (1)

textbook convention:


E used for storing ALU results (e.g. add)

M used for storing memory results (e.g. rmmovq)

(you don't have to do this...)

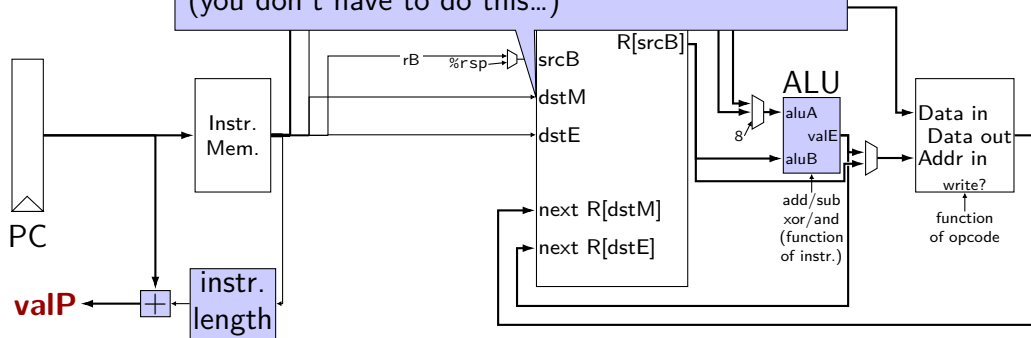

write back (1)

 


exercise: which of these instructions would there be a problem ?
nop, irmovq, mrmovq, rmmovq, addq, popq

SEQ: control signals for WB


two write inputs — two needed by popq
valM (memory output), valE (ALU output)

two register numbers
dstM, dstE

 
write disable — use dummy register number 0xF



write back (2a)

 

write back (2b)

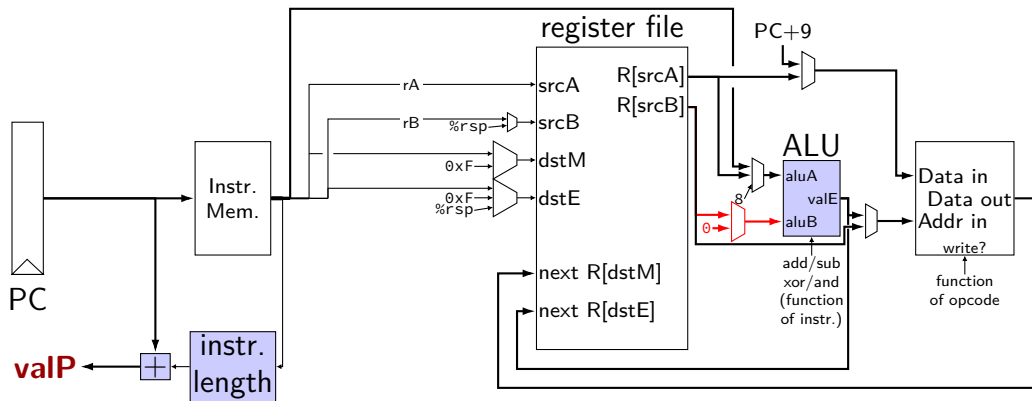


SEQ: Update PC

choose value for PC next cycle (input to PC register)


usually valP (following instruction)

exceptions: `call`, `jCC`, `ret`

PC update

 


circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXEs

 


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXes

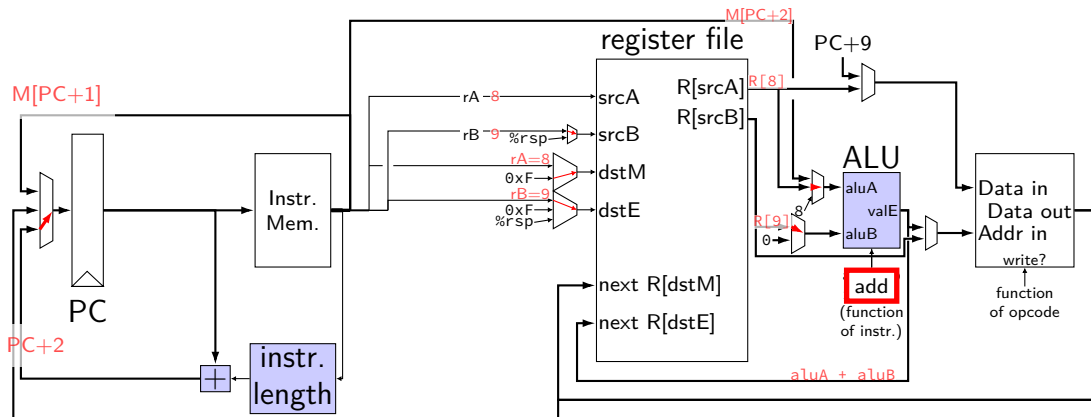


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select when running `addq %r8, %r9`?

circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **rmmovq**?

circuit: setting MUXEs

 


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **rmmovq**?

circuit: setting MUXEs

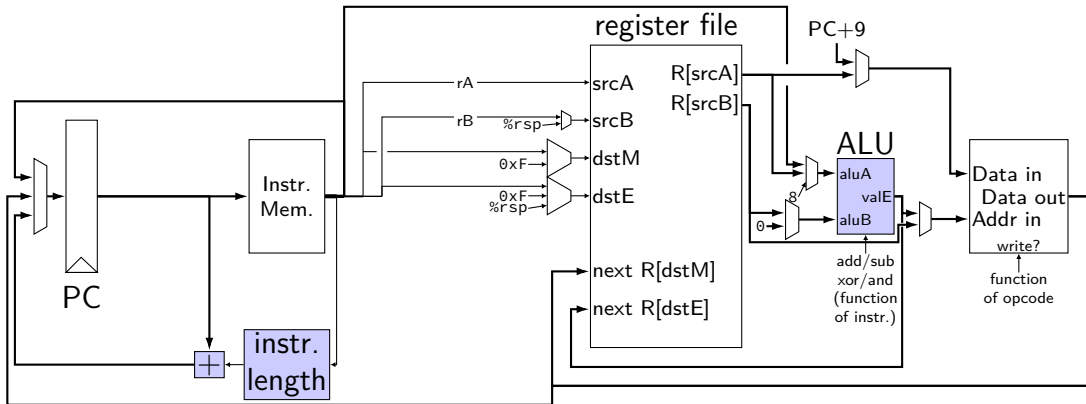


MUXEs — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `irmovq`?

circuit: setting MUXEs

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **mrmovq**?

circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for `jle`?

circuit: setting MUXes

 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **cmovle**?

circuit: setting MUXes

 


MUXes — PC, $dstM$, $dstE$, $aluA$, $aluB$, $dmemIn$, $dmemAddr$, ...
Exercise: what do they select for **ret**?

circuit: setting MUXes

 


MUXes — PC, *dstM*, *dstE*, *aluA*, *aluB*, *dmemIn*, *dmemAddr*, ...
Exercise: what do they select for **popq**?

circuit: setting MUXes


 


MUXes — PC, dstM, dstE, aluA, aluB, dmemIn, dmemAddr, ...
Exercise: what do they select for **call**?


Human pipeline: laundry

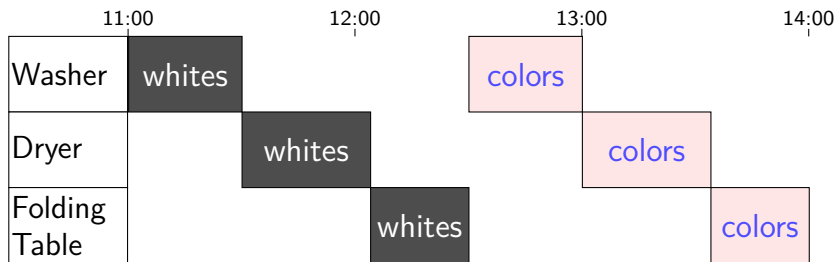

Human pipeline: laundry

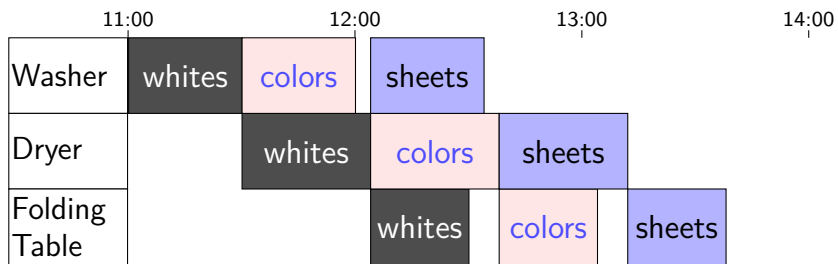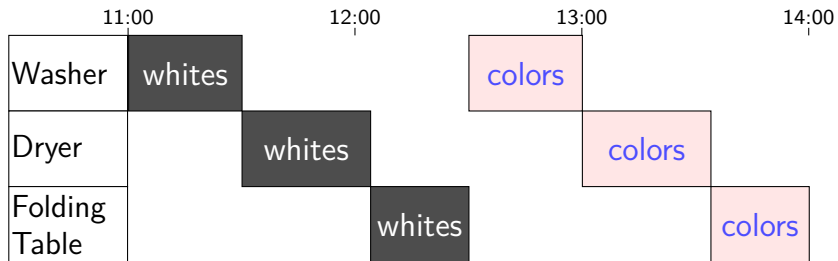


Waste (1)

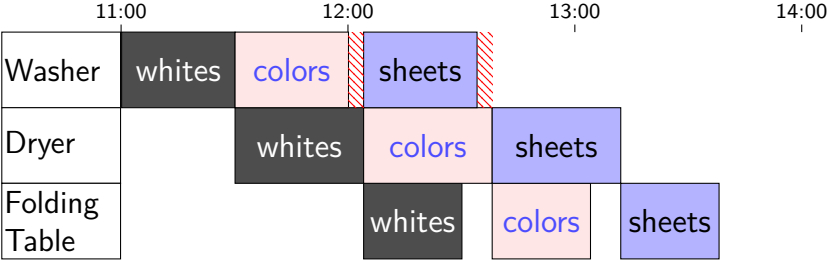


Waste (1)


wasted time!

 


Waste (2)

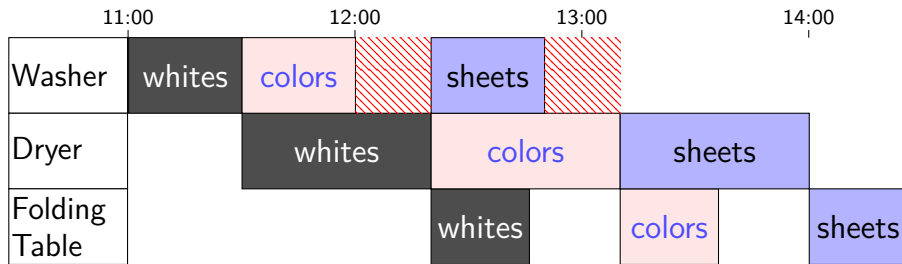


Latency — Time for One

 


Latency — Time for One

 


Latency — Time for One

 

Throughput — Rate of Many

 


Throughput — Rate of Many

 


$$\frac{1 \text{ load}}{0.83\text{h}} = 1.2 \text{ loads/h}$$

Throughput — Rate of Many


 


$$\frac{1 \text{ load}}{0.83\text{h}} = 1.2 \text{ loads/h}$$


times three circuit

 


times three circuit

  


times three circuit

 


 
100 ps latency \implies 10 results/ns throughput




times three and repeat

 


times three and repeat

  

pipelined times three

 

pipelined times three

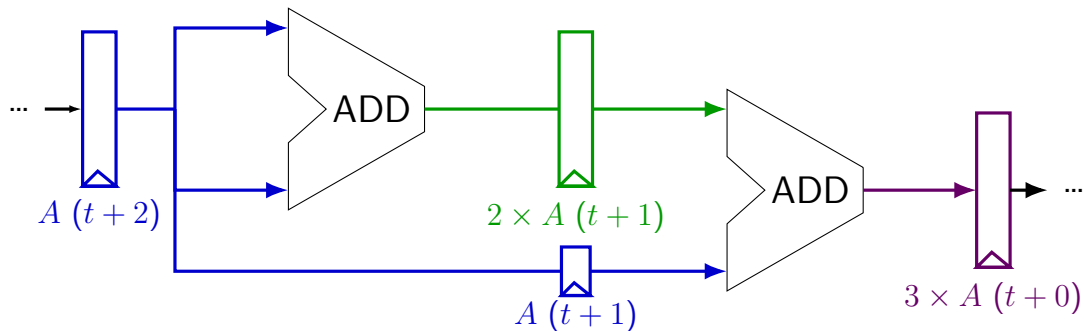

$A(t+2)$	7	17
$A(t+1)$	7	17
$2 \times A(t+1)$	14	34
$3 \times A(t+0)$		21