

Code and Circuits

CS 2130: Computer Systems and Organization 1


September 14, 2022

Announcements

- Homework 1 due tonight!
- Homework 2 available (due on Gradescope, 11pm Monday)



1-bit Register Circuit

rising clock edge

 


Building a Counter

Bios

  


Another Circuit

 


| x | y | tick |
|-------|---|------|
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 2 |
| <hr/> | | |
| 2 | 1 | 3 |
| 3 | 2 | 4 |
| <hr/> | | |
| 5 | 3 | 5 |
| 8 | 5 | 6 |

Another Circuit

 

Common Model in Computers

 

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we *already* know: $\&$, $|$, \wedge , \sim
- Operations we can build from gates: $+$, $-$
- Others we can build:

$*$

$$\begin{array}{r} 2130 \\ * \underline{1101} \\ \hline 2130 \\ 0000 \\ 2130 \\ + 2130 \\ \hline \end{array}$$

$/$
 $\%$

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we *already* know: $\&$, $|$, \wedge , \sim
- Operations we can build from gates: $+$, $-$
- Others we can build:
- Ternary operator: $? :$

$z = b ? x : y$

$z = (a == b ? 32 : x) \& y$
 $\&$ and $\&$ or

$\text{if}(b)$
 $z = x$
 else
 $z = y$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: z = x * y



Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$
- What about the following?

$$x = 1$$

$$x = 0$$



Equals


Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$
- What about the following?

$$x = 1$$

$$x = 0$$

 - **Single assignment:** each variable can only be assigned a value once



Comparisons

Each of our comparisons in code are straightforward to build:

- == - xor then nor bits of output

$$x == y \quad \sim \left(\overset{\text{or all bits}}{(x \wedge y)} \right)$$

!

$$x = 1001$$

$$y = 1001$$

$$\begin{array}{c} 0000 \\ \xrightarrow{\text{or}} \end{array} = 0$$

Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output

Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output
- `<` - consider $x < 0$

$$x - y < 0$$

Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output
- `<` - consider $x < 0$
- `>`, `<=`, `=>` are similar