

# Building a Computer

---

CS 2130: Computer Systems and Organization 1

February 8, 2023

# Announcements

- Homework 2 due next Monday

# Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we *already* know:  $\&$ ,  $|$ ,  $\wedge$ ,  $\sim$
- Operations we can build from gates:  $+$ ,  $-$
- Others we can build:
- Ternary operator:  $?$  :

# Equals

Equals: =

- Attach with wire (i.e., connect things)
- Ex:  $z = x * y$
- What about the following?

$$x = 1$$

$$x = 0$$

- **Single assignment:** each variable can only be assigned a value once

# Comparisons

Each of our comparisons in code are straightforward to build:

- == - xor then nor bits of output

$$\sim (x \wedge y)$$

!

# Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output

# Comparisons

Each of our comparisons in code are straightforward to build:

- == - xor then nor bits of output
- != - same as == without not of output
- < - consider  $x < 0$

$$x < y ?$$

$$x - y < 0$$

$$(x \gg 31 \& 1)$$

# Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output
- `<` - consider  $x < 0$
- `>`, `<=`, `=>` are similar



# Indexing


Indexing with square brackets: [ ]

- **Register bank** (or **register file**) - an array of registers
  - Can programmatically pick one based on index
  - I.e., can determine which register while running
- Two important operations:
  - $x = R[i]$  - Read from a register
  - $R[j] = y$  - Write to a register

# Reading

$x = R[i]$  - connect output of registers to  $x$  based on index  $i$


$z = R[k]$

 

# Aside: 4-input Mux

How do we build a 4-input mux? How many wires should  $i$  be?


$$i = 3$$
$$11$$

 

# Writing

$R[j] = y$  - connect  $y$  to input of registers based on index  $j$


$R[3] = y$

 

# Aside: Creating $==0$ gates

How do we build gates that check for  $j == w$ ?

$j == 0$

 

j	$==0$
00	1
01	0
10	0
11	0

$j == 1$



j	$==1$
00	0
01	1
10	0
11	0

Need one more thing to build computers

# Memory and Storage

## Registers

- 6 gates each per bit,  $\approx$  24 transistors
- Efficient, fast
- Expensive!
- Ex: local variables

1 byte = 8 bits  $\approx$  KiB

1024

## Memory

$\approx$  GiB

- Two main types: SRAM, DRAM
- DRAM: 1 transistor, 1 capacitor per bit
- DRAM is cheaper, simpler to build
- Ex: data structures, local variables


*These do not persist between power cycles*

# Memory and Storage
 
## Disk

≈ GiB-TiB

- Two main types: flash (solid state), magnetic disk
- Magnetic drive
  - Platter with physical arm above and below
  - Cheap to build
  - Very slow! Physically move arm while disk spins



- Ex: files

*Data on disk does persist between power cycles*



Putting it all together

# Our story so far

- Information modeled by voltage through wires (1 vs 0)
- Transistors
- Gates:             $\&$              $|$              $\sim$              $\wedge$
- Multi-bit values: representing integers
- Floating point
- Multi-bit operations using circuits
- Storing results using registers
- Memory

# Code

How do we run code? What do we need?

## Example Code

```
...  
8:  x = 16  
9:  y = x  
10: x += y  
...
```

What is the value of x after line 10?

# Bookkeeping

RAM





What do we need to keep track of?

- **Code** - the program we are running
  - RAM (Random Access Memory)
- **State** - things that may change value (i.e., variables)
  - Register file - can read and write values each cycle
- **Program Counter (PC)** - where we are in our code
  - Single register - byte number in memory for next instruction



# Building a Computer

  


# Encoding Instructions

## Encoding of Instructions (**icode** or **opcode**)


- Numeric mapping from icode to operation

### Example 3-bit icode

icode	meaning
0	$rA = rB$
1	$rA += rB$
2	$rA \&= rB$
...	...

 

# Building a Computer

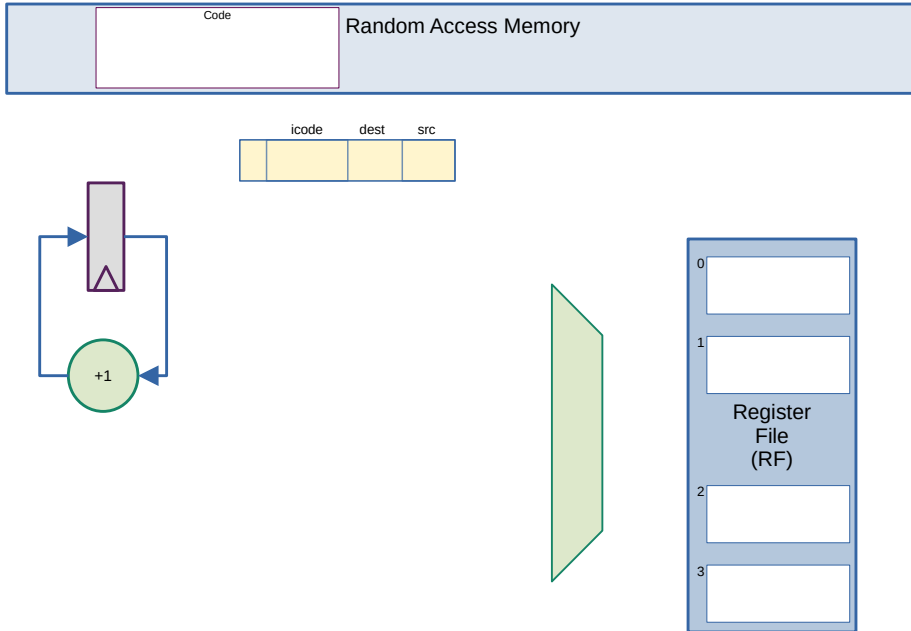









# Building a Computer

