
 


Computer Systems and Organization 1

Warm up!

 
Can I make an n -input AND from 2-input AND gates?




parity
0
1

Warm up!

What about XOR gates?

 

110 → 0
010 → 1
000 → 0

 

More bits, circuits, adders

CS 2130: Computer Systems and Organization 1

February 1, 2023

Announcements

- TA Office Hours start tonight!
 - Wednesdays, Rice 011
 - Thurs-Sun, Olsson 001
- Please join our Discord server
- Homework 1 due Monday

Quiz Review

$$0x6 = 6$$

$$0x16 > 16$$

↑ ↑
16' 10'
22

$$-a = na + 1$$

$$a - a = 0$$

$$a + -a = 0$$

$$a + na + 1 = 0$$

$$0xCA$$

$$\gg 3$$

$$\ll 3$$

$$\wedge 0xCA$$

$$\underline{1100} \ 1010$$

$$1111 \ 1001 = -7$$

$$\leftarrow \sim, +1 \quad 111 = 7$$

$$1100 \ 1000$$

$$\underline{1100 \ 1010}$$

$$000000010$$

$$a + na = -1$$

Operations

So far, we have discussed:

- Addition: $x + y$
 - Can get multiplication
- Subtraction: $x - y$
 - Can get division, but more difficult
- Unary minus (negative): $-x$
 - Flip the bits and add 1

Operations (on Integers)

Bit vector: fixed-length sequence of bits (ex: bits in an integer)

- Manipulated by bitwise operations

Bitwise operations: operate over the bits in a bit vector

- Bitwise not: $\sim x$ - flips all bits (unary)
- Bitwise and: $x \ \& \ y$ - set bit to 1 if x, y have 1 in same bit
- Bitwise or: $x \ | \ y$ - set bit to 1 if either x or y have 1
- Bitwise xor: $x \ ^ \ y$ - set bit to 1 if x, y bit differs

Operations (on Integers)

- Logical not: $!x$
 - $!0 = 1$ and $!x = 0, \forall x \neq 0$
 - Useful in C, no booleans
 - Some languages name this one differently
- Left shift: $x \ll y$ - move bits to the left
 - Effectively multiply by powers of 2
- Right shift: $x \gg y$ - move bits to the right
 - Effectively divide by powers of 2
 - Signed (extend sign bit) vs unsigned (extend 0)

Floating Point Numbers

Four cases:

- **Normalized:** What we saw last time

$$s \ eeee \ ffff = \pm 1.ffff \times 2^{eeee - \text{bias}}$$

- **Denormalized:** Exponent bits all 0

$$s \ eeee \ ffff = \pm 0.ffff \times 2^{1 - \text{bias}}$$

- **Infinity:** Exponent bits all 1, fraction bits all 0 (i.e., $\pm\infty$)
- **Not a Number (NaN):** Exponent bits all 1, fraction bits not all 0

Our story so far

- Transistors
- Information modeled by voltage through wires (1 vs 0)
- Gates:




- Multi-bit values: representing integers
 - Signed and unsigned
 - Bitwise operators on bit vectors
- Floating point

How to do the *work* of multi-bit?

Multi-bit Mux

Our first multi-bit example: mux

 


Adder

$$1 + 1 = 10_2$$

Add 2 1-bit numbers: a, b

$$\begin{array}{r} a \\ + b \\ \hline c \quad r \end{array}$$

a	b	c	r
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Adder

Can we use this in parallel to add multi-bit numbers?

Adder


Can we use this in parallel to add multi-bit numbers? What is missing?
Consider:

$$\begin{array}{r} 11 \\ + 01 \\ \hline 0 \end{array}$$


3-input Adder

Add 3 1-bit numbers: a, b, c

a	b	c_{in}	c_{out}	r
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

 
$$\begin{array}{r} 1 \\ 1 \\ 0 \\ \hline 10 \\ \hline \end{array}$$




Ripple-Carry Adder

 
$$\begin{array}{r} x_3 \ x_2 \ x_1 \ x_0 \\ + \ y_3 \ y_2 \ y_1 \ y_0 \\ \hline z_3 \ z_2 \ z_1 \ z_0 \end{array}$$




Ripple-Carry Adder: Lowest-order Bit

 


Ripple-Carry Adder: In General

 


Ripple-Carry Adder: In General

 


What does this circuit do?

 

What does this circuit do?

 


Increment Circuit

 


Gate Delay

What happens when I change my input?

 


Building a Counter

Building a Counter

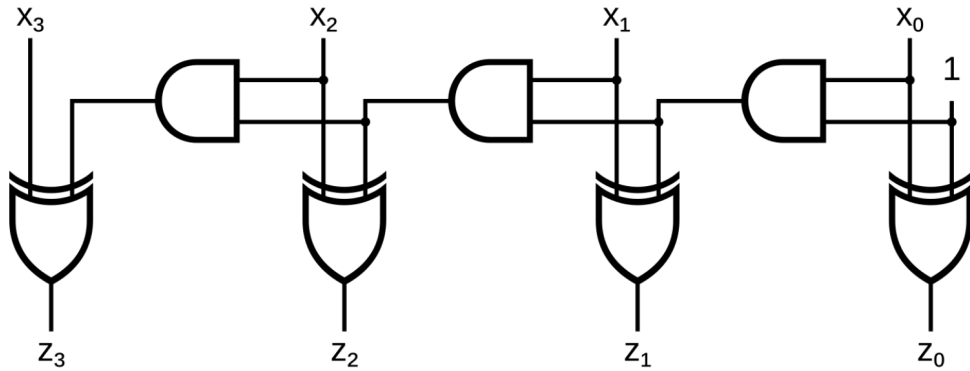


Building a Counter - Waiting


1-bit Register Circuit

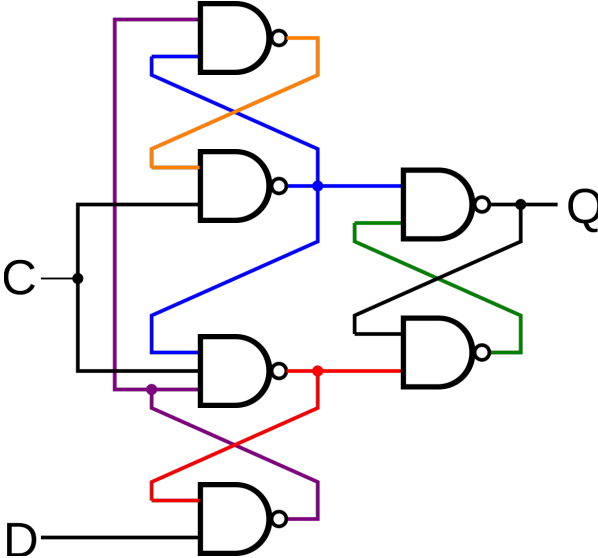


1-bit Register Circuit

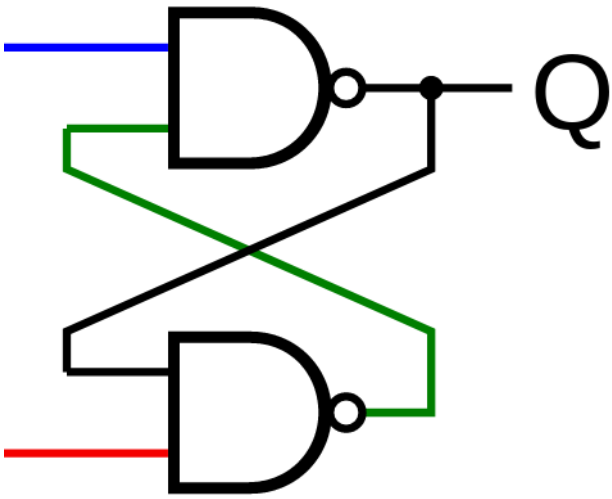

1-bit Register Circuit

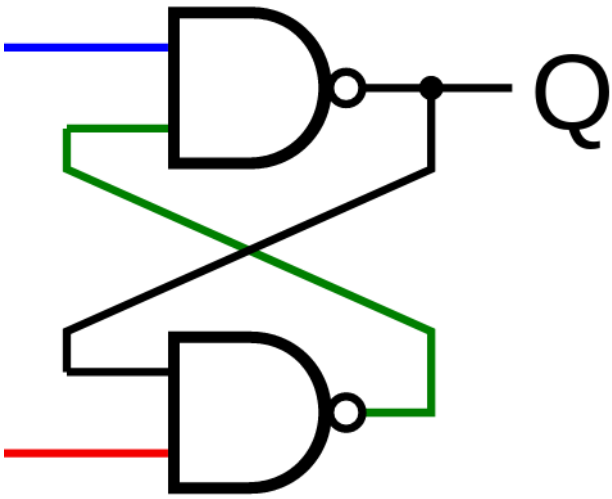

1-bit Register Circuit

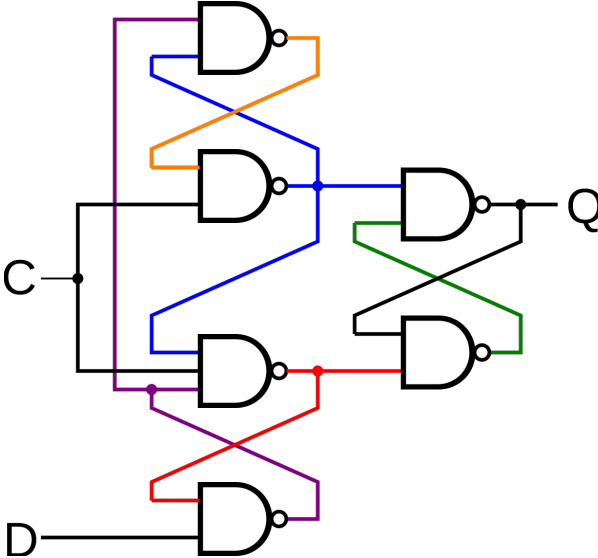

Building a Counter

