

# Circuits and Code

---


CS 2130: Computer Systems and Organization 1

February 6, 2023



# Announcements

- Homework 1 due tonight
- Homework 2 available today online, due next Monday
  - Please react to the Discord message in #general today if you want me to bring a paper copy for you on Wednesday!


# 1-bit Register Circuit

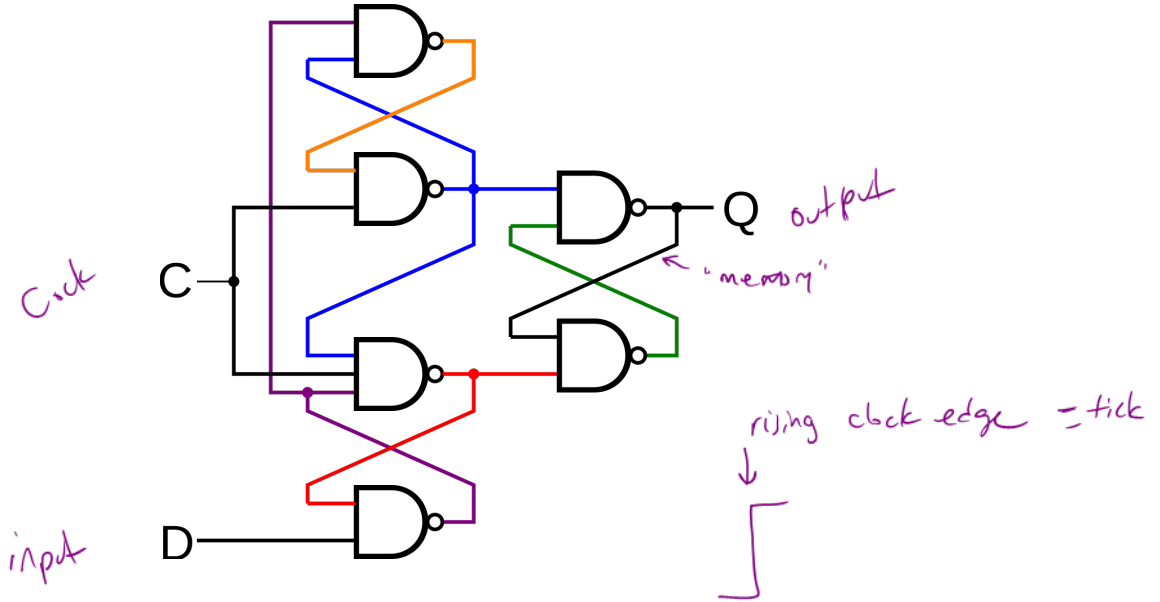

# Building a Counter

  


# Another Circuit

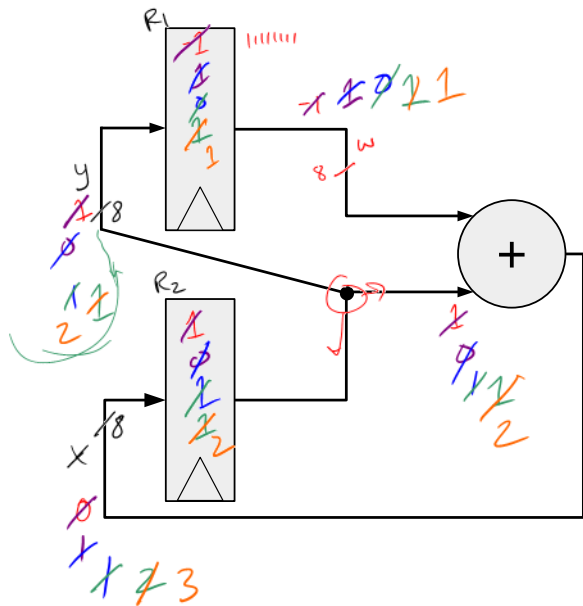


tick	x	y	$R_1$	$R_2$
0	0	1	-1	1
1	1	0	1	0
2	1	1	0	1
3	2	1	2	2
4	3	2	2	2
5	5	3		
6	8	5		
7	13	8		

# Another Circuit

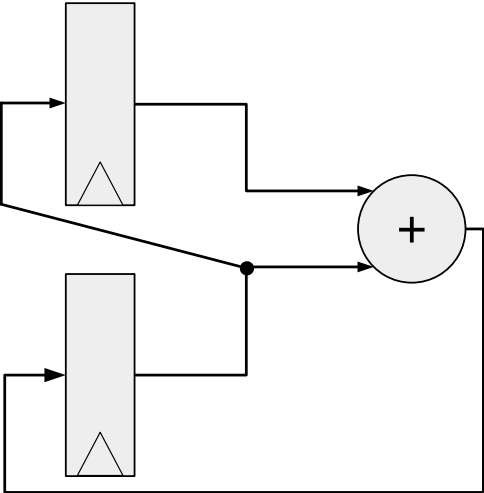

# Common Model in Computers

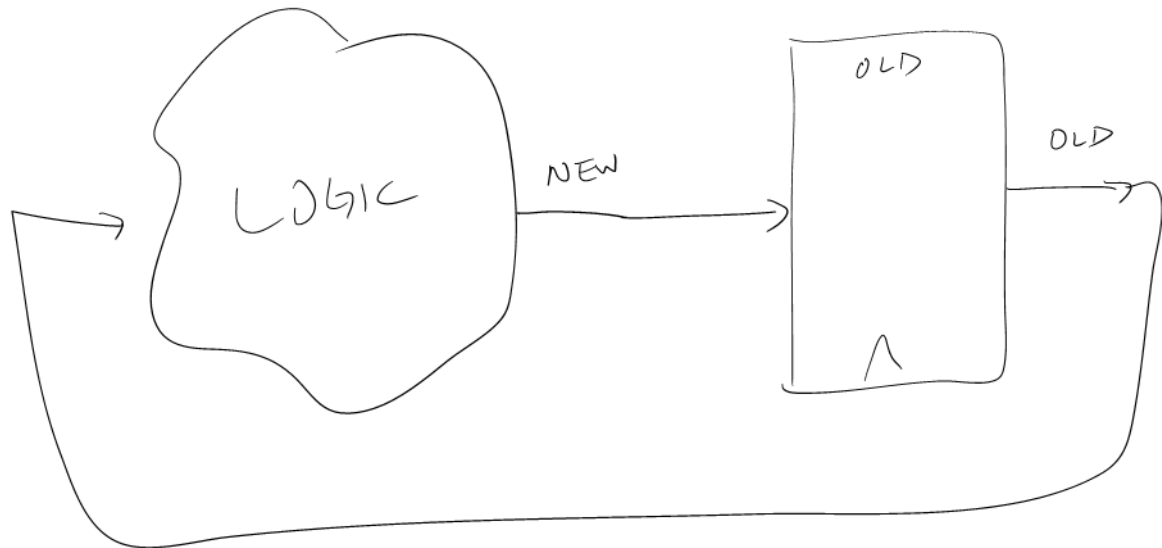

We can write code to build circuits



# Code to Build Circuits from Gates

Write code to build circuits from gates

x & y

- Gates we *already* know:  $\&$ ,  $|$ ,  $\wedge$ ,  $\sim$
- Operations we can build from gates:  $+$ ,  $-$
- Others we can build:

\* 
$$\begin{array}{r} 2130 \\ \times 1111 \\ \hline 2130 \\ 0000 \\ 213000 \\ + 2130000 \\ \hline \end{array}$$

8 <<

/ %

# Code to Build Circuits from Gates

Write code to build circuits from gates


- Gates we *already* know:  $\&$ ,  $|$ ,  $\wedge$ ,  $\sim$
- Operations we can build from gates:  $+$ ,  $-$
- Others we can build:
- Ternary operator:  $?$  :

$$z = (a == b ? x : y) * w$$
 
# Equals

Equals: =

- Attach with wire (i.e., connect things)
- Ex:  $z = x * y$




# Equals

Equals: =

- Attach with wire (i.e., connect things)
- Ex:  $z = x * y$
- What about the following?

$$x = 1$$

$$x = 0$$

 

# Equals

Equals: =

- Attach with wire (i.e., connect things)
- Ex:  $z = x * y$
- What about the following?

$$x = 1$$

$$x = 0$$

- **Single assignment:** each variable can only be assigned a value once

}

# Subtraction



$$z = x - y$$

$$z = x + \sim y + 1$$

$$a = \sim y$$

$$b = a + 1$$

$$z = x + \cancel{a} + b$$

  

# Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output

# Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output



# Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output
- `<` - consider  $x < 0$

# Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output
- `<` - consider  $x < 0$
- `>`, `<=`, `=>` are similar


# Indexing

Indexing with square brackets: [ ]

- **Register bank** (or **register file**) - an array of registers
  - Can programmatically pick one based on index
  - I.e., can determine which register while running
- Two important operations:
  - $x = R[i]$  - Read from a register
  - $R[j] = y$  - Write to a register
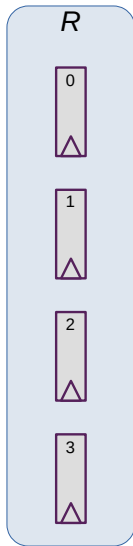
# Reading

$x = R[i]$  - connect output of registers to  $x$  based on index  $i$




## Aside: 4-input Mux

How do we build a 4-input mux? How many wires should  $i$  be?
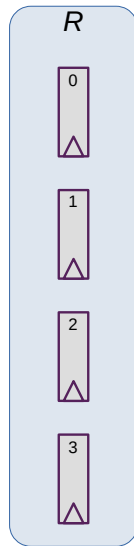
# Writing

$R[j] = y$  - connect  $y$  to input of registers based on index  $j$



## Aside: Creating $==0$ gates

How do we build gates that check for  $j == w$ ?

Need one more thing to build computers



# Memory and Storage

## Registers

≈ KiB

- 6 gates each, ≈ 24 transistors
- Efficient, fast
- Expensive!
- Ex: local variables

## Memory

≈ GiB

- Two main types: SRAM, DRAM
- DRAM: 1 transistor, 1 capacitor per bit
- DRAM is cheaper, simpler to build
- Ex: data structures, local variables

*These do not persist between power cycles*

# Memory and Storage

## Disk

≈ GiB-TiB

- Two main types: flash (solid state), magnetic disk
- Magnetic drive
  - Platter with physical arm above and below
  - Cheap to build
  - Very slow! Physically move arm while disk spins
  
- Ex: files

*Data on disk does persist between power cycles*

Putting it all together  
Next time!