
Circuits and Code

CS 2130: Computer Systems and Organization 1 February 6, 2023


Announcements

- Homework 1 due tonight
- · Homework 2 available today online, due next Monday
 - Please react to the Discord message in #general today if you want me to bring a paper copy for you on Wednesday!


1-bit Register Circuit

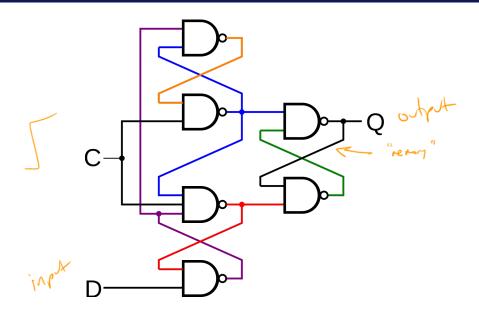


Building a Counter

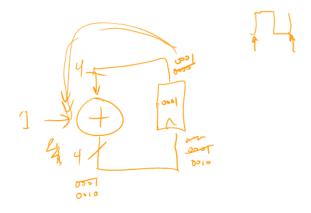


Another Circuit

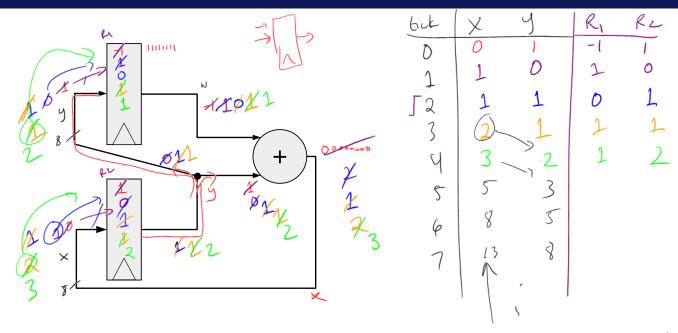

Another Circuit

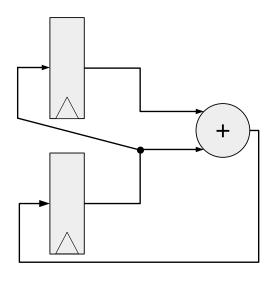

Common Model in Computers

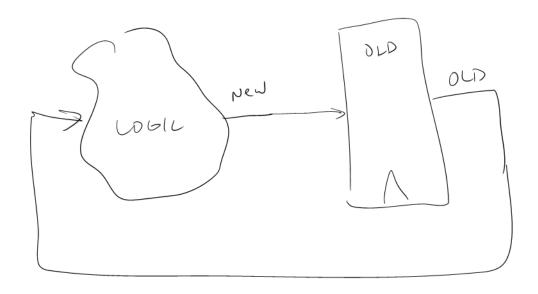


We can write code to build circuits

Code to Build Circuits from Gates

X & J

Write code to build circuits from gates

- Gates we already know: &, |, ^, ~
- Operations we can build from gates: +, -
- · Others we can build:

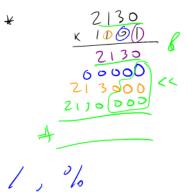

Code to Build Circuits from Gates


Write code to build circuits from gates

- Gates we already know: 8, |, ^, ~
- · Operations we can build from gates: +, -
- · Others we can build:
- Ternary operator: ? :

Equals

Equals: =

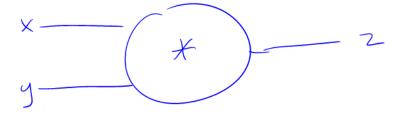- Attach with wire (i.e., connect things)
- Ex: z = x * y




Equals

Equals: =

- Attach with wire (i.e., connect things)
- Ex: z = x * y
- What about the following?

$$x = 1$$

$$x = 0$$

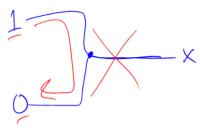

Equals

Equals: =


- Attach with wire (i.e., connect things)
- Ex: z = x * y
- · What about the following?
 - x = 1
 - x = 0
- Single assignment: each variable can only be assigned a value once




Subtraction

$$z = x + \sim y + 1$$

$$y - 2$$

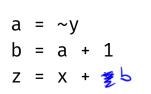


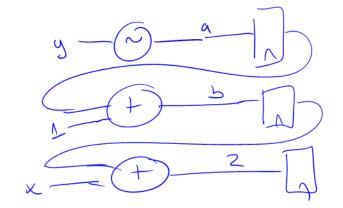

Each of our comparisons in code are straightforward to build:

• == - xor then nor bits of output

Y==)

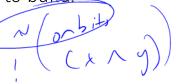

Each of our comparisons in code are straightforward to build:

- == xor then nor bits of output
- != same as == without not of output

Each of our comparisons in code are straightforward to build:

- == xor then nor bits of output
- != same as == without not of output

Each of our comparisons in code are straightforward to build:

- == xor then nor bits of output
- != same as == without not of output
- \cdot < consider x < 0
- · >, <=, => are similar


Indexing

```
Indexing with square brackets: [ ]
```

- Register bank (or register file) an array of registers
 - · Can programmatically pick one based on index
 - · I.e., can determine which register while running
- Two important operations:
 - x = R[i] Read from a register
 - R[j] = y Write to a register

Reading

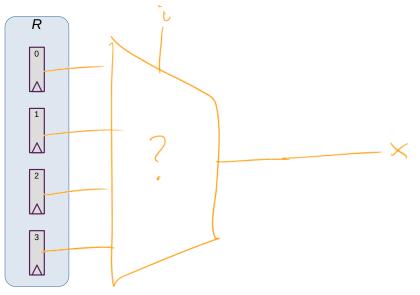x = R[i] - connect output of registers to x based on index i




Aside: 4-input Mux

How do we build a 4-input mux? How many wires should *i* be?

Writing

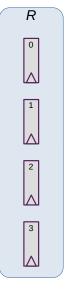R[j] = y - connect y to input of registers based on index j



Aside: Creating ==0 gates

How do we build gates that check for j == w?

Need one more thing to build computers

Memory and Storage

Registers

- 6 gates each, \approx 24 transistors
- · Efficient, fast
- Expensive!
- Ex: local variables

Memory

- Two main types: SRAM, DRAM
- DRAM: 1 transistor, 1 capacitor per bit
- · DRAM is cheaper, simpler to build
- Ex: data structures, local variables

These do not persist between power cycles

≈ KiB

≈ GiB

Memory and Storage

Disk \approx GiB-TiB

- Two main types: flash (solid state), magnetic disk
- Magnetic drive
 - Platter with physical arm above and below
 - · Cheap to build
 - Very slow! Physically move arm while disk spins

• Ex: files

Data on disk does persist between power cycles

Putting it all together Next time!