

Computer Systems and Organization 1

Warm up! Compute:

$$0x1a \wedge 0x72 = 0x68$$

$$0x1a = 0001\ 1010$$

$$0x72 = 0111\ 0010$$

$$\hline 0110\ 1000$$

$$6\quad 8$$

Bit-wise Operators, Git

CS 2130: Computer Systems and Organization 1

September 7, 2022

Announcements

- Homework 1 due Monday 9/12/2022
- TA office hours
 - **In-person:** Olsson 001, Wed-Sun, 5-7pm
 - **Online:** Discord, Wed-Sun, varies
 - Discord is now available
- My office hours
 - Tuesday, 4-5pm, Discord/Zoom
 - Wednesday, 4:30-6pm, Rice 210 (masks requested)
 - Thursday, 11am-12pm, Discord/Zoom

Quiz Review

$$0x \overset{16}{12} > \overset{10}{12}$$

18

$$0x 8 \quad 8$$

10


Quiz Review

3.1415 00000

~~101111~~
- 1010000

11010.

1.101×2^4

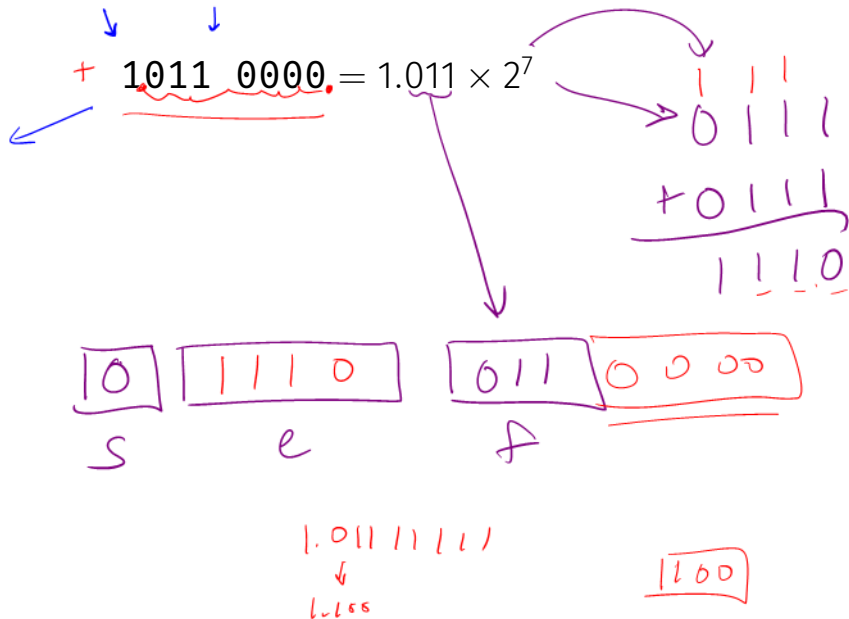

Operations (on Integers)

Bit vector: fixed-length sequence of bits (ex: bits in an integer)

- Manipulated by bitwise operations

Bitwise operations: operate over the bits in a bit vector


- Bitwise not: $\sim x$ - flips all bits (unary)
- Bitwise and: $x \& y$ - set bit to 1 if x, y have 1 in same bit
- Bitwise or: $x | y$ - set bit to 1 if either x or y have 1
- Bitwise xor: $x \wedge y$ - set bit to 1 if x, y bit differs

Operations (on Integers)


- Logical not: $!x$
 - $!0 = 1$ and $!x = 0, \forall x \neq \underline{0}$
 - Useful in C, no booleans
 - Some languages name this one differently
- Left shift: $x \ll y$ - move bits^x to the left _y
 - Effectively multiply by powers of 2
- Right shift: $x \gg y$ - move bits^x to the right _y
 - Effectively divide by powers of 2
 - Signed (extend sign bit) vs unsigned (extend 0)



Left Bit-shift Example

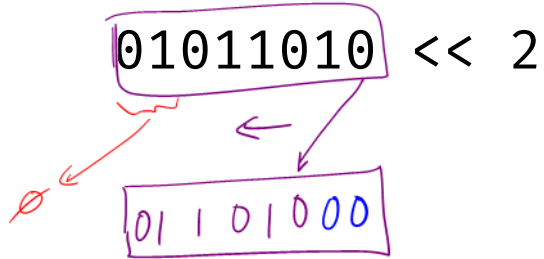

Right Bit-shift Example

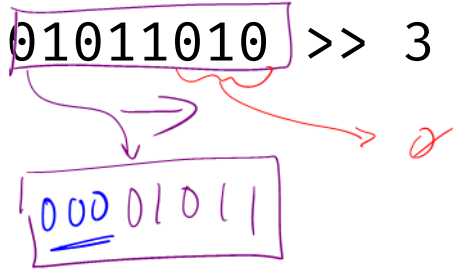

Bit-shift

Computing bit-shift effectively multiplies/divides by powers of 2

Consider decimal:


$$2130 \ll_{10} 2 = 213000 = 2130 \times \overset{10^2}{\underline{100}}$$

$$\underline{2130} \gg_{10} 1 = \underline{213} = 2130 / \underline{10}$$

Right Bit-shift Example 2

For **signed** integers, extend the sign bit (1)

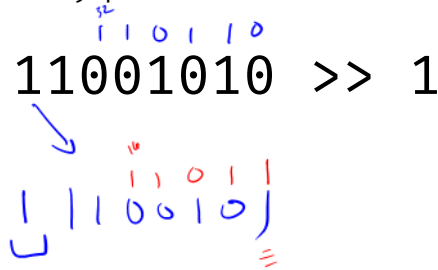- Keeps negative value (if applicable)
- Approximates divide by powers of 2



signed

- 54


- 27

git

git: distributed version control

- Created by Linus Torvalds (Linux)
- Free and open source software
- Separate from GitHub/GitLab/... which use git
- Website: git-scm.com

git in this Class

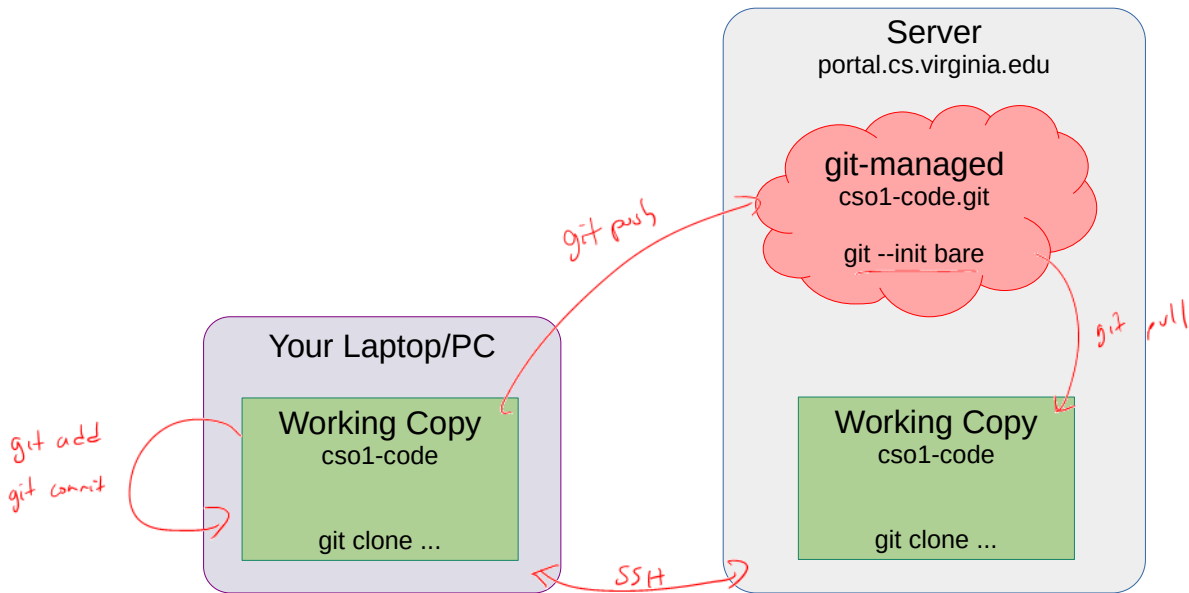

Review

- Transistors
- Information modeled by voltage through wires (1 vs 0)
- Gates

- Examples of and, not gates
- Multi-bit values: representing integers
 - Signed and unsigned
- Floating point

How to do the work of multi-bit?

Multi-bit Mux

Our first multi-bit example: mux

Adder

Add 2 1-bit numbers: a, b

Adder

What is missing? Consider:


$$\begin{array}{r} 11 \\ + 01 \\ \hline \end{array}$$

3-input Adder


Add 3 1-bit numbers: a, b, c

Aside: 3-input AND / XOR

Ripple-Carry Adder

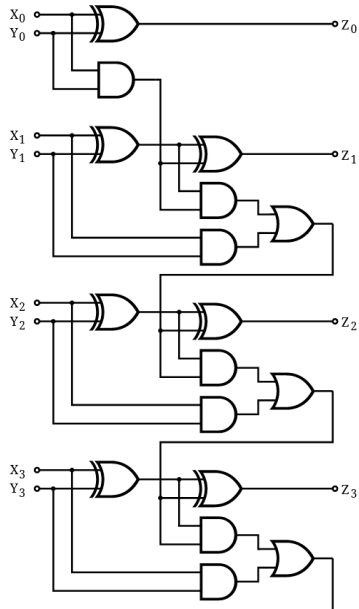

Ripple-Carry Adder

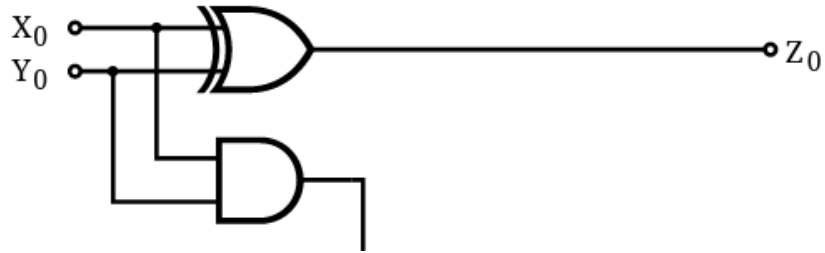

Ripple-Carry Adder

